

# ECE 111 - Homework #9

Week #9: ECE 311 Circuits II

1) Solve for Y

$$\bullet Y = \left( \frac{(7+j8)(6+j2)}{(6+j3)} \right)$$

$$\gg y = (7+j*8) * (6+j*2) / (6+j*3)$$

$$\mathbf{y = 7.6000 + 6.5333i}$$


ans:

$$\bullet Y = \left( \left( \frac{9+j8}{6-j10} \right) + \left( \frac{2+j9}{5-j5} \right) \right) \left( \frac{6+j7}{9+j10} \right)$$

$$\gg y = ( (9+j*8) / (6-j*10) + (2+j*9) / (5-j*5) ) * ( (6+j*7) / (9+j*10) )$$

$$\mathbf{y = -0.6456 + 1.4340i}$$

2) Determine the impedance Zab

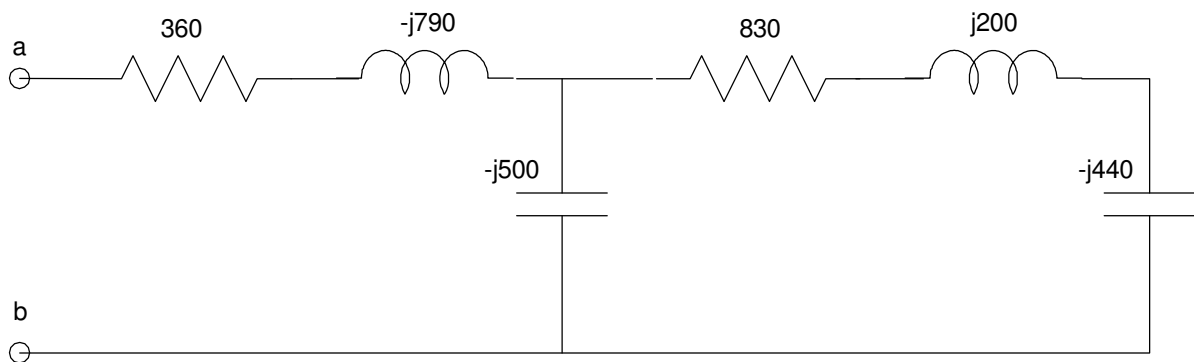

$$\gg Z1 = 360 - j*790;$$

$$\gg Z2 = -j*500;$$

$$\gg Z3 = 830 + j*200 - j*440;$$


$$\gg Z23 = 1 / (1/Z2 + 1/Z3)$$

$$Z23 = 1.6781e+002 -3.5038e+002i$$

$$\gg Zab = Z1 + Z23$$


$$\mathbf{Zab = 527.81 + 439.616i}$$

3) Determine the impedance  $Z_{ab}$

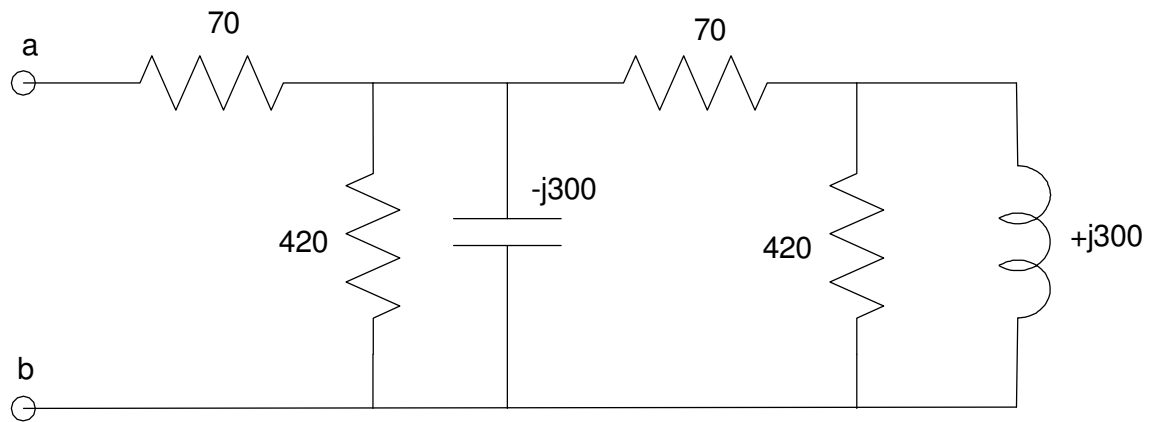

```
>> Z3 = 1 / (1/420 + 1/(j*300))
Z3 = 1.4189e+002 +1.9865e+002i
>> Z4 = 70 + Z3
Z4 = 2.1189e+002 +1.9865e+002i
>> Z5 = 1 / (1/Z4 + 1/420 + 1/(-j*300))
Z5 = 1.9652e+002 -3.9305e+001i
>> Zab = Z5 + 70
Zab = 266.52 -39.305i
>>
```

4) Assume  $V_{in} = 10$

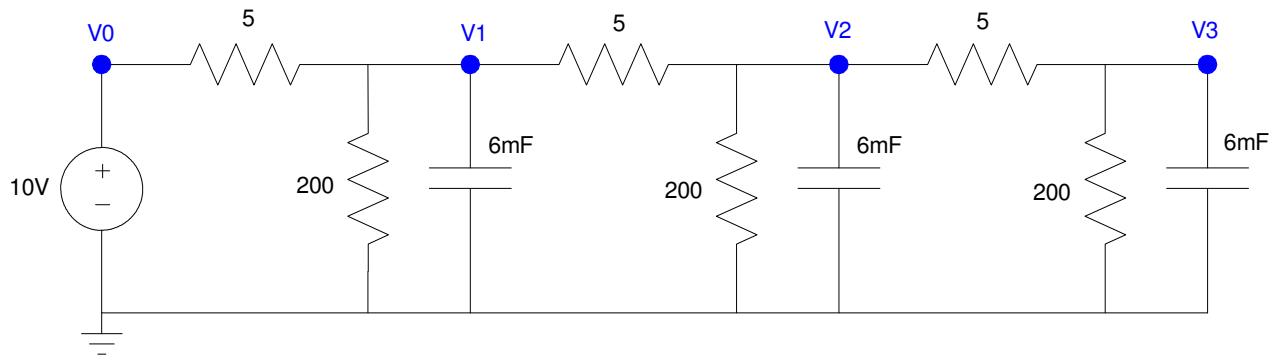

a) Determine the impedances of each element at 0 rad/sec

$$R \rightarrow R$$

$$C \rightarrow \infty$$

meaning you can ignore the capacitors at DC (the current will be zero. you can ignore zero)

b) Write the voltage node equations

$$V_0 = 10$$

$$\left( \frac{V_1 - V_0}{5} \right) + \left( \frac{V_1}{200} \right) + \left( \frac{V_1 - V_2}{5} \right) = 0$$

$$\left( \frac{V_2 - V_1}{5} \right) + \left( \frac{V_2}{200} \right) + \left( \frac{V_2 - V_3}{5} \right) = 0$$

$$\left( \frac{V_3 - V_2}{5} \right) + \left( \frac{V_3}{200} \right) = 0$$

c) Solve for V1, V2, and V3.

Group terms

$$V_0 = 10$$

$$-\left(\frac{1}{5}\right)V_0 + \left(\frac{1}{5} + \frac{1}{200} + \frac{1}{5}\right)V_1 - \left(\frac{1}{5}\right)V_2 = 0$$

$$-\left(\frac{1}{5}\right)V_1 + \left(\frac{1}{5} + \frac{1}{200} + \frac{1}{5}\right)V_2 - \left(\frac{1}{5}\right)V_3 = 0$$

$$-\left(\frac{1}{5}\right)V_2 + \left(\frac{1}{5} + \frac{1}{200}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{5}\right) & \left(\frac{1}{5} + \frac{1}{200} + \frac{1}{5}\right) & \left(\frac{-1}{5}\right) & 0 \\ 0 & \left(\frac{-1}{5}\right) & \left(\frac{1}{5} + \frac{1}{200} + \frac{1}{5}\right) & \left(\frac{-1}{5}\right) \\ 0 & 0 & \left(\frac{-1}{5}\right) & \left(\frac{1}{5} + \frac{1}{200}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve in Matlab

```
>> A = [1,0,0,0 ;
-1/5, 1/5+1/200+1/5, -1/5, 0;
0, -1/5, 1/5+1/200+1/5, -1/5;
0, 0, -1/5, 1/5+1/200]
```

```
    1.0000         0         0         0
   -0.2000    0.4050   -0.2000         0
         0   -0.2000    0.4050   -0.2000
         0         0   -0.2000    0.2050
```


```
>> B = [10;0;0;0]
```

```
    10
     0
     0
     0
```

```
>> V = inv(A)*B
```


```
v0    10.0000
v1     9.3278
v2     8.8888
v3     8.6720
```

5) Check your results in CircuitLab

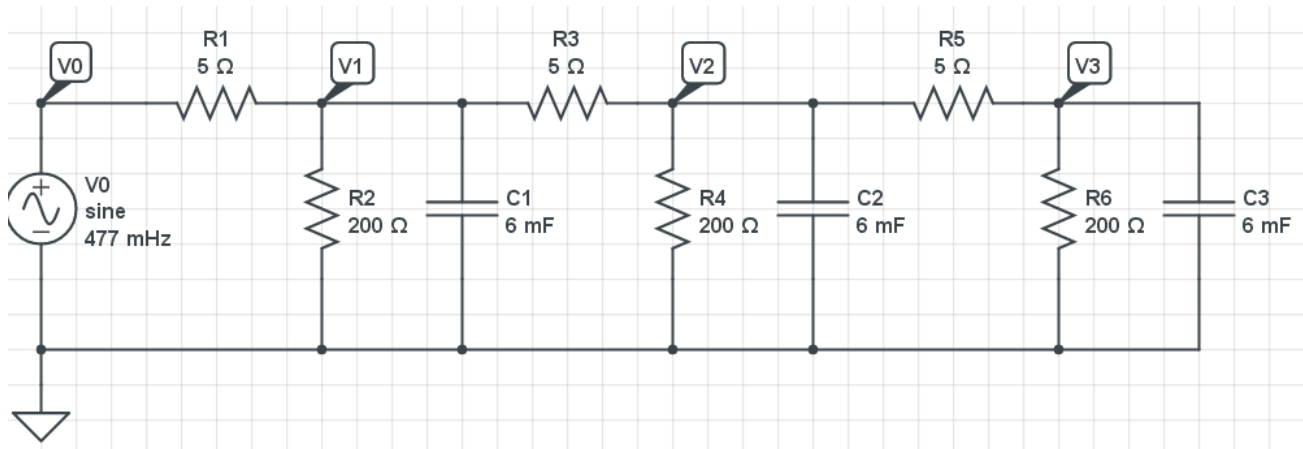

V0 is set up as

- 0V AC
- 10V offset (DC)

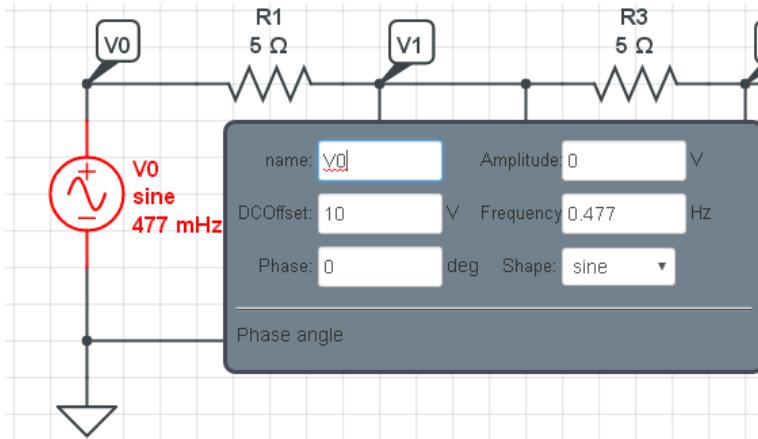

previous result from Matlab

```
V0 10.0000
V1  9.3278
V2  8.8888
V3  8.6720
```

Node	Value
V(V0)	10.00 V
V(V1)	9.328 V
V(V2)	8.889 V
V(V3)	8.672 V

+ Add Expression

6) Assume  $V_{in}$  is a 10V, 3 rad/sec ( 0.477Hz )

$$V_{in} = 10 \sin(3t)$$

a) Determine the impedances of each element at 3 rad/sec

$$R \rightarrow R$$

$$C \rightarrow \frac{1}{j\omega C} = -j55.56\Omega$$

b) Write the voltage node equations

Same as before but add a term (C)

$$V_0 = -j10$$

$$\left(\frac{V_1-V_0}{5}\right) + \left(\frac{V_1}{200}\right) + \left(\frac{V_1}{-j55.56}\right) + \left(\frac{V_1-V_2}{5}\right) = 0$$

$$\left(\frac{V_2-V_1}{5}\right) + \left(\frac{V_2}{200}\right) + \left(\frac{V_2}{-j55.56}\right) + \left(\frac{V_2-V_3}{5}\right) = 0$$

$$\left(\frac{V_3-V_2}{5}\right) + \left(\frac{V_3}{200}\right) + \left(\frac{V_3}{-j55.56}\right) = 0$$

Grouping terms and placing in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{5}\right) & \left(\frac{1}{5} + \frac{1}{200} + \frac{1}{-j55.56} + \frac{1}{5}\right) & \left(\frac{-1}{5}\right) & 0 \\ & \left(\frac{-1}{5}\right) & \left(\frac{1}{5} + \frac{1}{200} + \frac{1}{-j55.56} + \frac{1}{5}\right) & \left(\frac{-1}{5}\right) \\ & & \left(\frac{-1}{5}\right) & \left(\frac{1}{5} + \frac{1}{-j55.56} + \frac{1}{200}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

c) Solve for  $V_1$ ,  $V_2$ , and  $V_3$  as complex numbers

$$A = [1, 0, 0, 0 ; \\ -1/5, 1/5+1/200+1/(-j*55.56)+1/5, -1/5, 0; \\ 0, -1/5, 1/5+1/200+1/(-j*55.56)+1/5, -1/5; \\ 0, 0, -1/5, 1/5+1/200+1/(-j*55.56)]$$

$$B = [-j*10; 0; 0; 0]$$

$$V = \text{inv}(A) * B$$

$$A = \begin{bmatrix} 1.0000 & 0 & 0 & 0 \\ -0.2000 & 0.4050 + 0.0180i & -0.2000 & 0 \\ 0 & -0.2000 & 0.4050 + 0.0180i & -0.2000 \\ 0 & 0 & -0.2000 & 0.2050 + 0.0180i \end{bmatrix}$$

$$B = \begin{bmatrix} 0 \\ -10.0000i \\ 0 \\ 0 \end{bmatrix}$$

```
V =  
V0      0 -10.0000i  
V1 -1.8978 - 8.6408i  
V2 -3.0654 - 7.6684i  
V3 -3.6196 - 7.1636i
```

```
>> abs(V)
```

```
ans =  
10.0000  
8.8467  
8.2584  
8.0261
```

```
>>
```

d) Express V1, V2, and V3 in terms of a cosine function:

- real = sine
- imag = -cosine


From Matlab

- $V0 = 10 \sin(3t)$
- $V1 = -1.8978 \cos(3t) + 8.6408 \sin(3t)$
- $V2 = -3.0654 \cos(3t) + 7.6684 \sin(3t)$
- $V3 = -3.6196 \cos(3t) + 7.1636 \sin(3t)$

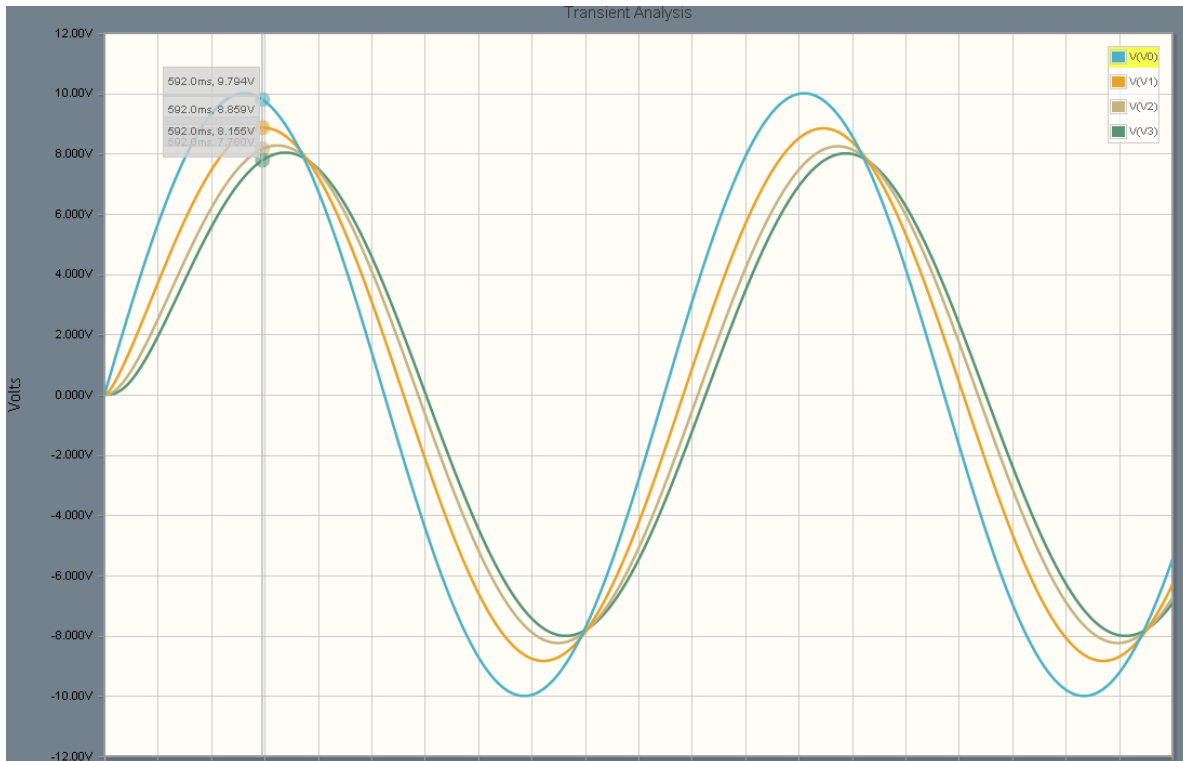7) Check your results in CircuitLab using a transient simulation for 6 seconds

Change V0 so that

- it's AC amplitude is 10V
- The offset (DC) is 0V
- Run a time-domain simulation



The peak of the waveforms is the amplitude computed in Matlab:

```
>> abs(V)

V0    10.0000    10.00V peak (blue)
V1     8.8467     8.859V peak (orange)
V2     8.2584     8.242V peak (tan)
V3     8.0261     8.006V peak (green)
```

Note: polar form is easier to use for lab data:

- The peak is the magnitude of the voltage in polar form
- The angle is the delay in terms of cycles (-30 degrees is a delay of 30/360 of one cycle)