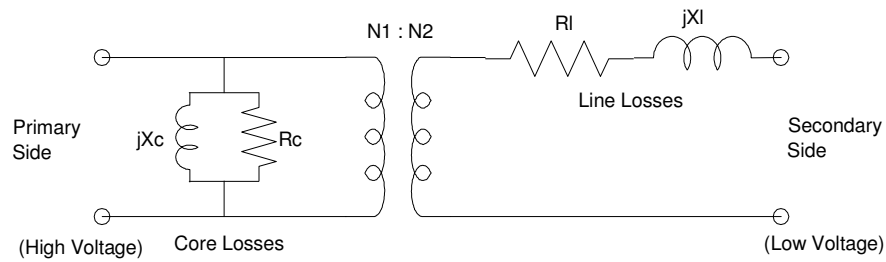


ECE 111: Homework 15

Week #15 - ECE 331 Energy Conversion. Due Deember 14th

Please submit as a Word or pdf file to BlackBoard or email to Jacob_Glower@yahoo.com with header ECE 111 HW#15
www.BisonAcademy.com

1) Determine the circuit model for a 13.2V : 240V transformer is tested with the following test results:



Transformer Model

	V	Power	pf
Open-Circuit Test	V1 = 9.6kV	85 W	0.06
Short-Circuit Test	V2 = 24V	15 W	0.97

Open Circuit Test:

$$P = V \cdot I \cdot pf$$

$$I = \left(\frac{P}{V \cdot pf} \right) = \left(\frac{85W}{9600V \cdot 0.06} \right) = 0.1476A$$

$$Z = \left(\frac{V}{I} \right) \angle \arccos(pf) = \left(\frac{9600V}{0.1476A} \right) \angle 86.56^\circ$$

$$Z = 65054 \angle 86.56^\circ = 3903.2 + j64,937$$

This is the series model (resistors in series add). The parallel model uses the inverse

$$\frac{1}{Z} = 9.2231 \cdot 10^{-7} - j1.5344 \cdot 10^{-5}$$

$$R_c = \left(\frac{1}{9.2231 \cdot 10^{-7}} \right) = 1.0842M\Omega$$

$$X_c = \left(\frac{1}{1.5344 \cdot 10^{-5}} \right) = 65.172k\Omega$$

In Matlab

```
>> V = 9600;
>> P = 85;
>> pf = 0.06;
>> I = P / (V*pf)
```

```
I = 0.1476
```

```
>> Z = (V/I) * exp(j*acos(pf))
```

```

Z = 3.9032e+003 +6.4937e+004i
>> 1/Z
ans = 9.2231e-007 -1.5344e-005i
>> Rc = 1/ real(1/Z)
Rc = 1.0842e+006
>> Xc = 1 / abs(imag(1/Z))
Xc =
6.5172e+004

```

Line Model:

$$I = \left(\frac{P}{V \cdot pf} \right) = \left(\frac{15W}{24V \cdot 0.97} \right) = 0.6443A$$

$$Z = \left(\frac{V}{A} \right) \angle \arccos(pf) = \left(\frac{24V}{0.6443A} \right) \angle 14.07^\circ$$

$$Z = 36.1306 + j9.0552$$

This is the series model ($R_L + jX_L$)

$$R_L = 36.1306\Omega$$

$$jX_L = j9.0552\Omega$$

In Matlab

```

>> P = 15;
>> V = 24;
>> pf = 0.97;
>> I = P / (V*pf)

I =    0.6443


>> Z = (V/I) * exp(j*acos(pf))

Z = 36.1306 + 9.0552i

>>

```

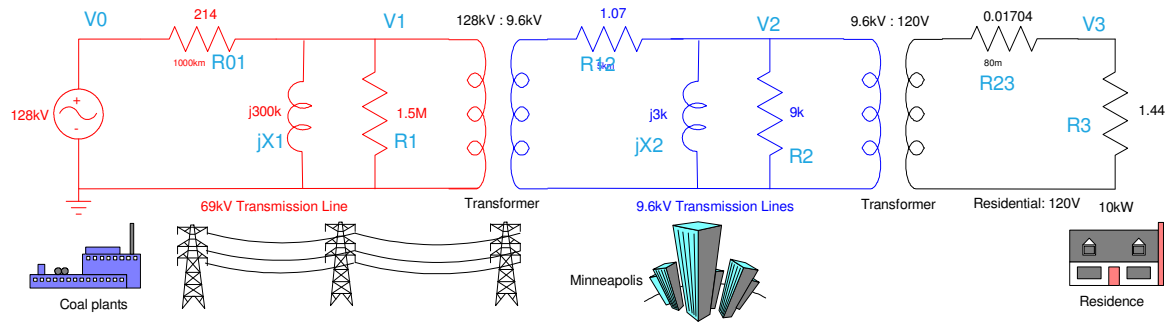2) Convert the voltages and impedances to the 120V node (right side)



Voltages convert as the turn ratio:


$$128kV \Rightarrow (128kV) \left(\frac{9.6kV}{128kV} \right) \left(\frac{120V}{9.6kV} \right) = 120V$$

Impedances convert as the turn ratio squared

$$R_{01} \Rightarrow 214 \left(\frac{120V}{128kV} \right)^2 = 0.000188\Omega$$

In matlab
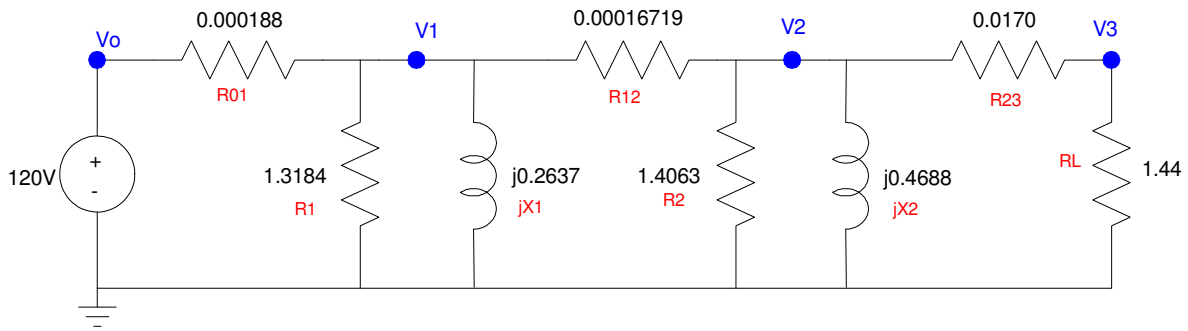
```
>> R01 = 214 * (120/128000)^2
R01 = 1.8809e-004
>> X1 = 300000 * (120/128000)^2
X1 = 0.2637
>> R1 = 1.5e6 * (120/128000)^2
R1 = 1.3184
>> R12 = 1.07 * (120/9600)^2
R12 = 1.6719e-004
>> X2 = 3e3 * (120/9600)^2
X2 = 0.4688
>> R2 = 9e3 * (120/9600)^2
R2 = 1.4063
>> R23 = 0.01704
R23 = 0.0170
>> R3 = 1.44
R3 = 1.4400
```



3) Determine the voltages at each node

Write the voltage node equations

$$V_0 = 120$$

$$\left(\frac{V_1 - V_0}{R_{01}}\right) + \left(\frac{V_1}{R_1}\right) + \left(\frac{V_1}{jX_1}\right) + \left(\frac{V_1 - V_2}{R_{12}}\right) = 0$$

$$\left(\frac{V_2 - V_1}{R_{12}}\right) + \left(\frac{V_2}{R_2}\right) + \left(\frac{V_2}{jX_2}\right) + \left(\frac{V_2 - V_3}{R_{23}}\right) = 0$$

$$\left(\frac{V_3 - V_2}{R_{23}}\right) + \left(\frac{V_3}{R_3}\right) = 0$$

Group terms

$$V_0 = 120$$

$$-\left(\frac{1}{R_{01}}\right)V_0 + \left(\frac{1}{R_{01}} + \frac{1}{R_1} + \frac{1}{jX_1} + \frac{1}{R_{12}}\right)V_1 - \left(\frac{1}{R_{12}}\right)V_2 = 0$$

$$-\left(\frac{1}{R_{12}}\right)V_1 + \left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{jX_2} + \frac{1}{R_{23}}\right)V_2 - \left(\frac{1}{R_{23}}\right)V_3 = 0$$

$$-\left(\frac{1}{R_{23}}\right)V_2 + \left(\frac{1}{R_{23}} + \frac{1}{R_3}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{R_{01}}\right) & \left(\frac{1}{R_{01}} + \frac{1}{R_1} + \frac{1}{jX_1} + \frac{1}{R_{12}}\right) & \left(\frac{-1}{R_{12}}\right) & 0 \\ 0 & \left(\frac{-1}{R_{12}}\right) & \left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{jX_2} + \frac{1}{R_{23}}\right) & \left(\frac{-1}{R_{23}}\right) \\ 0 & 0 & \left(\frac{-1}{R_{23}}\right) & \left(\frac{1}{R_{23}} + \frac{1}{R_3}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 120 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve (using Matlab)

```
>> a1 = [1,0,0,0];
>> a2 = [-1/R01,1/R01+1/R1+1/(j*X1)+1/R12,-1/R12,0];
>> a3 = [0,-1/R12,1/R12+1/R2+1/(j*X2)+1/R23,-1/R23];
>> a4 = [0,0,-1/R23,1/R23+1/R3];
>> A = [a1;a2;a3;a4]

>> A = [a1;a2;a3;a4]

A =

1.0e+004 *

    0.0001                0                0                0
   -0.5317             1.1299 - 0.0004i    -0.5981                0
         0             -0.5981                0.6041 - 0.0002i   -0.0059
         0                0                -0.0059             0.0059

>> B = [120;0;0;0]

    120
         0
         0
         0

>> V = inv(A)*B

1.0e+002 *

    1.2000 + 0.0000i
    1.1995 + 0.0013i
    1.1992 + 0.0018i
    1.1852 + 0.0017i

>> abs(V)

V0    120.0000
V1    119.9513
V2    119.9232
V3    118.5208
```

The customer's voltage drops to 118.52V

4) Determine the efficiency of this system a) Ignoring the core losses, and b) Including the core losses

```

V0 = V(1);
V1 = V(2);
V2 = V(3);
V3 = V(4);

P01 = (abs(V1-V0))^2 / R01
P12 = (abs(V1-V2))^2 / R12
P23 = (abs(V2-V3))^2 / R23

P1 = (abs(V1))^2 / R1
P2 = (abs(V2))^2 / R2
P3 = (abs(V3))^2 / R3

eff1 = P3 / (P3 + P01 + P12 + P23)
eff2 = P3 / (P3 + P01 + P12 + P23 + P1 + P2)


```

results in

```

P01 = 107.5859
P12 = 15.6382
P23 = 115.4339
P1 = 1.0914e+004
P2 = 1.0227e+004
P3 = 9.7550e+003

```

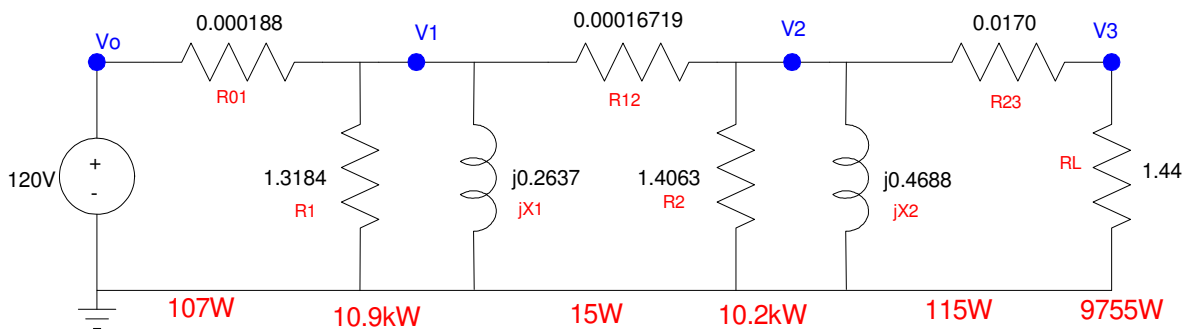

The efficiency when ignoring the core losses is 97.6%

- 98.8% of the power transmitted gets to the customer as long as you're serving a city (so the core losses are spread out over a large number of customers)

eff1 = 0.9761

The efficiency when including the core losses is only 31.3%

- If there is only one customer, only 31% of the energy transmitted gets to the customer
- It's not efficient or economic to build a power grid to serve a single customer

eff2 = 0.3133

