

ECE 111 - Homework #9


Week #9: ECE 311 Circuits II - Due 11am, Tuesday, October 25th

1) Solve for Y


$$\bullet Y = \left(\frac{(5+j2)(7-j3)}{(2-j6)} \right)$$

$$\bullet Y = \left(\left(\frac{5+j2}{2-j6} \right) + \left(\frac{7-j3}{2+j5} \right) \right) \left(\frac{8+j3}{7+j9} \right)$$


2) Determine the impedance Zab

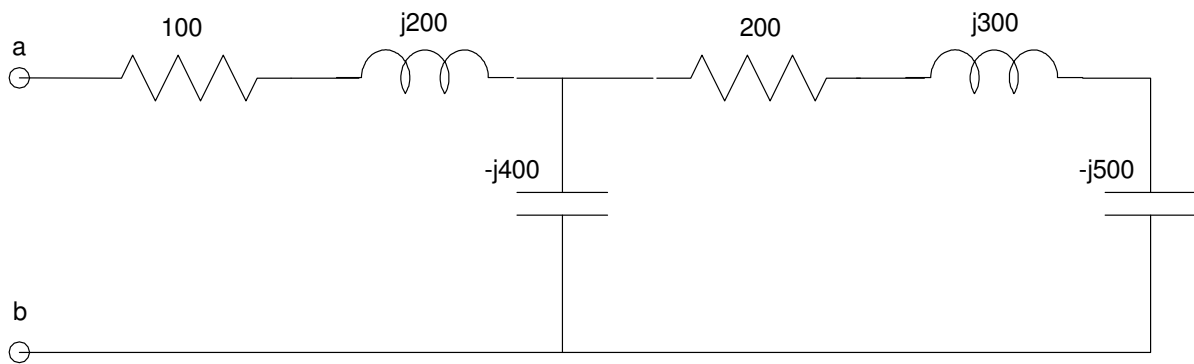

3) Determine the impedance Zab

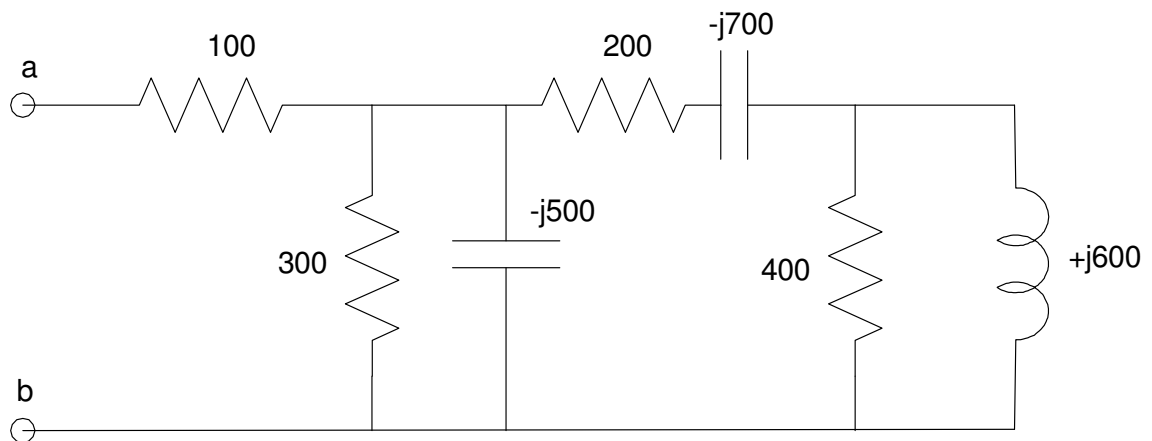

4) Assume $V_0 = 10$

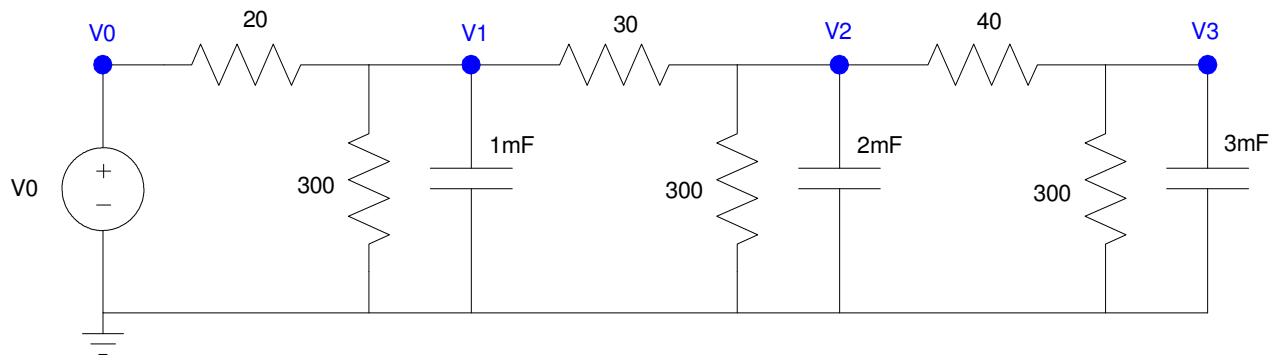

- Determine the impedances of each element at 0 rad/sec
- Write the voltage node equations
- Solve for V_1 , V_2 , and V_3 .

5) Check your results in CircuitLab

6) Assume V_0 is a 10V, 5 rad/sec (0.796Hz)

$$V_0 = 10 \sin(5t)$$

- Determine the impedances of each element at 5 rad/sec
- Write the voltage node equations
- Solve for V_1 , V_2 , and V_3 as complex numbers
- Express V_1 , V_2 , and V_3 in terms of sine and cosine function:
 - hint: $V_1 = a + jb$ (phasor representation) means $V_1(t) = a \cos(5t) - b \sin(5t)$

7) Check your results in CircuitLab using a transient simulation for 6 seconds