

ECE 111 - Homework #5

Week #5: EE 206 Circuits I. - Due 8am Tuesday, February 15th

1) A resistor has the following volts / amps / resistance / power. Determine the missing parameters:

| Volts | Amps | Ohms | Watts |
|------------|---------------|------------------|-------------|
| 24V | 1.5A | 16 Ohms | 36 W |
| 24V | 6A | 4 | 144W |
| 20V | 1.5A | 13.3 Ohms | 30 |
| 24V | 16.67A | 1.44 Ohms | 400 |


Note:

$$V = IR$$


$$P = VI$$

Kirchoff's Laws:

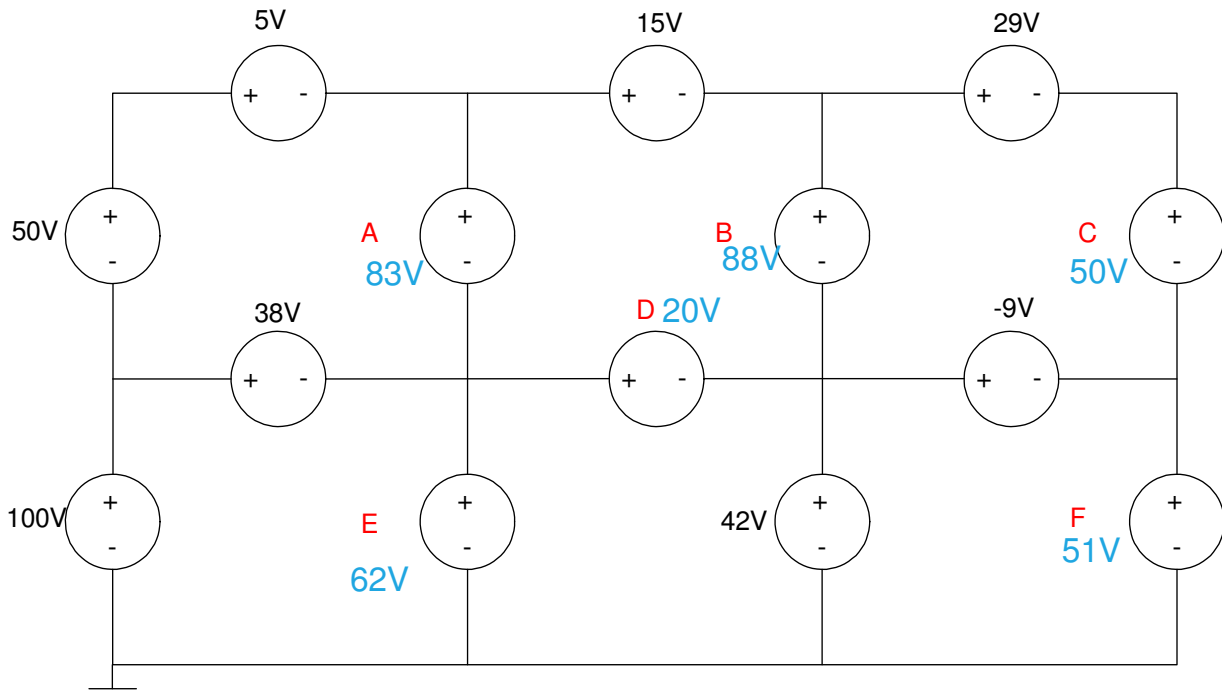2) Use conservation of voltage to determine the unknown voltages



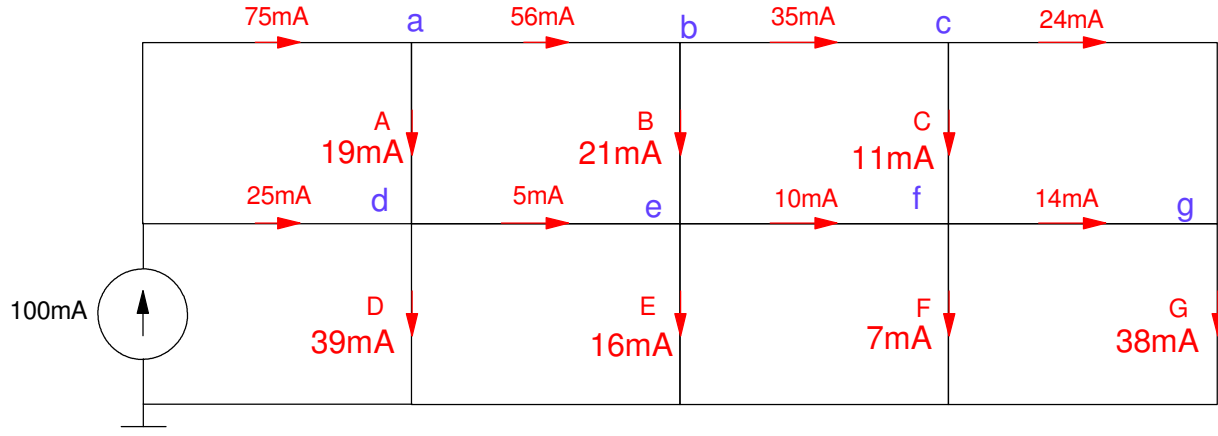3) Use conservation of current to determine the unknown currents



Current In = Current Out

node a)

$$75\text{mA} = A + 56\text{mA} \quad A = 19\text{mA}$$

node b)

$$56\text{mA} = B + 35\text{mA} \quad B = 21\text{mA}$$

node c)

$$35\text{mA} = C + 24\text{mA} \quad C = 11\text{mA}$$

node d)

$$25\text{mA} + A = D + 5\text{mA} \quad A = 19\text{mA (from before)}$$

$$D = 39\text{mA}$$


node e)

$$5\text{mA} + B = E + 10\text{mA} \quad B = 21\text{mA (from before)}$$

$$E = 16\text{mA}$$

Resistors in Series and Parallel

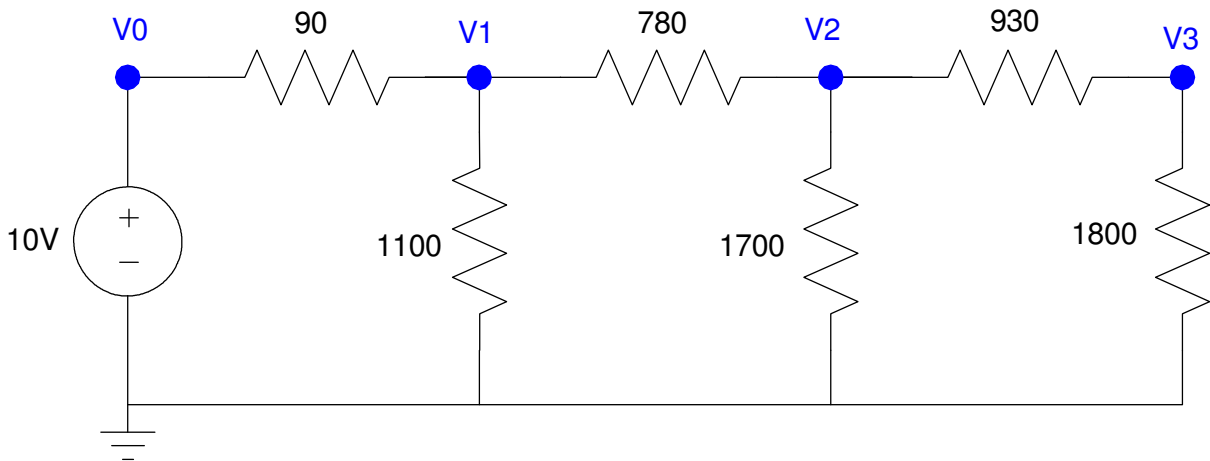4) Find the total resistance seen by the 10V source



The trick is to combine resistors in series and parallel.

In series (all the current through R1 also goes through R2)

$$R = R_1 + R_2$$

In parallel (both resistors are connected to Va on one side, Vb on the other side)

$$R_1 || R_2 = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

930 & 1800 are in series (they add)

$$930 + 1800 = 2730$$

2730 & 1700 are in parallel

$$2730 || 1700 = 1047.63$$

1047.63 & 780 are in series (they add)

$$1047.63 + 780 = 1827.63$$

1827.63 & 1100 are in parallel


$$1827.63 || 1100 = 686.69$$

686.69 & 90 are in series (they add)

$$686.69 + 90 = 776.69$$

answer: 776.69 Ohms

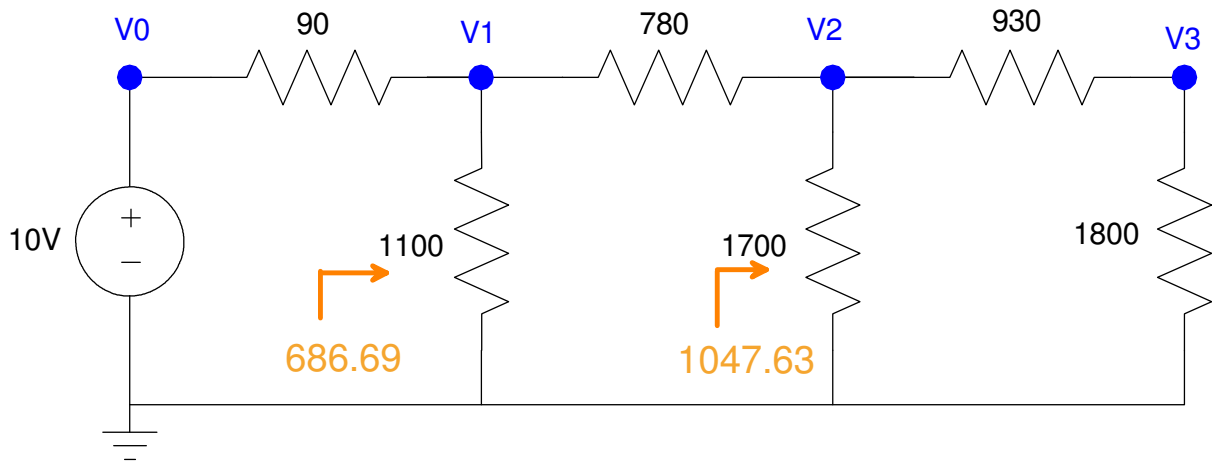5) Use voltage division to find V1, V2, and V3.



By inspection

$$V_0 = 10$$

Find the net resistance looking right at V1 (686.69 ohms from problem #4).

V1: By voltage division

$$V_1 = \left(\frac{686.69}{686.69+90} \right) V_0$$

$$V_1 = 8.841V$$

V2:

$$V_2 = \left(\frac{1047.63}{1047.63+780} \right) V_1$$


$$V_2 = 5.068V$$

V3:

$$V_3 = \left(\frac{1800}{1800+930} \right) V_2$$

$$V_3 = 3.342V$$

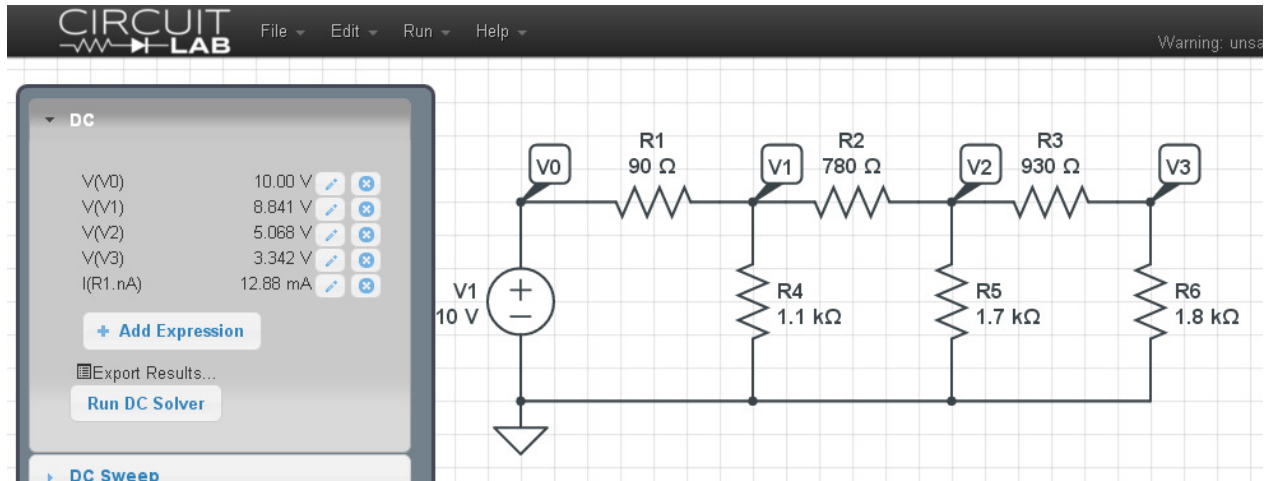6) Use CircuitLab to find V1, V2, V3, and the total resistance seen by the 10V source.



| | V0 | V1 | V2 | V3 |
|------------|--------|--------|--------|--------|
| Calculated | 10.00V | 8.841V | 5.068V | 3.342V |
| Simulated | 10.00V | 8.841V | 5.068V | 3.342V |

The current through R1 tells you the net resistance as well:

$$I = 12.88\text{mA}$$

$$R = \left(\frac{V}{I}\right) = \left(\frac{10\text{V}}{12.88\text{mA}}\right) = 776.40\Omega$$

In problem #4, the resistance was calculated as

$$R = 776.69\Omega$$

The difference is rounding error with the current

$$I = \left(\frac{10\text{V}}{776.69\Omega}\right) = 12.875\text{mA}$$

which is rounded to 12.88mA (resulting in the difference in the resistances)