


ECE 111 - Homework #8

Week #8: ECE 351 Electromagnetics -- Due 8am Tuesday, March 8th
Please submit as a Word or pdf file and email to Jacob_Glower@yahoo.com with header ECE 111 HW#8

1) Assume the current flowing through a one Henry inductor is shown below. Sketch the voltage.


$$V = L \frac{dI}{dt}$$

The derivative is the slope: change in $I(t)$ / change in time

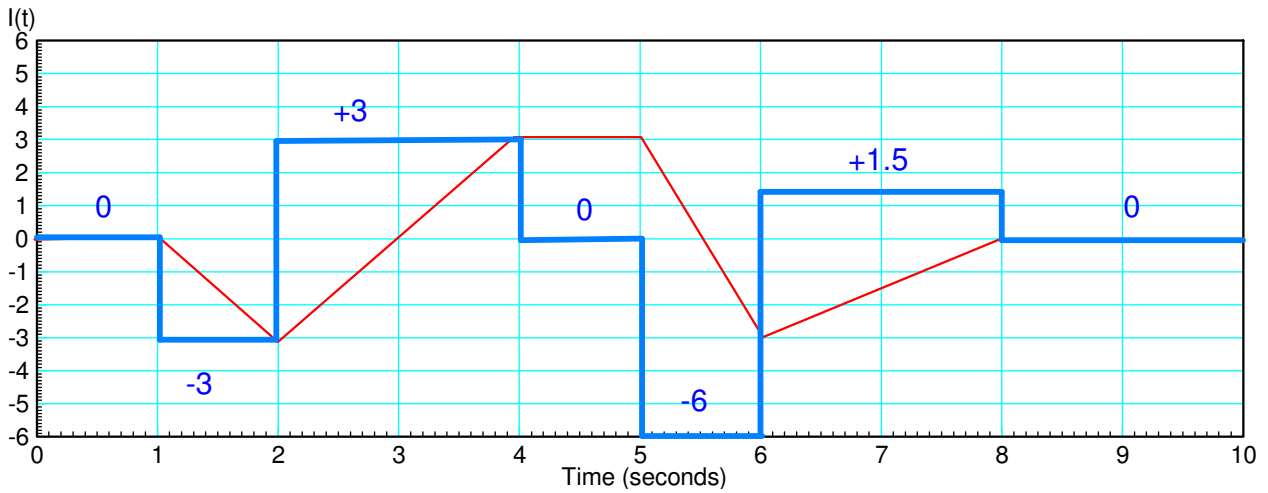

Problem 2-3) 4-Node RLC Circuit

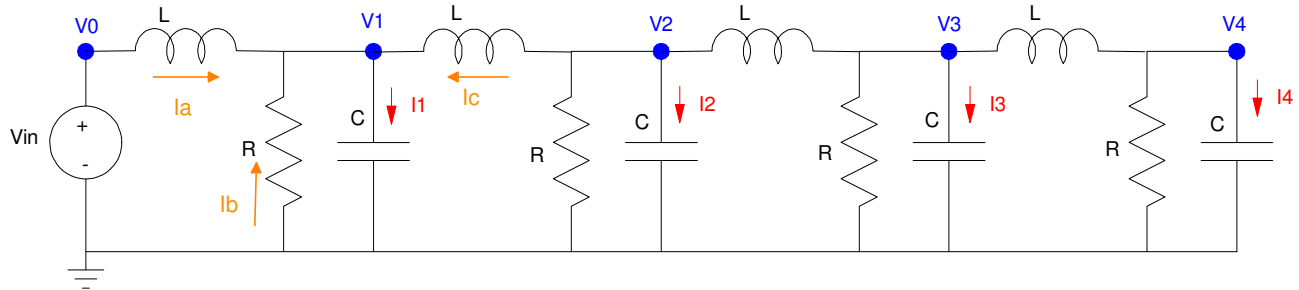2) Write the dynamic equations for the following 4-stage RLC circuit. (i.e. write the node equations)



$R = 400\Omega$, $C = 0.033F$, $L = 0.2H$. Repeat for 30 nodes for problems 4-6

Note

$$I = C \frac{dV}{dt} = C \dot{V}$$

$$V = L \frac{dI}{dt} = L \dot{I}$$

Node V1:

$$I_1 = C \dot{V}_1 = I_a + I_b + I_c$$

$$C \dot{V}_1 = I_a + \left(\frac{0 - V_1}{R} \right) + I_c$$

Take the derivative (sY means 'the derivative of Y'):

$$C \ddot{V}_1 = sI_a - \left(\frac{1}{R} \right) \dot{V}_1 + sI_c$$

For an inductor

$$V = L \dot{I}$$

$$V_0 - V_1 = L \dot{I}_a$$

$$\dot{I}_a = \left(\frac{V_0 - V_1}{L} \right)$$

Substitute for dI_a/dt and dI_c/dt

$$C\ddot{V}_1 = \left(\frac{V_0 - V_1}{L}\right) - \left(\frac{1}{R}\right)\dot{V}_1 + \left(\frac{V_2 - V_1}{L}\right)$$

Simplify

$$\ddot{V}_1 = \left(\frac{1}{LC}\right)V_0 - \left(\frac{2}{LC}\right)V_1 + \left(\frac{1}{LC}\right)V_2 - \left(\frac{1}{RC}\right)\dot{V}_1$$

$$\ddot{V}_2 = \left(\frac{1}{LC}\right)V_1 - \left(\frac{2}{LC}\right)V_2 + \left(\frac{1}{LC}\right)V_3 - \left(\frac{1}{RC}\right)\dot{V}_2$$

$$\ddot{V}_3 = \left(\frac{1}{LC}\right)V_2 - \left(\frac{2}{LC}\right)V_3 + \left(\frac{1}{LC}\right)V_4 - \left(\frac{1}{RC}\right)\dot{V}_3$$

$$\ddot{V}_4 = \left(\frac{1}{LC}\right)V_3 - \left(\frac{1}{LC}\right)V_4 - \left(\frac{1}{RC}\right)\dot{V}_4$$

Plugging in numbers:

$$\ddot{V}_1 = 151.52V_0 - 303.04V_1 + 1515.2V_2 - 0.076\dot{V}_1$$

$$\ddot{V}_2 = 151.52V_1 - 303.04V_2 + 151.52V_3 - 0.076\dot{V}_2$$

$$\ddot{V}_3 = 151.52V_2 - 303.04V_3 + 151.52V_4 - 0.076\dot{V}_3$$

$$\ddot{V}_4 = 151.52V_3 - 151.52V_4 - 0.076\dot{V}_4$$

3) Assume $V_{in} = 10V$ and the initial conditions are zero ($V_1 = V_2 = V_3 = V_4 = 0$). Solve for the voltages at $t = 3$ seconds. *Hint: Solve numerically using Matlab*

```
V0 = 10;
V1 = 0;
V2 = 0;
V3 = 0;
V4 = 0;
```

```
dV1 = 0;
dV2 = 0;
dV3 = 0;
dV4 = 0;
```

```
V = [];
```

```
t = 0;
dt = 0.01;
```

```
while(t < 3)
```

```
    ddV1 = 151.52*V0 - 303.04*V1 + 151.52*V2 - 0.076*dV1;
    ddV2 = 151.52*V1 - 303.04*V2 + 151.52*V3 - 0.076*dV2;
    ddV3 = 151.52*V2 - 303.04*V3 + 151.52*V4 - 0.076*dV3;
    ddV4 = 151.52*V3 - 151.52*V4 - 0.076*dV4;
```


```
    dV1 = dV1 + ddV1*dt;
    dV2 = dV2 + ddV2*dt;
    dV3 = dV3 + ddV3*dt;
    dV4 = dV4 + ddV4*dt;
```

```
    V1 = V1 + dV1*dt;
    V2 = V2 + dV2*dt;
    V3 = V3 + dV3*dt;
    V4 = V4 + dV4*dt;
```

```
t = t + dt;
```

```
    hold off
    plot([0,3],[-15,30],'w+');
    hold on
    plot([0,1,2,3,4],[V0,V1,V2,V3,V4],'.-');
    pause(0.01);
```

```
end
```

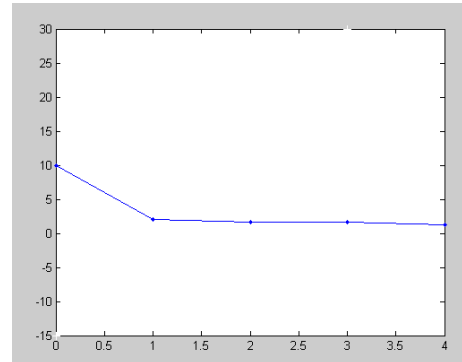


Problem 4-6) 30-Node RLC Circuit (hint: modify the program Wave.m)

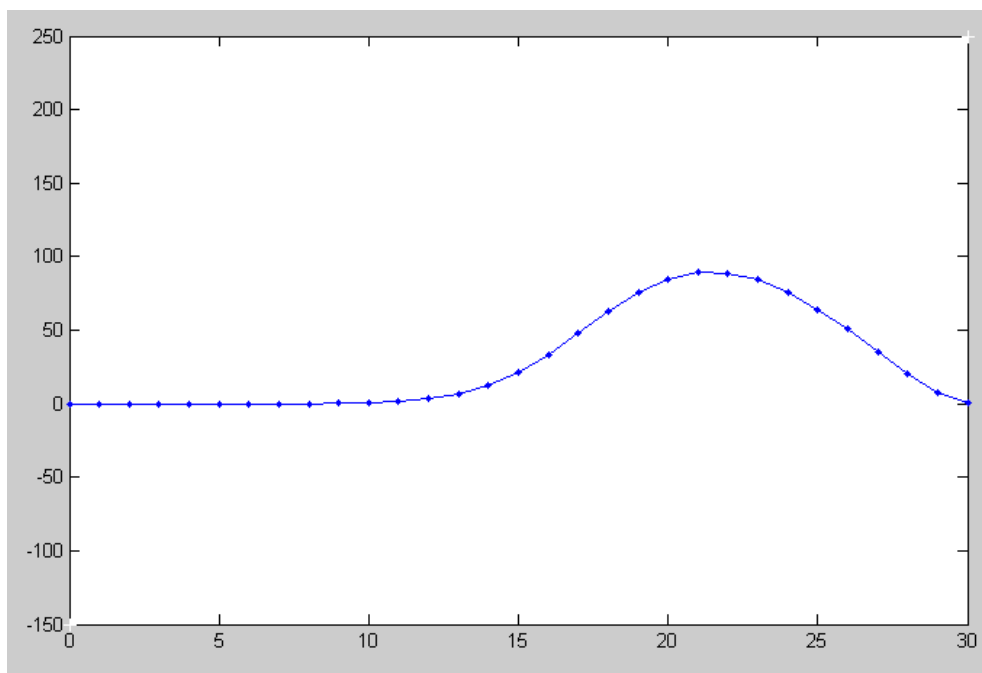
4) Expand the RLC circuit from problem #2 to 30 nodes. Plot the voltage at $t = 4$ seconds (just after the reflection) for $1 / R_{30}C = 0.01$

```
V = zeros(30,1);
dV = zeros(30,1);
t = 0;
dt = 0.01;
while(t < 5)
    if (t < 1.5) V0 = 100* ( sin(2*t).^2);
        else V0 = 0;
        end
    ddV(1) = 151.52*V0 - 303.04*V(1) + 151.52*V(2) - 0.076*dV(1);
    for i=2:29
        ddV(i) = 151.52*V(i-1) - 303.04*V(i) + 151.52*V(i+1) - 0.076*dV(i);
        end
    ddV(30) = 151.52*V(29) - 151.52*V(30) - 0.076*dV(30);
    for i=1:30
        dV(i) = dV(i) + ddV(i)*dt;
        V(i) = V(i) + dV(i)*dt;
        end
    t = t + dt;


hold off
plot([0,30],[-150,250],'w+');
hold on
plot([0:30],[V0;V],'.-');
pause(0.01);
end
```



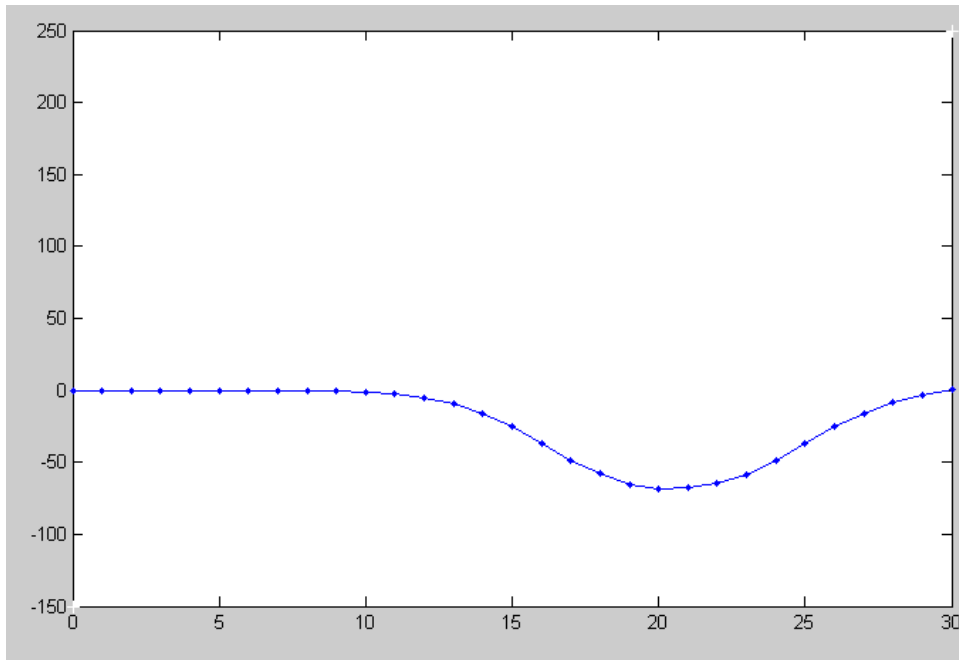5) Plot the voltage at $t = 4$ seconds for $1 / R_{30} C = 100$



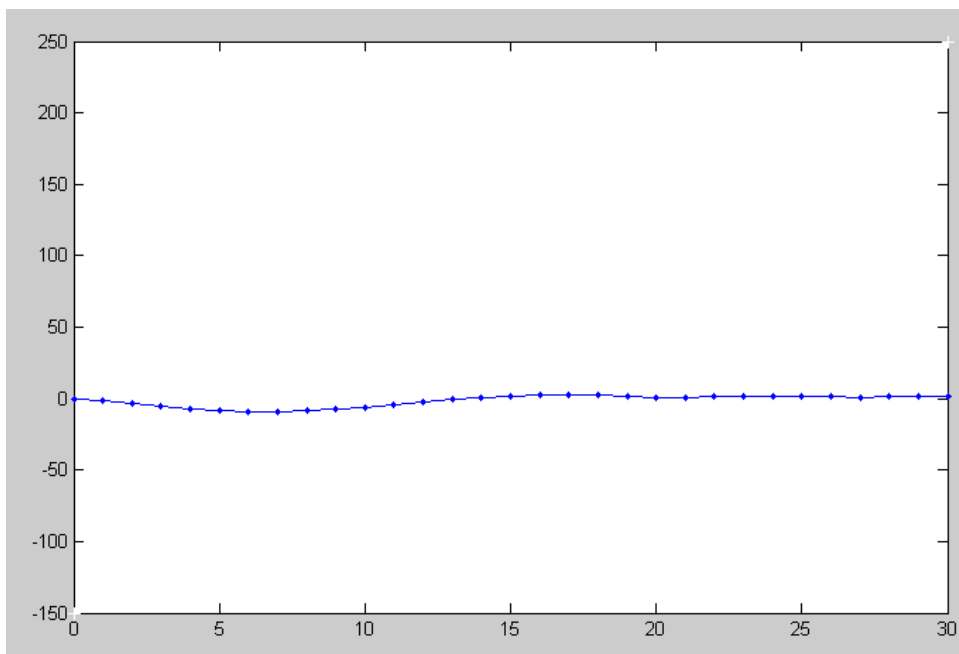6) Determine experimentally R_{30} so that the reflection is almost zero



$1/R_{30} C = 15$

