

ECE 111 - Homework #9

Week #9: ECE 311 Circuits II - Due 8am, Tuesday, March 22nd
Please submit as a Word or pdf file and email to Jacob_Glower@yahoo.com with header ECE 111 HW#9

1) Solve for Y

$$Y = \left(\frac{(2+j5)(1+j6)}{(7-j2)} \right)$$

$$\gg Y = (2+j*5) * (1+j*6) / (7-j*2)$$


$$Y = -4.3396 + 1.1887i$$

$$Y = \left(\left(\frac{2+j5}{7-j2} \right) + \left(\frac{1+j6}{2-j7} \right) \right) \left(\frac{5+j6}{3+j8} \right)$$

$$\gg Y = ((2+j*5) / (7-j*2) + (1+j*6) / (2-j*7)) * (5+j*6) / (3+j*8)$$

$$Y = -0.2564 + 1.1491i$$

2) Determine the impedance Zab

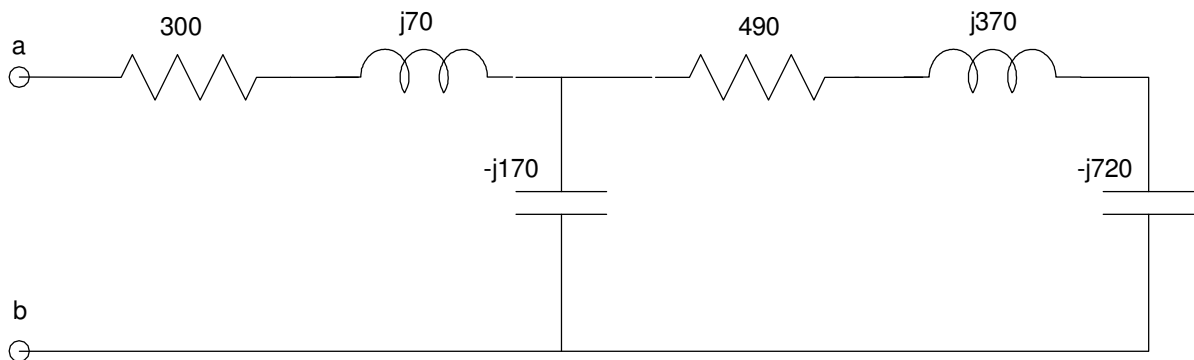


$$(490 + j370) + (-j720) = 490 - j350$$

$$(490 - j350) \parallel (-j170) = 27.739 - j140.562$$

$$(27.739 - j140.562) + (300 + j70) = 327.739 - j70.562$$

$$\text{ans: } 327.739 - j70.562$$

3) Determine the impedance Z_{ab}

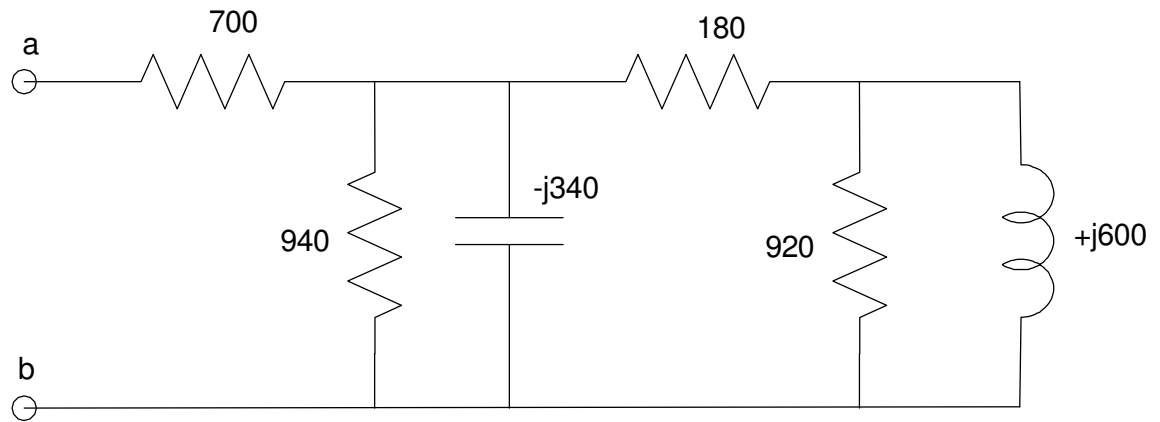

$$(j600) \parallel (920) = 274.536 + j420.955$$


$$(274.536 + j420.955) + (180) = 454.536 + j420.955$$

$$(454.536 + j420.955) \parallel (-j340) \parallel (940) = 265.867 - j218.121$$

$$(265.867 - j218.121) + (700) = 965.867 - j218.121$$

$$\mathbf{ans = 965.867 - j218.121}$$

4) Assume $V_0 = 10$

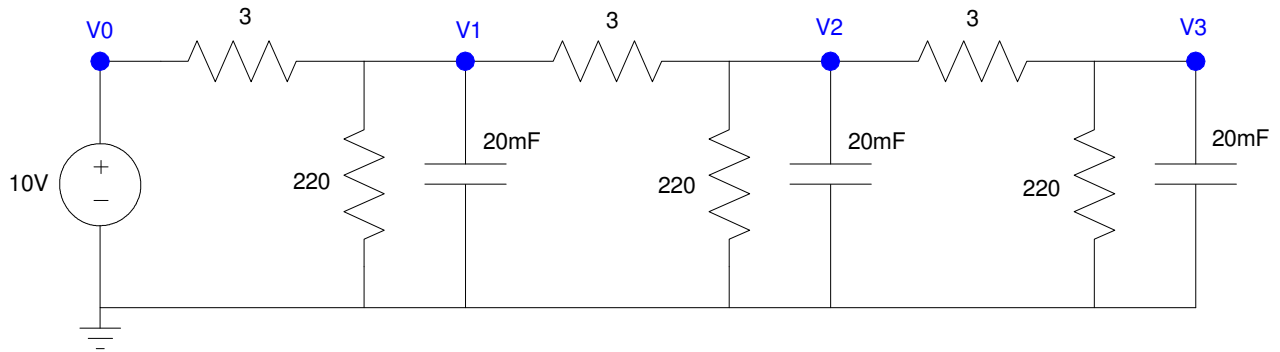

a) Determine the impedances of each element at 0 rad/sec

$$V_0 = 10$$

$C = \text{infinity}$ (ignore: the current is zero)

b) Write the voltage node equations

$$V_0 = 10$$

$$\left(\frac{V_1 - V_0}{3}\right) + \left(\frac{V_1}{220}\right) + \left(\frac{V_1 - V_2}{3}\right) = 0$$

$$\left(\frac{V_2 - V_1}{3}\right) + \left(\frac{V_2}{220}\right) + \left(\frac{V_2 - V_3}{3}\right) = 0$$

$$\left(\frac{V_3 - V_2}{3}\right) + \left(\frac{V_3}{220}\right) = 0$$

c) Solve for V_1 , V_2 , and V_3 .

Group terms

$$V_0 = 10$$

$$-\left(\frac{1}{3}\right)V_0 + \left(\frac{1}{3} + \frac{1}{220} + \frac{1}{3}\right)V_1 - \left(\frac{1}{3}\right)V_2 = 0$$

$$-\left(\frac{1}{3}\right)V_1 + \left(\frac{1}{3} + \frac{1}{220} + \frac{1}{3}\right)V_2 - \left(\frac{1}{3}\right)V_3 = 0$$

$$-\left(\frac{1}{3}\right)V_2 + \left(\frac{1}{3} + \frac{1}{220}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{3}\right) & \left(\frac{2}{3} + \frac{1}{220}\right) & \left(\frac{-1}{3}\right) & 0 \\ 0 & \left(\frac{-1}{3}\right) & \left(\frac{2}{3} + \frac{1}{220}\right) & \left(\frac{-1}{3}\right) \\ 0 & 0 & \left(\frac{-1}{3}\right) & \left(\frac{1}{3} + \frac{1}{220}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve using Matlab

```
A = [1,0,0,0 ; -1/3,2/3+1/220,-1/3,0 ; 0,-1/3,2/3+1/220,-1/3 ; 0,0,-1/3,1/3+1/220]
```

```
1.0000      0      0      0
-0.3333    0.6712   -0.3333    0
      0   -0.3333    0.6712   -0.3333
      0      0   -0.3333    0.3379
```

```
>> B = [10;0;0;0]
```

```
10
 0
 0
 0
```



```
>> V = inv(A)*B
```

```
10.0000
 9.6153
 9.3617
 9.2357
```

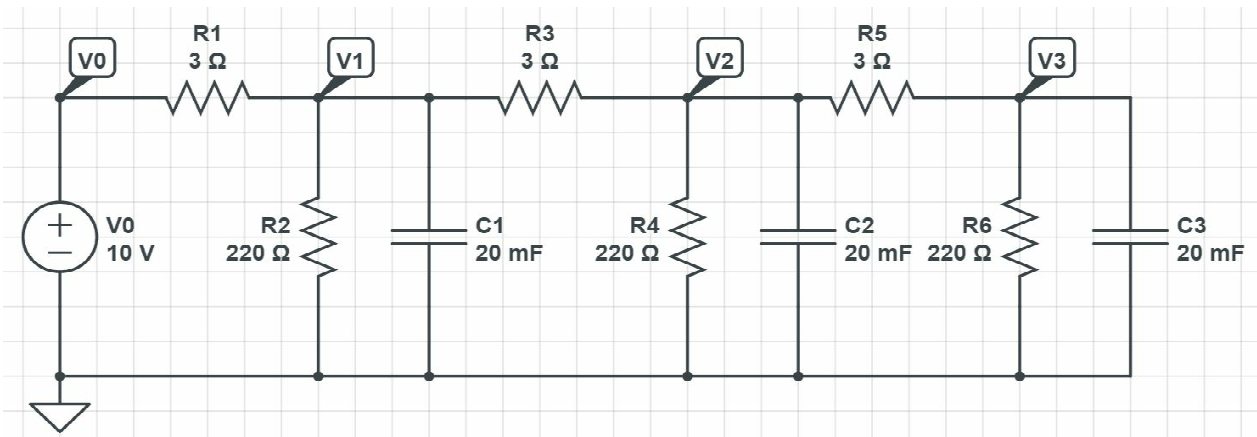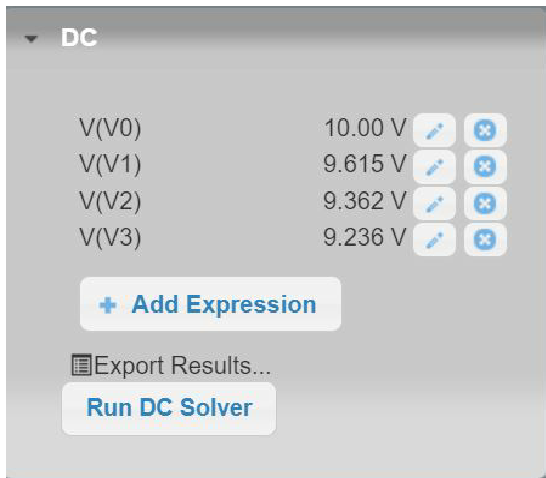5) Check your results in CircuitLab

```
>> V = inv(A)*B
```

```
10.0000  
9.6153  
9.3617  
9.2357
```



6) Assume V_0 is a 10V, 4 rad/sec (0.637Hz)

$$V_0 = 10 \sin(4t)$$


a) Determine the impedances of each element at 4 rad/sec

V_0 :

$$0 \cos(4t) + 10 \sin(4t) \Rightarrow (0 - j10)$$

4mF
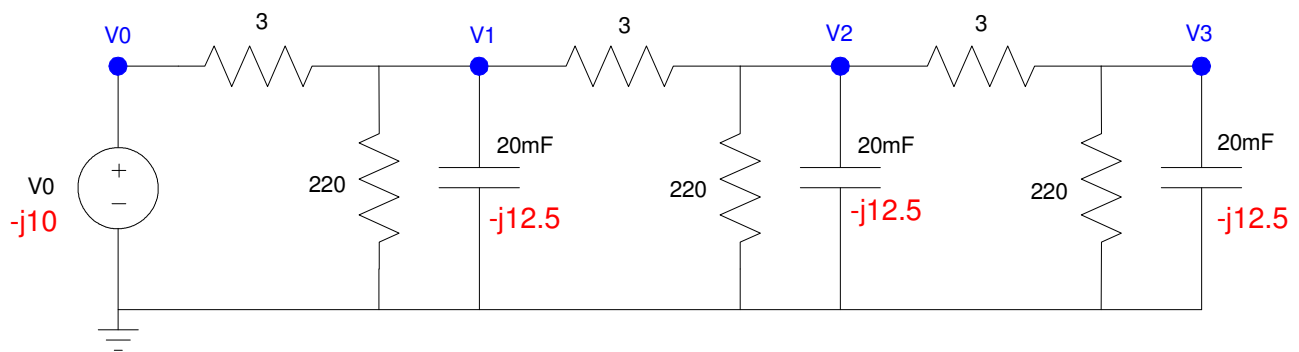
$$C \Rightarrow \frac{1}{j\omega C} = \frac{1}{j(4)(0.02)} = -j12.5\Omega$$



b) Write the voltage node equations

- same as before just add one term for the capacitor

$$V_0 = -j10$$

$$\left(\frac{V_1 - V_0}{3} \right) + \left(\frac{V_1}{220} \right) + \left(\frac{V_1}{-j12.5} \right) + \left(\frac{V_1 - V_2}{3} \right) = 0$$

$$\left(\frac{V_2 - V_1}{3} \right) + \left(\frac{V_2}{220} \right) + \left(\frac{V_2}{-j12.5} \right) + \left(\frac{V_2 - V_3}{3} \right) = 0$$

$$\left(\frac{V_3 - V_2}{3} \right) + \left(\frac{V_3}{220} \right) + \left(\frac{V_3}{-j12.5} \right) = 0$$

c) Solve for V1, V2, and V3 as complex numbers

- same as before just add the capacitor term

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{3}\right) & \left(\frac{2}{3} + \frac{1}{220} + \frac{1}{-j12.5}\right) & \left(\frac{-1}{3}\right) & 0 \\ 0 & \left(\frac{-1}{3}\right) & \left(\frac{2}{3} + \frac{1}{220} + \frac{1}{-j12.5}\right) & \left(\frac{-1}{3}\right) \\ 0 & 0 & \left(\frac{-1}{3}\right) & \left(\frac{1}{3} + \frac{1}{220} + \frac{1}{-j12.5}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

```
A = [1,0,0,0 ];
A = [A ; -1/3,2/3+1/220-1/(j*12.5),-1/3,0 ];
A = [A ; 0,-1/3,2/3+1/220-1/(j*12.5),-1/3 ];
A = [A ; 0,0,-1/3,1/3+1/220-(1/(j*12.5))]
```

```
1.0000          0          0          0
-0.3333          0.6712 + 0.0800i  -0.3333          0
0          -0.3333          0.6712 + 0.0800i  -0.3333
0          0          -0.3333          0.3379 + 0.0800i
```

```
B = [-j*10;0;0;0]
```

```
0 -10.0000i
0
0
0
```

```
V = inv(A)*B
```

```
V =
```



```
V0          0 -10.0000i
V1 -3.1170 - 6.6724i
V2 -4.6750 - 4.1839i
V3 -5.2927 - 2.8745i
```

d) Express V1, V2, and V3 in terms of sine and cosine function:

- hint: $V_1 = a + jb$ (phasor representation) means $V_1(t) = a \cos(4t) - b \sin(4t)$

```
V0 =          0 cos(4t) + 10.0000 sin(4t)
V1 = -3.1170 cos(4t) + 6.6724 sin(4t)
V2 = -4.6750 cos(4t) + 4.1839 sin(4t)
V3 = -5.2927 cos(4t) + 2.8745 sin(4t)
```

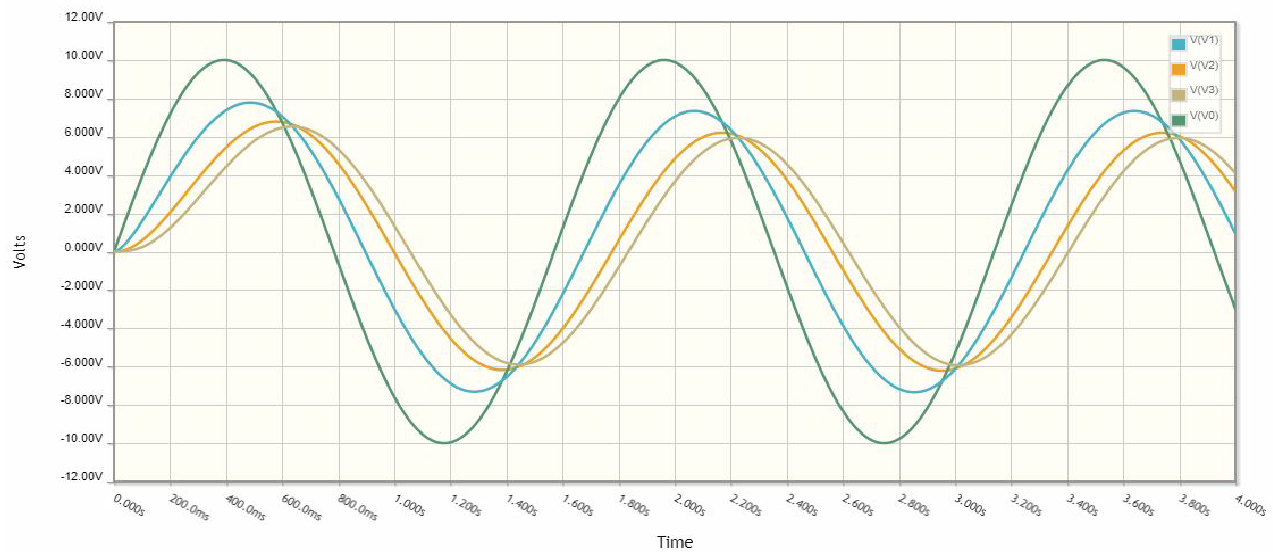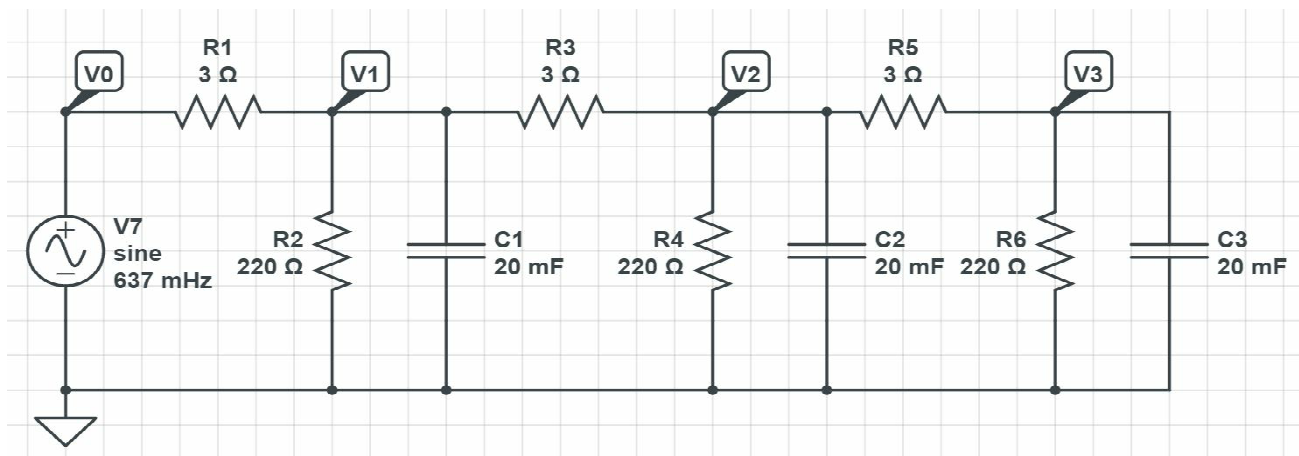7) Check your results in CircuitLab using a transient simulation for 6 seconds



The peak matches the magnitude of the voltages computed in Matlab

```
>> abs(V)
```

```
V0 10.0000  
V1  7.3646  
V2  6.2738  
V3  6.0229
```