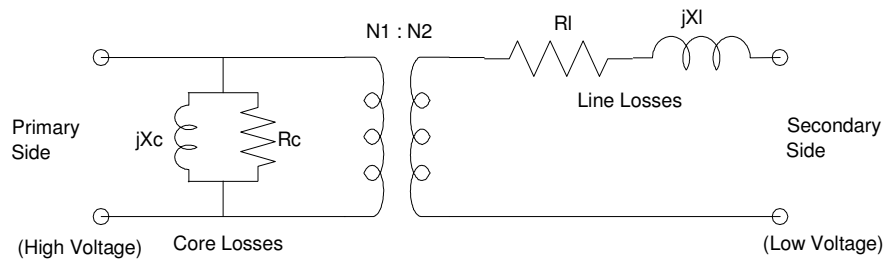


ECE 111: Homework 15

Week #15 - ECE 331 Energy Conversion. Due 8am, Tuesday May 3rd
Please submit as a Word or pdf file to BlackBoard or email to Jacob_Glower@yahoo.com with header ECE 111 HW#15
www.BisonAcademy.com

1) Determine the circuit model for a 9.6kV : 240V transformer is tested with the following test results:



Transformer Model

	V	Power	pf
Open-Circuit Test	V1 = 9.6kV	105 W	0.03
Short-Circuit Test	V2 = 24V	22 W	0.95

Open-Circuit Test (R_c & jX_c)

$$P = V \cdot I \cdot pf$$

$$105W = 9600V \cdot I \cdot 0.03$$

$$I = 0.3646A$$

$$pf = \cos(\theta)$$

$$\theta = 88.2809^\circ$$

$$Z = \left(\frac{V}{I}\right) \angle \theta = \left(\frac{V}{I}\right) \cdot \exp(j\theta)$$

$$Z = 789.94 + j26320$$

This is the series model. To find the parallel model, use $1/Z$

$$\frac{1}{Z} = 1.1393 \cdot 10^{-6} - j3.7960 \cdot 10^{-5}$$

This is the parallel R and X

$$R_c = \left(\frac{1}{1.1393 \cdot 10^{-6}}\right) = 877.71k\Omega$$

$$jX_c = \left(\frac{1}{-j3.7960 \cdot 10^{-5}}\right) = j26.343k\Omega$$

In Matlab

```
>> V = 9600;  
>> P = 105;  
>> I = 105/(9600*0.03)  
  
I = 0.3646  
  
>> Z = (V/I) * exp(j*acos(0.03))  
  
Z = 7.8994e+002 +2.6320e+004i  
  
>> 1/Z  
  
ans = 1.1393e-006 -3.7960e-005i  
  
>> Rc = 1 / real(1/Z)  
  
Rc = 8.7771e+005  
  
>> jXc = 1 / ( j*imag(1/Z) )  
  
jXc = 0 +2.6343e+004i
```


Open-Circuit Test (RL and jXL)

Same procedure but stop at Z

```
>> P = 22;  
>> V = 24;  
>> pf = 0.95;  
>> I = P / (V*pf)  
  
I = 0.9649  
  
>> Z = (V/I) * exp(j*acos(pf))  
  
Z = 23.6291 + 7.7665i
```


$$R_L = 22.629 \text{ Ohms}$$

$$jX_L = j7.7665 \text{ Ohms}$$

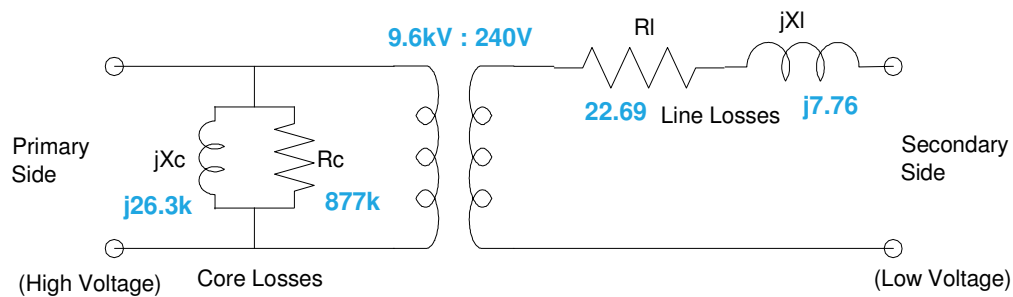

For the utility grid on the back of the page....

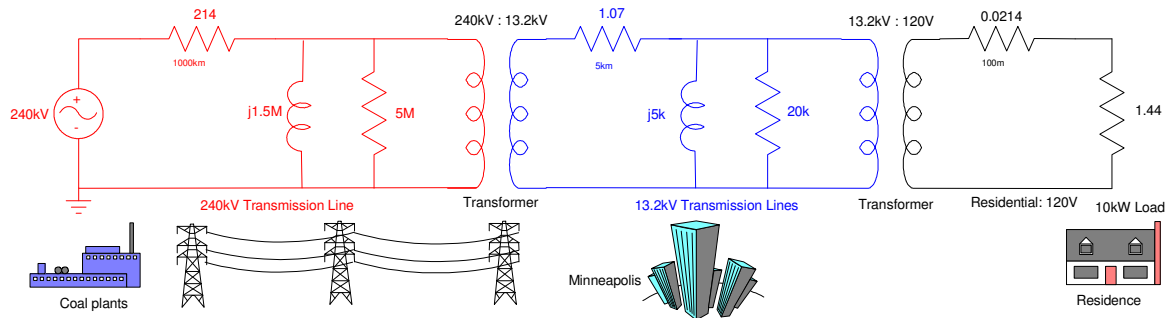2) Convert the voltages and impedances to the 120V node (right side)



240kV section (red)

```
>> V0 = 120;  
>> R01 = 214 * (120/240000)^2  
R01 = 5.3500e-005  
  
>> R1 = 1.5e6 * (120/240000)^2  
R1 = 0.3750  
  
>> X1 = 5e6 * (120/240000)^2  
X1 = 1.2500
```


13.2kV section (blue)

```
>> R12 = 1.07 * (120/13200)^2  
R12 = 8.8430e-005  
  
>> R2 = 20e3 * (120/13200)^2  
R2 = 1.6529  
  
>> X2 = 5e3 * (120/13200)^2  
X2 = 0.4132
```

120V section (black)

```
>> R23 = 0.0214;  
>> R3 = 1.44;
```

3) Determine the voltages at each node

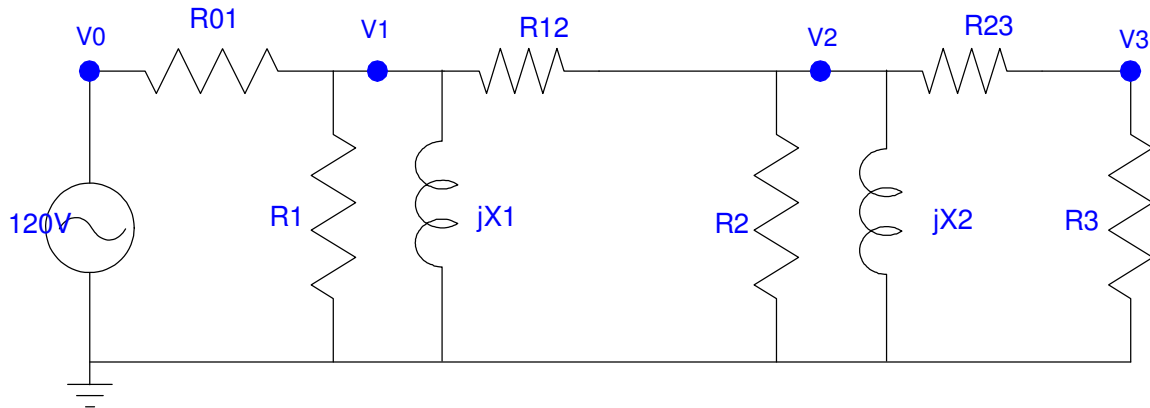

Write the voltage node equations

$$V_0 = 120$$

$$\left(\frac{V_1 - V_0}{R_{01}}\right) + \left(\frac{V_1}{R_1}\right) + \left(\frac{V_1}{jX_1}\right) + \left(\frac{V_1 - V_2}{R_{12}}\right) = 0$$

$$\left(\frac{V_2 - V_1}{R_{12}}\right) + \left(\frac{V_2}{R_2}\right) + \left(\frac{V_2}{jX_2}\right) + \left(\frac{V_2 - V_3}{R_{23}}\right) = 0$$

$$\left(\frac{V_3 - V_2}{R_{23}}\right) + \left(\frac{V_3}{R_3}\right) = 0$$

Group terms

$$V_0 = 120$$

$$\left(\frac{-1}{R_{01}}\right) V_0 + \left(\frac{1}{R_{01}} + \frac{1}{R_1} + \frac{1}{jX_1} + \frac{1}{R_{12}}\right) V_1 + \left(\frac{-1}{R_{12}}\right) V_2 = 0$$

$$\left(\frac{-1}{R_{12}}\right) V_1 + \left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{jX_2} + \frac{1}{R_{23}}\right) V_2 + \left(\frac{-1}{R_{23}}\right) V_3 = 0$$

$$\left(\frac{-1}{R_{23}}\right) V_2 + \left(\frac{1}{R_{23}} + \frac{1}{R_3}\right) V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{R_{01}}\right) & \left(\frac{1}{R_{01}} + \frac{1}{R_1} + \frac{1}{jX_1} + \frac{1}{R_{12}}\right) & \left(\frac{-1}{R_{12}}\right) & 0 \\ 0 & \left(\frac{-1}{R_{12}}\right) & \left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{jX_2} + \frac{1}{R_{23}}\right) & \left(\frac{-1}{R_{23}}\right) \\ 0 & 0 & \left(\frac{-1}{R_{23}}\right) & \left(\frac{1}{R_{23}} + \frac{1}{R_3}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 120 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve using Matlab

```
>> a1 = [1,0,0,0];
>> a2 = [-1/R01, 1/R01+1/R1+1/(j*X1)+1/R12, -1/R12, 0];
>> a3 = [0,-1/R12, 1/R12+1/R2+1/(j*X2)+1/R23,-1/R23];
>> a4 = [0,0,-1/R23,1/R23+1/R3];
>> A = [a1;a2;a3;a4]
```

```
1.0e+004 *
```

```
0.0001          0          0          0
-1.8692         3.0003 - 0.0001i  -1.1308          0
0              -1.1308         1.1356 - 0.0002i  -0.0047
0              0              -0.0047         0.0047
```

```
>> B = [120;0;0;0]
```

```
120
0
0
0
```

```
>> V = inv(A)*B
```

```
V0 120.00 - 000.00i
V1 119.97 + 000.02i
V2 119.96 + 000.05i
V3 118.20 + 000.05i
```


```
>> abs(V)
```

```
V0 120.0000
V1 119.9746
V2 119.9609
V3 118.2043
```

4) Determine the efficiency of this system

- Ignoring the core losses
 - Assumes a large number of customers share these losses
- Including the core losses

Assumes a single customer

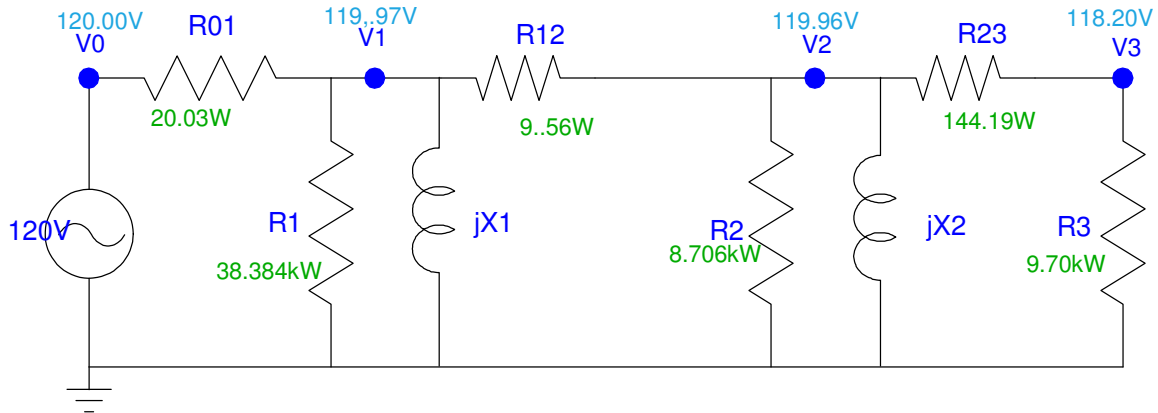

```
>> V0 = V(1);
>> V1 = V(2);
>> V2 = V(3);
>> V3 = V(4);
>> P01 = abs(V0 - V1)^2 / R01

P01 = 20.0352

>> P1 = abs(V1)^2 / R1

P1 = 3.8384e+004

>> P12 = abs(V1 - V2)^2 / R12

P12 = 9.5679

>> P2 = abs(V2)^2 / R2

P2 = 8.7063e+003

>> P23 = abs(V2 - V3)^2 / R23

P23 = 144.1967

>> P3 = abs(V3)^2 / R3

P3 = 9.7030e+003
```

If you include everything, the efficiency is 17%

```
>> eff = P3 / (P01 + P1 + P12 + P2 + P23 + P3)

eff = 0.1703
```

If you ignore the core losses (spread these out of thousands of customers), the efficiency is 98%

$$\gg \text{eff} = P_3 / (P_{01} + P_{12} + P_{23} + P_3)$$

$$\text{eff} = 0.9824$$

Meaning:

- If you only have one customer, you can't afford to transmit power 1000km (the efficiency is too low). If that's the case, tell the customer to buy a generator.
- If you have a large number of customers (1000+), using transformers and Tesla's solution allows you to transmit power at 98% efficiency.

This works due to the transmission line losses being

$$P = I^2 R$$

When you increase the voltage 1000x, the current drops 1000x (power stays constant: $P = VI$).

By reducing the current 1000x, the power losses drop by one million times.

