

# ECE 321: Handout #9


## Butterworth and Chebychev Filters

1) The transfer function for a 4th-order Chebychev filter with a corner at 1 rad/sec is

$$G(s) = \left( \frac{0.639}{(s+0.72\angle\pm 38.5^\circ)(s+1.11\angle\pm 77.8^\circ)} \right)$$

a) Determine R and C for a 4th-order Chebychev filter with a corner at 1 rad/sec

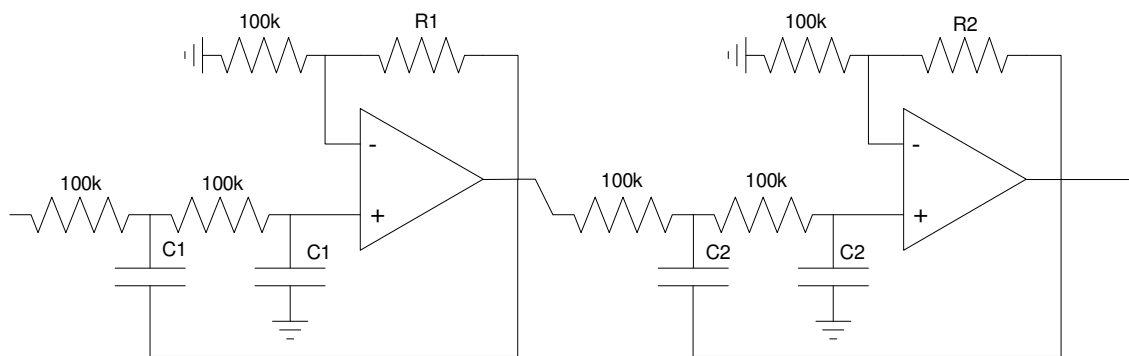b) Determine R and C for a 4th-order Chebychev filter with a corner at 250Hz



## Solution

Treat this as two cascaded filters

$$G(s) = \left( \frac{0.72^2}{(s+0.72\angle\pm 38.5^\circ)} \right) \left( \frac{1.11^2}{(s+1.11\angle\pm 77.8^\circ)} \right)$$

Stage 1:

$$\frac{1}{RC} = 0.72$$

$$R = 100k \quad C = 13.889\mu F$$

$$3 - k = 2 \cos(38.5^\circ)$$

$$k = 1.435 = 1 + \frac{R_a}{R_b}$$


Stage 2:

$$\frac{1}{RC} = 1.11$$

$$R = 100k \quad C = 9.009\mu F$$

$$3 - k = 2 \cos(77.8^\circ)$$

$$k = 2.577 = 1 + \frac{R_a}{R_b}$$

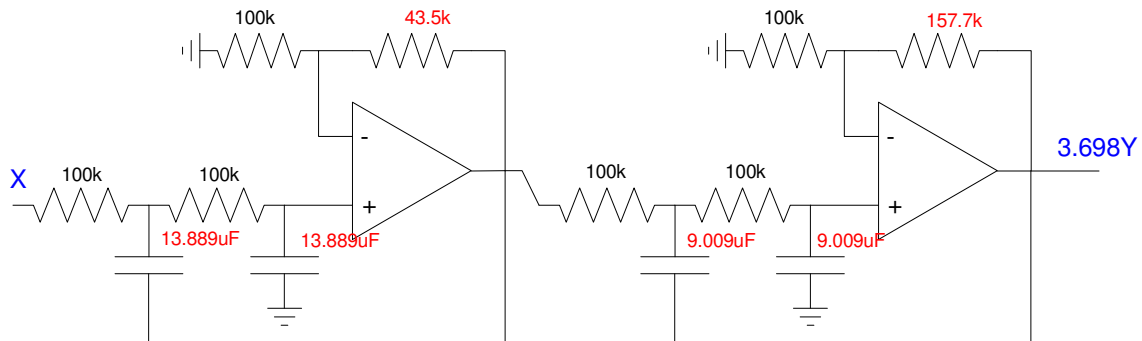

The DC gain is

$$DC = (1.435)(2.577) = 3.698$$

2) Design a 4th-order Butterworth filter with a corner at 250Hz

Solution: It's the same circuit as before, just make the capacitors smaller

$$C(250Hz) \rightarrow \left( \frac{1 \text{ rad/sec}}{250Hz \cdot 2\pi} \right) C = \left( \frac{1}{1570.796} \right) C$$

$$13.889\mu F \rightarrow \left( \frac{13.889\mu F}{1570.796} \right) = 8.84nF$$

$$9.009\mu F \rightarrow \left( \frac{9.009\mu F}{1570.796} \right) = 5.73nF$$

