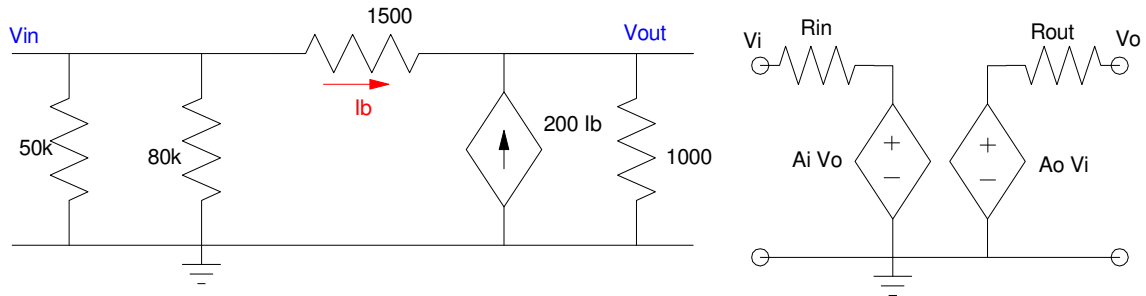


# ECE 321: Handout #13

## 2-Port Models

1) Find the 2-port model for the following circuit




# Solution

## Rin:

- Set  $V_o = 0V$
- Measure the resistance looking in.

$$R_{in} = 50k \parallel 80k \parallel 1500$$

$$R_{in} = 1430\Omega$$

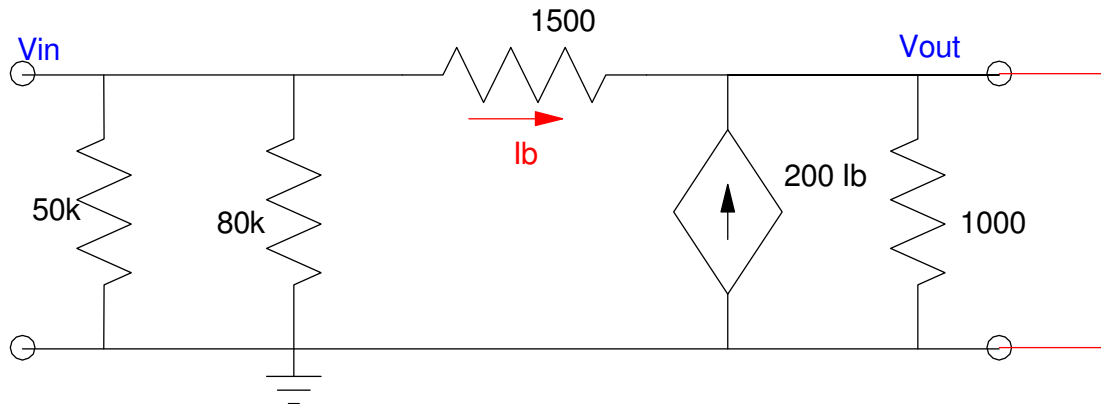


## Ai:

- Set  $V_o = 1V$
- Measure the voltage at  $V_{in}$

$$V_{in} = \left( \frac{50k \parallel 80k}{50k \parallel 80k + 1500} \right) \cdot 1V$$

$$V_{in} = 0.9535V$$

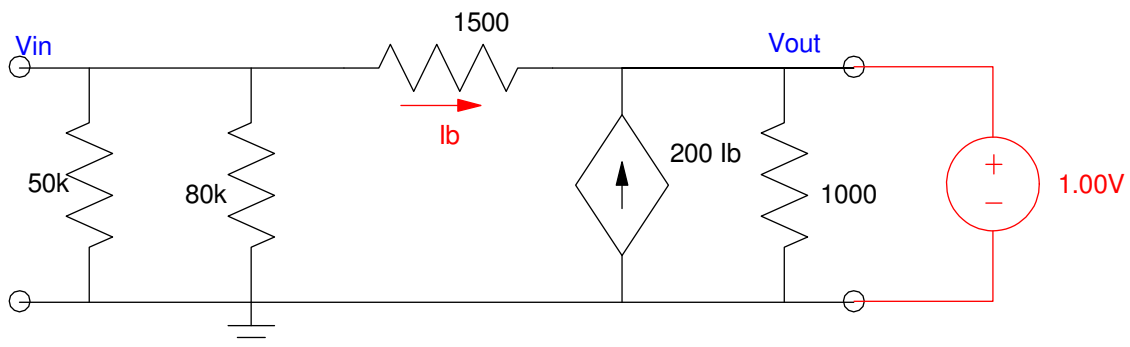


Rout:

- Short  $V_{in}$
- Measure the resistance at  $V_{out}$ . If this isn't obvious,
- Apply +1V to  $V_{out}$  and compute the current

$$I = \left( \frac{1V-0V}{1500} \right) + \left( \frac{1V}{1000} \right) - 200 \left( \frac{0V-1V}{1500} \right)$$

$$I = \left( \frac{1V-0V}{1500} \right) + \left( \frac{1V}{1000} \right) + 200 \left( \frac{1V-0V}{1500} \right) = 135.0mA$$
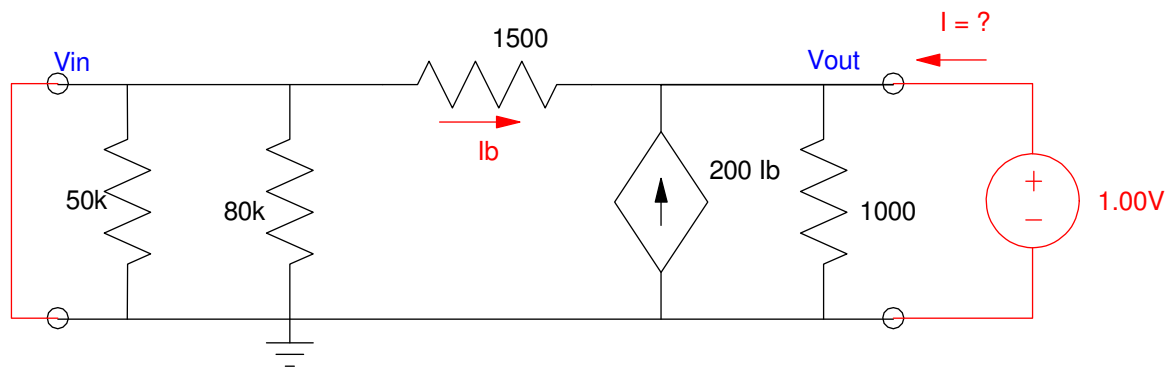
$$R_{out} = \frac{1V}{135mA} = 7.407\Omega$$



Aout: Apply 1V at the input, measure  $V_{out}$

Writing the voltage node equation at  $V_{out}$

$$\left( \frac{V_o-1}{1500} \right) + \left( \frac{V_o}{1000} \right) - 200 \left( \frac{1-V_o}{1500} \right) = 0$$

$$V_o = 0.9926V$$

