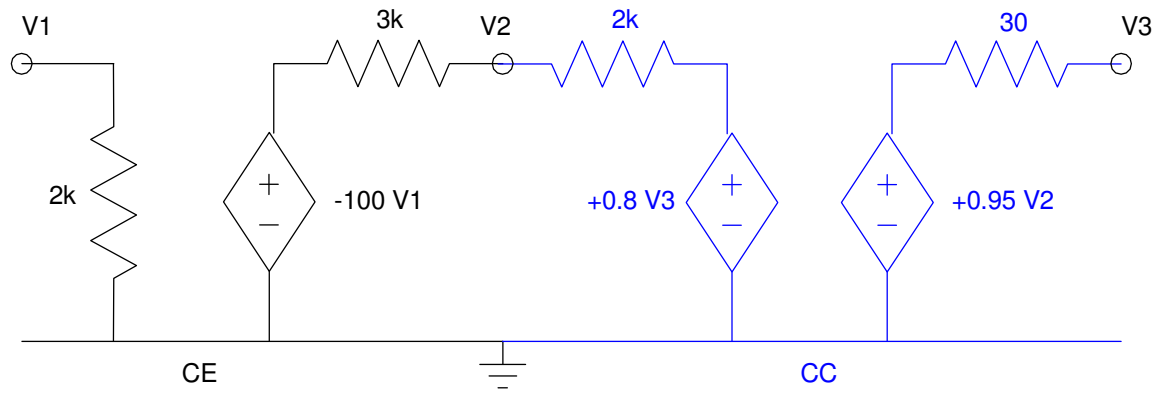


ECE 321: Handout #16

Multi-Stage Amplifiers


Determine the 2-port model for a CE : CC amplifier



Solution:

By inspection

- $R_{in} = 2k$
- $A_i = 0$

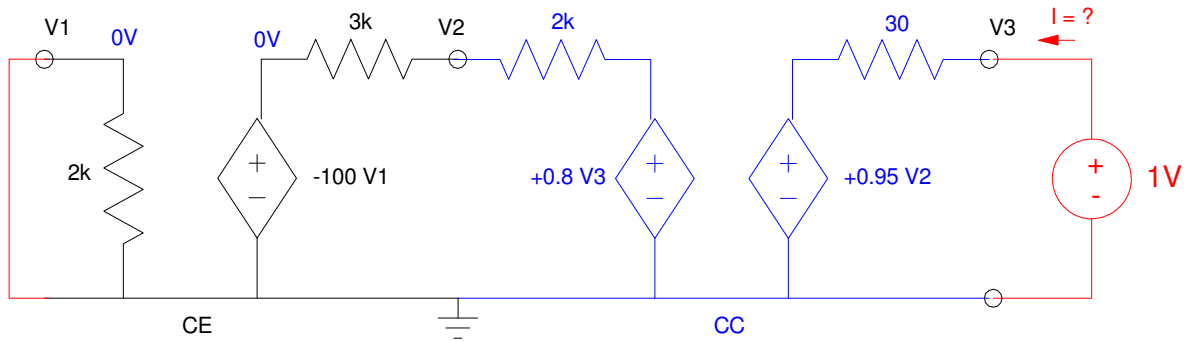

Rout:

- Tie V1 to ground
- Connect 1V to V3
- Compute the current

By voltage division, V2 is...

$$V_2 = \left(\frac{3k}{3k+2k} \right) \cdot 0.8V$$

$$V_2 = 0.48V$$


I is then

$$I = \left(\frac{1V-0.48V}{30} \right) = 17.33mA$$

$$R_{out} = \frac{1V}{17.33mA} = 57.69\Omega$$

Ao:

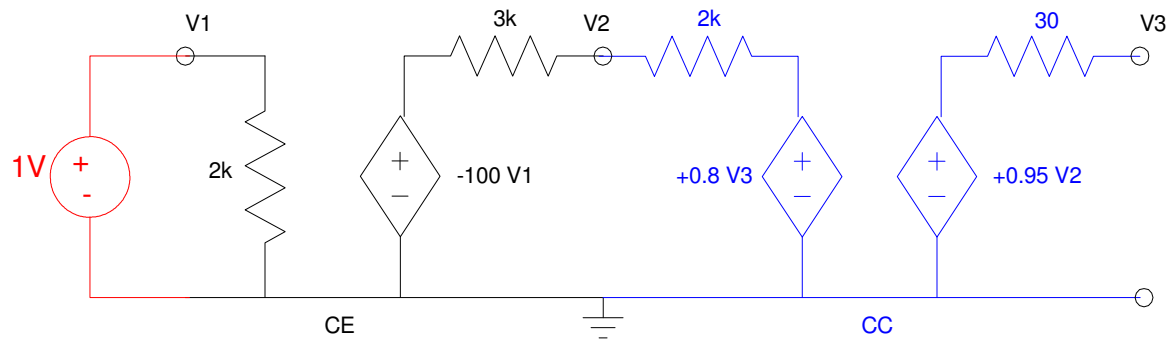- Connect V_{in} to +1V
- Compute V_{out}



Writing the voltage node equation at V_2

$$\left(\frac{V_2 - (-100)}{3k} \right) + \left(\frac{V_2 - 0.8V_3}{2k} \right) = 0$$

$$V_3 = 0.95V_2$$

Substituting

$$\left(\frac{V_2 + 100}{3} \right) + \left(\frac{V_2 - 0.8 \cdot 0.95V_2}{2} \right) = 0$$

$$V_2 = -73.53V$$

Then

$$V_3 = 0.95V_2 = -69.85$$

The resulting 2-port model is then

