

ECE 321 - Homework #1

revised: November 4, 2021

Op Amp Amplifiers, Push-Pull Amplifiers. Due Monday, November 8th

Please make the subject "ECE 321 HW#1" if submitting homework electronically to Jacob_Glower@yahoo.com (or on blackboard)

For all problems, assume you are using

- MCP602 Op Amps (max current = 50mA)
- 2SC6144 transistors ($\beta = 200$, 10A max, $V_{be} = 0.7V$)

Amplifier:

Design a circuit to implement

1a) $Y = +3X$

1b) $Y = -3X$

1c) $Y = 12 - 4X$

Mixer

2) Design a circuit to mix three signals together:

- $Y = 6A + 1B + 3C$

Push-Pull Amplifier

3) Design a circuit so that $Y = X$


- $X = -5V$ to $+5V$, 10mA max
- $Y = -5V$ to $+5V$, 200mA (25 ohm speaker (net))

4) Simulate in CircuitLab

Lab (Hardware)

The following circuit

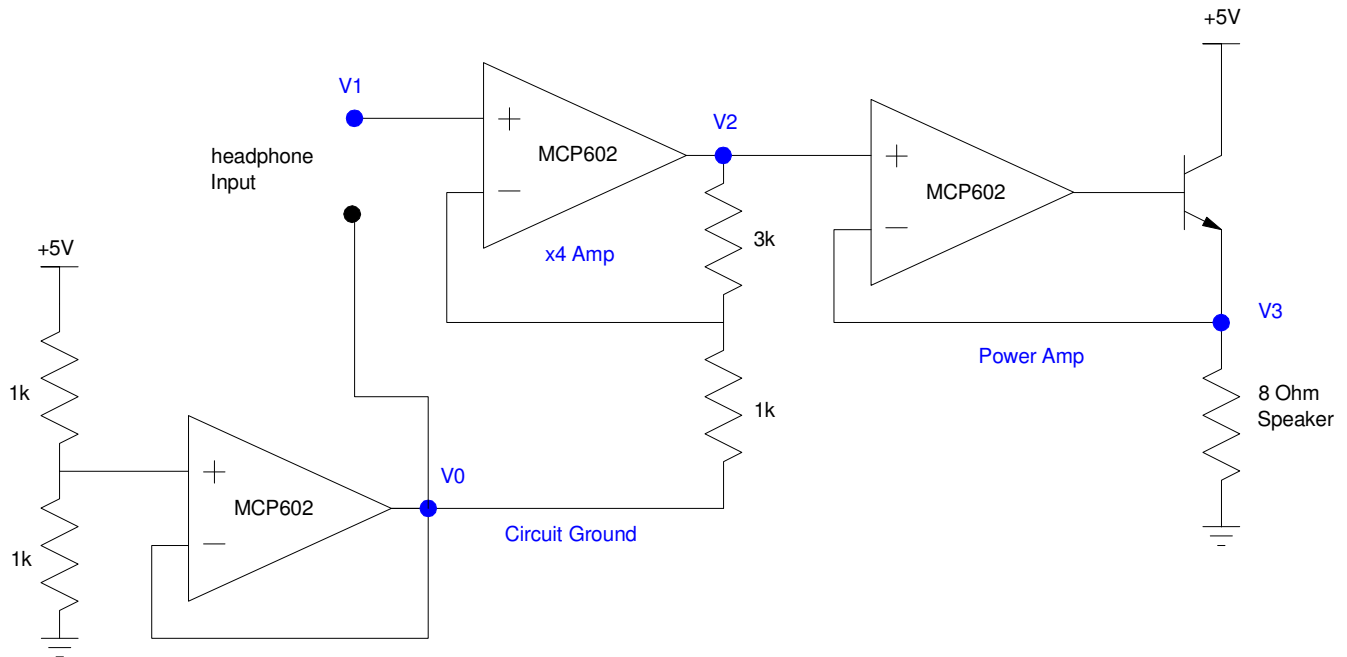- Creates a 2.5V power supply from a single +5V supply (V0). This 2.5V supply then acts like circuit ground
- Amplifies the output of a cell phone (or computer or 555 timer) (V1), and
- Drives an 8 Ohm speaker (V3)



5) Calculate the voltages and currents when

- $V1 = 1.5V$
- $V1 = 2.5V$
- $V1 = 3.5V$

6) Simulate this circuit in CircuitLab with

- $V1 = 1V_{pp}$, 1kHz sine wave

7) Build this circuit in hardware. With a sine wave input, (1kHz) verify that that

- $V2 = 4 \cdot V1$ (relative to circuit ground)
- $V3 = V2$ (relative to circuit ground)

8) Demo

- Replace V1 with an audio signal and verify the song plays on the speaker