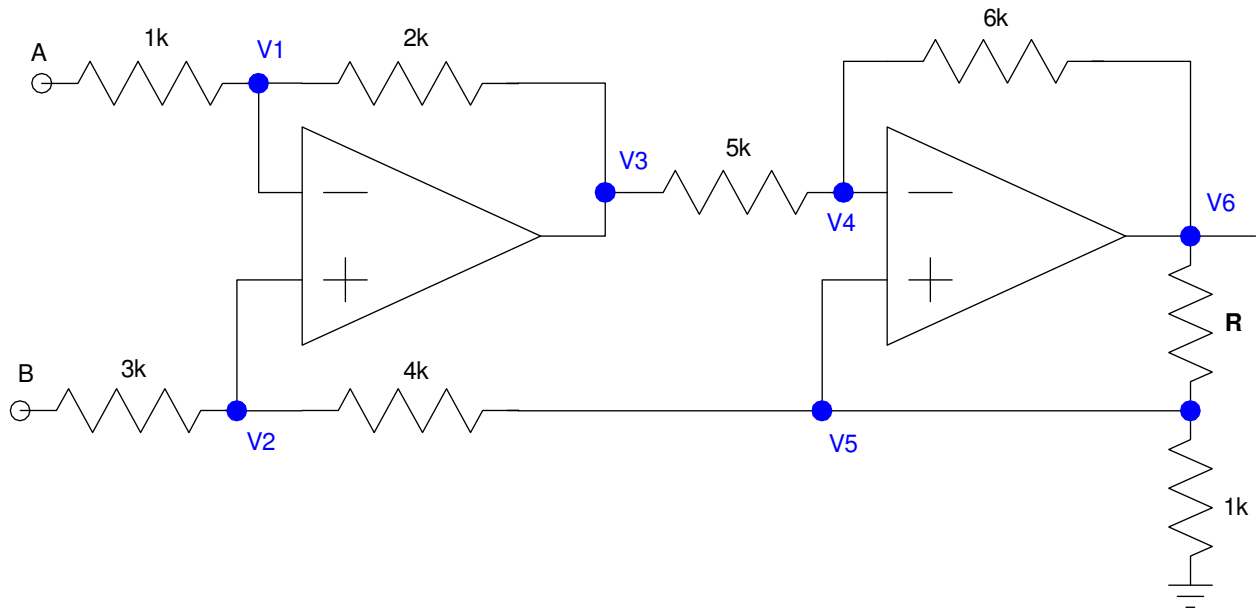


# ECE 321 - Quiz #1 - Name \_\_\_\_\_

Op-Amp Amplifiers & mixers., Push-Pull Amplifiers


1) Give 6 equations which allow you to solve for the 6 unknown voltages. You do not need to solve.

- Assume ideal op-amps.
- Assume  $R = 1100 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$ . For example, May 14th gives  $R = 1614$ .



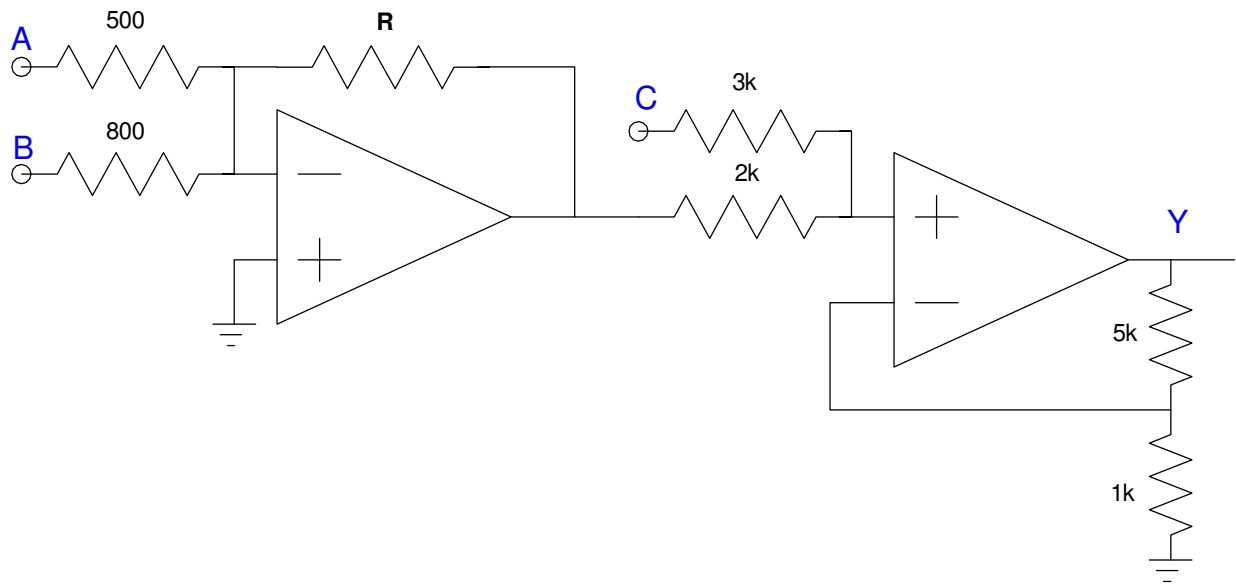2) Determine Y as a function of A, B, and C.

- Assume ideal op-amps
- Assume  $R = 1100 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$ . For example, May 14th gives  $R = 1614$ .



3) Design a circuit which outputs

$$Y = 5A + 2B + 7C$$

*note: the gain on C is positive*

4) Design a circuit which outputs


$$Y = 5A + 2B - 7C$$

*note: the gain on C is negative*

5) Determine the voltages and currents for the following push-pull amplifier. Assume

- Ideal op-amps
- $R = 1100 + 100 * (\text{your birth month}) + (\text{your birth day})$
- TIP31 and TIP32 transistors:
  - $\beta = 200$
  - $|V_{be}| = 0.7V$

R	V1	V2	V3	I4	I5
$1100 + 100 * \text{mo} + \text{day}$					

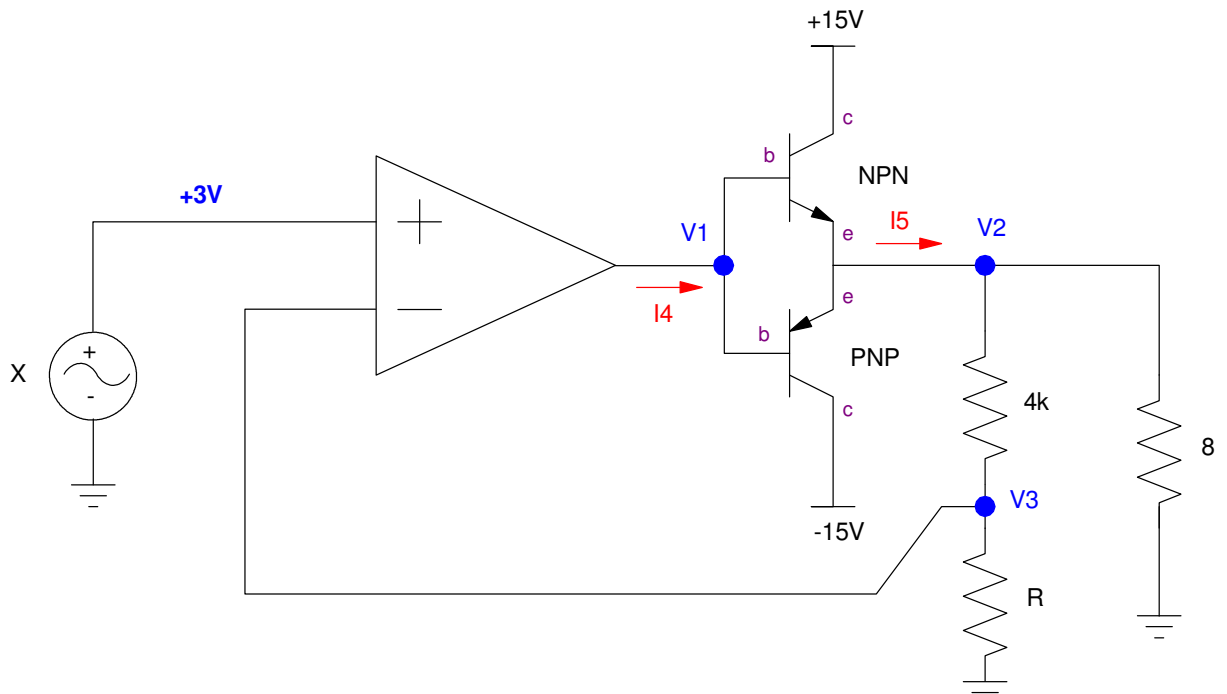

6) Determine the voltages and currents for the following push-pull amplifier. Assume

- Ideal op-amps
- $R = 1100 + 100 * (\text{your birth month}) + (\text{your birth day})$
- TIP31 and TIP32 transistors:
  - $\beta = 200$
  - $|V_{be}| = 0.7V$

R	V1	V2	V3	I4	I5	I6
$1100 + 100 * \text{mo} + \text{day}$						

