



ECE 321 - Quiz #3 - Name _____

BJT Amplifiers & 2-Port Models

1) BJT Amplifier: DC Analysis. Determine the Thevenin equivalent of R1 and R2 as well as the Q-point. Assume ideal silicon transistors:

- $V_{be} = 0.7V$
- $\beta = 40$
- $R_2 = 1100 + 100 * (\text{your birth month}) + (\text{your birth day})$. May 14th would give $R = 1614$ Ohms

R2	Vb	Rb	Vce	Ic
$1100 + 100 * \text{mo} + \text{day}$				

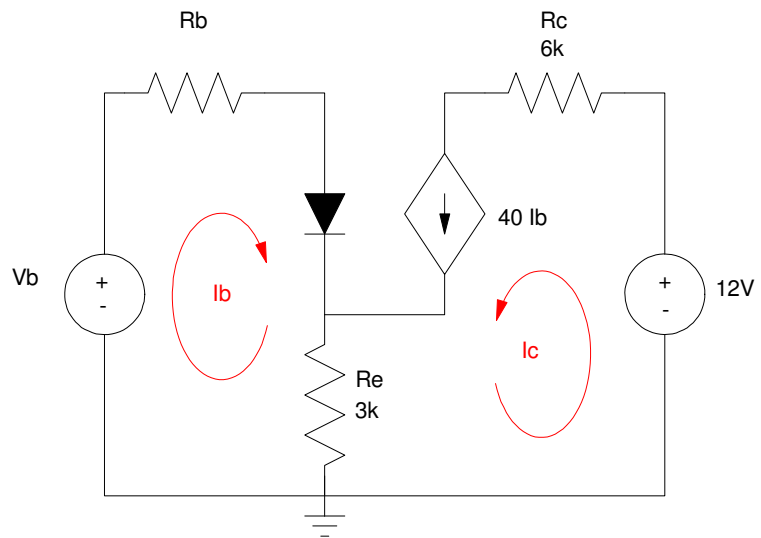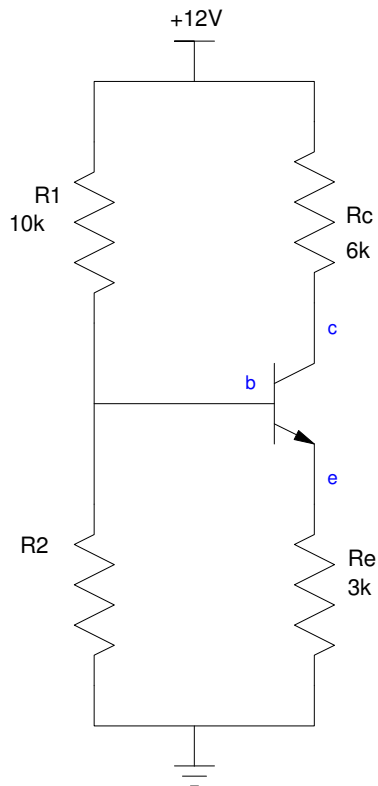



2) BJT Amplifier: DC Design. Determine R1 and R2 so that

- The Q point is $V_{ce} = 6.00V$ and
- The Q point is stabilized for variations in β

Assume


- Ideal silicon transistors ($V_{be} = 0.7V$, $\beta = 40$)
- $R_c = 1100 + 100 * (\text{birth month}) + (\text{birth day})$. May 14th gives $R_c = 1614 \text{ Ohms}$

R_c 1100 + 100*mo + day	R1	R2	V_b	Rb

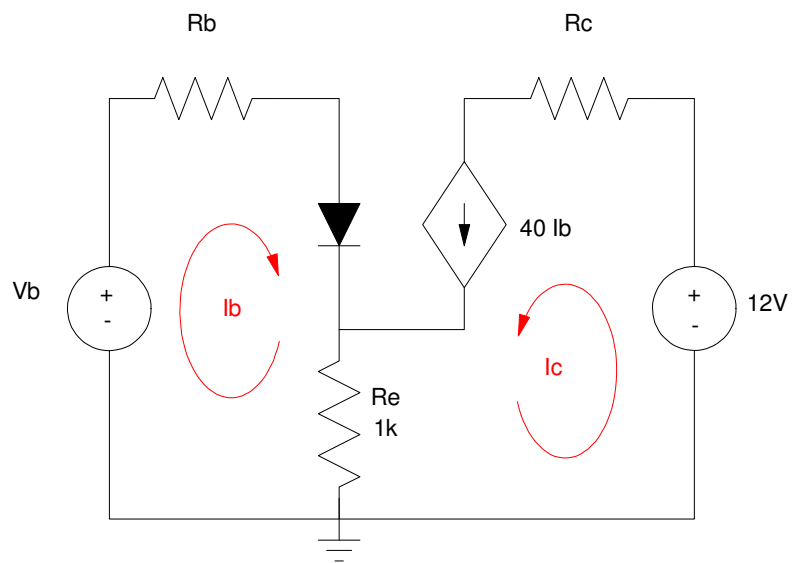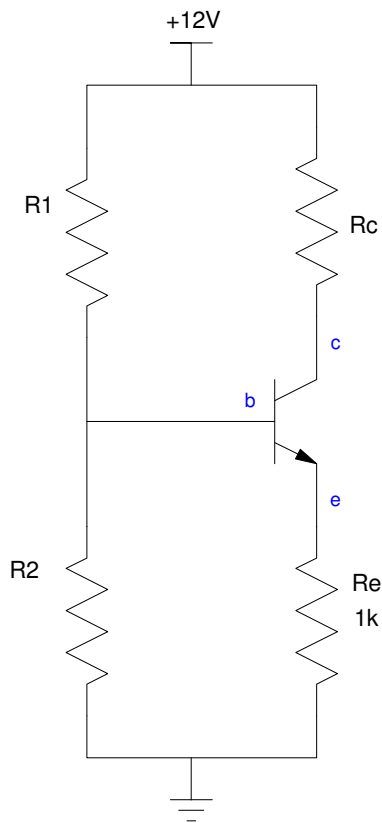


3) BJT: AC Analysis: Draw the small signal model for the following BJT amplifier. Assume

- $r_f = 1500\Omega$
- $\beta = 40$

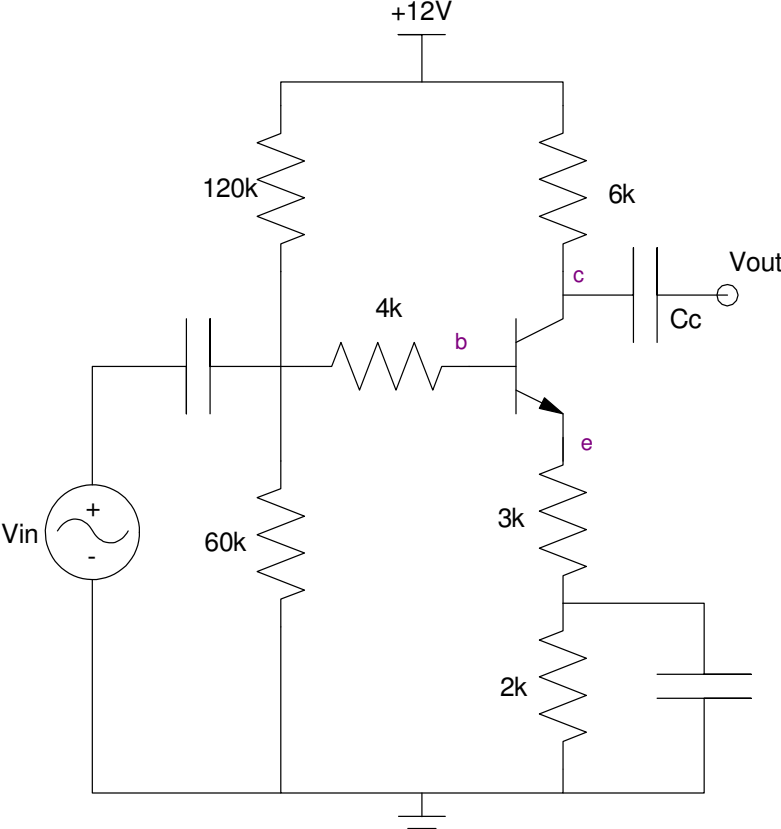

4) 2-Port Models. Determine the 2-port model for the following circuit:

R	R _{in}	A _{in}	R _{out}	A _o
1100 + 100*mo + day				

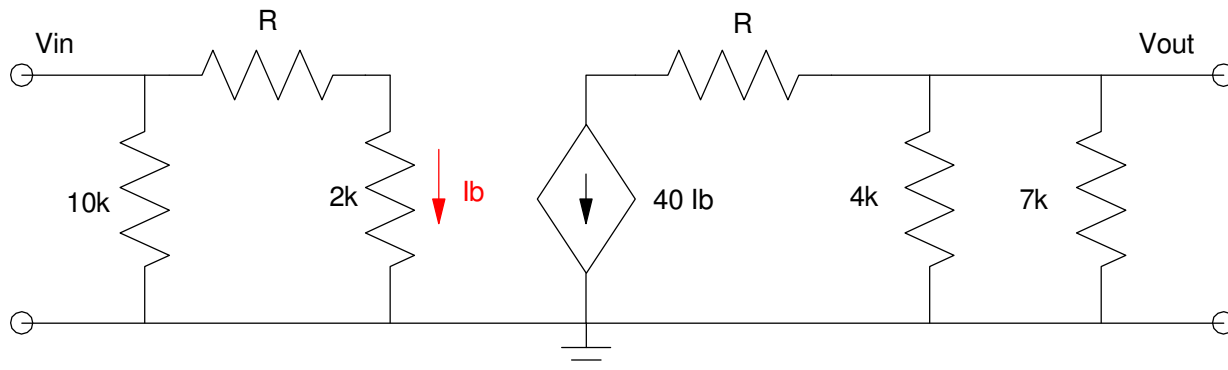

5) 2-Port model (experimental): Determine the 2-port parameters based upon the following experimental data:

Case 1:

- $V_{in} = 1\text{mV @ } 1\text{kHz}$
- $R_1 = 0\text{ Ohms}$
- $R_2 = 10\text{M Ohms}$

results in $V_{out} = 57\text{mV}$

Case 2:

- $V_{in} = 1\text{mV @ } 1\text{kHz}$
- $R_1 = X\text{ Ohms}$
- $R_2 = 10\text{M Ohms}$

results in $V_{out} = 43\text{mV}$

Case 3


- $V_{in} = 1\text{mV @ } 1\text{kHz}$
- $R_1 = 0\text{ Ohms}$
- $R_2 = X\text{ Ohms}$

results in $V_{out} = 37\text{mV}$

Assume

- $X = 1100 + 100 * (\text{your birth month}) + (\text{your birth date})\text{ Ohms}$
- $A_i = 0$

X 1100 + 100*mo + day	R _{in}	A _i	R _{out}	A _o
		0		

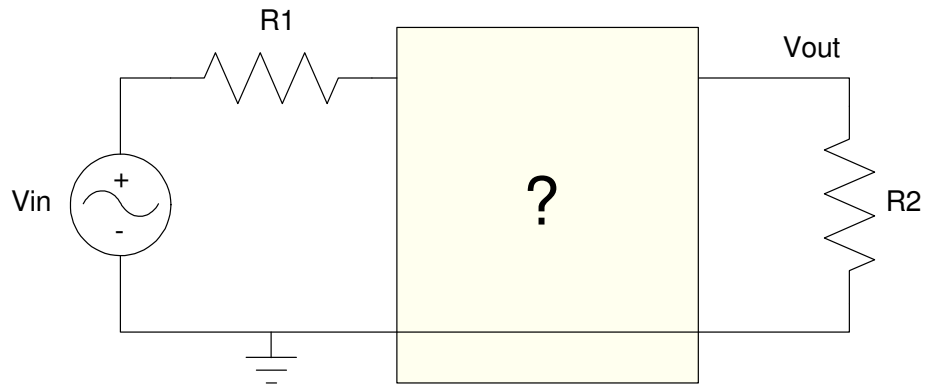

6) Assume X and Y are related by the following transfer function

$$Y = \left(\frac{100(s+m)}{(s^3+ms^2+ds+10)} \right) X$$

$$x(t) = 4 + 5 \cos(mt) + d \sin(mt)$$

where

- m is your birth month (1..12), and
- d is your birth date (1..31)

Find y(t)

m birth month (1..12)	d birth date (1..31)	y(t)