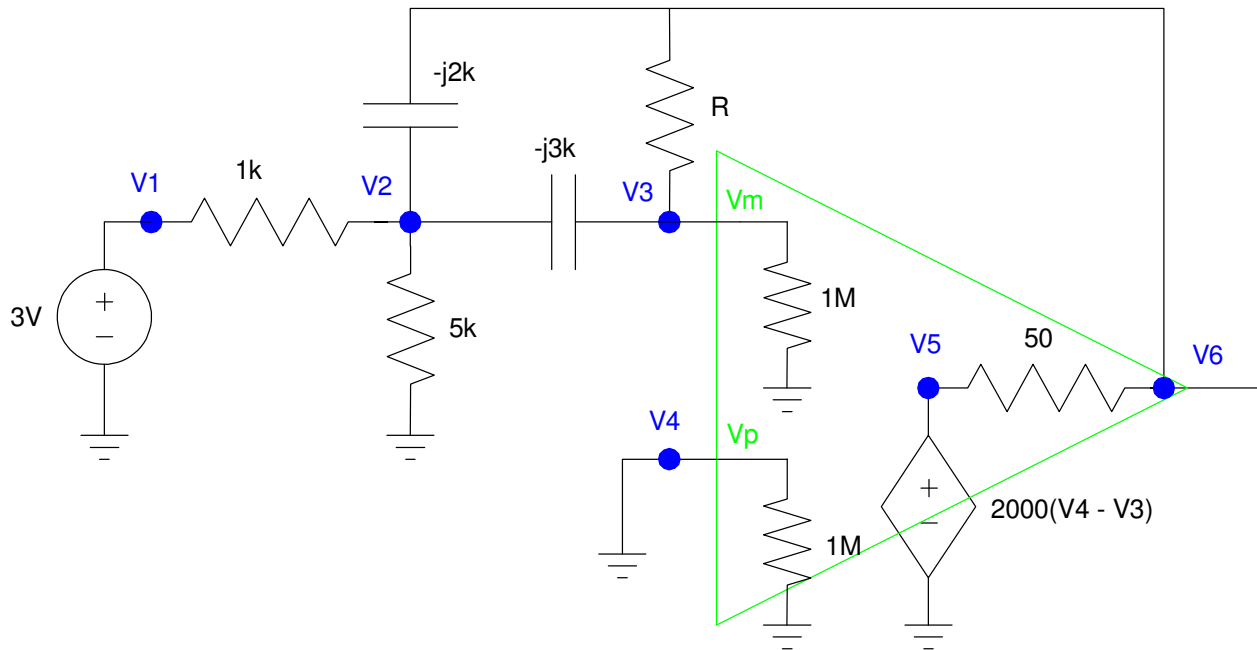


ECE 321 - Quiz #1 - Name _____

Op-Amp Amplifiers & mixers. Due midnight, April 9th
Open-Book. Open Notes. Calculators, Matlab permitted.

1) **Non-Ideal Op Amp:** Write the voltage node equations for V1..V5. You don't need to solve

- Assume $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514$.



$$V_1 = 3$$

$$\left(\frac{V_2 - V_1}{1k}\right) + \left(\frac{V_2 - V_6}{-j2k}\right) + \left(\frac{V_2 - V_3}{-j3k}\right) + \left(\frac{V_2}{5k}\right) = 0$$

$$\left(\frac{V_3 - V_2}{-j3k}\right) + \left(\frac{V_3 - V_6}{R}\right) + \left(\frac{V_3}{1M}\right) = 0$$


$$V_4 = 0$$

$$V_5 = 2000(V_4 - V_3)$$

$$\left(\frac{V_6 - V_2}{-j2k}\right) + \left(\frac{V_6 - V_3}{R}\right) + \left(\frac{V_6 - V_5}{50}\right) = 0$$

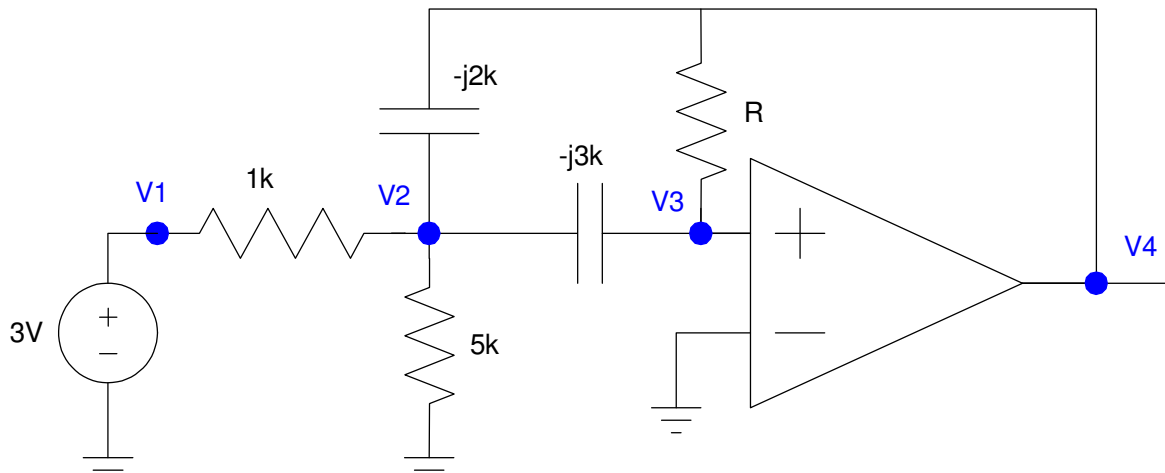2) **Ideal Op-Amp.** Give 4 equations which allow you to solve for the four unknown voltages. You do not need to solve.

- Assume ideal op-amps.
- Assume $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514$.



$$V_1 = 3$$

$$\left(\frac{V_2 - V_1}{1k} \right) + \left(\frac{V_2 - V_6}{-j2k} \right) + \left(\frac{V_2 - V_3}{-j3k} \right) + \left(\frac{V_2}{5k} \right) = 0$$


$$\left(\frac{V_3 - V_2}{-j3k} \right) + \left(\frac{V_3 - V_6}{R} \right) + \left(\frac{V_3}{1M} \right) = 0$$

$$(V_p = V_m)$$

$$V_3 = 0$$

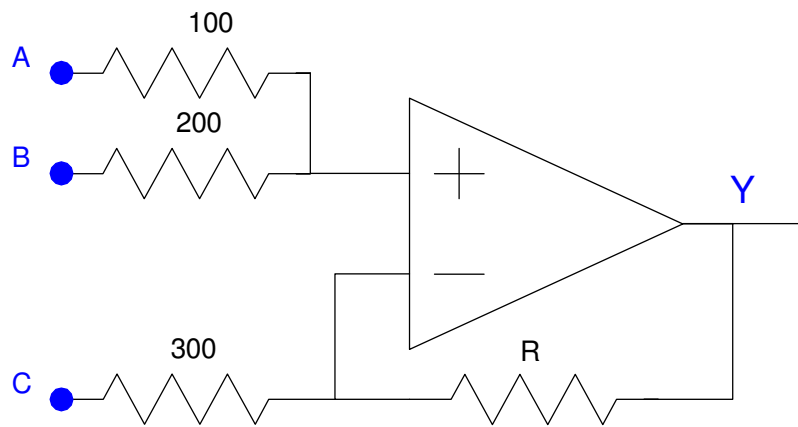3) Determine Y as a function of A, B, and C.

- Assume ideal op-amps
- Assume $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514$.



By superposition: $B = C = 0$

$$V_p = \left(\frac{2}{3}\right)A$$

$$Y = \left(1 + \frac{R}{300}\right)V_p = \left(1 + \frac{R}{300}\right)\left(\frac{2}{3}\right)A$$

$A = C = 0$

$$V_p = \left(\frac{1}{3}\right)B$$

$$Y = \left(1 + \frac{R}{300}\right)\left(\frac{1}{3}\right)B$$

$A = B = 0$

$$Y = -\left(\frac{R}{300}\right)C$$

By superposition

$$Y = \left(1 + \frac{R}{300}\right)\left(\frac{2}{3}\right)A + \left(1 + \frac{R}{300}\right)\left(\frac{1}{3}\right)B - \left(\frac{R}{300}\right)C$$


$R = 1514$ Ohms

$$Y = 4.0311A + 2.0156B - 5.0467C$$

4) Determine the voltages V1..V7 for the following circuit.

- Assume ideal op-amps.
- Assume $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514$.

V1	V2	V3	V4	V5	V6	V7
5.321V	4V	2V	0.679V	3.547V	3.547V	9.294V

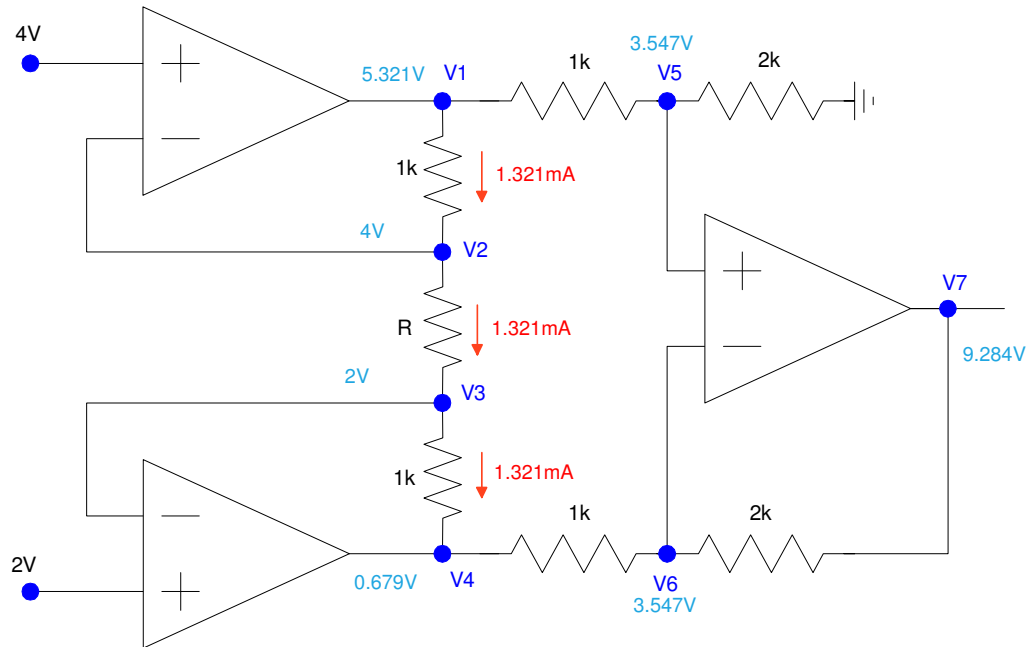

With negative feedback, $V_p = V_m$

- $V_2 = 4V$
- $V_3 = 2V$
- $V_5 = V_6$

The current from V2 to V3 is

$$I = \left(\frac{4V - 2V}{1514} \right) = 1.321mA$$

$$V_1 = V_2 + 1k \cdot I = 5.321V$$

$$V_4 = 2 - 1k \cdot I = 0.679V$$

$$V_5 = \left(\frac{2}{3} \right) V_1 = 3.547V$$

To find V7, two approaches

$$\left(\frac{V_6 - V_4}{1k} \right) + \left(\frac{V_6 - V_7}{2k} \right) = 0$$

or note that the last stage is an instrumentation amplifier with a gain of 2

$$V_7 = 2(V_1 - V_4)$$


5) Design a circuit to implement

$$Y = 2X - 4$$

Many solutions. If you use an instrumentation amplifier, rewrite as

$$Y = 2(X - 2)$$
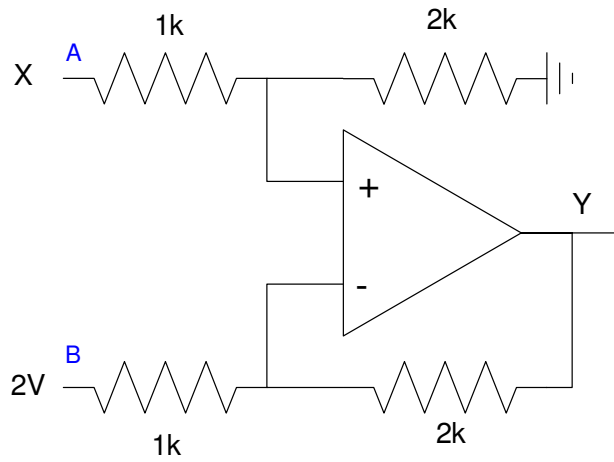
$$Y = \left(\frac{R_1}{R_2}\right)(A - B)$$





6) Design a circuit to implement

$$Y = 2A - 3B$$

There are many solutions. Using an instrumentation amplifier

$$Y = 3\left(\frac{2}{3}A - B\right)$$

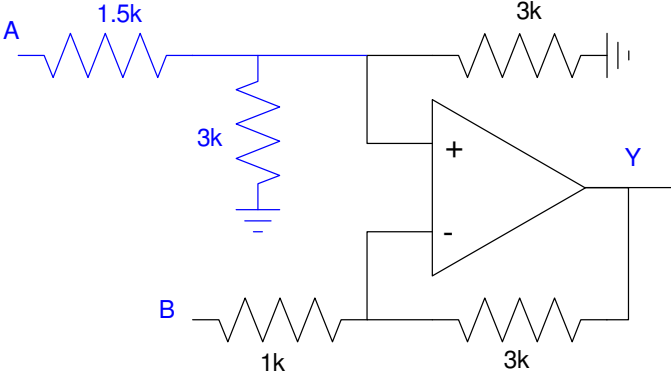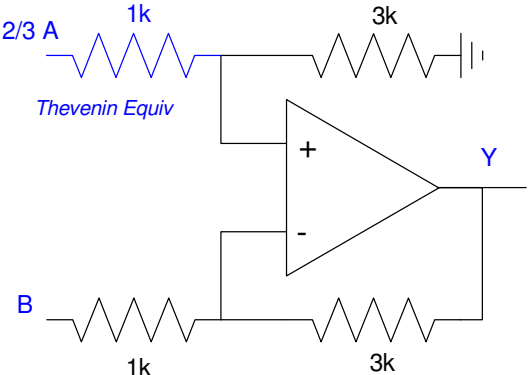

Using inverting amplifiers

