

ECE 321 - Quiz #2 - Name _____

Push-Pull Amplifiers, Temperature Sensors. Calculators, Matlab permitted.

1) Push-Pull Amplifier: Voltage Output. Assume ideal silicon diodes and ideal silicon transistors with


- $V_{be} = 0.7V$
- Current gain = $\beta = 50$
- $V_{ce(sat)} = 0.2V$

Also assume that

- All voltages are limited to -15V to +15V.
- $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514$ Ohms

Determine the voltages and currents when $X = +3V$.

R 1000 + 100*Mo + Day	V1	V2	V3	I4	I5
1514	8.224V $V_2 + 0.7V$	7.524V $(1 + R/1k) V_3$	3V $V_p = V_m$	18.5mA	945.8mA

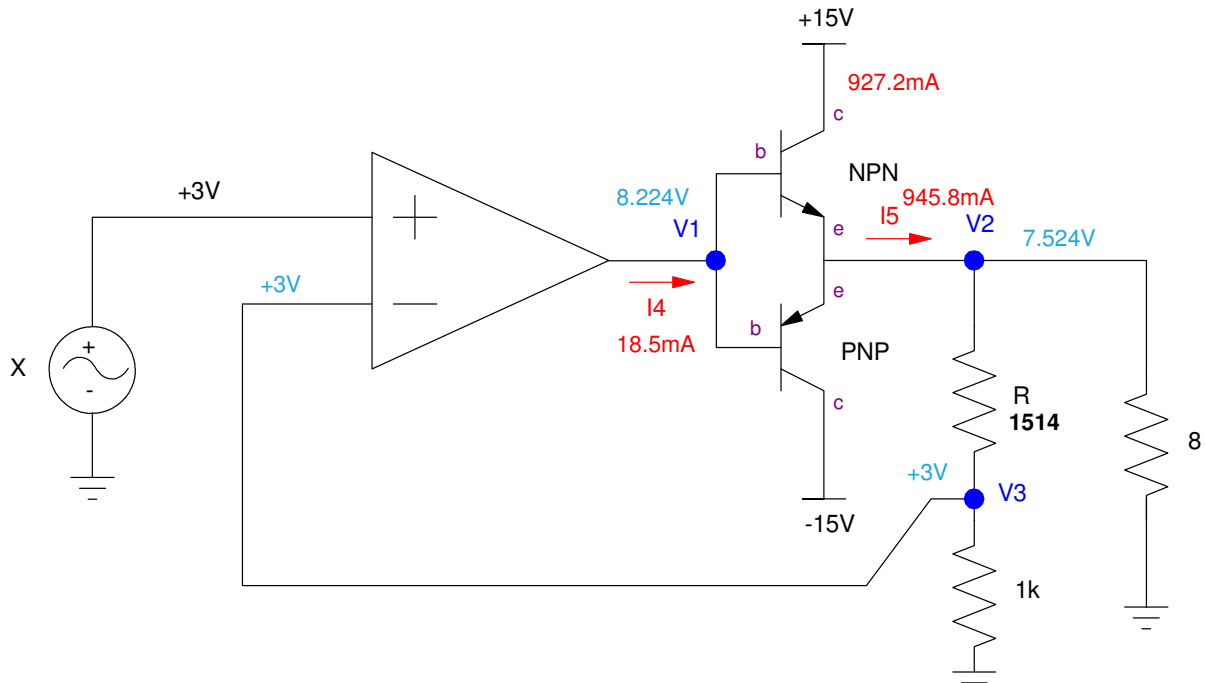

$$V_3 = V_m = V_p = 3V$$

$$V_2 = \left(1 + \frac{1514}{1000}\right) V_3 = 7.524V$$

$$V_1 = V_2 + 0.7V = 8.224V$$

$$I_5 = \left(\frac{V_2}{R+1000}\right) + \left(\frac{V_2}{8}\right) = 945.8mA$$

$$I_4 = \left(\frac{1}{\beta+1}\right) I_5 = 18.5mA$$

2) Push-Pull Amplifier: Voltage Output. Assume ideal silicon diodes and ideal silicon transistors with


- $V_{be} = 0.7V$
- Current gain = $\beta = 50$
- $V_{ce(sat)} = 0.2V$

Also assume that

- The push-pull amplifier is fed by +5V and -5V,
- The op-amp's output is limited to 0V to +5V, and
- $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514$ Ohms

Determine the voltages and currents when $X = +3V$.

R 1000 + 100*Mo + Day	V1	V2	V3	I4	I5
1514	5.00V power supply limit	4.30V $V1 - 0.7V$	1.710V voltage division	10.6mA	539.2mA

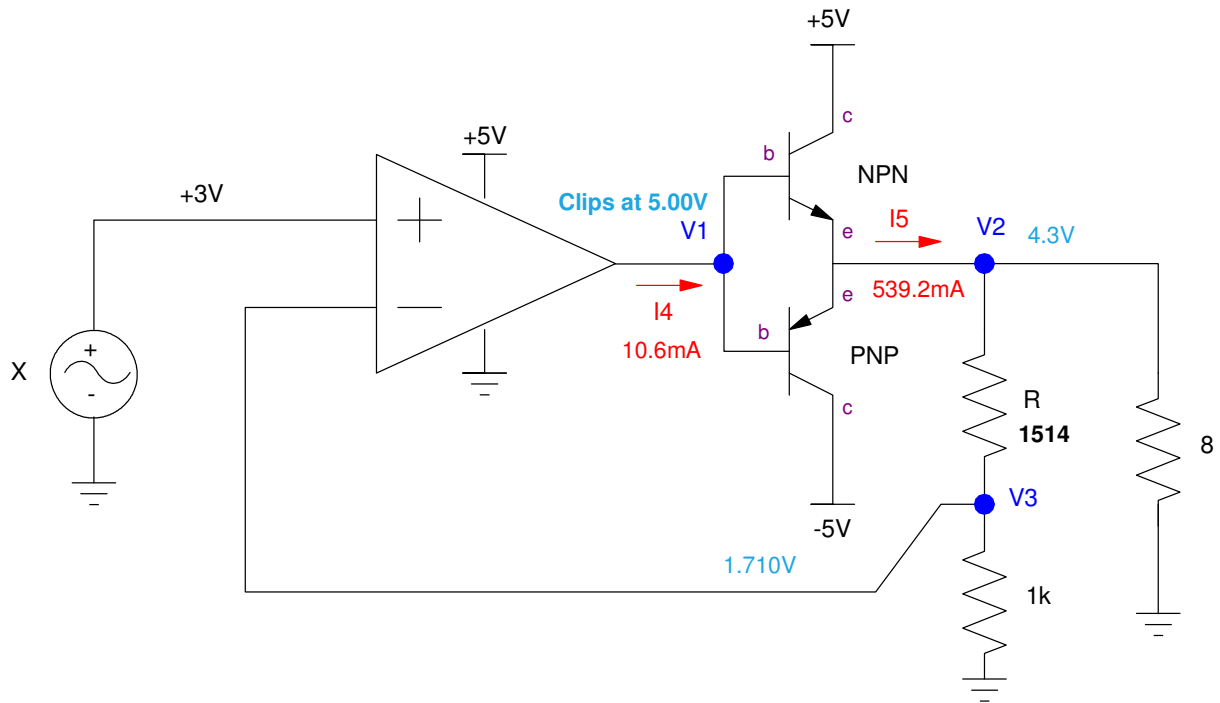

The op-amp *tries* to force $V_p = V_m$. To do this, you need the results from problem #1. ($V1 = 8.22V$). $V1$ clips at +5V due to the power supply limit, resulting in $V1 = 5V$.

$$V2 = V1 - 0.7V = 4.3V$$

$$V3 = 1.710V \text{ by voltage division}$$

Note that V_p is no longer equal to V_m . The op-amp does the best it can given the power supply limitation


3) Push-Pull Amplifier: Current Output. Assume ideal silicon diodes and ideal silicon transistors with

- $|V_{be}| = 0.7V$
- Current gain = $\beta = 50$
- $|V_{ce(sat)}| = 0.2V$

Determine the voltages and currents when $X = +2V$. Assume

- $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514$ Ohms

R 1000 + 100*Mo + Day	V1	V2	V3	I4	I5
1514	4.60V V2 + 0.7V	3.90V V3 + 1.9V	2.00V Vp = Vm	26.42uA	1.321mA

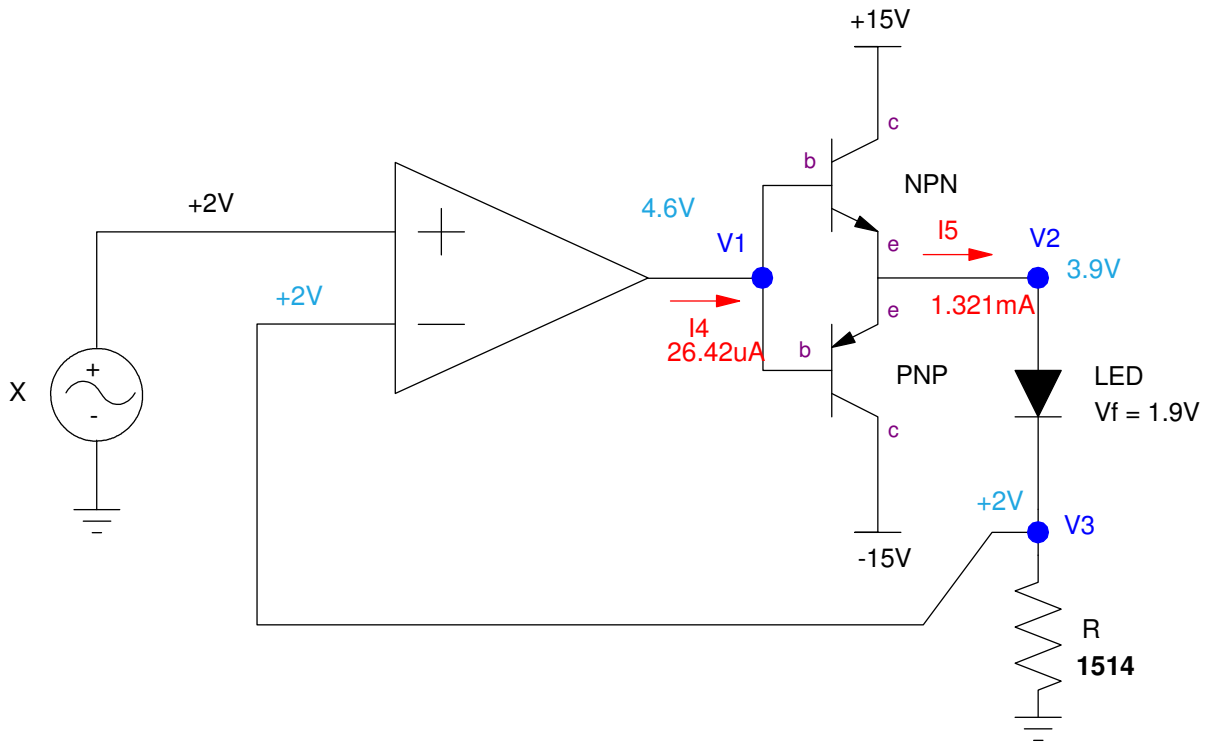


4) RTD. Assume the voltage - resistance relationship for an iron RTD temperature sensor is

$$R_t = 1000 \cdot (1 + 0.00651T) \Omega$$

where T is the temperature in degrees C. Design a circuit which outputs

- 0V at 0C and
- +10V at +40C

Let $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514$ Ohms

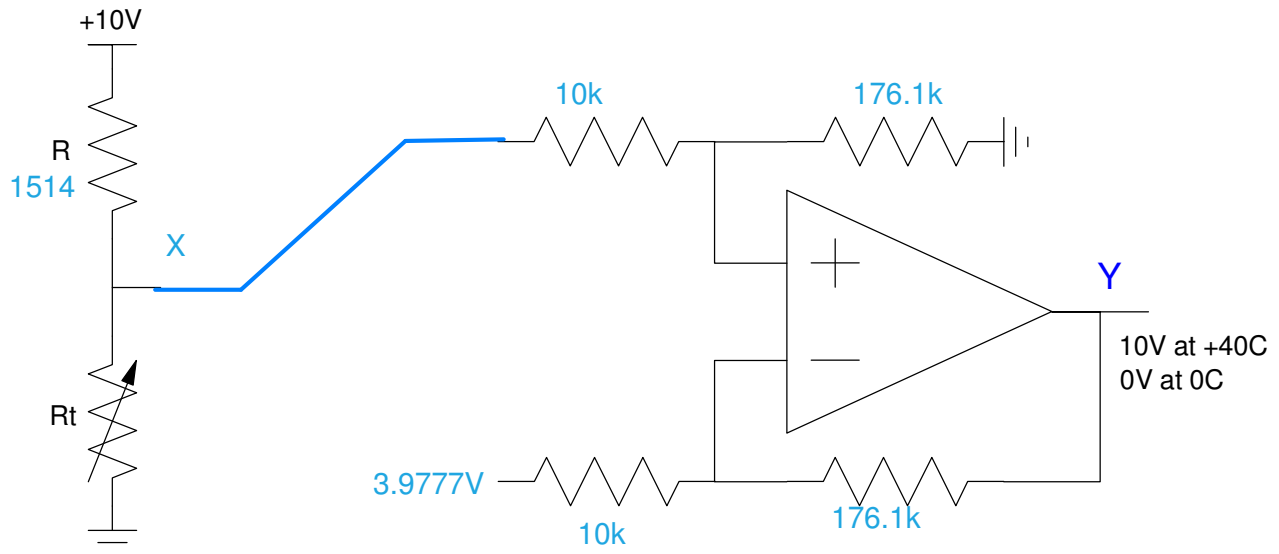

At 0C

- $R_t = 1000$ Ohms
- $X = 3.9777V$
- $Y = 0V$

At +40C

- $R_t = 1261.6$ Ohms
- $X = 4.5453V$
- $Y = 10V$

As X goes up, Y goes up. Connect to the + input.

$Y = 0$ when $X = 3.9777V$. Make the offset 3.9777V

The gain needed is

$$gain = \left(\frac{10V - 0V}{4.5453V - 3.9777V} \right) = 17.62$$


5) Thermistor. Assume the voltage - resistance relationship for a thermistor is

$$R_t = 1000 \cdot \exp\left(\frac{4440}{T+273} - \frac{4440}{298}\right) \Omega$$

where T is the temperature in degrees C. Design a circuit which outputs

- 0V at 0C and
- +10V at +40C

Let $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514 \text{ Ohms}$

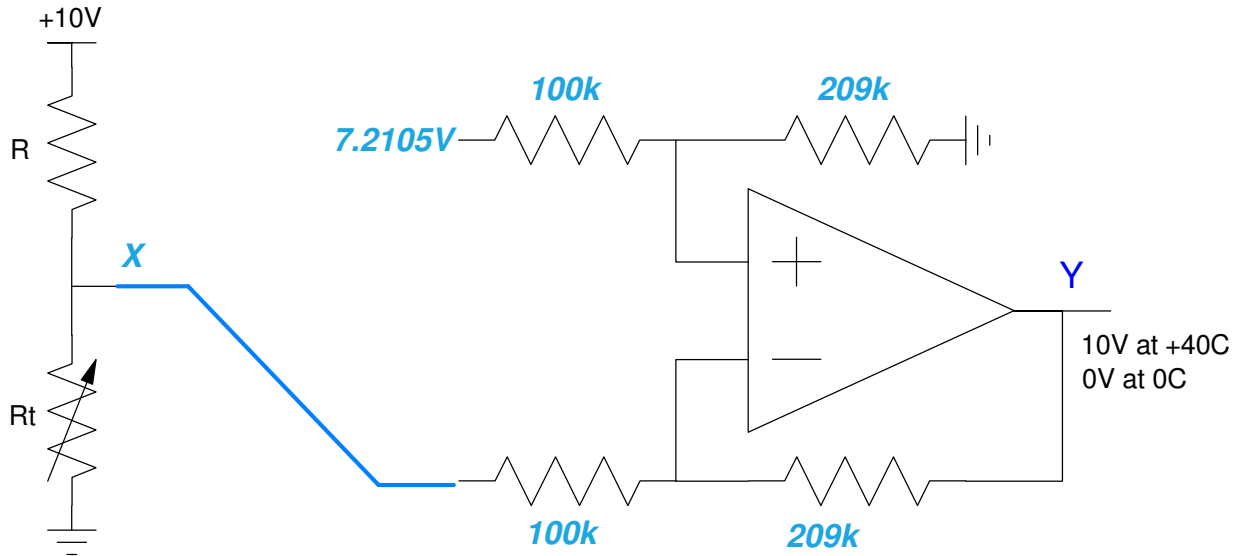

At 0C

- $R_t = 3931.4 \text{ Ohms}$
- $X = 7.2105\text{V}$
- $Y = 0\text{V}$

At +40C

- $R_t = 498.67 \text{ Ohms}$
- $X = 2.4439\text{V}$
- $Y = 10\text{V}$

As X goes down, Y goes up. Connect to the minus input

$Y = 0$ when $X = 7.2105\text{V}$. Make the offset 7.2105V

The gain needed is

$$\text{gain} = \left(\frac{10\text{V}-0\text{V}}{7.2105\text{V}-2.4439\text{V}}\right) = 2.0979$$

Make the resistor ration 2.0979 : 1

6) Temperature Sensor: 555 Timer. Assume

- $R_a = 500 \text{ Ohms}$
- $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{your birthday})$

Determine the frequency the 555 timer will output when


- $R_t = 3320 \text{ Ohms}$ (0C), and
- $R_t = 533 \text{ Ohms}$ (+40C)

note:

$$T = \text{period} = (R_1 + 2R_2) \cdot C \cdot \ln(2)$$

$$f = \frac{1}{T} \text{ Hz}$$

R 1000 + 100*Mo + Day	0C (Rt = 3320)		+40C (Rt = 533)	
1514	R2	Hz	R2	Hz
	1084 Ohms	346 Hz	614 Ohms	446.9 Hz

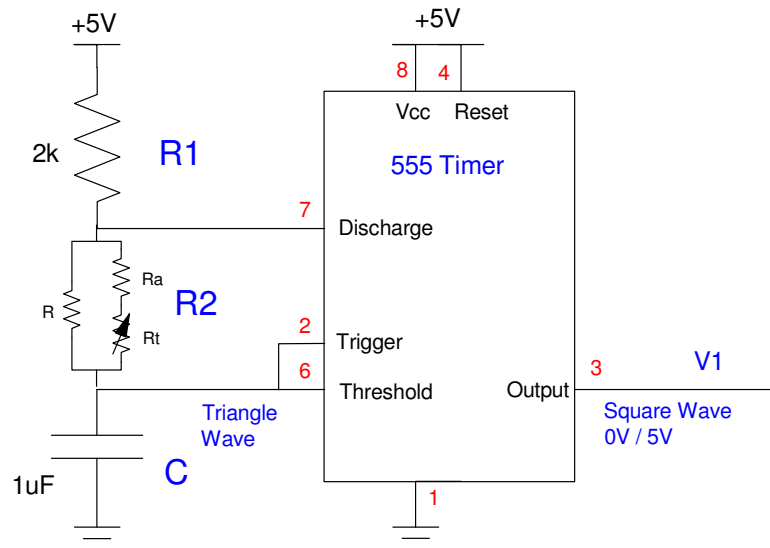

0C:

$$R_2 = \left(\frac{(R_t + R_a)R}{R_t + R_a + R} \right) = 1084.26 \Omega$$

$$\text{period} = T = (R_1 + 2R_2) \cdot C \cdot \ln(2) = 2.889 \text{ ms}$$

$$f = \frac{1}{T} = 346 \text{ Hz}$$

40C

$$R_2 = \left(\frac{(R_t + R_a)R}{R_t + R_a + R} \right) = 614 \Omega$$

$$\text{period} = T = (R_1 + 2R_2) \cdot C \cdot \ln(2) = 2.238 \text{ ms}$$

$$f = \frac{1}{T} = 446.9 \text{ Hz}$$

