

ECE 321 - Quiz #2 - Name _____

Push-Pull Amplifiers, Temperature Sensors

Calculators, Matlab permitted.

1) Push-Pull Amplifier: Voltage Output. Assume ideal silicon diodes and ideal silicon transistors with


- $V_{be} = 0.7V$
- Current gain = $\beta = 50$
- $V_{ce(sat)} = 0.2V$

Also assume that

- All voltages are limited to $-15V$ to $+15V$.
- $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514$ Ohms

Determine the voltages and currents when $X = +3V$.

| R $1000 + 100 * Mo + Day$ | V1 | V2 | V3 | I4 | I5 |
|------------------------------|----|----|----|----|----|
| | | | | | |

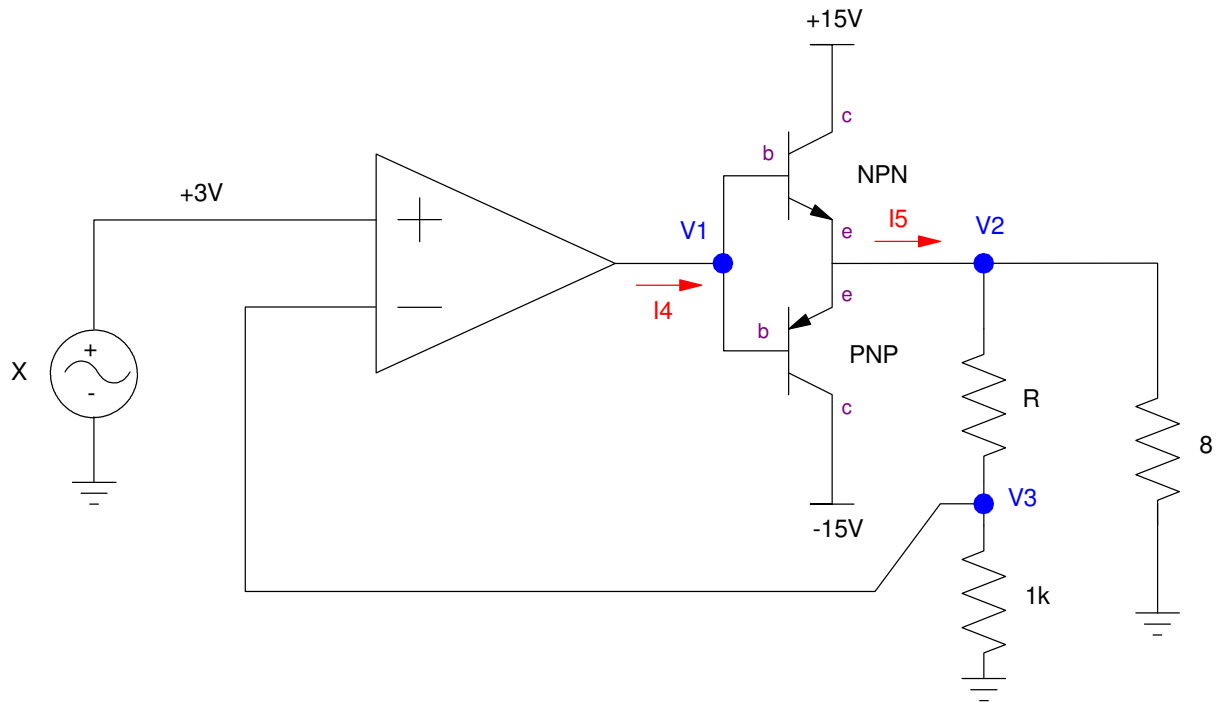

2) Push-Pull Amplifier: Voltage Output. Assume ideal silicon diodes and ideal silicon transistors with


- $V_{be} = 0.7V$
- Current gain = $\beta = 50$
- $V_{ce(sat)} = 0.2V$

Also assume that

- The push-pull amplifier is fed by +5V and -5V,
- The op-amp's output is limited to 0V to +5V, and
- $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514$ Ohms

Determine the voltages and currents when $X = +3V$.

| R | V1 | V2 | V3 | I4 | I5 |
|-------------------------|----|----|----|----|----|
| $1000 + 100 * Mo + Day$ | | | | | |
| | | | | | |

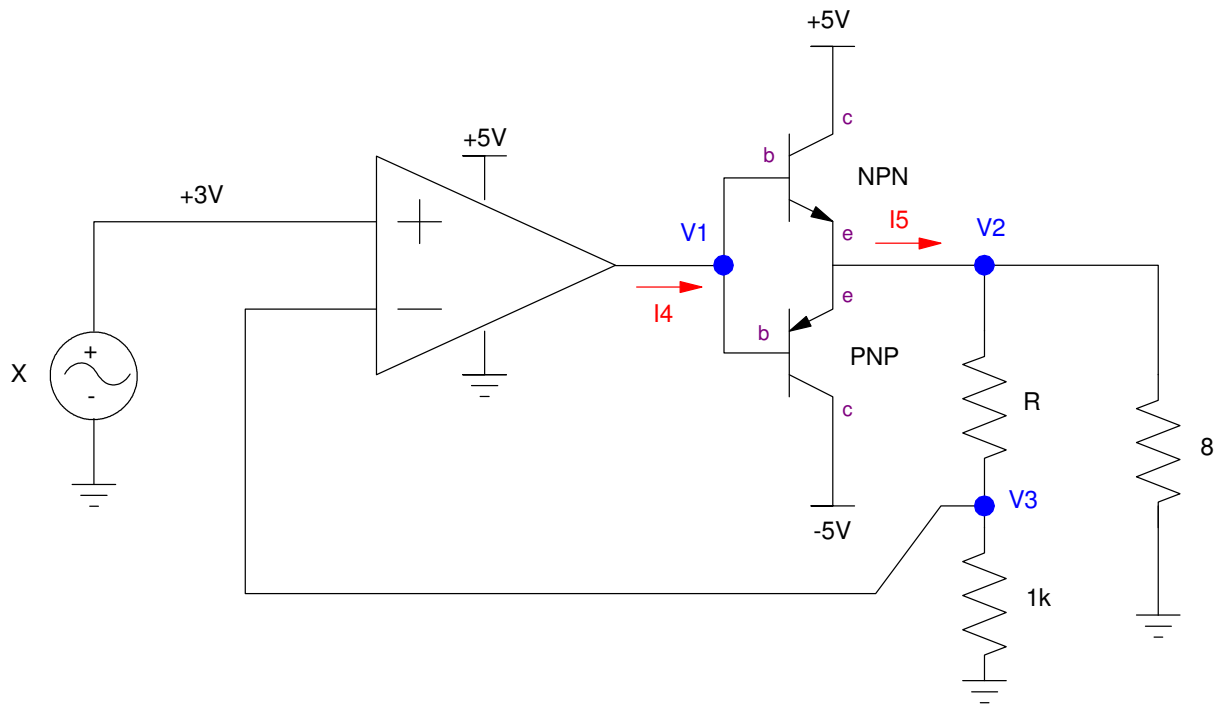


3) Push-Pull Amplifier: Current Output. Assume ideal silicon diodes and ideal silicon transistors with

- $|V_{be}| = 0.7V$
- Current gain = $\beta = 50$
- $|V_{ce(sat)}| = 0.2V$

Determine the voltages and currents when $X = +2V$. Assume

- $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514$ Ohms

| R 1000 + 100*Mo + Day | V1 | V2 | V3 | I4 | I5 |
|--------------------------|----|----|----|----|----|
| | | | | | |

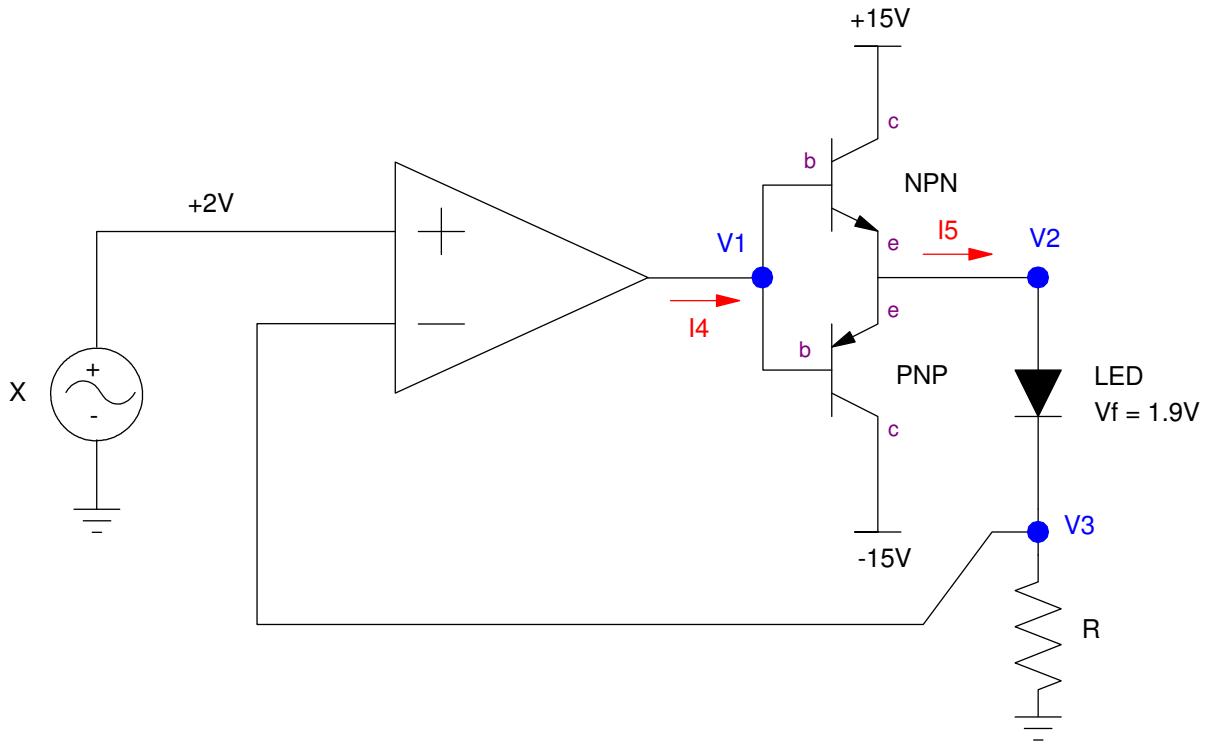



4) RTD. Assume the voltage - resistance relationship for an iron RTD temperature sensor is

$$R_t = 1000 \cdot (1 + 0.00651T) \Omega$$

where T is the temperature in degrees C. Design a circuit which outputs

- 0V at 0C and
- +10V at +40C

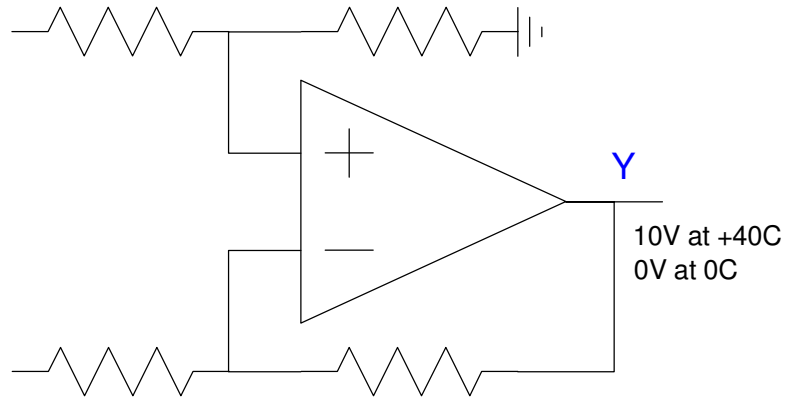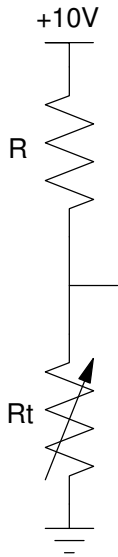Let $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514 \text{ Ohms}$




5) Thermistor. Assume the voltage - resistance relationship for a thermistor is

$$R_t = 1000 \cdot \exp\left(\frac{4440}{T+273} - \frac{4440}{298}\right) \Omega$$

where T is the temperature in degrees C. Design a circuit which outputs

- 0V at 0C and
- +10V at +40C

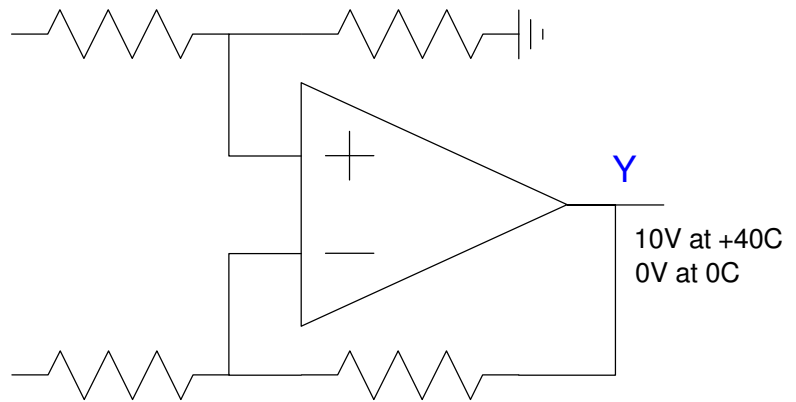Let $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514$ Ohms



6) Temperature Sensor: 555 Timer. Assume

- $R_a = 500 \text{ Ohms}$
- $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{your birthday})$

Determine the frequency the 555 timer will output when

- $R_t = 3320 \text{ Ohms (0C)}$, and
- $R_t = 533 \text{ Ohms (+40C)}$

note:

$$T = \text{period} = (R_1 + 2R_2) \cdot C \cdot \ln(2)$$

$$f = \frac{1}{T} \text{ Hz}$$

| R 1000 + 100*Mo + Day | 0C (Rt = 3320) | | +40C (Rt = 533) | |
|--------------------------|----------------|----|-----------------|----|
| | R2 | Hz | R2 | Hz |
| | | | | |

