

# ECE 321 - Homework #1

Op Amp Amplifiers & Mixers. Due Wednesday, April 7th

Please make the subject "ECE 321 HW#1" if submitting homework electronically to Jacob\_Glower@yahoo.com (or on blackboard)

For all problems, assume you are using

- MCP602 Op Amps (2.7V - 6.0V, max current = 22mA)
- 2SC6144 transistors
- $\beta = 200$ ,  $I_{A \text{ max}} = 10A$ ,  $V_{be} = 0.7V$

## 555 Timer


Problem 1) Design a circuit using a 555 timer so that it outputs a 500hz triangle wave

The period is


$$T = (R_1 + 2R_2) \cdot C \cdot \ln(2) = 2ms$$

Let

- $T = 2ms$
- $R_1 = 1k$
- $R_2 = 3.3k$
- $C = 0.379\mu F$

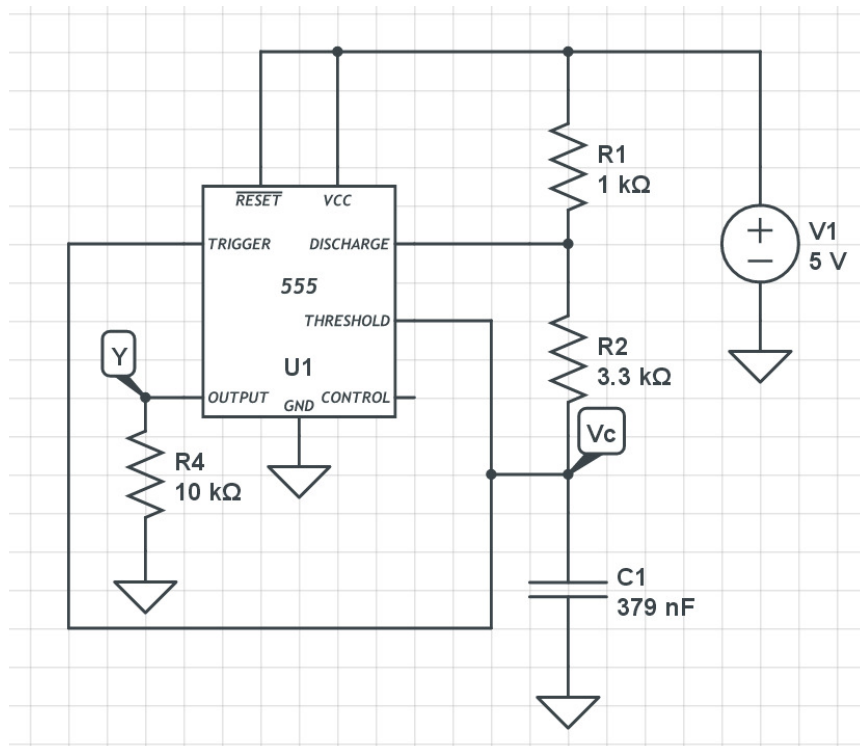

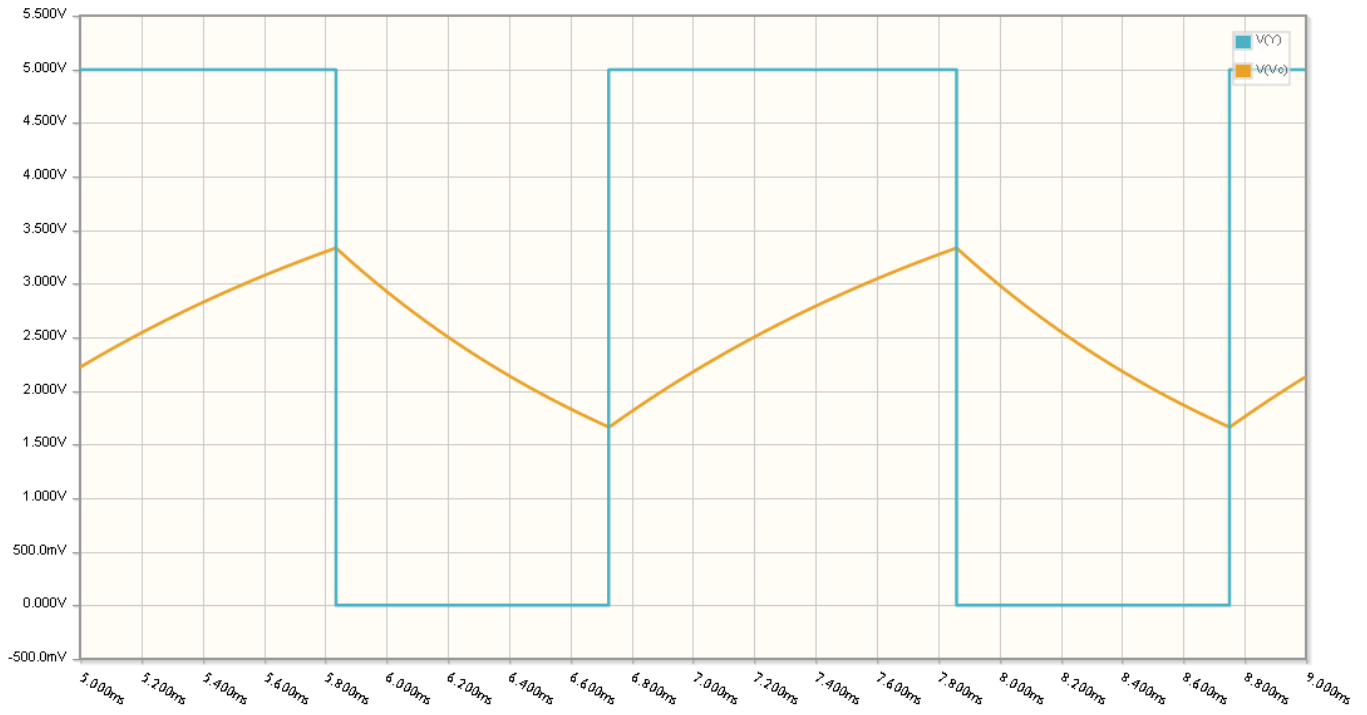
Problem 2) Verify your design in CircuitLab



Period = 2.045ms (489Hz)

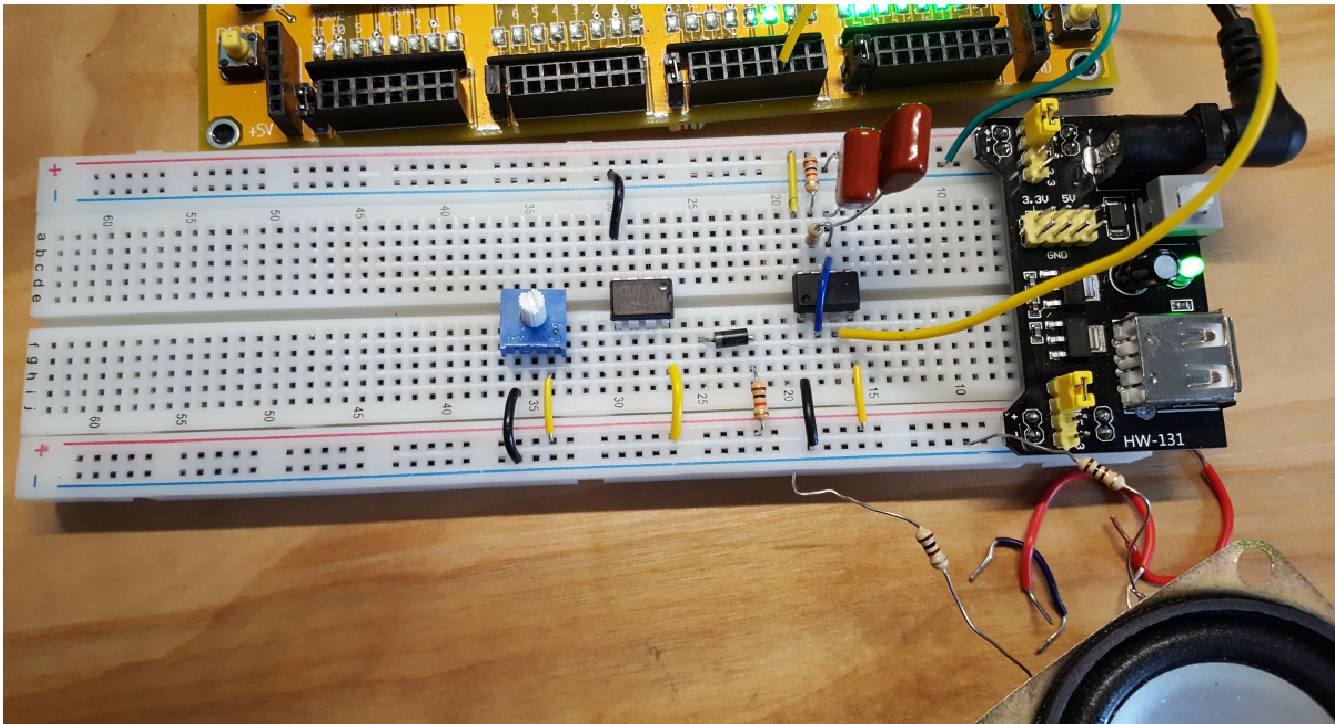Problem 3) Build this circuit in hardware and verify its operation

- Using two 0.18uF capacitors in parallel (what I could scrounge up - 0.36uF total)



Using a multimeter on the capacitor voltage

- DC voltage = 2.570V ( vs. 2.500V expected )
- AC voltage = 0.446V<sub>rms</sub>

Peak-to-peak voltage is  $2\sqrt{2}$  times larger for sine waves. Multiplying


- AC voltage  $\approx (2\sqrt{2}) \cdot 0.446V_{rms} = 1.261V_{pp}$  ( vs. 1.66V<sub>pp</sub> expected )

## Voltage Amplifier & Mixer:

Problem 4) Design a circuit to mix two audio signals


- A = the output of your 555 timer: (1.66Vpp triangle wave, 500Hz)
- B = the output of your cell phone (1Vpp, 20-20kHz sine wave)


$$Y = 2A + 5B$$

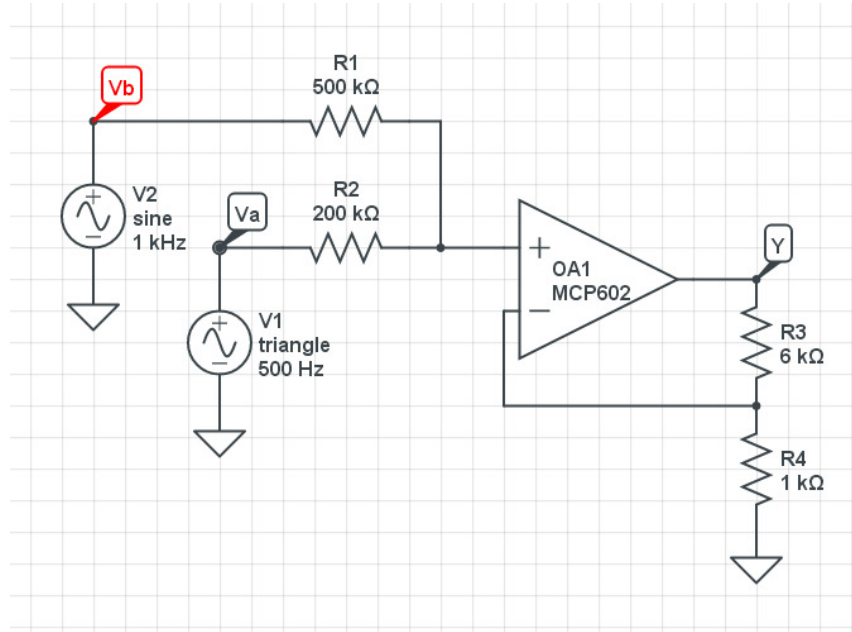

Problem 5) Verify the operation of your mixer in CircuitLab

Use superposition

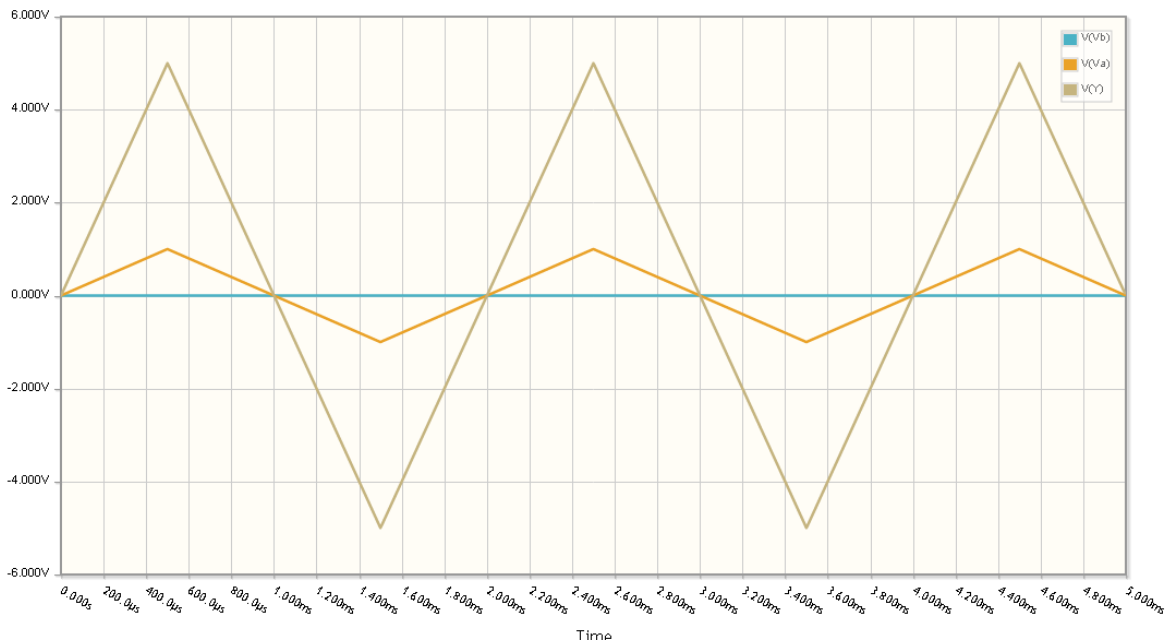

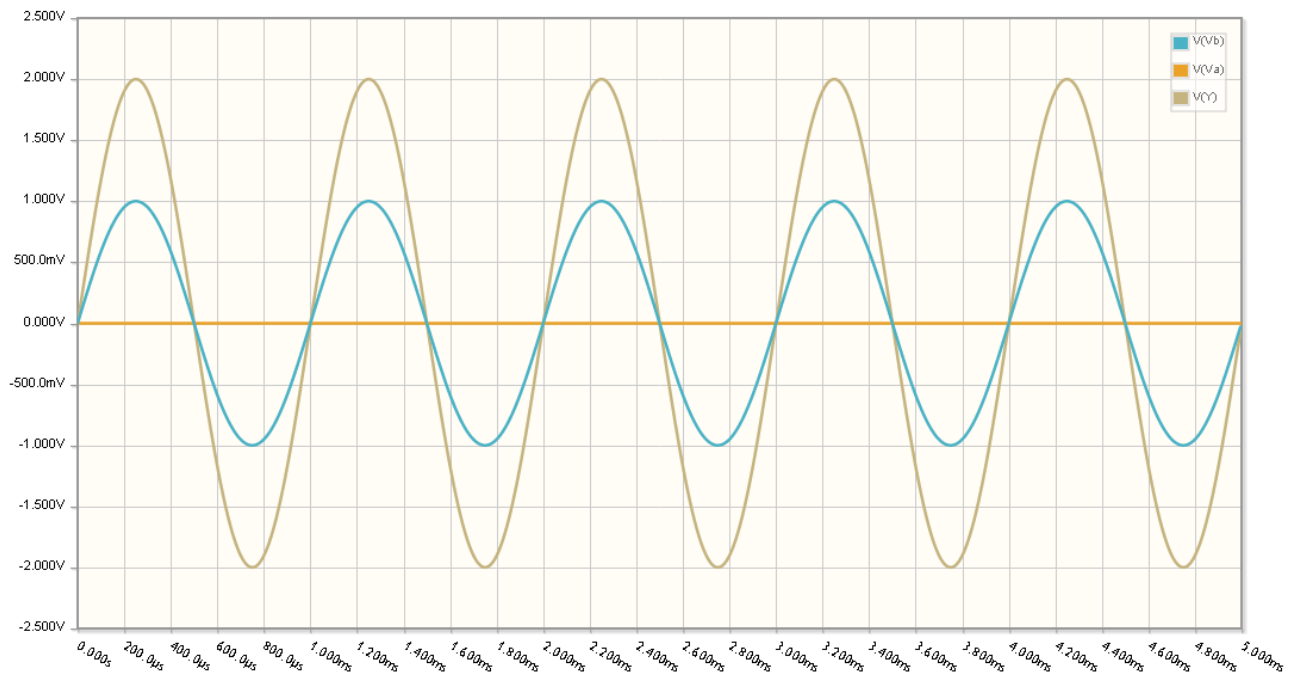

Problem 6) Verify the operation of your circuit in hardware: Apply a 1kHz sine wave to input A then B

Input A

- $V_{in} = 0.317V_{rms}$
- $V_{out} = 0.649V_{rms}$
- gain = 2.047

Input B

- $V_{in} = 0.317V_{rms}$
- $V_{out} = 1.500V_{rms}$
- gain = 4.73

