

# ECE 321 - Homework #2


Push-Pull Amplifiers & Temperature Sensors. Due Monday, April 12th

Please make the subject "ECE 321 HW#2" if submitting homework electronically to Jacob\_Glower@yahoo.com (or on blackboard)

## Push-Pull Amplifiers

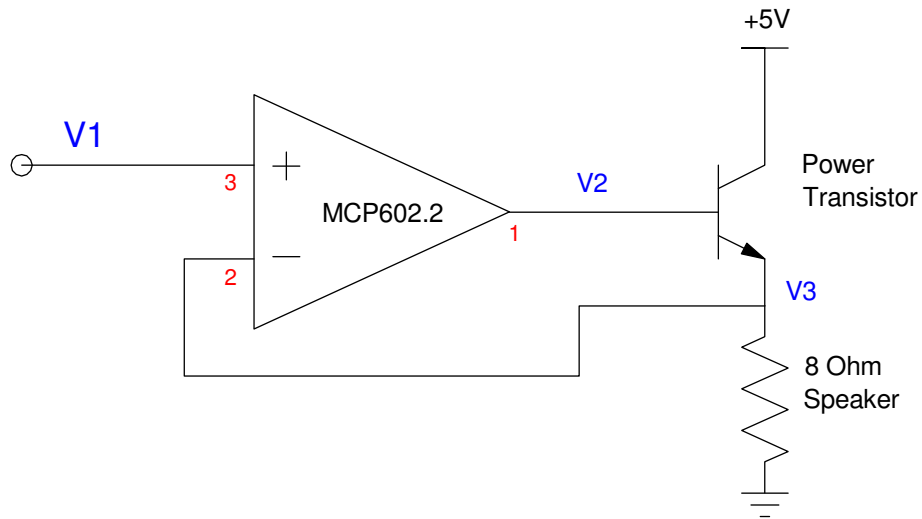1) Assume you only have access to a +5V power supply. Design a push-amplifier to drive an 8-Ohm speaker

- Input: 0..5V analog signal, capable of 22mA
- Output: 8 Ohm speaker
- Relationship:  $Y = X$





2) Simulate this design in CircuitLab. Verify

- Its operation (you can now drive an 8-Ohm speaker), and
- Its limitations (what voltage range are you able to output? 0V .. 5V?)

There are a couple of ways to do this.

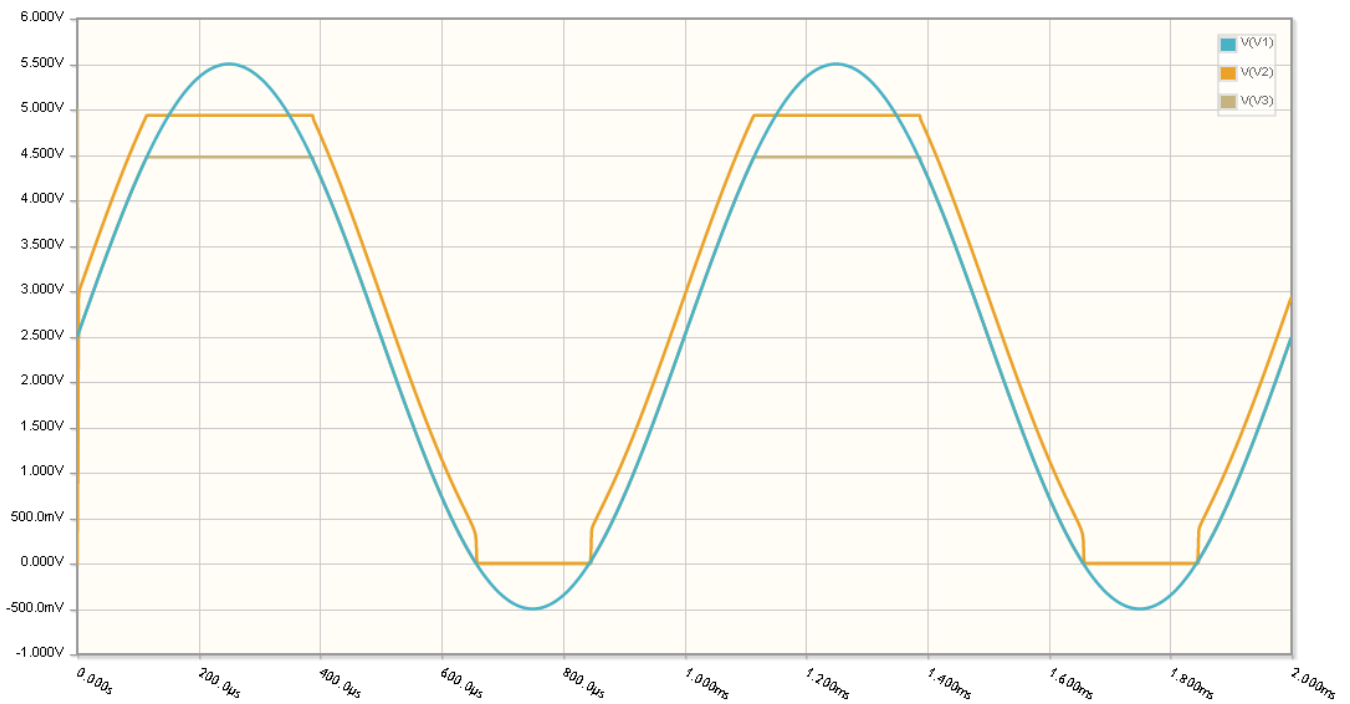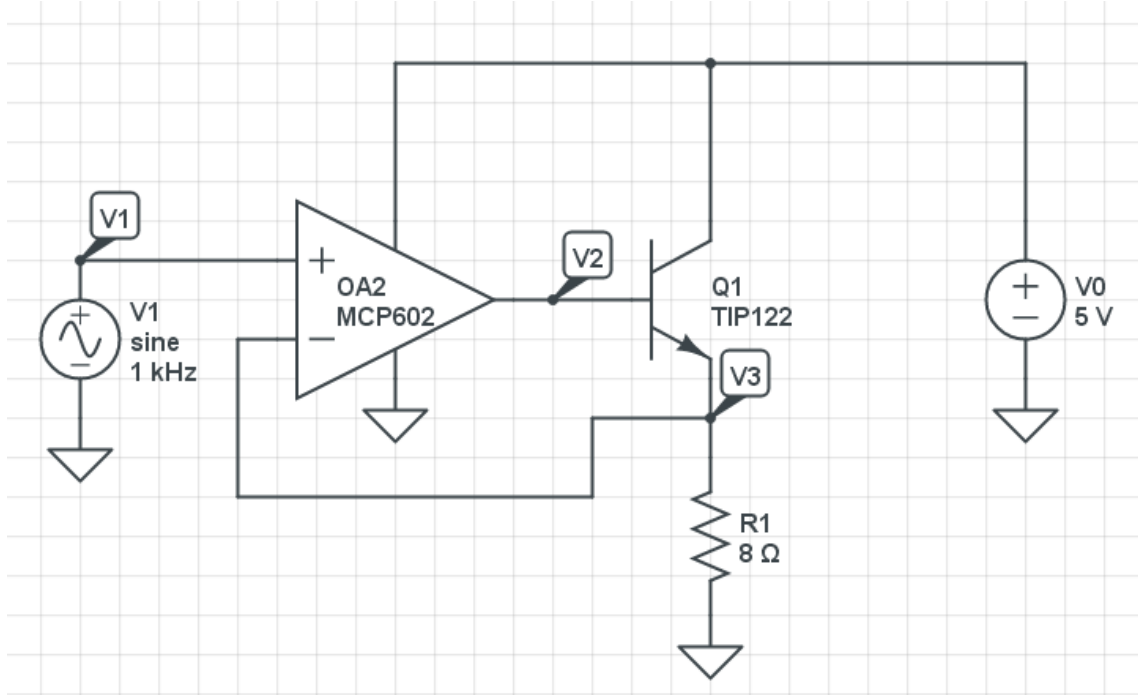
- DC Test: Apply constant voltages at V1 and check to see that V1 = V3.
- AC Test: Sweep the voltage in V1 and note where V1 = V3.




V1 = V3 for 0V < V1 < 4.5V

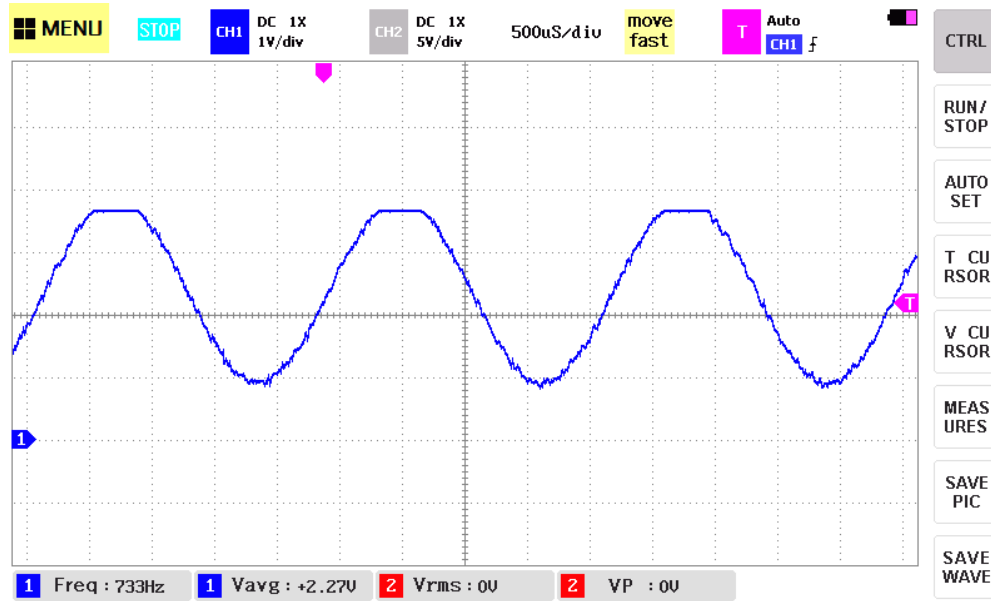3) Build this circuit in hardware to amplify the output of your mixed. Verify


- Its operation (you can now drive an 8-Ohm speaker), and
- Its limitations (what voltage range are you able to output? 0V .. 5V?)



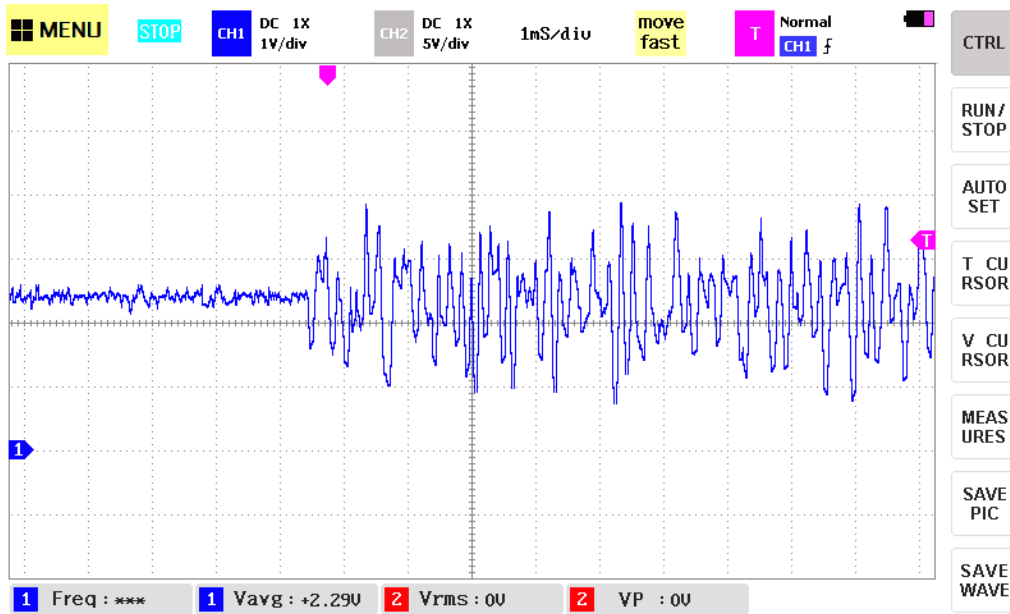sine wave input: Output clips at 0V and + 3.7V



Cow Bell: Time Response

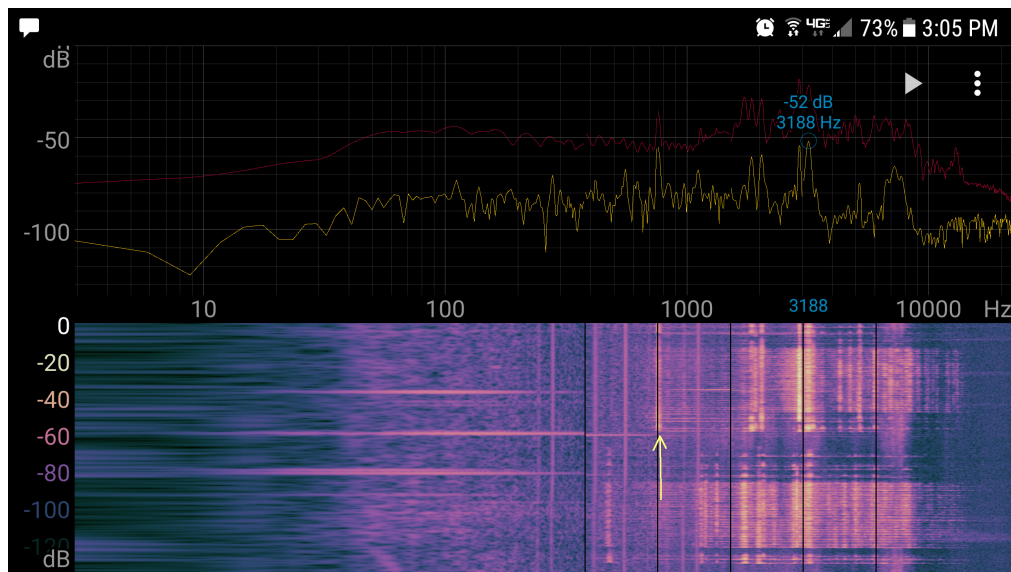

Don't Fear the Reaper: Frequency Content. Cow Bell at 604Hz

## Temperature Sensors

Assume you are using a thermistor where the temperature - resistance relationship is

$$R = 1000 \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$


where T is the temperature in degrees C.

4) Design a linearizing circuit so that the resistance is approximately linear from 10C to +30C. Plot the resulting resistance vs. temperature relationship.

Using fminsearch and a lot of trial and error, one solution that works is

- Ra = 100
- Rb = 820.0471
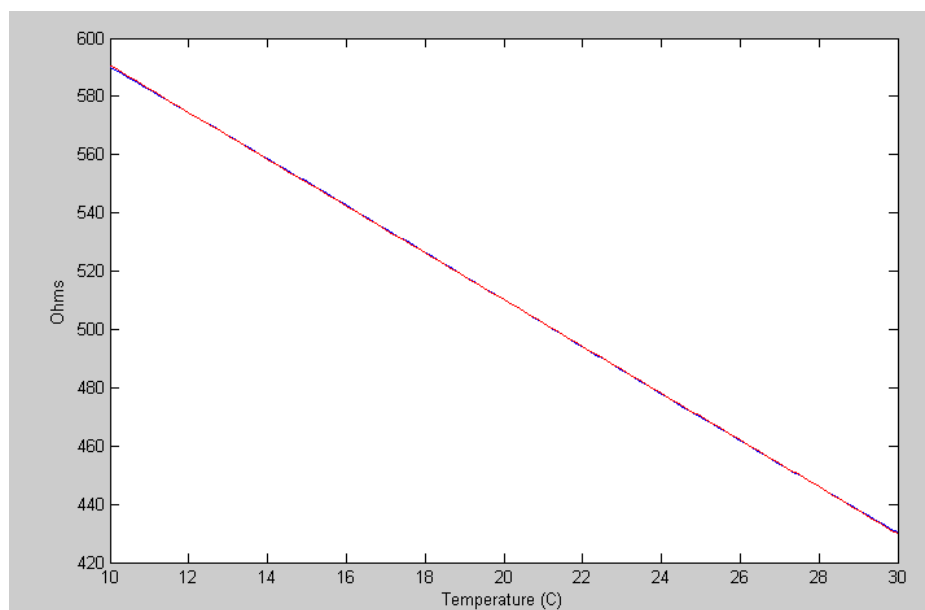
```
function [ J ] = costR( Z )  
  
    a = 100;  
    b = Z(1);  
  
    T = [10:0.1:30]';  
    R = 1000 * exp(3905 ./ (T+273) - 3905/298);  
  
    Z = (R+a)*b ./ (R+a+b);  
  
    B = [T, T.^0];  
    A = inv(B'*B)*B'*Z;  
  
    plot(T,Z,'b',T,B*A,'r');  
    pause(0.01);  
  
    E = Z - B*A;  
  
    J = sum(E.^2);  
  
end
```



5) Using the linearizing circuit from problem 4, design a circuit which outputs

- 0V at 10C
- +5V at +30C
- Proportional in between.

Plot the resulting output voltage vs. temperature.

At 10C

- $Z = 589.9731 \text{ Ohms}$
- $V_x = 1.139\text{V}$
- $V_y = 0\text{V}$


At 30C

- $Z = 430.3386 \text{ Ohms}$
- $V_x = 0.885\text{V}$
- $V_y = 5\text{V}$

The gain is


$$\text{gain} = \left( \frac{5\text{V} - 0\text{V}}{0.885\text{V} - 1.139\text{V}} \right) = -19.715$$

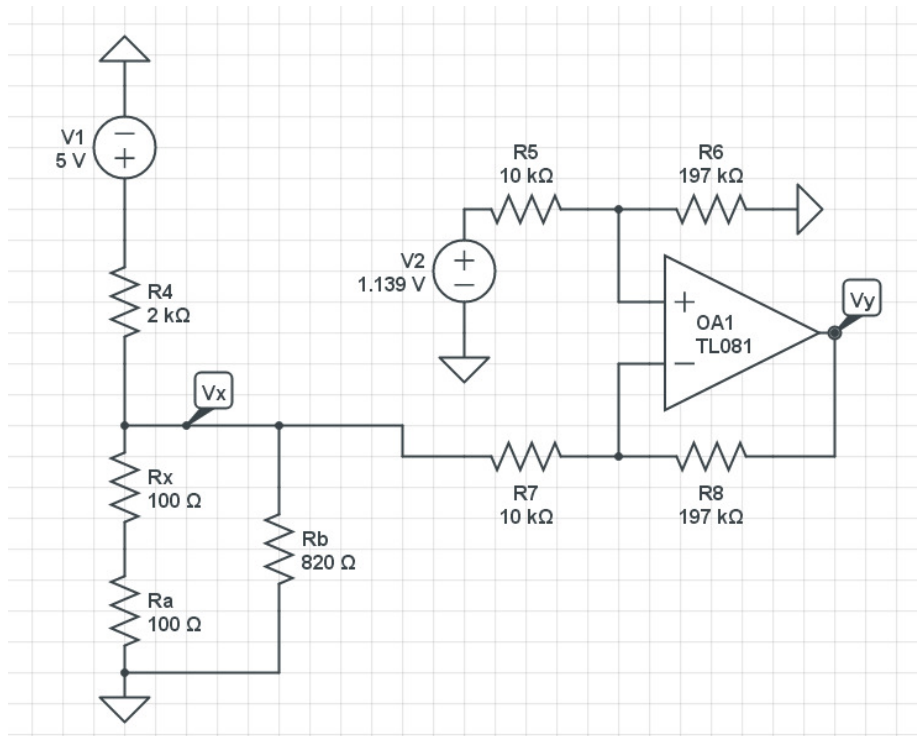The output is 0V when  $V_x = 1.139\text{V}$ . Connect the offset to 1.139V


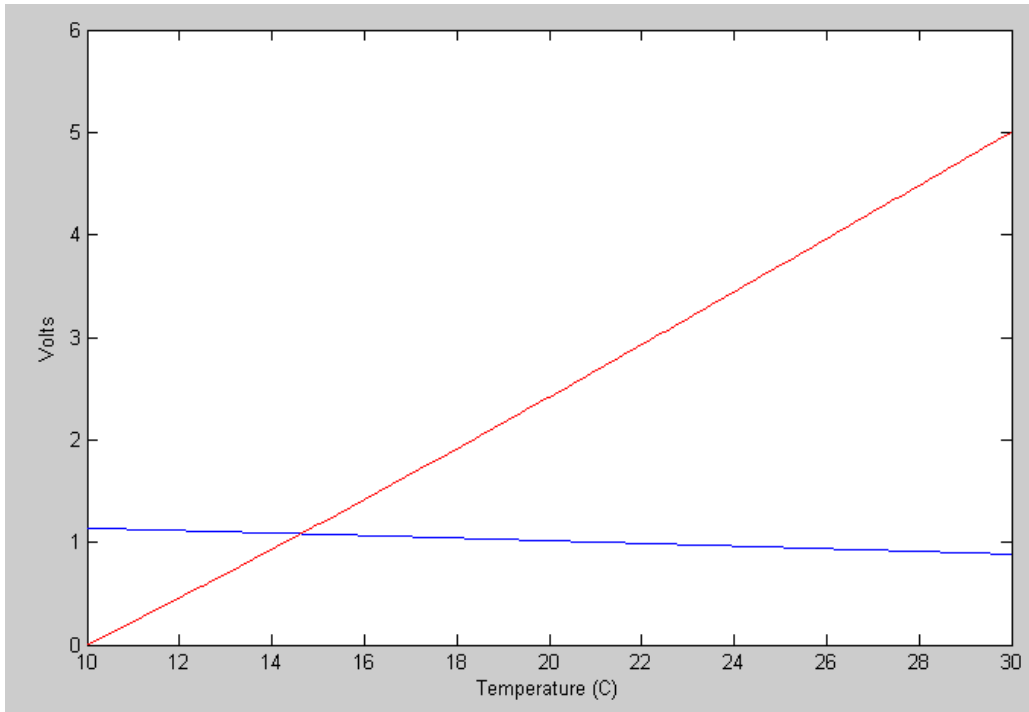
## Plotting the voltage vs. temperature

```
Ra = 100  
Rb = 820.0471  
  
T = [10:0.1:30]';  
R = 1000 * exp(3905 ./ (T+273) - 3905/298);  
  
Z = (R + Ra)*Rb ./ (R + Ra + Rb);  
  
Vx = Z ./ (Z + 2000) * 5;  
Vy = 19.715*(1.139 - Vx);  
plot(T,Vx,'b',T,Vy,'r')  
xlabel('Temperature (C)');  
ylabel('Volts');
```



Voltage at Vx (blue) and Vy (red)

6) Using the linearizing circuit from problem 4, design a 555 timer which outputs 500Hz at +10C

- Determine the frequency it outputs from 0C to +40C


At 10C,  $R = 2002 \text{ Ohms}$ ,  $Z = 589.9731 \text{ Ohms}$

For 500Hz

$$2ms = (R_1 + 2R_2) \cdot C \cdot \ln(2)$$

Let

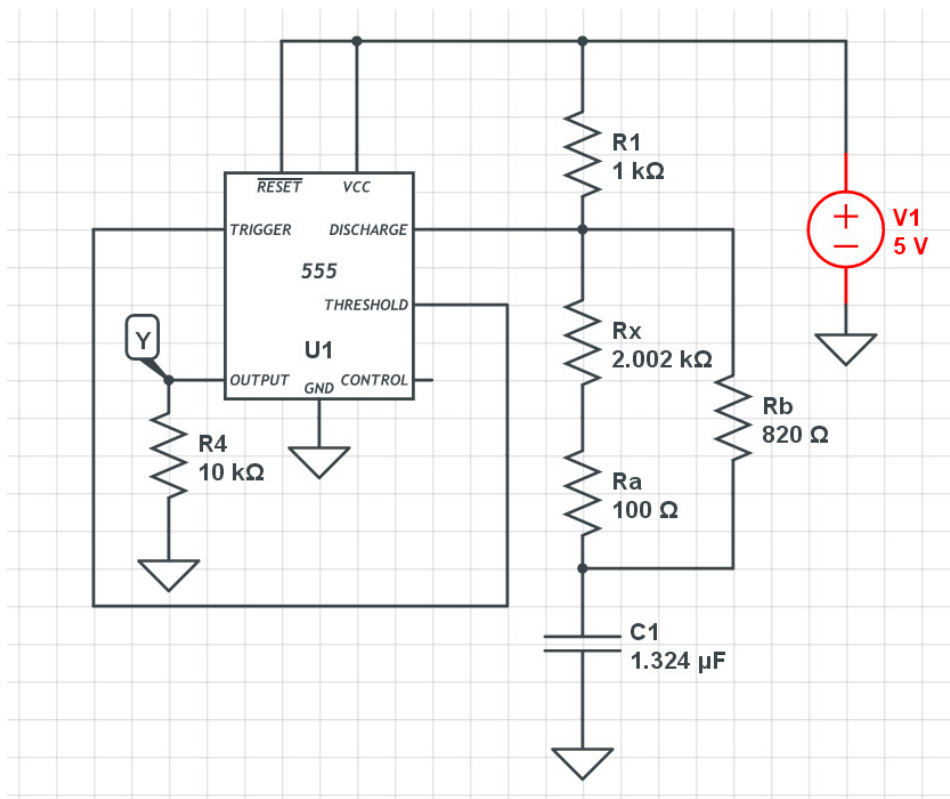
- $R_1 = 1k$
- $R_2 = Z = 589.9731 \text{ Ohms}$
- $C = 1.324\mu\text{F}$



555 timer with a linearizing circuit for the thermistor (Rx)


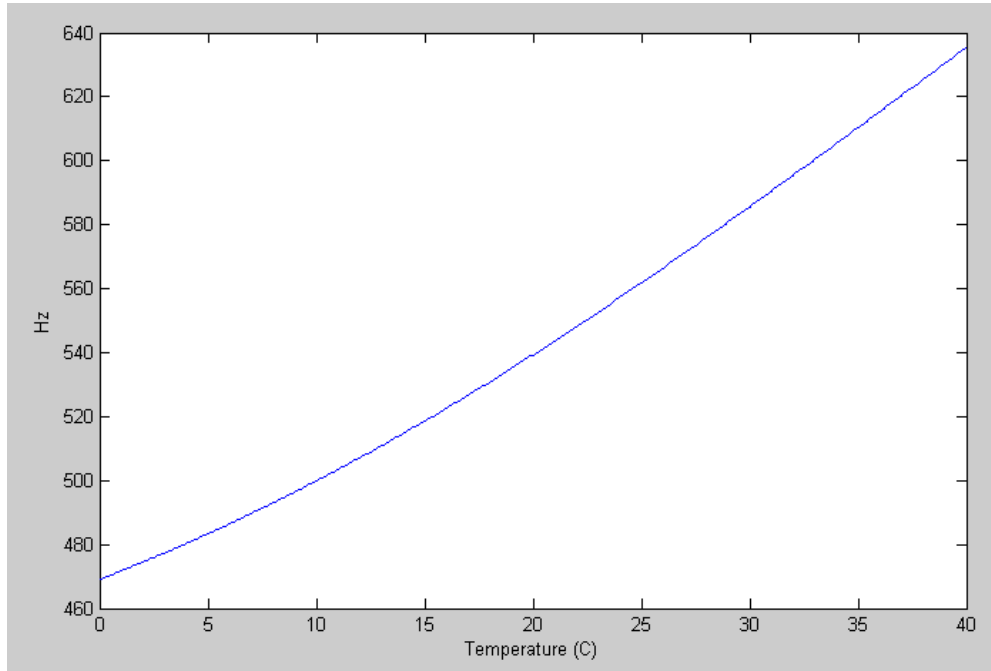
```
>> T = [0:0.1:40]';
>> R = 1000 * exp(3905 ./ (T+273) - 3905/298);
>> Ra = 100;
>> Rb = 820.0471;
>> Z = (R + Ra)*Rb ./ (R + Ra + Rb);
>> R1 = 1000;
>> C = 1.324e-6;
>> Period = (R1 + 2*Z)*C*log(2);
>> Hz = 1 ./ Period;
>> plot(T,Hz);
>> xlabel('Temperature (C)');
>> ylabel('Hz')
```



Frequency vs. Temperature for the 555 timer with a linearizing circuit