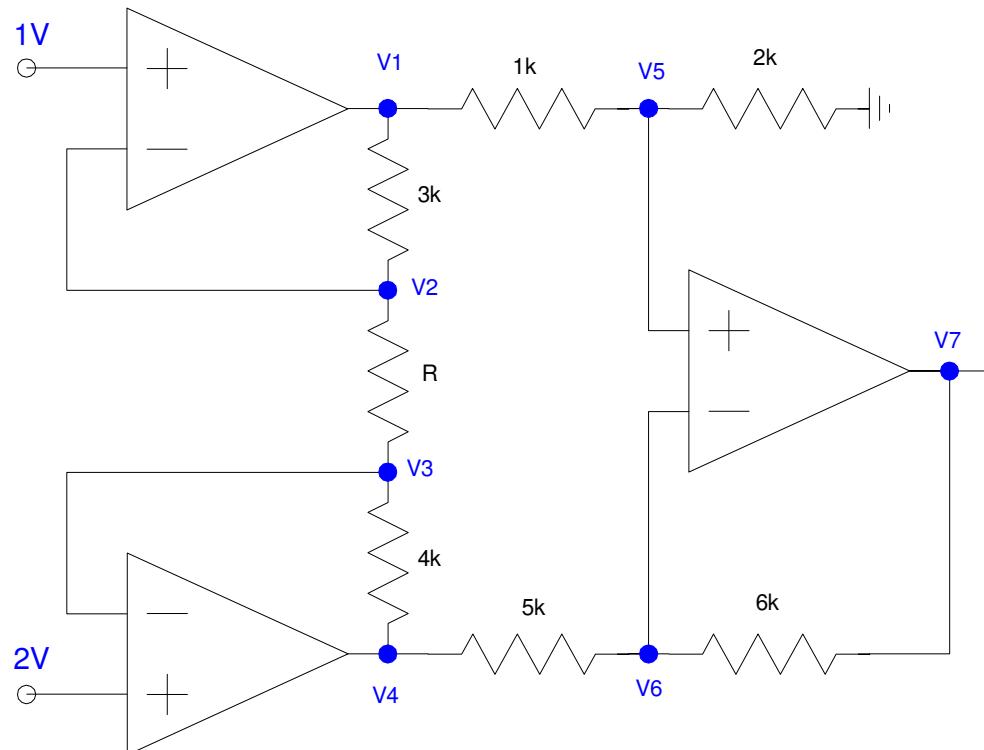


# ECE 321 - Quiz #1 - Name \_\_\_\_\_

Op-Amp Amplifiers & mixers., Push-Pull Amplifiers


1) Give 7 equations which allow you to solve for the 7 unknown voltages. You do not need to solve.

- Assume ideal op-amps.
- Assume  $R = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$ .



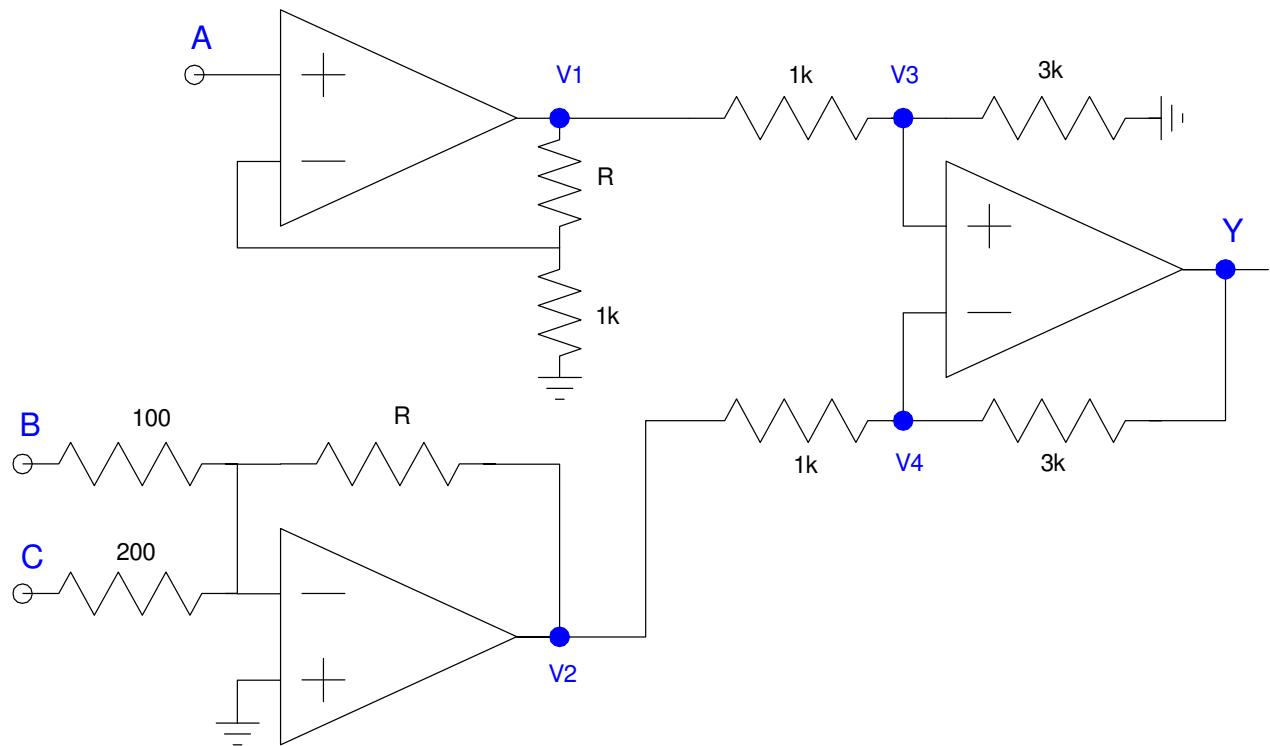2) Determine Y as a function of A, B, and C.

- Assume ideal op-amps
- Assume  $R = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$ .



3) Design a circuit which outputs

$$Y = 4 + 2A + 3B$$

*note: the gain on A and B are positive*

4) Design a circuit which outputs


$$Y = 4 - 2A - 3B$$

*note: the gain on A and B are negative*

5) Determine the voltages and currents for the following push-pull amplifier. Assume

- Ideal op-amps
- $R = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$
- Transistors with:
  - $\beta = 30$
  - $|V_{be}| = 0.7V$

$R$ $900 + 100 \cdot \text{mo} + \text{day}$	$V_1$	$V_2$	$V_3$	$I_4$	$I_5$

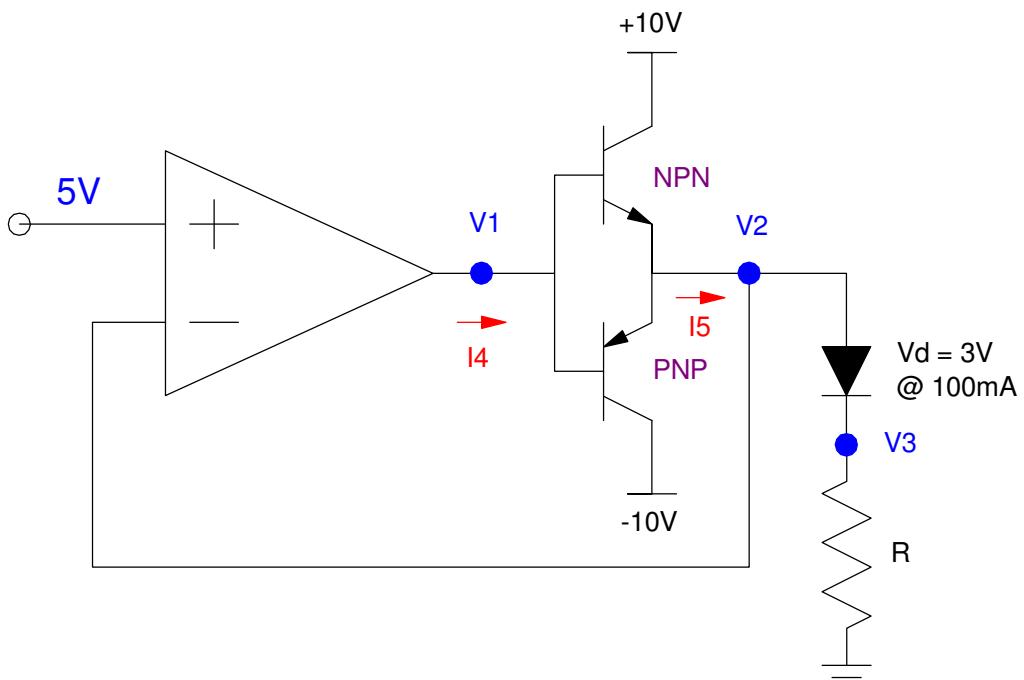

6) Determine the voltages and currents for the following push-pull amplifier. Assume

- Ideal op-amps
- $R = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$
- Transistors with
  - $\beta = 30$
  - $|V_{be}| = 0.7V$

$R$ $900 + 100 \cdot \text{mo} + \text{day}$	V1	V2	V3	I4	I5

