


# ECE 321 - Quiz #4 - Name \_\_\_\_\_

## BJT Amplifiers & 2-Port Models

1) BJT Amplifier: DC Analysis. Determine the Thevenin equivalent of R<sub>1</sub> and R<sub>2</sub> as well as the Q-point.  
Assume ideal silicon transistors:

- |V<sub>be0</sub>| = 0.7V
- $\beta = 30$
- $R_e = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$

$R_e$ $900 + 100 \cdot \text{mo} + \text{day}$	$V_b$	$R_b$	$V_{ce}$	$I_c$

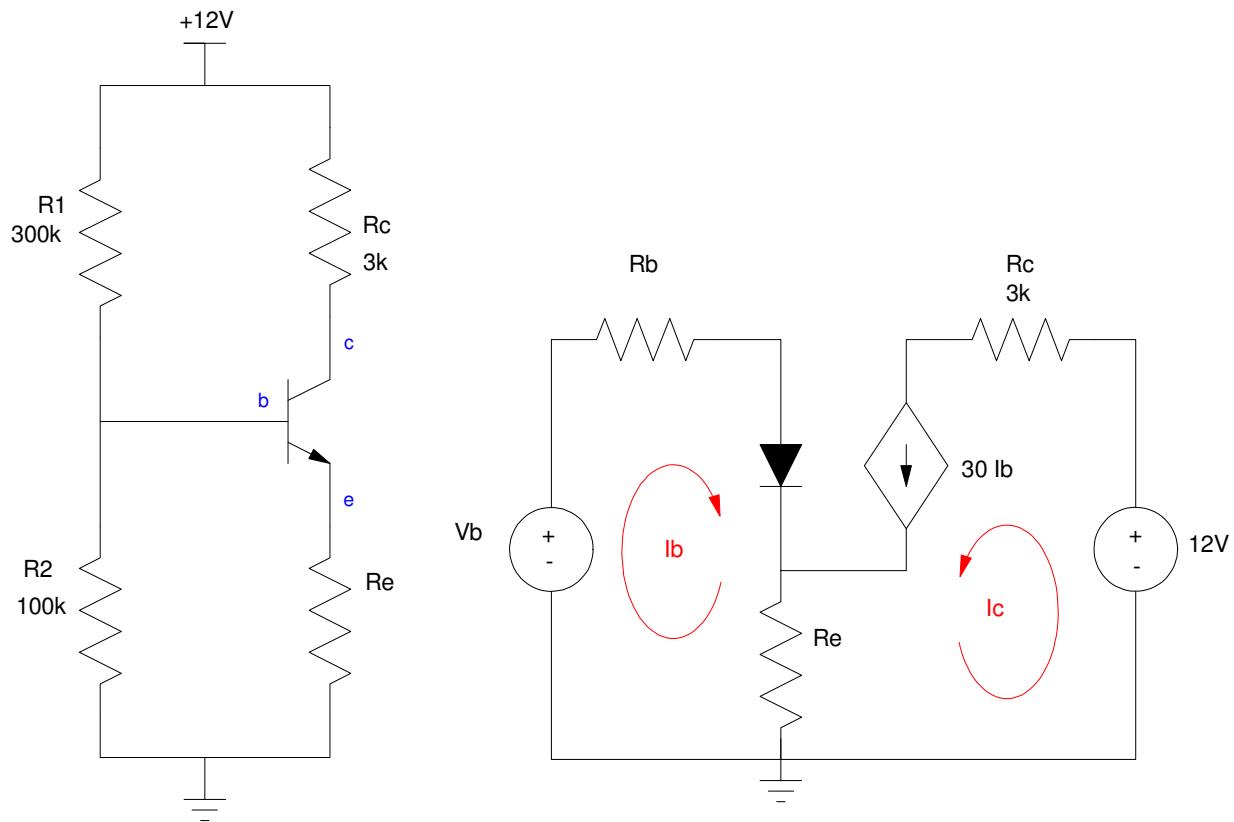


2) BJT Amplifier: DC Design. Determine R<sub>1</sub> and R<sub>2</sub> so that

- The Q point is V<sub>ce</sub> = 6.00V and
- The Q point is stabilized for variations in  $\beta$

Assume


- Ideal silicon transistors ( $V_{be} = 0.7V$ ,  $\beta = 30$ )
- $R_e = 900 + 100*(\text{birth month}) + (\text{birth day})$ .

$R_e$ $900 + 100*\text{mo} + \text{day}$	R <sub>1</sub>	R <sub>2</sub>	V <sub>b</sub>	R <sub>b</sub>

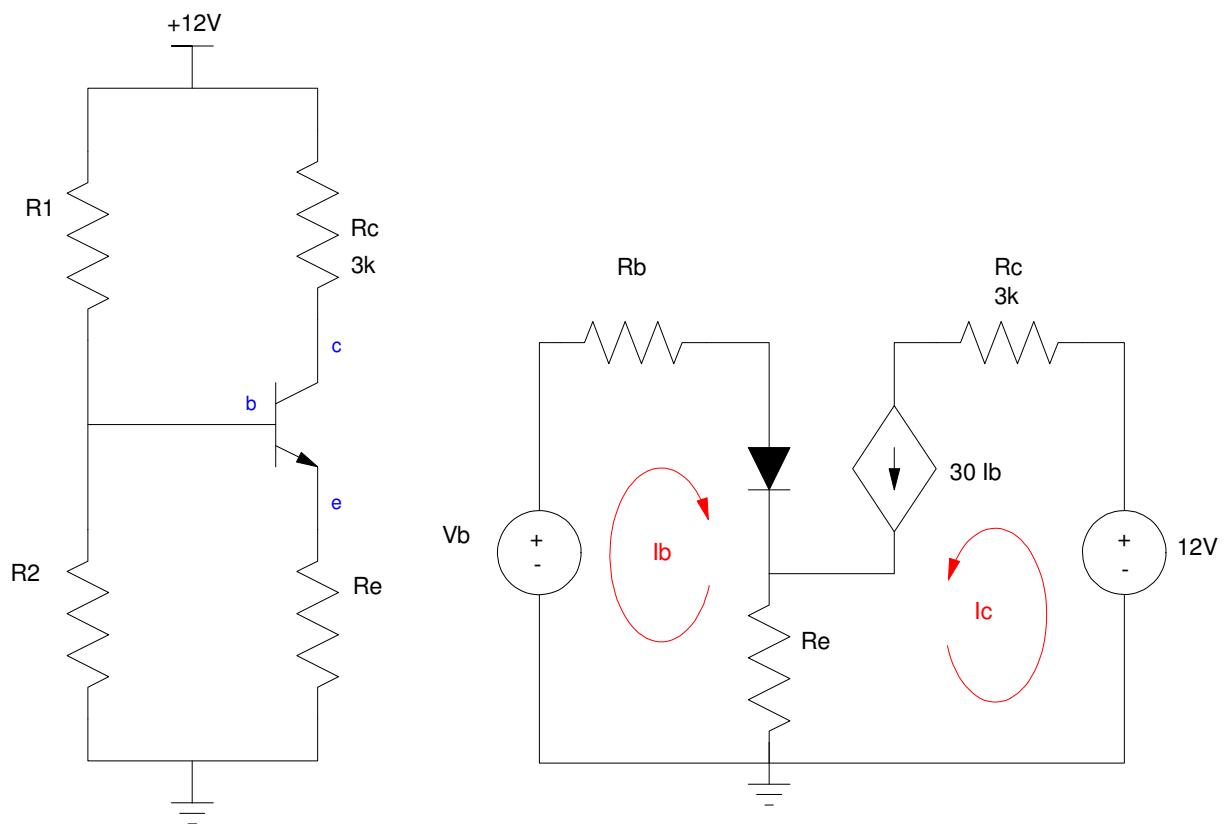


3) BJT: AC Analysis: Draw the small signal model for the following BJT amplifier. Assume

- $r_f = 2000\Omega$
- $\beta = 30$

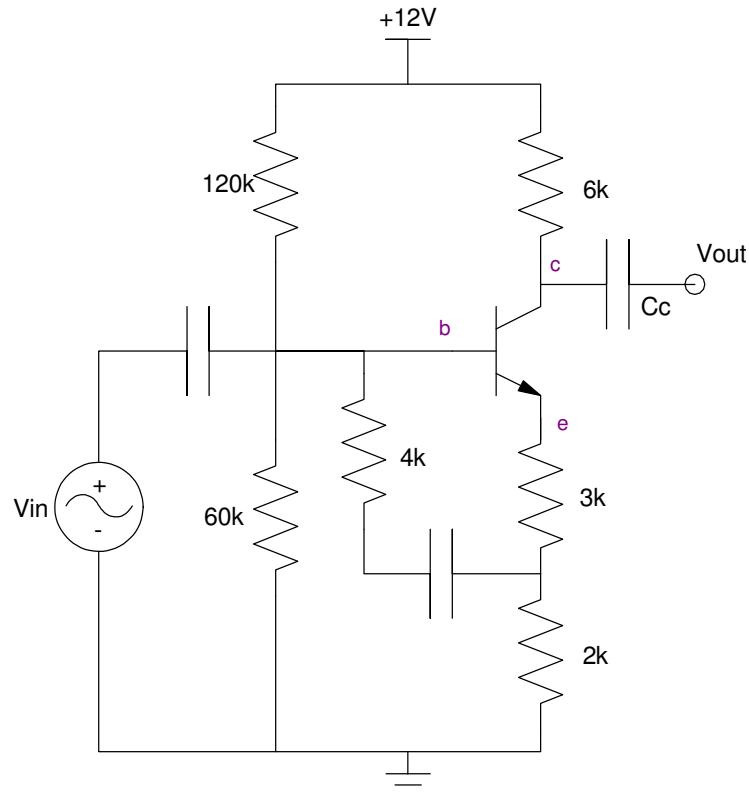


4) 2-Port Models. Determine the 2-port model for the following circuit:

R 900 + 100*mo + day	Rin	Ain	Rout	Ao

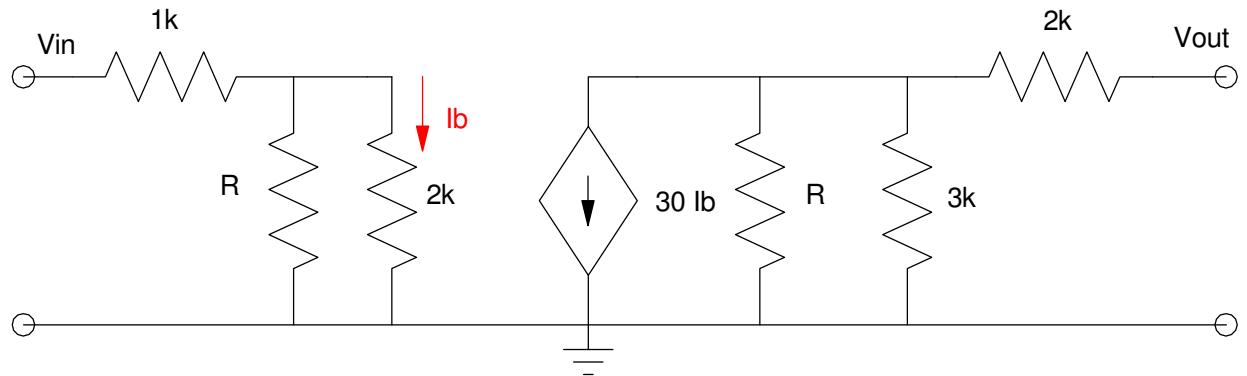

5) 2-Port Models. Determine the 2-port model for the following circuit:

R	Rin	Ain	Rout	Ao
$900 + 100 \cdot mo + day$				

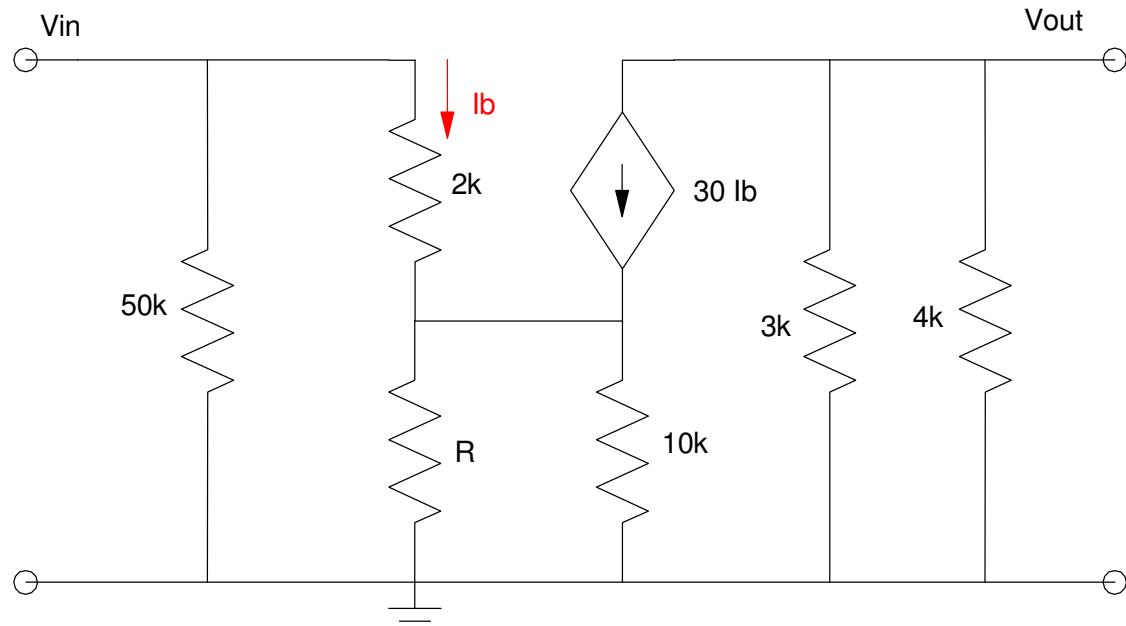

6) Determine the 2-port model for three cascaded CE amplifiers

R 900 + 100*mo + day	Rin	Ain	Rout	Ao

