

# ECE 321 - Homework #2

Temperature Sensors, Audio & Strain Sensors, Calibration & Noise. Due Monday, April 11th

Please make the subject "ECE 321 HW#2" if submitting homework electronically to Jacob\_Glower@yahoo.com (or on blackboard)

## Temperature Sensors

Assume you are using a thermistor where the temperature - resistance relationship is

$$R = 1000 \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$

where T is the temperature in degrees C.

1) Design a linearizing circuit so that the resistance is approximately linear from 0C to +30C. Plot the resulting resistance vs. temperature relationship.

Set up a file in Matlab to compute the impedance at 15C vs. the average of 0C and 30C

```
function [ J ] = Thermistor( Z )
Ra = Z(1);
Rb = Ra;

T = [0,15,30];
R = 1000 * exp(3905 ./ (T+273) - 3905/298);
Z = (R + Ra)*Rb ./ (R + Ra + Rb);

E = Z(2) - (Z(1) + Z(3))/2;
J = E*E;
end
```

Solve using fminsearch


```
>> [Ra,e] = fminsearch('Thermistor',1000)

Ra = 592.6961

e = 2.7813e-013
```

Ra = Rb = 592.6961 Ohms
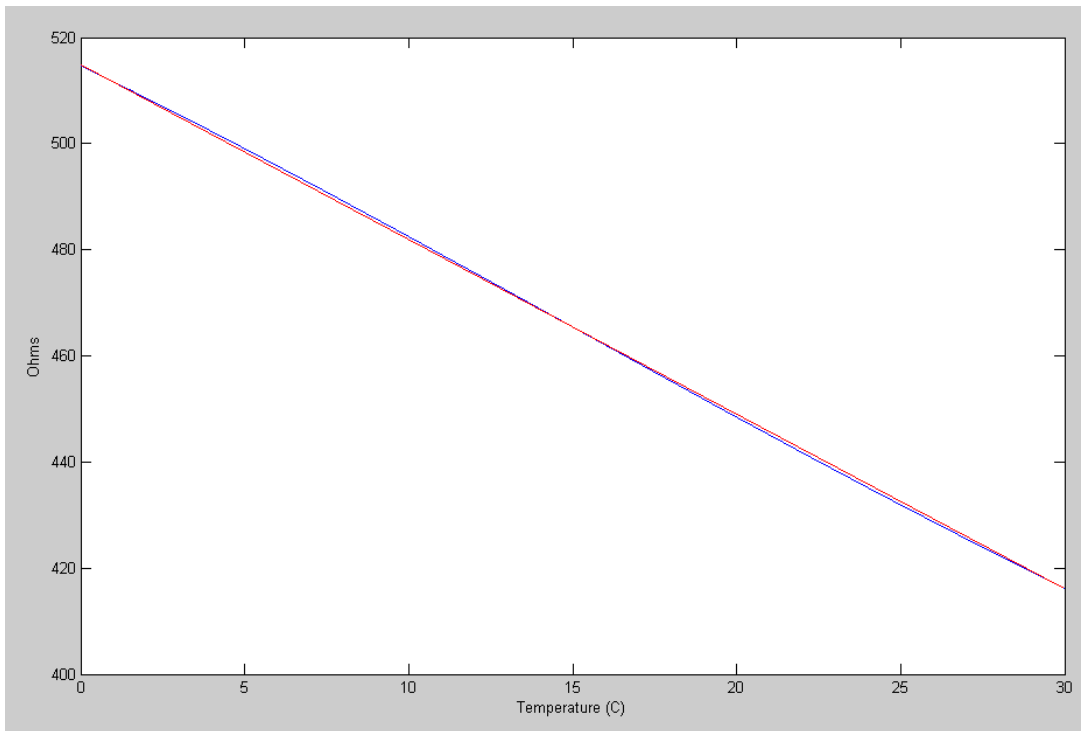
```
>> Rb = Ra;
>> T = [0:0.01:30]';
>> R = 1000*exp(3905 ./ (T+273) - 3905/298);
>> Z = (R+Ra)*Rb ./ (Ra + Rb + R);
>> plot(T,Z,'b',T([1,3000]),Z([1,3000]),'r');
>> xlabel('Temperature (C)');
>> ylabel('Ohms');
```




Linearizing Circuit Impedance for  $R_a = R_b = 592.6961$  Ohms

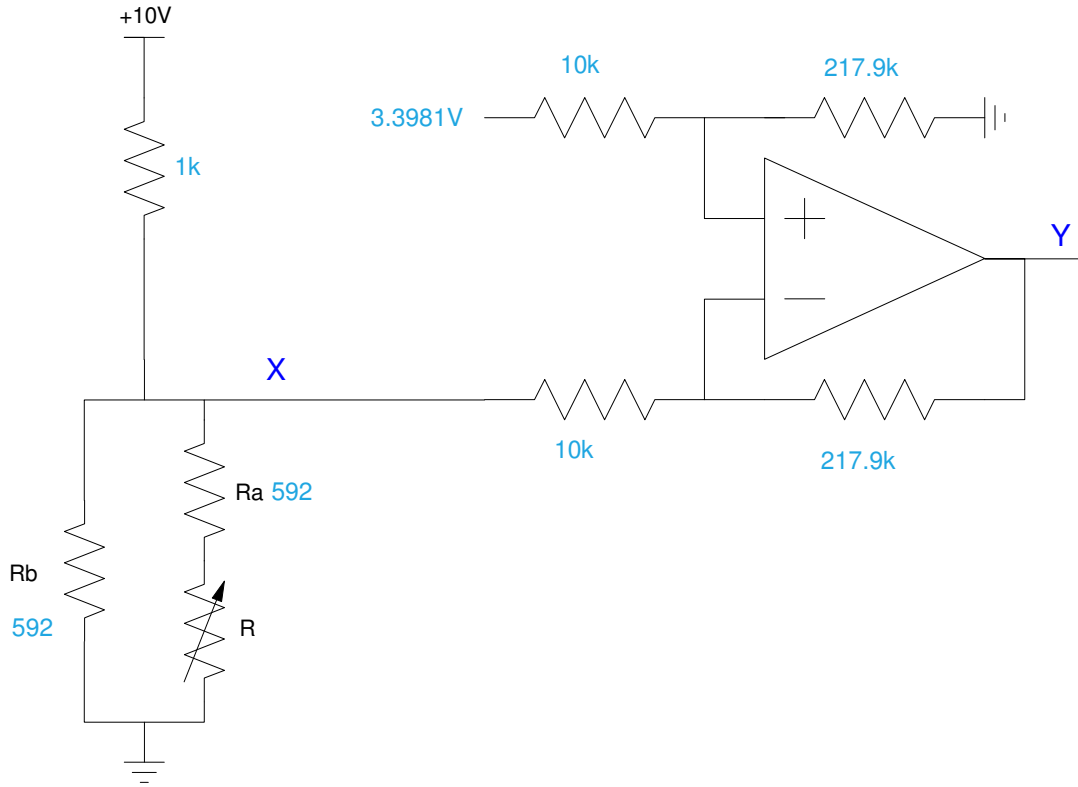2) Using the linearizing circuit from problem 4, design a circuit which outputs

- 0V at 0C
- +5V at +30C
- Proportional in between.

Plot the resulting output voltage vs. temperature.



Assume a 1k resistor for the voltage divider

0C:

- $Z = 514.722 \text{ Ohms}$
- $X = 3.3981\text{V}$
- $Y = 0\text{V}$

30C

- $Z = 416.2825 \text{ Ohms}$
- $X = 2.9393\text{V}$
- $Y = 10\text{V}$

As X goes down, Y goes up. Connect to the minus input

$Y = 0\text{V}$  when  $X = 3.3981\text{V}$ . Make the offset 3.3981V


The gain needed is

$$\text{gain} = \left( \frac{10\text{V} - 0\text{V}}{3.3981\text{V} - 2.9393\text{V}} \right) = 21.79$$

Make the gain of the instrumentation amplifier 21.79


The resulting voltage vs. temperature is
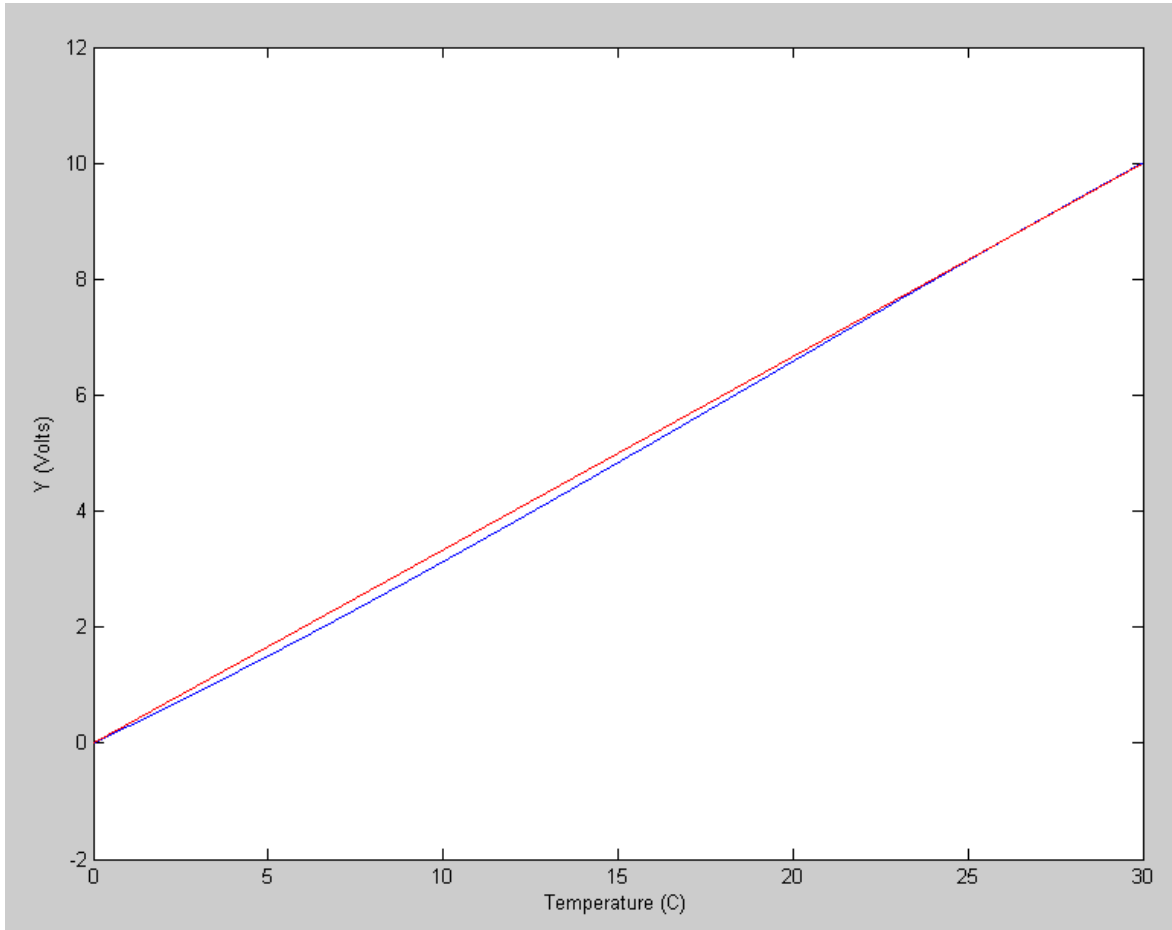
```
>> X = Z ./ (Z + 1000) * 10;  
>> Y = 21.7928 * (3.3981 - X);  
>> plot(T,Y);  
>> plot(T,Y,'b',T([1,3000]),Y([1,3000]),'r');  
>> xlabel('Temperature (C)');  
>> ylabel('Y (Volts)');
```



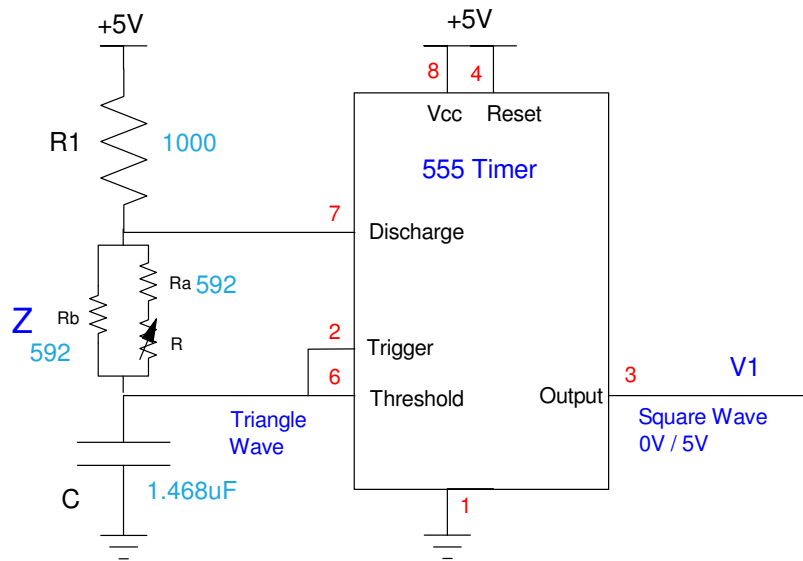3) Using the linearizing circuit from problem 4, design a 555 timer which outputs 500Hz at +10C

- Determine the frequency it outputs from 0C to +30C



$$t_{on} = (R_1 + Z) \cdot C \cdot \ln(2)$$

$$t_{off} = Z \cdot C \cdot \ln(2)$$

The period is then

$$period = (R_1 + 2Z) \cdot C \cdot \ln(2)$$

frequency is 1/period

At 10C,

$$Z = 482.54 \text{ Ohms.}$$


Let  $R_1 = 1000 \text{ Ohms}$

$$period = 2ms = (1000\Omega + 2 \cdot 482.54\Omega) \cdot C \cdot \ln(2)$$

$$C = 1.468\mu F$$

Plotting the frequency vs. temperature
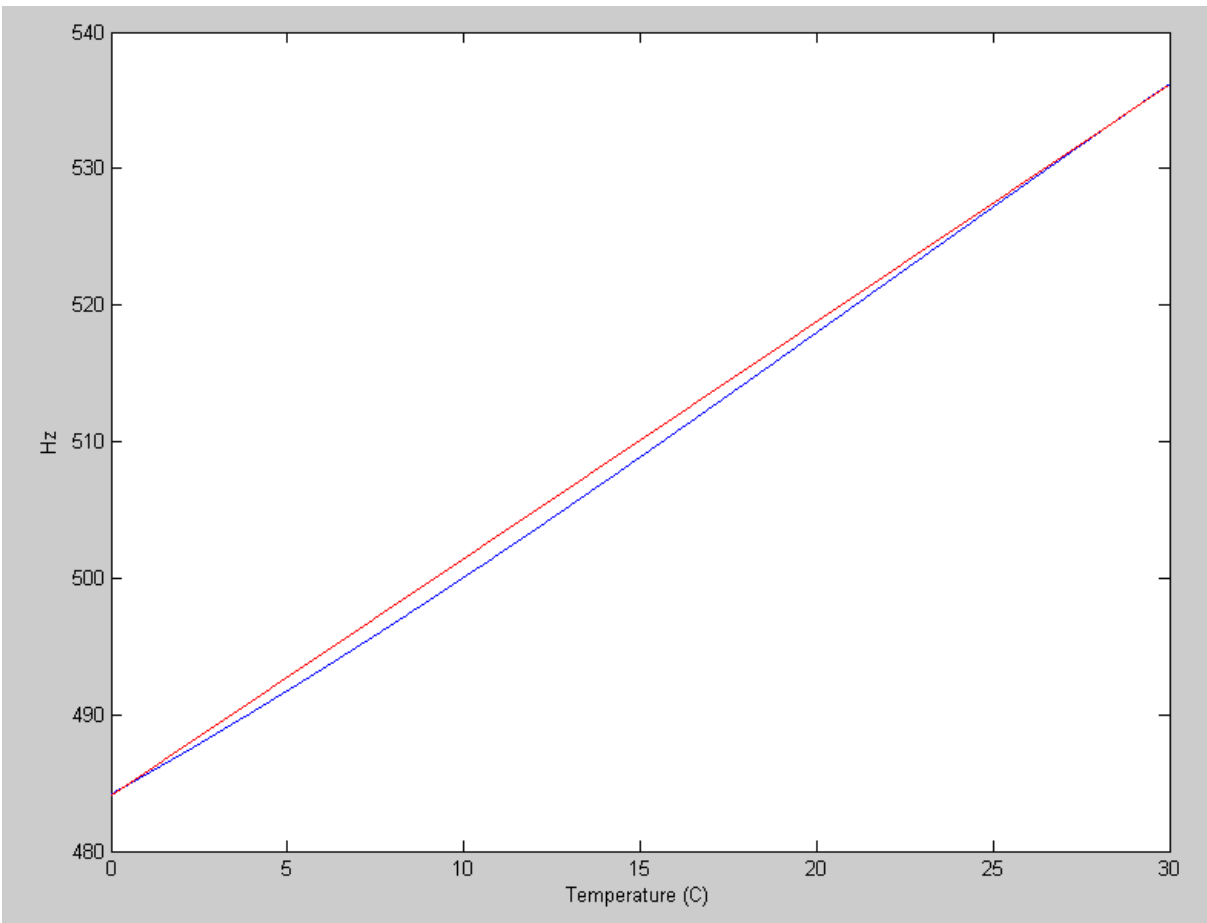
```
>> C = 1.4683e-6;
>> period = (1000 + 2*Z) * C * log(2);
>> Hz = 1 ./ period;
>> plot(T, Hz)
>> plot(T, Hz, 'b', T([1, 3000]), Hz([1, 3000]), 'r')
>> xlabel('Temperature (C)');
>> ylabel('Hz');
```



Output frequency of a 555 timer with a linearizing circuit

## Calibration

4) Assume a thermistor is used with a 1k resistor to convert resistance to voltage:

$$V = \left( \frac{R}{R+1000} \right) 10V$$

Determine a calibration function to determine temperature given the voltage as

$$T \approx aV + b$$

over the range of (0C, +30C). What is the maximum error in your curve fit?

```
>> T = [0:0.01:30]';  
>> R = 1000*exp(3905 ./ (T+273) - 3905/298);  
>> V = R ./ (R + 1000) * 10;  
>> B = [V, V.^0];  
>> A = inv(B'*B)*B'*T
```


```
a   -9.1578  
b   70.8925
```

```
>> plot(T,V,'b',T,B*A,'r')  
>> plot(V,T,'b',V,B*A,'r')  
>> xlabel('Voltage (V)');  
>> ylabel('Temperature (C)');
```

```
>> max(abs(T - B*A))
```

```
ans =    0.5125
```

The maximum error is 0.5125 degrees C

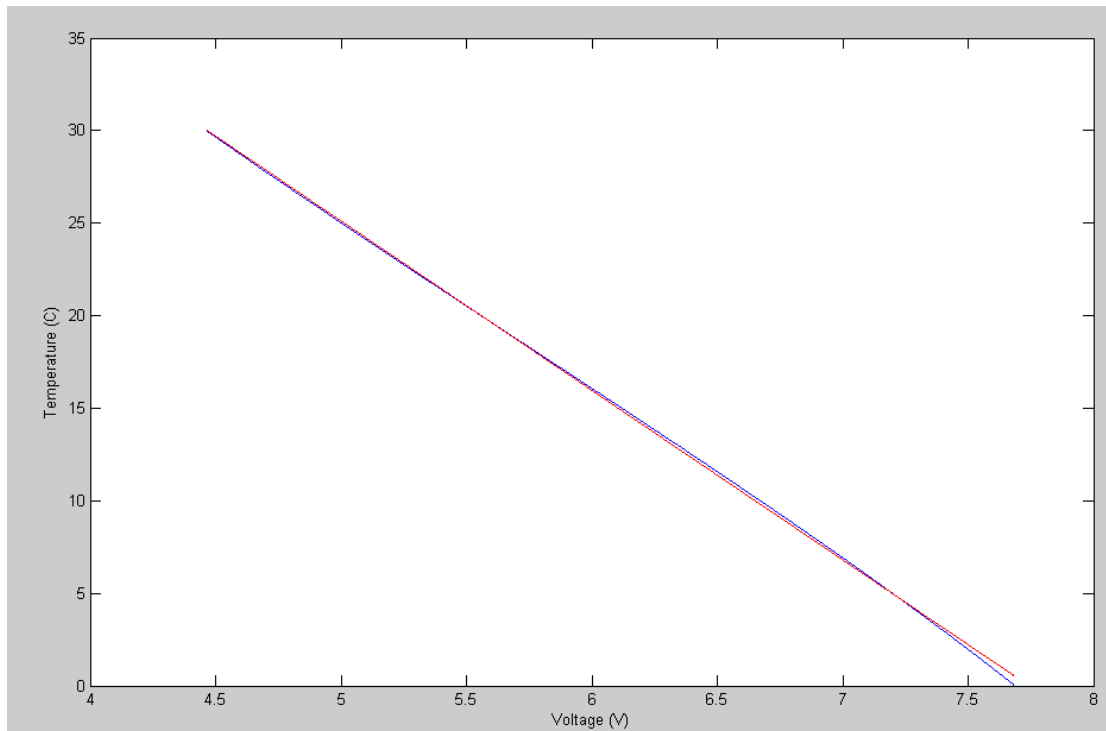

Voltage vs. Temperature & Linear Curve Fit

5) Repeat problem #4 with a cubic curve fit.

$$T \approx aV^3 + bV^2 + cV + d$$


```
>> T = [0:0.01:30]';  
>> R = 1000*exp(3905 ./ (T+273) - 3905/298);  
>> V = R ./ (R + 1000) * 10;  
>> B = [V.^3, V.^2, V, V.^0];  
>> A = inv(B'*B)*B'*T
```

```
a   -0.1457  
b    2.5048  
c   -23.2255  
d    96.7149
```

```
>> plot(V,T,'b',V,B*A,'r')  
>> xlabel('Voltage (V)');  
>> ylabel('Temperature (C)');  
>> max(abs(T - B*A))
```

```
ans =    0.0247
```

The maximum error is 0.0247 degrees C

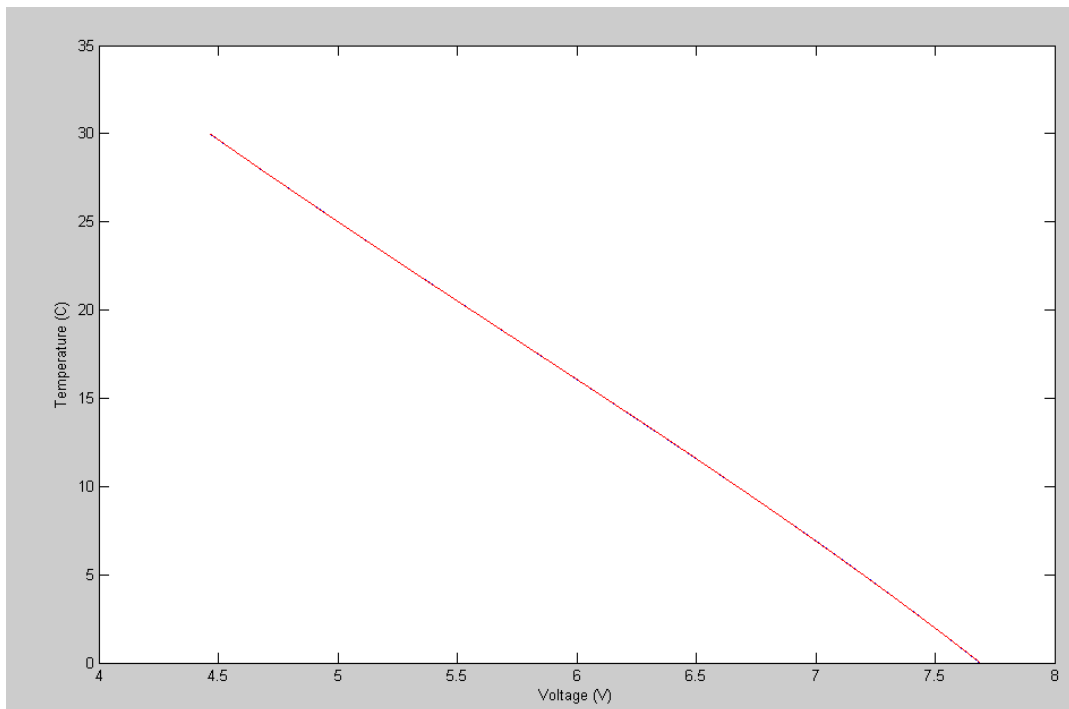

Voltage vs. Temperature and Cubic Curve Fit




## Audio / Strain Sensors

6) A strain sensor is connected to a metal rod to measure the force applied to the center of the beam. Assume

- The beam's thickness is 1mm,
- The beam's length is 100mm,
- The beam deflects 6mm when a force of 200lb is applied to it, and
- The strain - resistance relationship of the strain sensor is

$$R = 120(1 + 2.14\epsilon)\Omega$$

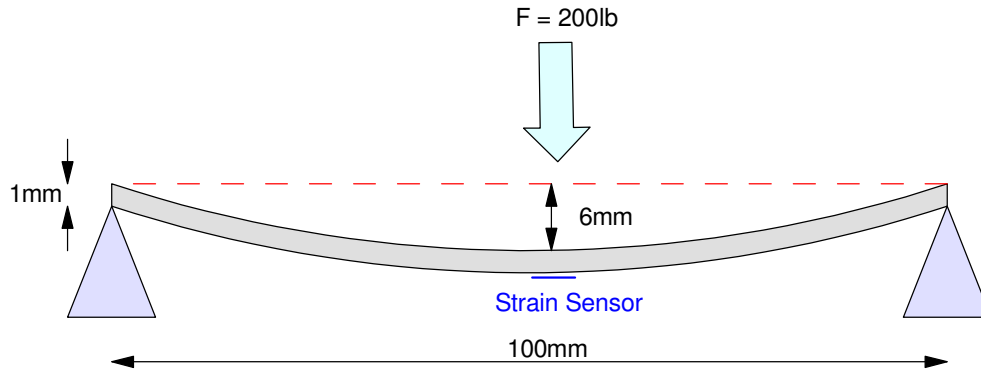a) Determine the strain and the resistance when the beam deflects by 6mm



First, find the radius of the arc

$$R^2 = 50^2 + (R - 6)^2$$

$$R = 211.33\text{mm}$$

The strain is then

$$\epsilon = \left( \frac{0.5\text{mm center line to outside}}{211.33\text{mm}} \right) = 0.002366$$

b) Design a circuit which outputs

- 0V at 0lb force and
- 10V at 200lb force

At 0lb force

$$R = 120$$

At 200lb force

$$R = 120 \cdot (1 + 2.14\epsilon)\Omega = 120.6075\Omega$$

Use a voltage divider with a 120 ohm resistor

At 0lb

$$X = 5.000V$$

At 200lb

$$X = \left( \frac{120.6075}{120.6075 - 120} \right) 10V = 5.012626V$$


The offset should be 2.5000V so that  $Y = 0V$  at 0lb input

As  $X$  increases,  $Y$  increases. Connect to the the plus input

The gain needed is

$$gain = \left( \frac{10V - 0V}{5.012626V - 5.000V} \right) = 792.03$$

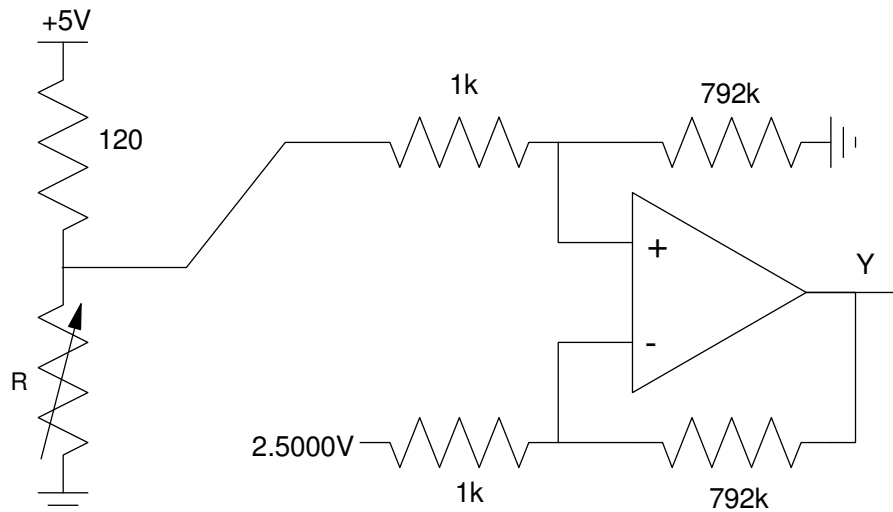(note: if you use two strain gages, the gain is 1/2 of 792. If you use four strain gages, the gain is 1/4th of 792)




## Sound to Light

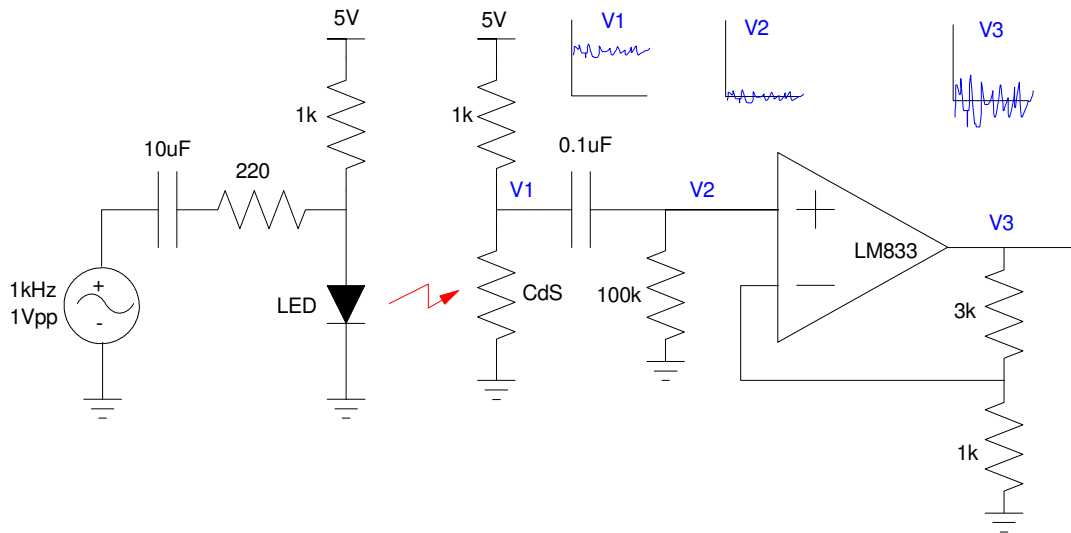7) Assume the CdS light sensor has a resistance of

$$R = 1000 + 50 \sin(\omega t) \text{ Ohms}$$

determine the voltages at V1, V2, and V3 (both DC and AC. Peak-to-peak voltages are OK (and easier) for the AC voltages).



$$V_1(1000\Omega) = 2.500V$$

$$V_1(1050\Omega) = \left( \frac{1050}{1050+1000} \right) 5V = 2.56098V$$

----

$$V_1(DC) = 2.50V$$

$$V_1(AC) = 60.98mV_p$$

V2 passes the AC and blocks the DC term (2.5V)

$$V_2(DC) = 0V$$

At 1kHz, 0.1uF has an impedance of -j1592 Ohms

$$V_2(AC) = \left( \frac{100k}{100k-j1592} \right) 60.98V_p$$

$$V_2(AC) = 60.97mV_p$$

$$V_3 = 4 \cdot V_2$$

$$V_3(DC) = 0V$$

$$V_3(AC) = 243.88mV_p$$

### **Hardware (option #1)**

8) Design a circuit to amplify a condenser microphone to 0..5V

Note: You can also use a speaker as a microphone. From duality

- If you apply a voltage to a speaker, it produces sound
- If you apply sound to a speaker, it produces voltage

9) Test your audio amplifier with your amplifier with the push-pull amplifier from homework set #1 and your amplifier in problem #8.

### **Hardware (option #2)**

8) Build the light-to-sound circuit for problem #7. Measure the voltages for a 1kHz sine wave input.

9) Test your light-to-sound circuit with the push-pull amplifier from homework set #1 and an audio signal from your cell phone (or similar device).