


ECE 321 - Final Exam - Name _____

Spring 2023

1. OpAmp Circuits: Determine y as a function of A , B , C , and D . Assume

- Ideal op-amps
- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$.

| R $800 + 100 \cdot \text{mo} + \text{day}$ | $Y = aA + bB + cC + dD$ |
|---|--|
| 1314 | $Y = -11.41A - 15.00B - 6.81C - 5.18D$ |

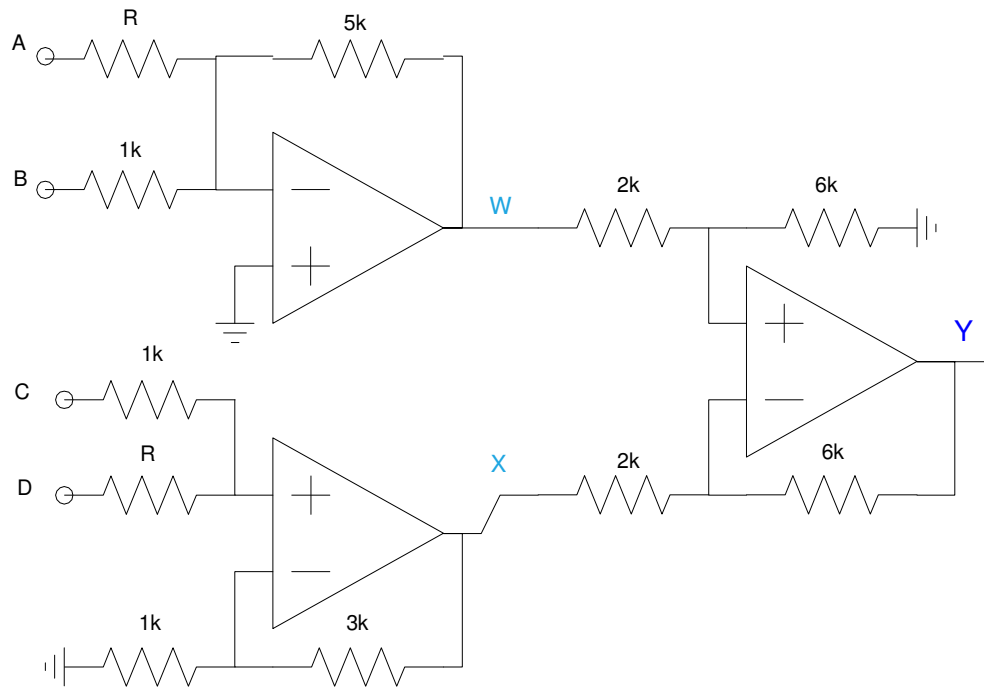

$$W = -\left(\frac{5k}{1314}\right)A - \left(\frac{5k}{1k}\right)B$$


$$X = \left(1 + \frac{3k}{1k}\right) \left(\left(\frac{1314}{1k+1314}\right)C + \left(\frac{1k}{1314+1k}\right)D \right)$$

$$Y = 6(W - X)$$

2. Push-Pull: Determine the voltages and currents for the following push-pull amplifier when $X = -4V$. Assume

- $R = 800 + 100 * (\text{birth month}) + (\text{birth day})$.
- $|V_{ce}| = 0.7V$ (ideal silicon diodes)
- $\beta = 30$

| R 800 + 100*mo + day | V1 | V2 | V3 | I4 | I5 |
|-------------------------|----------------|----------------|---------------|----------------|---------------|
| 1314 | -9.9560 | -9.2560 | -4.000 | 37.45mA | 1.161A |

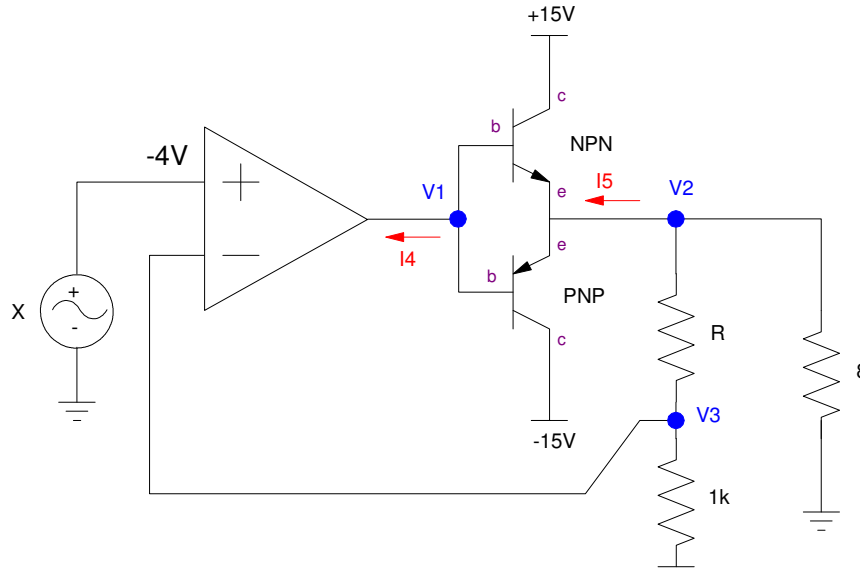

$$V_3 = -4V$$

$$V_2 = \left(1 + \frac{R}{1k}\right) V_3 = -9.256V$$

$$V_1 = V_2 - 0.7 = -9.9560V$$

$$I_5 = \frac{V_2}{8} + \frac{V_2}{1k+R} = 1.161A$$

$$I_4 = \frac{I_5}{\beta+1} = 37.45mA$$

3. Instrumentation Amplifier: Assume an RTD has the temperature - resistance relationship of


$$R_x = 1000 \cdot (1 + 0.0043T)\Omega$$

where T is the temperature in degrees C. Design a circuit which outputs

- +10V at +40C, and
- 0V at 0C

Assume

- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$

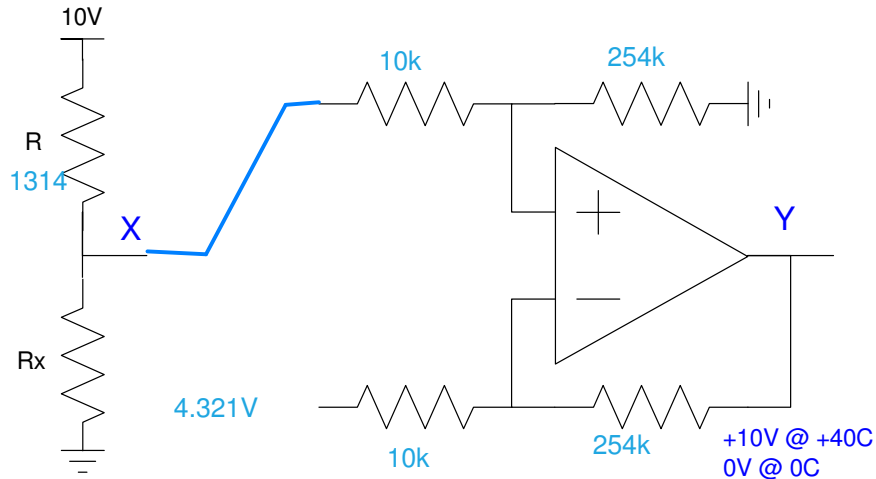

At 0C

$$R_x = 1000$$

$$X = \left(\frac{R_x}{R_x + 1314} \right) 10V = 4.321V$$

At 40C

$$R_x = 1172\Omega$$

$$X = \left(\frac{R_x}{R_x + 1314} \right) 10V = 4.7144V$$

Offset = 4.321V (where Y = 0)

Connect to the + input (Y goes up as X goes up)


$$gain = \left(\frac{10V - 0V}{4.7144V - 4.321V} \right) = 25.45$$

4. Filters: Let

- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$.

Determine the poles and the DC gain

| R 800 + 100*mo + day | Transfer Function $Y = G(s) \cdot X$ |
|-------------------------|--|
| 1314 | $\left(\frac{8.4621 \cdot 76.10 \cdot 38.05 \cdot 761.03^2}{(s+76.10)(s+38.05)(s+761.03 \angle \pm 51.72^\circ)} \right)$ |

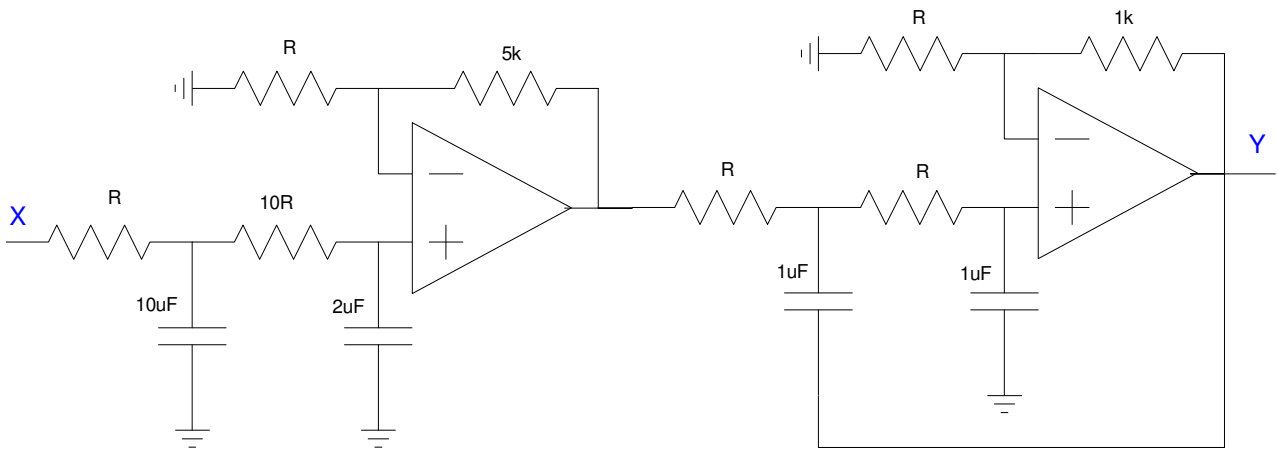

pole 1: 76.1035 38.0518 761.0350 51.7216 8.4621

$$pole = -\left(\frac{1}{RC}\right) = -\left(\frac{1}{1314 \cdot 10\mu F}\right) = -76.103$$

$$pole = -\left(\frac{1}{RC}\right) = -\left(\frac{1}{1340 \cdot 2\mu F}\right) = -38.0518$$

$$pole_3 = -\left(\frac{1}{RC}\right) = -\left(\frac{1}{1314 \cdot 1\mu F}\right) = -761.03$$

$$k = 1 + \frac{1k}{R} = 1.7610$$

$$3 - k = 2 \cos \theta$$

$$\theta = 57.721^\circ$$

$$DC = \left(1 + \frac{5k}{R}\right) \left(1 + \frac{1k}{R}\right) = 8.4621$$

5) Filter Analysis: Determine $y(t)$ given

$$Y = \left(\frac{20s}{s^2 + 2s + 100} \right) X$$

$$x(t) = 4 + m \cos(10t) + d \sin(10t)$$

$$x(t) = 4 + 5 \cos(10t) + 14 \sin(10t)$$

where

- m is your birth month(1..12) and
- d is your birth date (1..31)

DC:

$$s = 0$$

$$X = 4$$

$$Y = \left(\frac{20s}{s^2 + 2s + 100} \right)_{s=0} \cdot (4)$$

$$Y = 0$$

AC:

$$s = j10$$

$$X = 5 - j14$$

$$Y = \left(\frac{20s}{s^2 + 2s + 100} \right)_{s=j10} \cdot (5 - j14)$$

$$Y = 50 - j140$$

$$y(t) = 50 \cos(10t) + 140 \sin(10t)$$

real = cosine, -imag = sine



Total

$$Y = 0 + 50 \cos(10t) + 140 \sin(10t)$$

6. CE Amplifiers (DC analysis): Determine the Q-point for the following circuit. Assume

- $R_2 = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$
- $\beta = 30$
- $|V_{be}| = 0.7V$ (ideal silicon diode)

| R2 | Vb | Rb | Vce | Ic |
|--------------------|-----------------|--------------------|-----------------|----------------|
| 800 + 100*mo + day | | | | |
| 1314 | 2.1559 V | 1077.9 Ohms | 8.8107 V | 349.2uA |

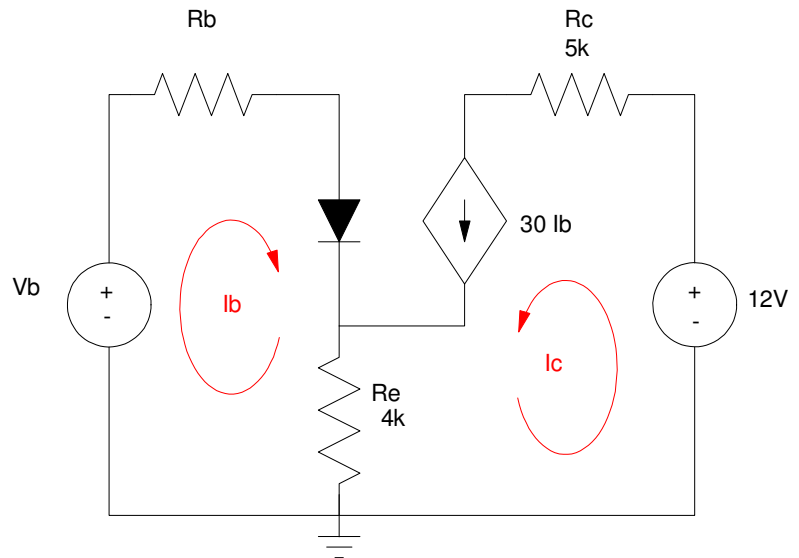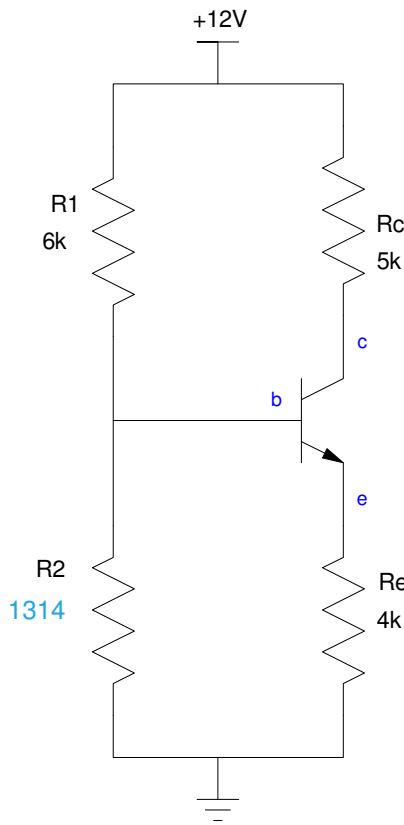

$$R_b = R_1 || R_2 = 1077.9\Omega$$

$$V_b = \left(\frac{R_2}{R_1 + R_2} \right) 12V = 2.1559V$$

$$I_b = \left(\frac{V_b - 0.7}{R_b + (1 + \beta)R_e} \right) = 11.64\mu A$$

$$I_c = \beta I_b = 349.2\mu A$$



$$V_{ce} = 12 - R_c I_c - R_e (I_b + I_c) = 8.8107V$$

7. 2-Port model: Determine the 2-port parameters for the following circuit. Assume

- $R = 800 + 100 * (\text{your birth month}) + (\text{your birth date})$ Ohms

| R 800 + 100*mo + day | R _{in} | A _i | R _{out} | A _o |
|-------------------------|-------------------|----------------|-------------------|----------------|
| 1314 | 962.6 Ohms | 0.7326 | 41.36 Ohms | 0.9759 |

0.9626 0.7326 41.3643 0.9759

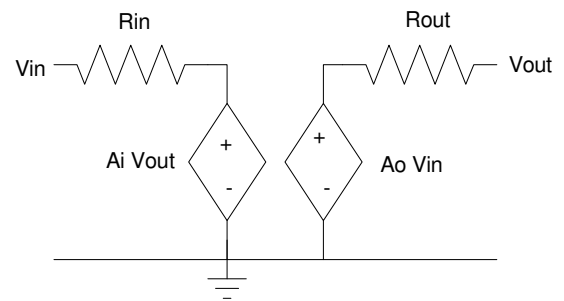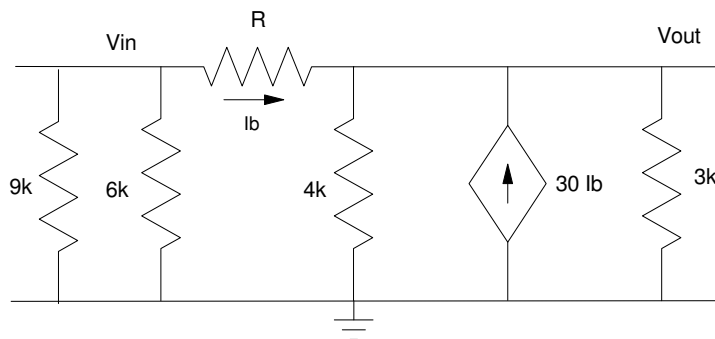

R_{in}: Short V_{out}, measure the resistance at the input.

$$R_{in} = 9k || 6k || R = 962.6\Omega$$

A_{in}: Apply 1V at V_{out}, measure V_{in}. By voltage division

$$A_{in} = \left(\frac{9k || 6k}{9k || 6k + R} \right) = 0.7326$$

R_{out}: Short V_{in}. Apply 1V to V_{out} and compute the current draw

$$I = \left(\frac{1}{3k} \right) + \left(\frac{1}{4k} \right) + \left(\frac{1}{R} \right) + 30 \left(\frac{1}{R} \right) = 24.18mA$$

$$R_{out} = \frac{1V}{24.18mA} = 41.36\Omega$$


A_{out}: Apply 1V to V_{in}, compute V_{out}. Do a voltage node equation at V_{out}

$$\left(\frac{V_o - 1}{R} \right) + \left(\frac{V_o}{4k} \right) + 30 \left(\frac{V_o - 1}{R} \right) + \left(\frac{V_o}{3k} \right) = 0$$

$$V_o = 0.9759V$$

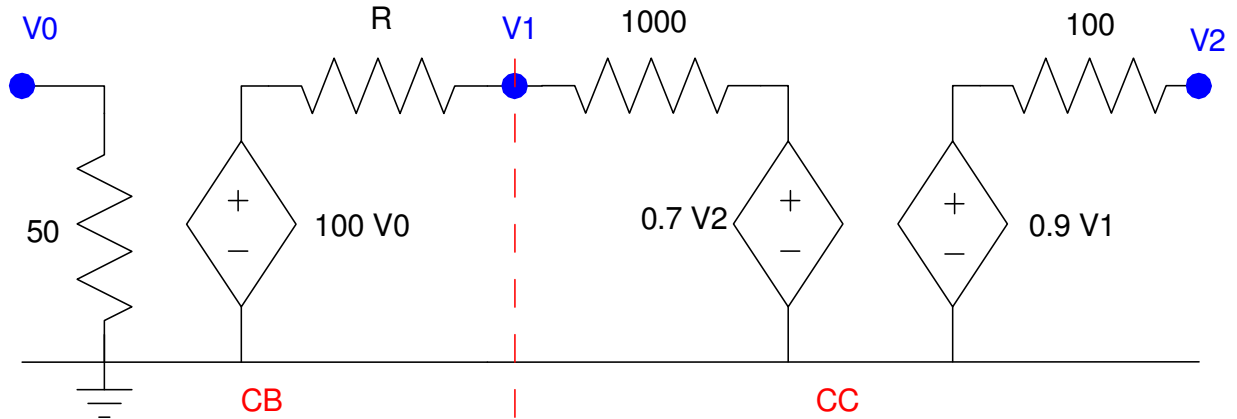8. 2-Port model: Determine the 2-port parameters for a Common-Base amplifier cascaded with a Common Collector amplifier. Assume

- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$ Ohms



| R 800 + 100*mo + day | Rin | Ain | Rout | Aout |
|-------------------------|-----------|----------|--------------------|--------------|
| 1314 | 50 | 0 | 155.70 Ohms | 60.55 |

By inspection

$$R_{in} = 50$$

$$A_{in} = 0$$

Rout: Short V0, Apply 1V to V2. Compute the current draw

$$V_1 = \left(\frac{R}{R+1000} \right) 0.7V = 0.3975V$$

$$I = \left(\frac{1V - 0.9 \cdot 0.3975V}{100\Omega} \right) = 6.423mA$$

$$R_{out} = \frac{1V}{I} = 155.7\Omega$$