


ECE 321 - Final Exam - Name _____

Spring 2023

1. OpAmp Circuits: Determine y as a function of A, B, C, and D. Assume

- Ideal op-amps
- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$.


R 800 + 100*mo + day	$Y = aA + bB + cC + dD$

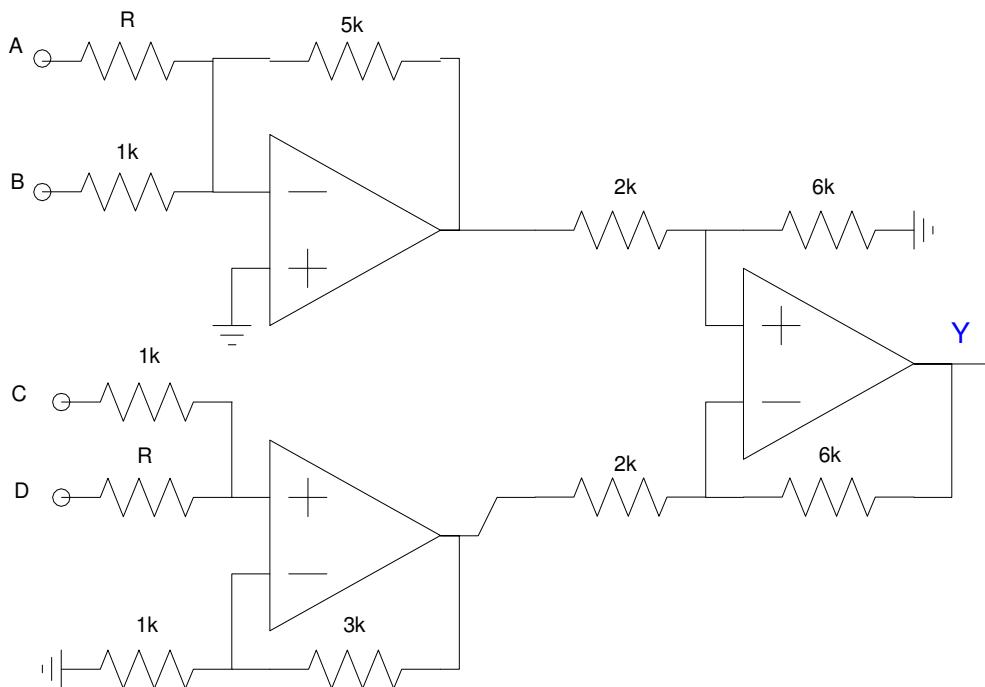

2. Push-Pull: Determine the voltages and currents for the following push-pull amplifier when X = -4V. Assume

- $R = 800 + 100 \cdot (\text{birth month}) + (\text{birth day})$.
- $|V_{ce}| = 0.7V$ (ideal silicon diodes)
- $\beta = 30$

R $800 + 100 \cdot \text{mo} + \text{day}$	V1	V2	V3	I4	I5

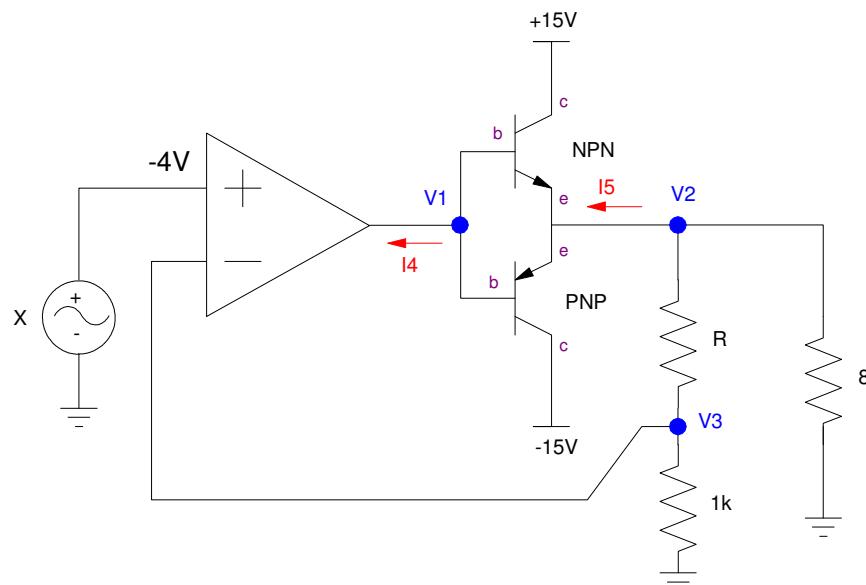

3. Instrumentation Amplifier: Assume an RTD has the temperature - resistance relationship of



$$R_t = 1000 \cdot (1 + 0.0043T) \Omega$$

where T is the temperature in degrees C. Design a circuit which outputs

- +10V at +40C, and
- 0V at 0C

Assume

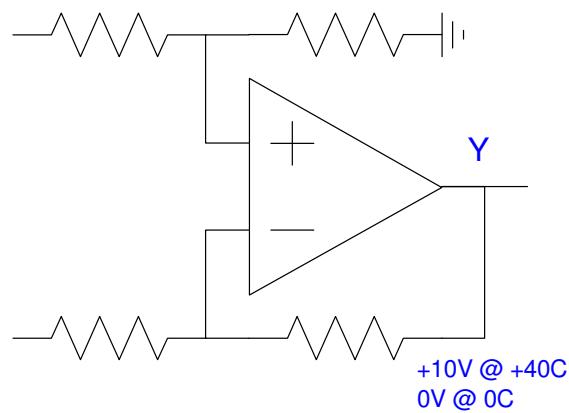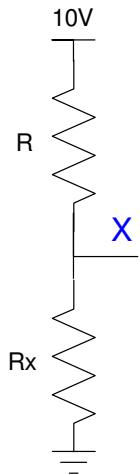- $R = 800 + 100*(\text{your birth month}) + (\text{your birth date})$




4. Filters: Let

- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$.

Determine the poles and the DC gain

R $800 + 100 \cdot \text{mo} + \text{day}$	Transfer Function $Y = G(s) * X$

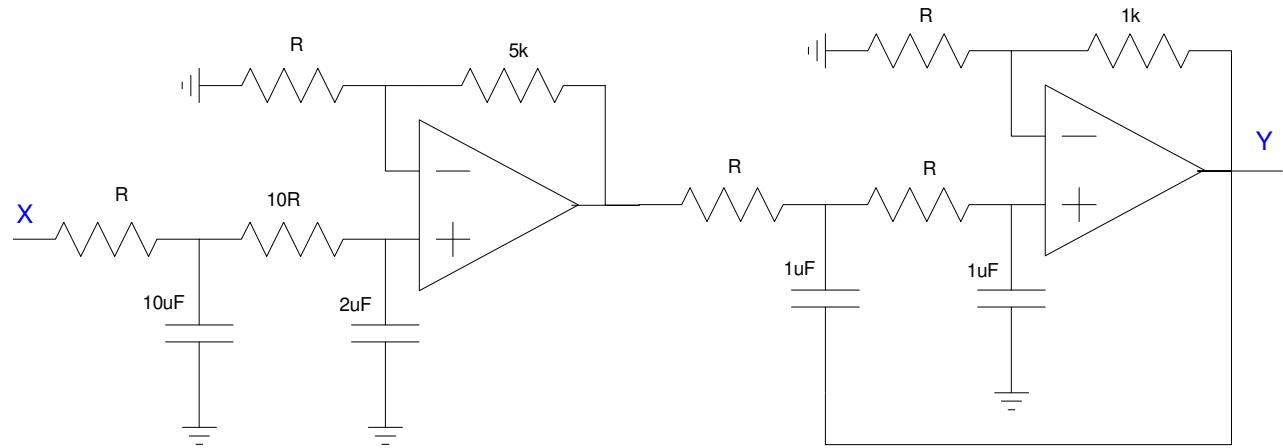

5) Filter Analysis: Determine $y(t)$ given

$$Y = \left(\frac{20s}{s^2 + 2s + 100} \right) X$$

$$x(t) = 4 + m \cos(10t) + d \sin(10t)$$



where

- m is your birth month(1..12) and
- d is your birth date (1..31)

6. CE Amplifiers (DC analysis): Determine the Q-point for the following circuit. Assume

- $R_2 = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$
- $\beta = 30$
- $|V_{be}| = 0.7V$ (ideal silicon diode)



R_2 $800 + 100 \cdot \text{mo} + \text{day}$	V_b	R_b	V_{ce}	I_c

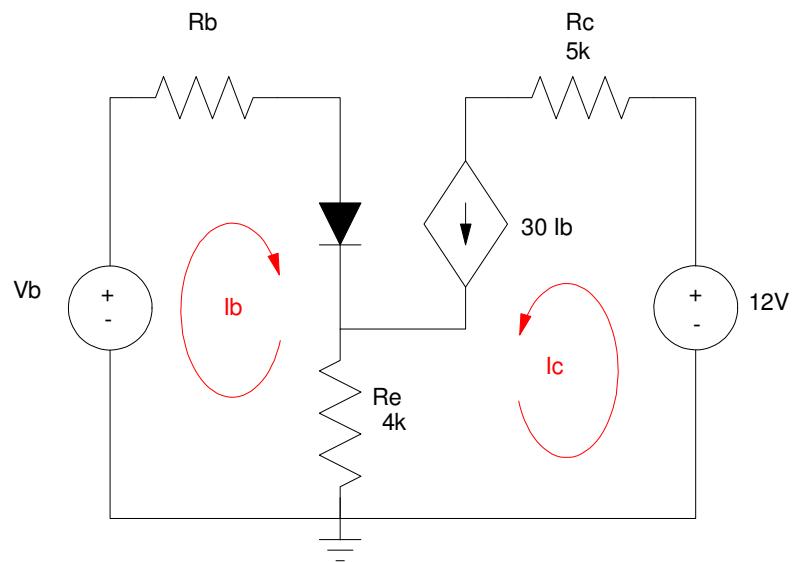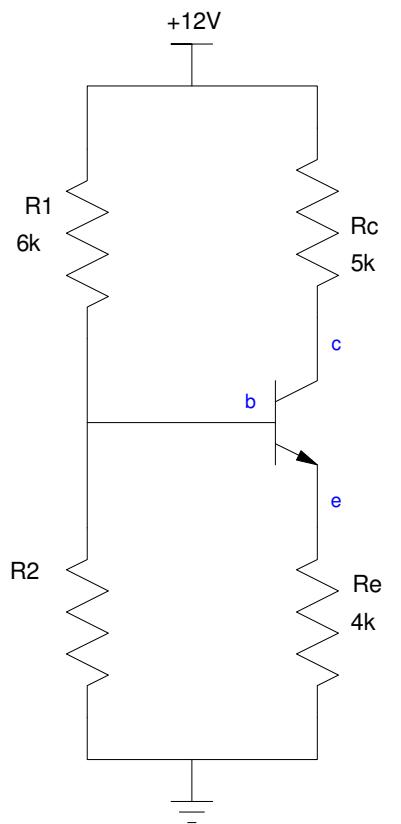

7. 2-Port model: Determine the 2-port parameters for the following circuit. Assume


- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date}) \text{ Ohms}$

R $800 + 100 \cdot \text{mo} + \text{day}$	R_{in}	A_i	R_{out}	A_o

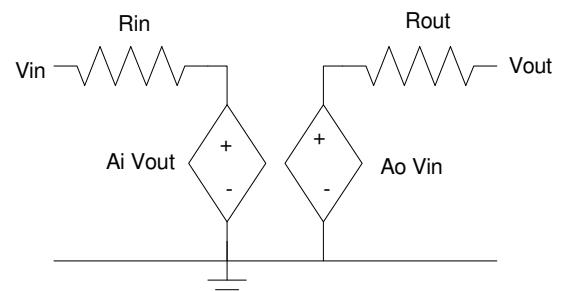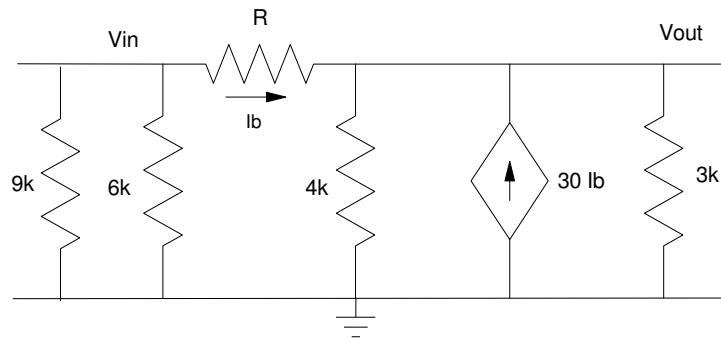

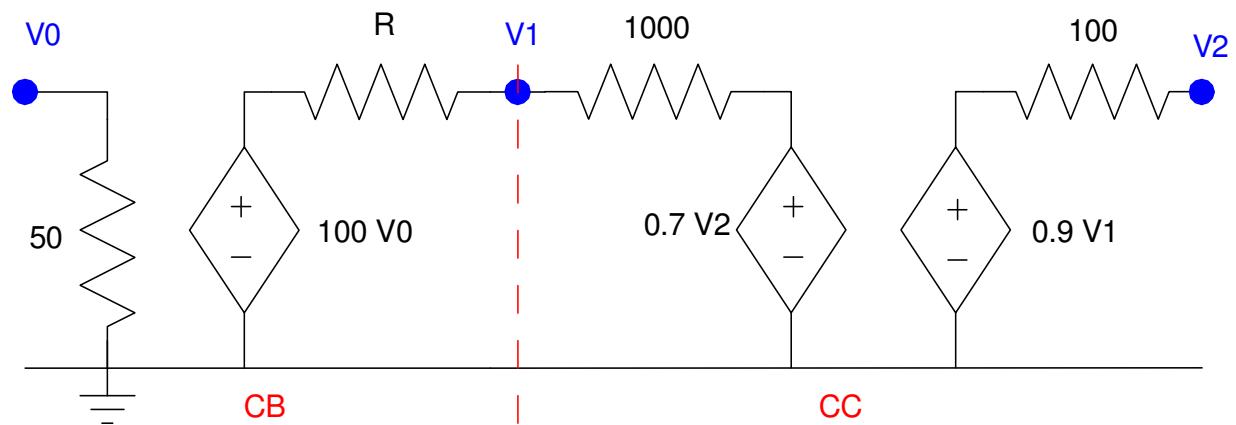8. 2-Port model: Determine the 2-port parameters for a Common-Base amplifier cascaded with a Common Collector amplifier. Assume

- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date}) \text{ Ohms}$



R $800 + 100 \cdot \text{mo} + \text{day}$	R_{in}	A_{in}	R_{out}	A_{out}