

ECE 321 - Homework #3

Calibration & Noise, Active Filters. Due Monday, April 17th
Please email to jacob.glower@ndsu.edu, or submit as a hard copy, or submit on BlackBoard

Filters

1) Assume X and Y are related by the following transfer function:

$$Y = \left(\frac{80}{(s+5)(s+10)} \right) X$$

- What is the differential equation relating x and y?
- Determine y(t) assuming

$$x(t) = 6 + 2 \cos(4t) + 3 \sin(4t)$$

Filter Design


2) Give an op-amp circuit to implement the following filter

$$Y = \left(\frac{400}{(s+2)(s+8)(s+10)} \right) X$$

3) Give an op-amp circuit to implement the following filter

$$Y = \left(\frac{200}{(s^2+s+20)(s^2+5s+30)} \right) X$$

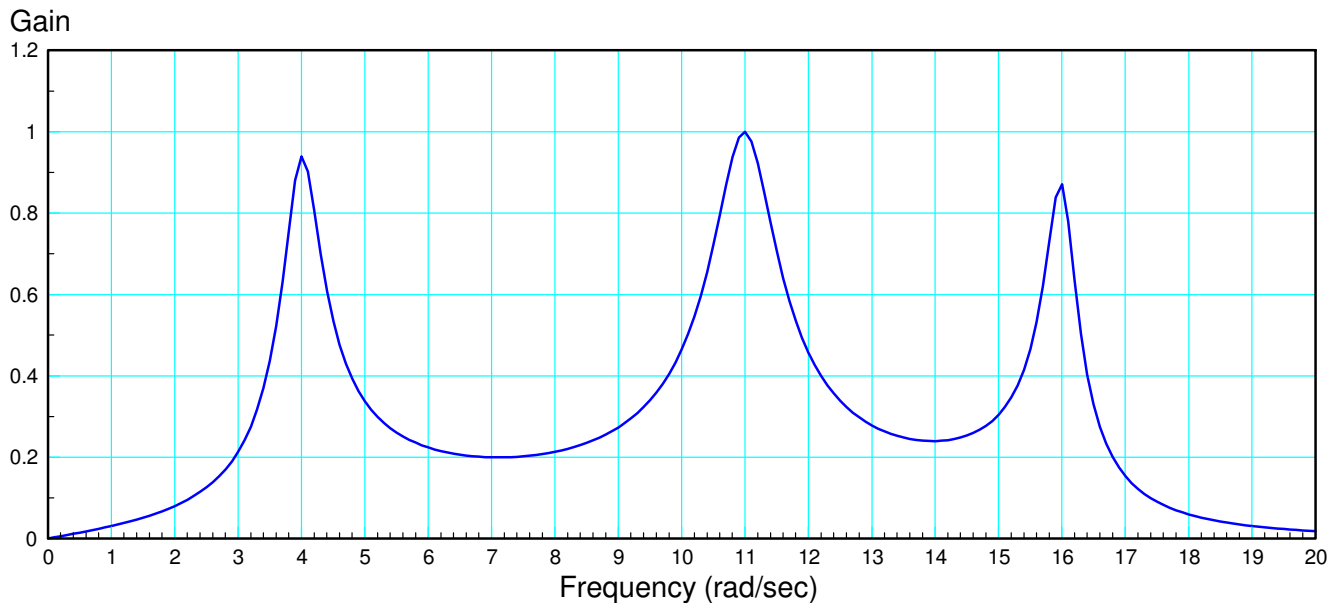4) Give the transfer function of a filter with the following gain vs. frequency




Filter Design using *fminsearch()*

5) Design a filter of the form

$$Y = \left(\frac{a}{(s+b)(s^2+cs+d)(s^2+es+f)} \right) X$$

to give a gain vs. frequency as close to the following plot as possible over the range of (0, 10) rad/sec.

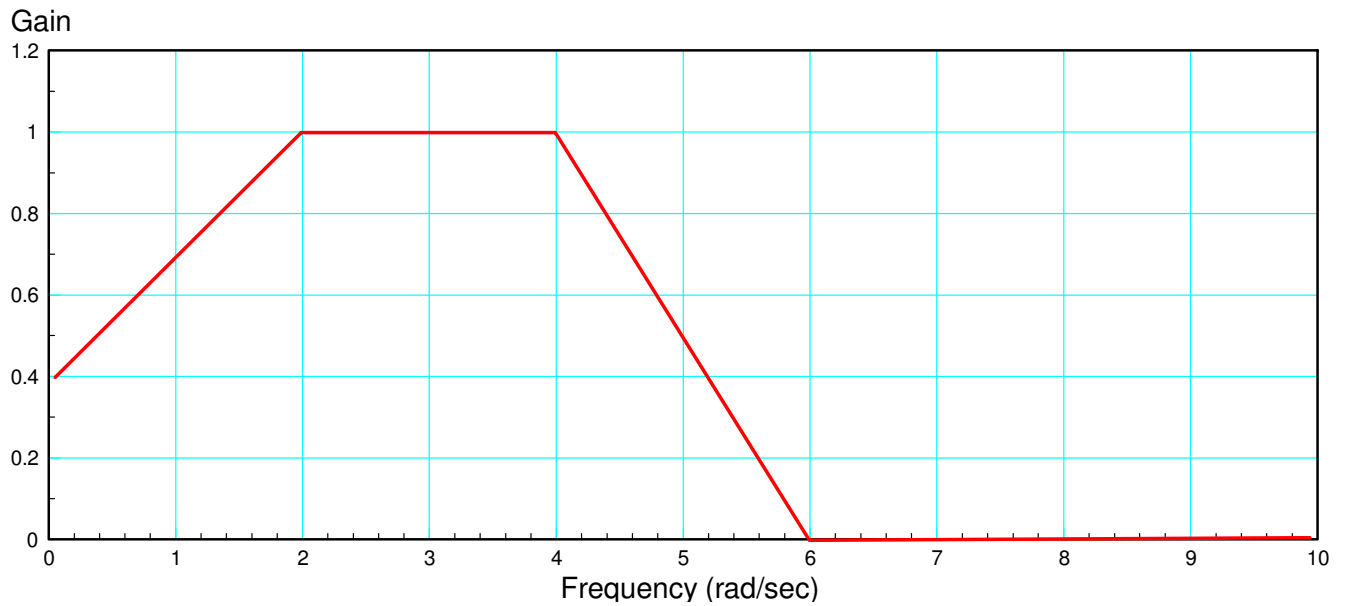Plot your filter's actual frequency response vs. its ideal response (red line).



6) Design circuit to implement the filter you designed in problem #5

7) Check your filter using CircuitLab