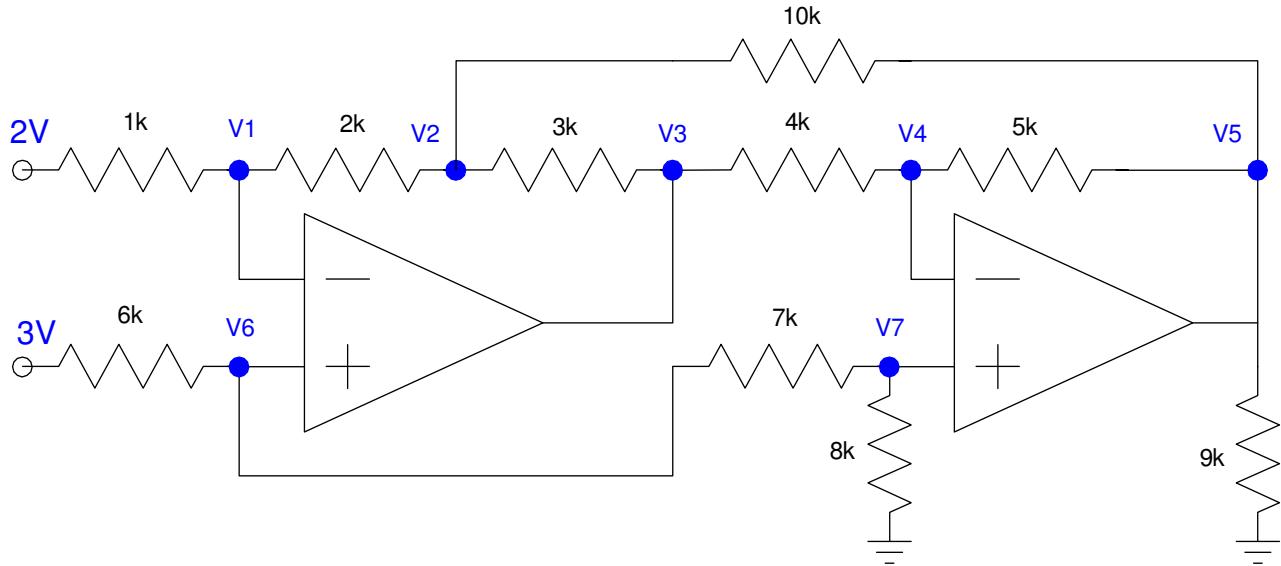


# ECE 321 - Quiz #1 - Name \_\_\_\_\_

Op-Amp Amplifiers & mixers., Push-Pull Amplifiers - Spring 2023

1) Give 7 equations which allow you to solve for the 7 unknown voltages. You do not need to solve.

- Assume ideal op-amps.



Start with the easy ones:  $V_p = V_m$

$$V_1 = V_6$$

$$V_4 = V_7$$

Now do the rest of the node equations

$$\left( \frac{V_1 - 2}{1k} \right) + \left( \frac{V_1 - V_2}{2k} \right) = 0$$

$$\left( \frac{V_2 - V_1}{2k} \right) + \left( \frac{V_2 - V_3}{3k} \right) + \left( \frac{V_2 - V_5}{10k} \right) = 0$$


$$\left( \frac{V_4 - V_3}{4k} \right) + \left( \frac{V_4 - V_5}{5k} \right) = 0$$

$$\left( \frac{V_6 - 3}{6k} \right) + \left( \frac{V_6 - V_7}{7k} \right) = 0$$

$$\left( \frac{V_7 - V_6}{7k} \right) + \left( \frac{V_7}{8k} \right) = 0$$

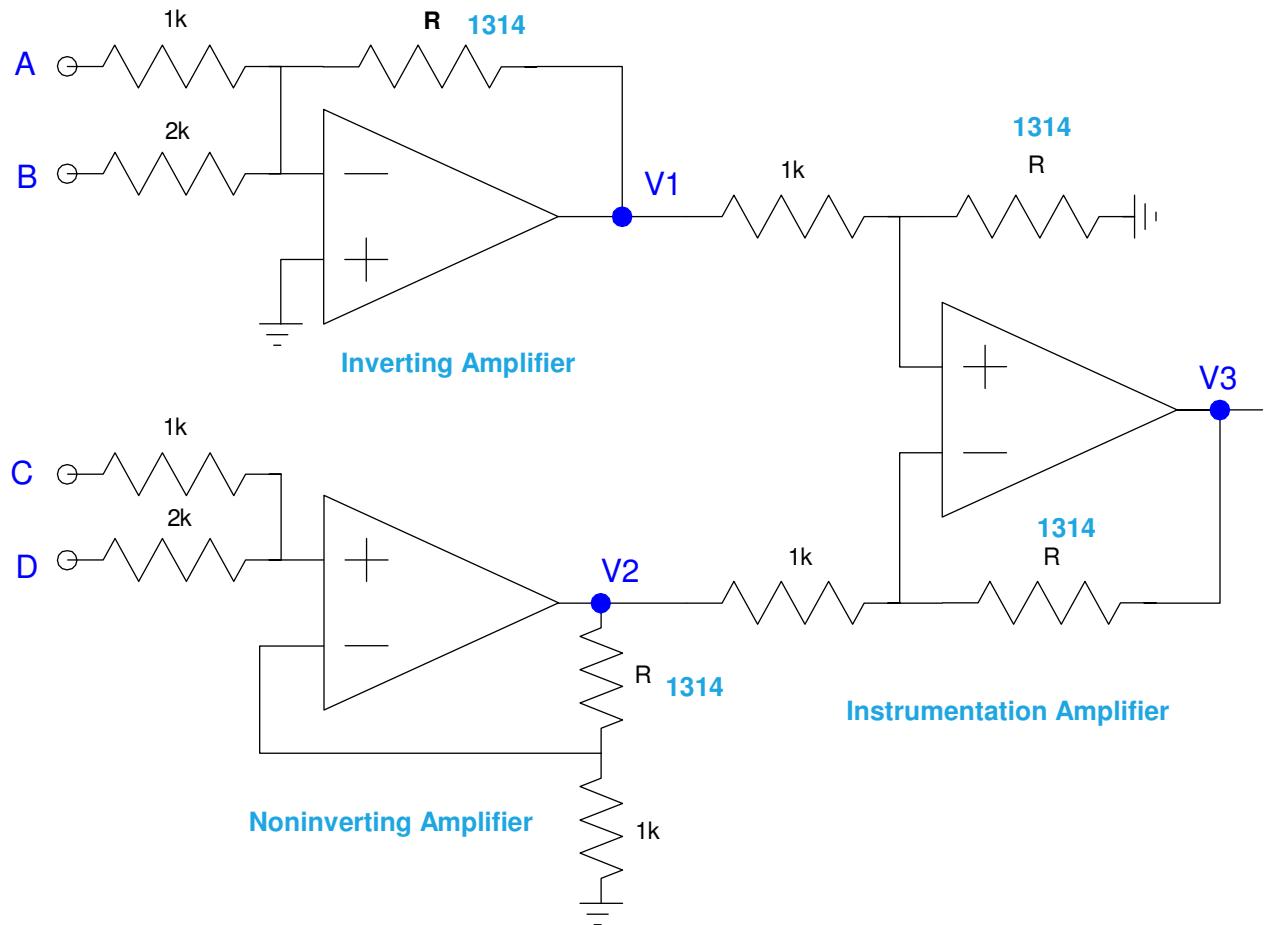2) Determine V<sub>1</sub>, V<sub>2</sub>, and V<sub>3</sub> as a function of A, B, C, and D.

- Assume ideal op-amps
- Assume R = 800 + 100\*(your birth month) + (your birth day).



$$V_1 = -\left(\frac{1314}{1k}\right)A - \left(\frac{1314}{2k}\right)B$$

$$V_2 = \left(1 + \frac{1314}{1k}\right) \left(\frac{2C+D}{3}\right)$$

$$V_3 = \left(\frac{1314}{1k}\right)(V_1 - V_2)$$

3) Design a circuit which outputs


$$Y = 1.3A + 2.5B + 3.7C$$

note: the gain on A and B are positive

Add a dummy variable

$$X = \left( \frac{1.3A + 2.5B + 3.7C}{7.5} \right)$$


$$Y = 7.5X$$

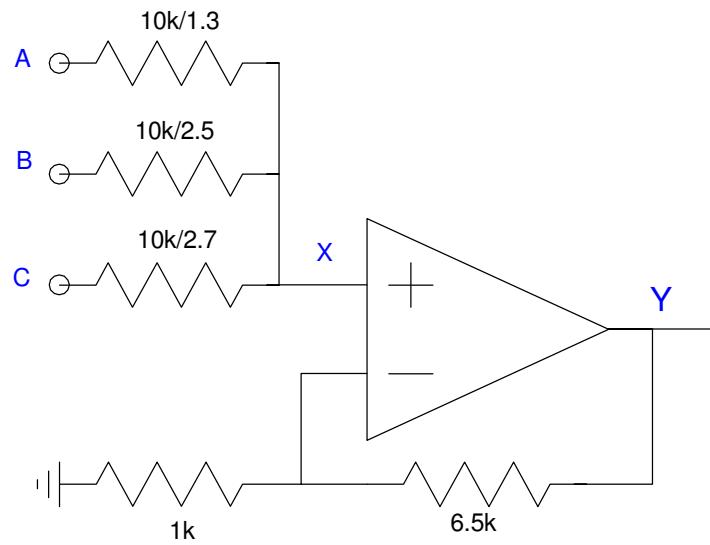

4) Design a circuit which outputs


$$Y = 1.3A - 2.5B + 3.7C$$

note: the gain on B is negative

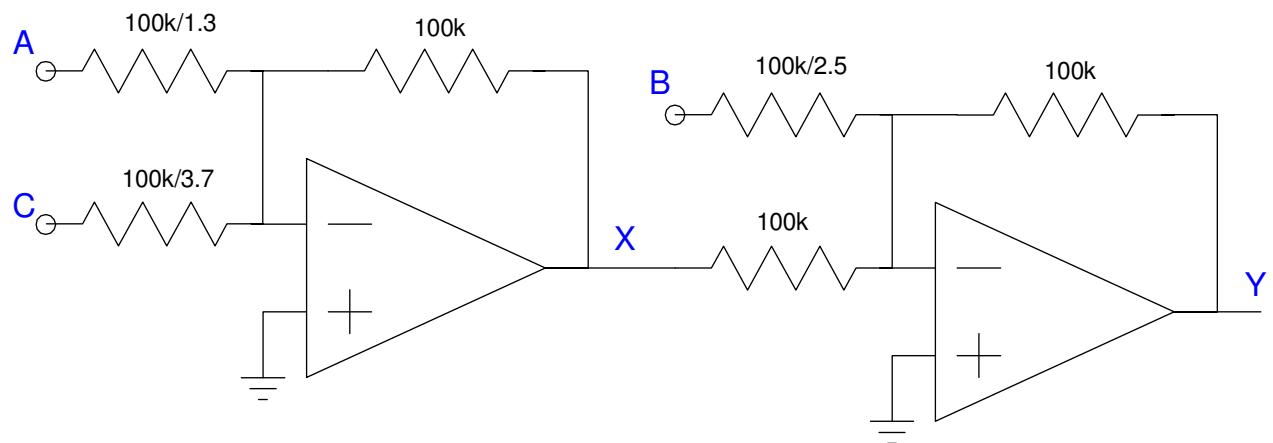

5) Determine the voltages and currents for the following push-pull amplifier. Assume


- Ideal op-amps
- $X = 1.5\text{VDC}$
- $R = 800 + 100 * (\text{your birth month}) + (\text{your birth day})$
- Transistors with:
  - $\beta = 25$
  - $|V_{be}| = 0.7\text{V}$

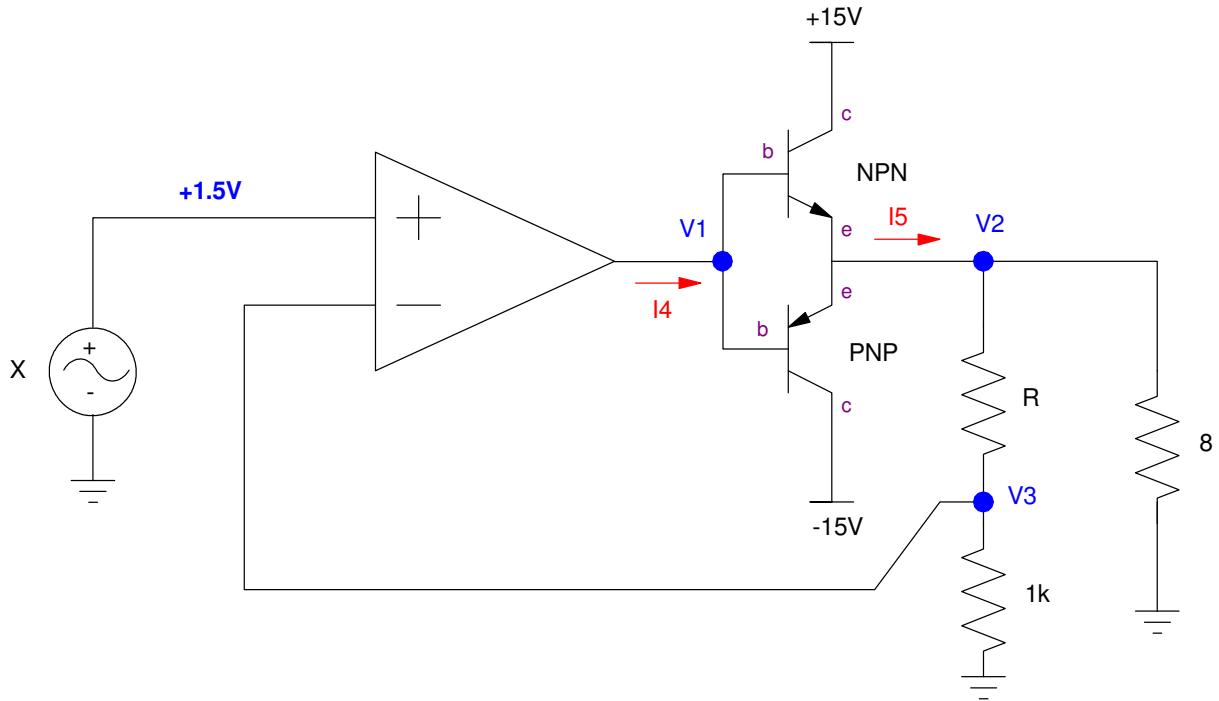

$R$ $800 + 100 * \text{mo} + \text{day}$	$V_1$	$V_2$	$V_3$	$I_4$	$I_5$
<b>1314</b>	<b>4.171V</b> $V_2 + 0.7\text{V}$	<b>3.471V</b> $V_3 * (1 + R/1\text{k})$	<b>1.5V</b> $V_p = V_m$	<b>16.5mA</b> $I_5 / 26$	<b>428.6mA</b>

6) Determine the voltages and currents for the following push-pull amplifier. Assume

- Ideal op-amps
- $X = 1.5\text{VDC}$
- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$
- Transistors with
  - $\beta = 25$
  - $|V_{be}| = 0.7\text{V}$

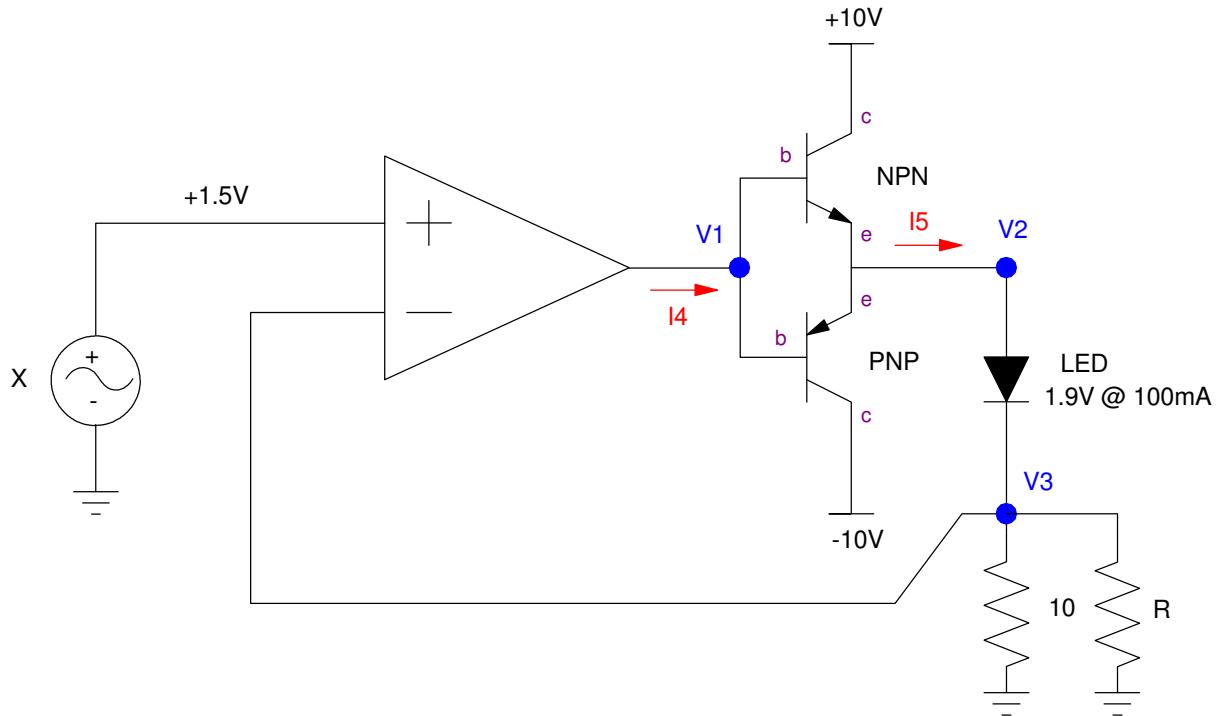

$R$ $800 + 100 \cdot \text{mo} + \text{day}$	$V_1$	$V_2$	$V_3$	$I_4$	$I_5$
<b>1314</b>	<b>4.1V</b> $V_2 + 0.7\text{V}$	<b>3.4V</b> $V_3 + 1.9\text{V}$	<b>1.5V</b> $V_p = V_m$	<b>5.8mA</b> $I_5 / 26$	<b>151.1mA</b>