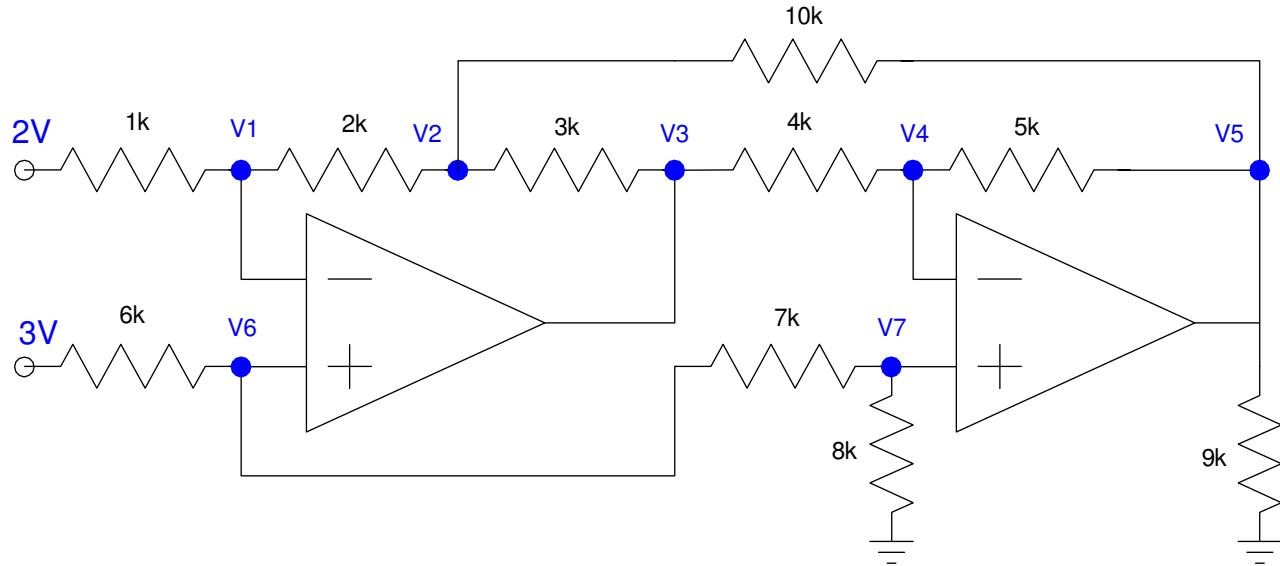


ECE 321 - Quiz #1 - Name _____

Op-Amp Amplifiers & mixers., Push-Pull Amplifiers - Spring 2023


1) Give 7 equations which allow you to solve for the 7 unknown voltages. You do not need to solve.

- Assume ideal op-amps.



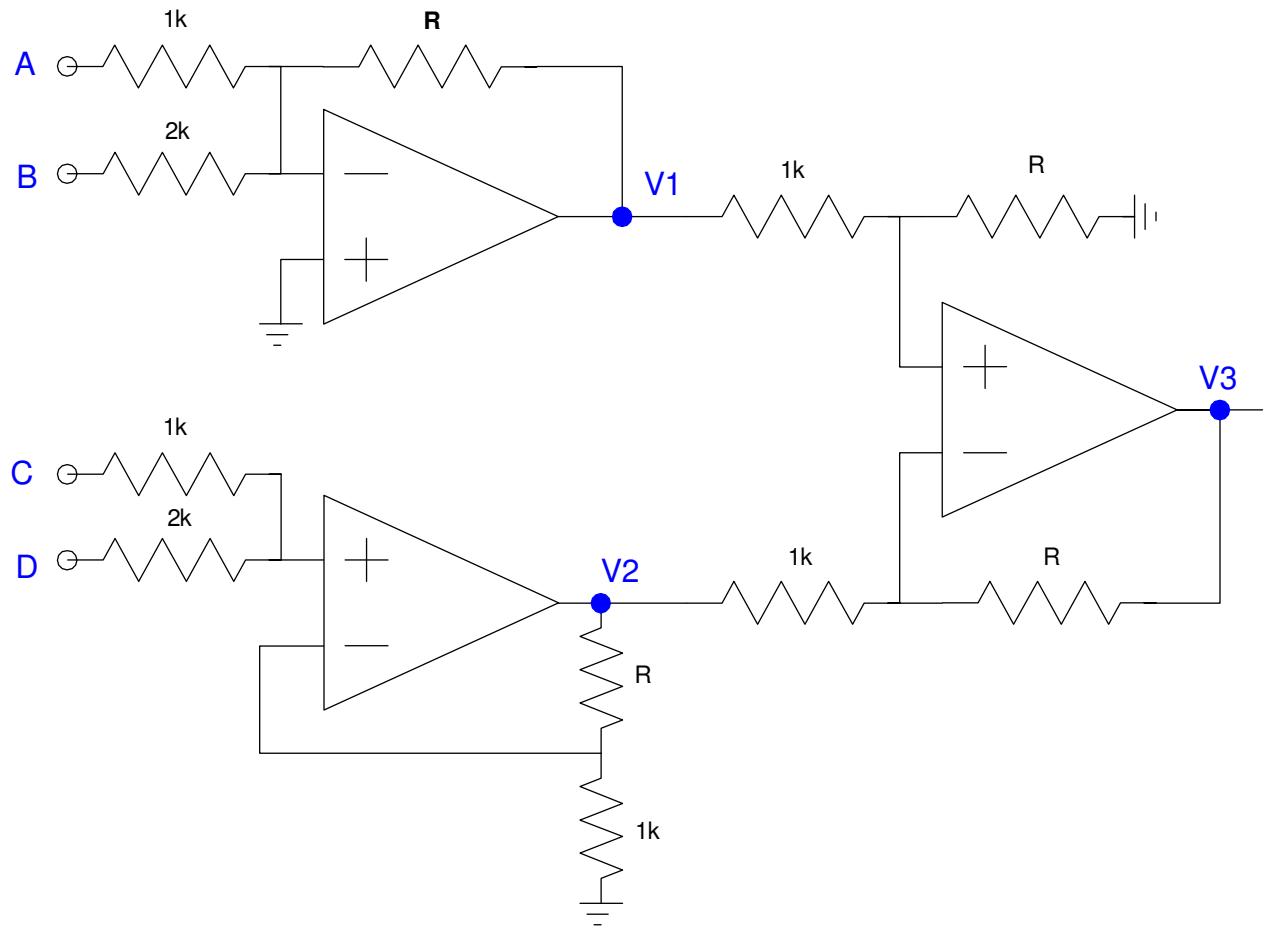2) Determine V₁, V₂, and V₃ as a function of A, B, C, and D.

- Assume ideal op-amps
- Assume $R = 800 + 100 * (\text{your birth month}) + (\text{your birth day})$.



3) Design a circuit which outputs

$$Y = 1.3A + 2.5B + 3.7C$$

note: the gain on A and B are positive


4) Design a circuit which outputs

$$Y = 1.3A - 2.5B + 3.7C$$

note: the gain on B is negative

5) Determine the voltages and currents for the following push-pull amplifier. Assume


- Ideal op-amps
- $X = 1.5\text{VDC}$
- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$
- Transistors with:
 - $\beta = 25$
 - $|V_{be}| = 0.7\text{V}$

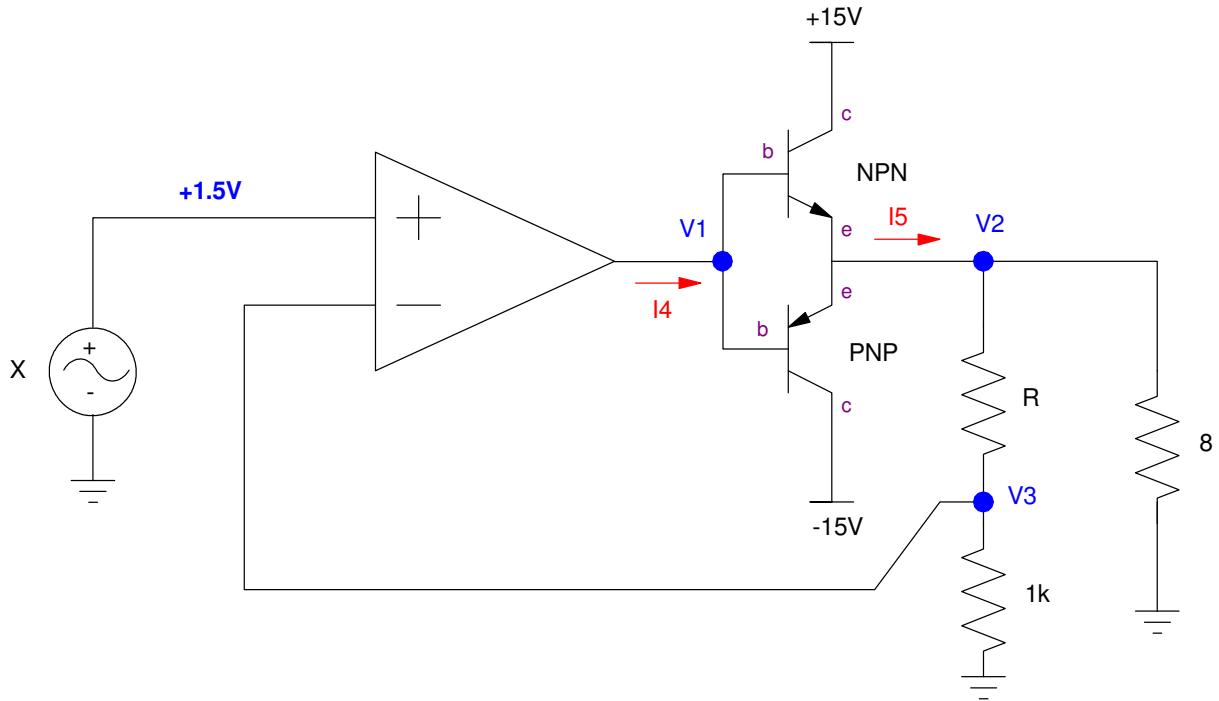

R $800 + 100 \cdot \text{mo} + \text{day}$	V_1	V_2	V_3	I_4	I_5

6) Determine the voltages and currents for the following push-pull amplifier. Assume

- Ideal op-amps
 - $X = 1.5VDC$
 - $R = 800 + 100^*(\text{your birth month}) + (\text{your birth day})$
 - Transistors with
 - $\beta = 25$
 - $|V_{be}| = 0.7V$

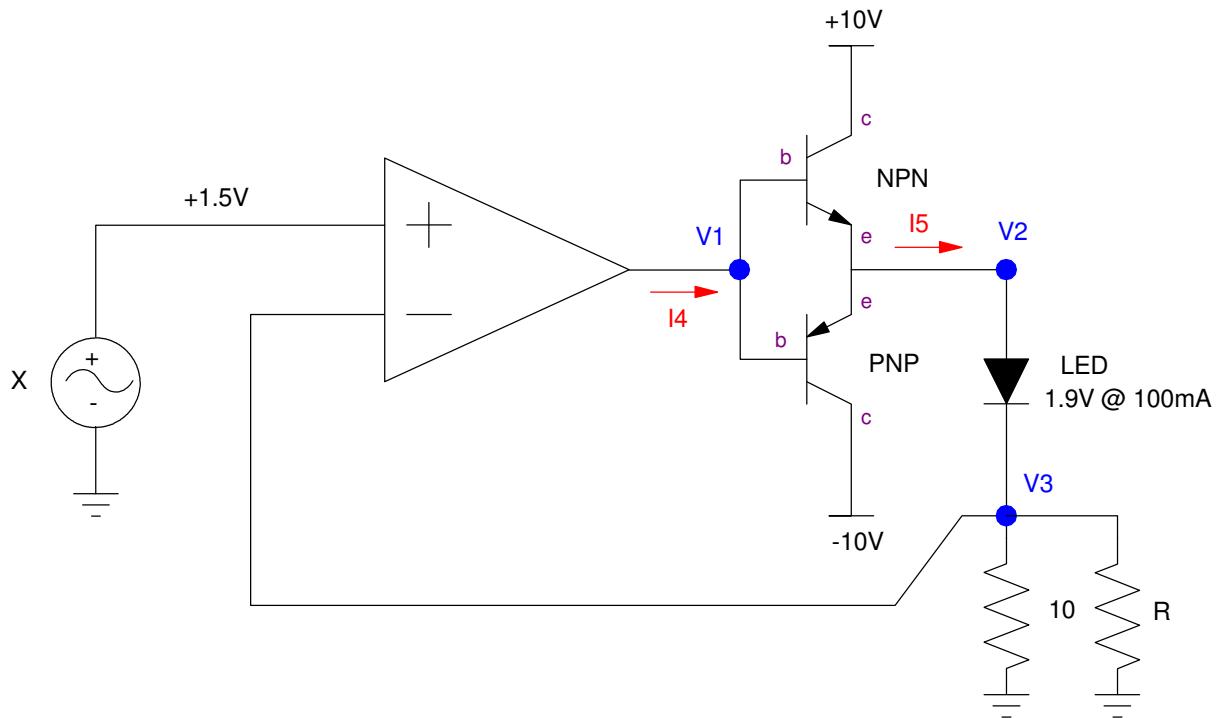

R 800 + 100*mo + day	V1	V2	V3	I4	I5