

ECE 321 - Homework #3

Calibration & Noise, Active Filters. Due Monday, April 17th
Please email to jacob.glower@ndsu.edu, or submit as a hard copy, or submit on BlackBoard

Filters

1) Assume X and Y are related by the following transfer function:

$$Y = \left(\frac{80}{(s+5)(s+10)} \right) X$$

a) What is the differential equation relating x and y?

Cross multiply

$$(s^2 + 15s + 50)Y = (80)X$$

Note that sY means *the derivative of Y*

$$y'' + 15y' + 50y = 80x$$

b) Determine y(t) assuming

$$x(t) = 6 + 2 \cos(4t) + 3 \sin(4t)$$

Use superposition:

$$x(t) = 6$$

$$s = 0$$

$$X = 6$$

$$Y = \left(\frac{80}{(s+5)(s+10)} \right)_{s=0} \cdot (6)$$

$$Y = 9.6$$

$$x(t) = 2 \cos(4t) + 3 \sin(4t)$$

$$s = j4$$

$$X = 2 - j3$$

$$Y = \left(\frac{80}{(s+5)(s+10)} \right)_{s=j4} \cdot (2 - j3)$$

$$Y = -3.7463 - j1.4829$$

$$y(t) = -3.7463 \cos(4t) + 1.4829 \sin(4t)$$

The total answer is DC + AC

$$y(t) = 9.6 - 3.7463 \cos(4t) + 1.4829 \sin(4t)$$

Filter Design

2) Give an op-amp circuit to implement the following filter


$$Y = \left(\frac{400}{(s+2)(s+8)(s+10)} \right) X$$

Rewrite as

$$Y = \left(\frac{2}{s+2} \right) \left(\frac{8}{s+8} \right) \left(\frac{10}{s+10} \right) (2.5)$$

Build using a 3-stage RC filter along with an amplifier with a gain of 2.5

- note: there are other solutions

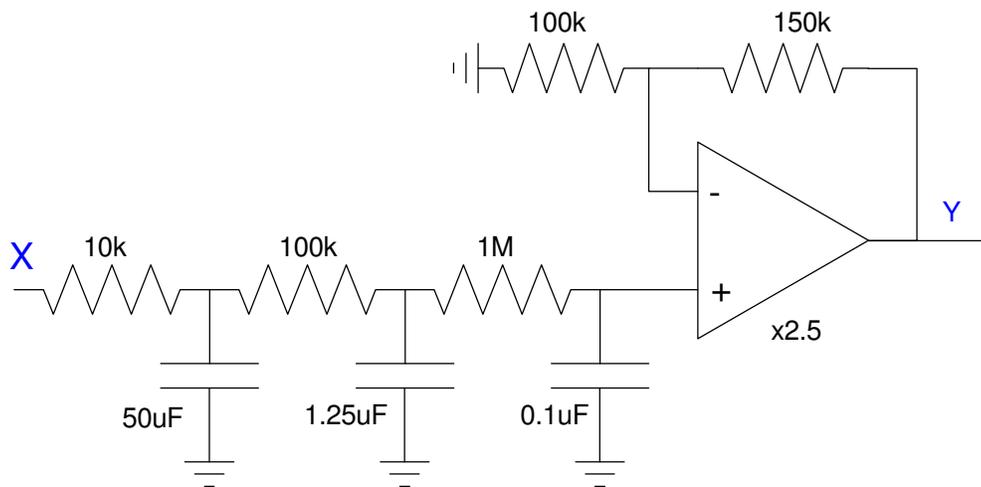

3) Give an op-amp circuit to implement the following filter

$$Y = \left(\frac{200}{(s^2+s+20)(s^2+5s+30)} \right) X$$

Design as a two-stage active low-pass filter. Rewrite in polar form

$$Y = \left(\frac{200}{(s+4.4721 \angle \pm 83.58^\circ)(s+5.4772 \angle \pm 64.8427^\circ)} \right) X$$

Stage 1:

$$\frac{1}{RC} = 4.4721$$

$$3 - k = 2 \cos \theta$$

$$k = 2.7764$$

Stage 2:

$$\frac{1}{RC} = 5.4772$$


$$k = 2.1498$$

DC gain

$$DC = 0.333 = 2.7764 \cdot 2.1498 \cdot k_3$$

$$k_3 = 0.0558$$

or the output is 17.91Y

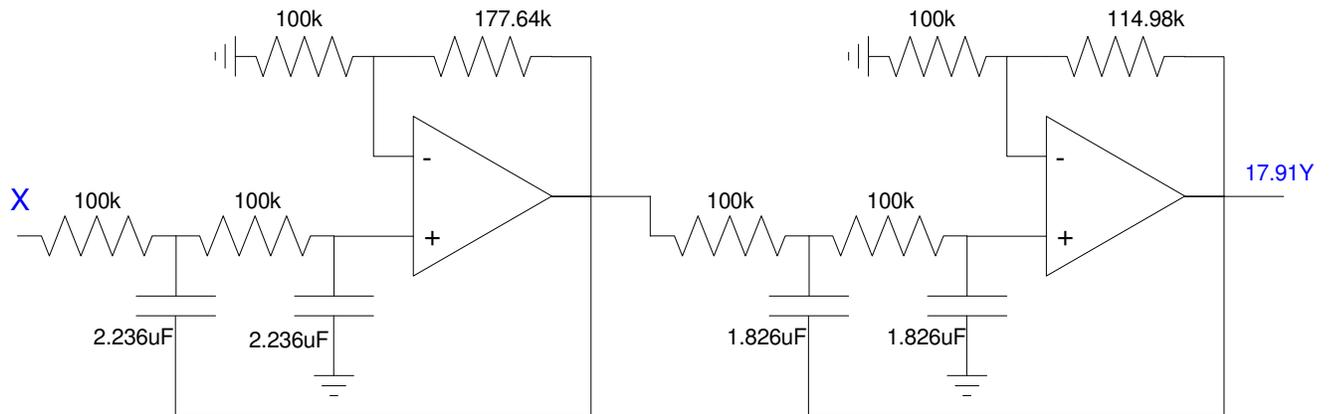

4) Give the transfer function of a filter with the following gain vs. frequency

This has three resonances (three sets of complex poles:

Resonance #1

- Frequency = 4 rad/sec = complex part of pole
- Bandwidth = 0.5 rad/sec = 2 x real part of pole

Resonance #2

- Frequency = 11 rad/sec = complex part of pole
- Bandwidth = 1 rad/sec = 2 x real part of pole


Resonance #3

- Frequency = 16 rad/sec = complex part of pole
- Bandwidth = 0.5 rad/sec = 2 x real part of pole

DC gain = 0 (zero at $s = 0$)

$$G(s) \approx \left(\frac{ks}{(s+0.25\pm j4)(s+0.5\pm j11)(s+0.25\pm j16)} \right)$$

Pick 'k' so that the maximum gain is 1

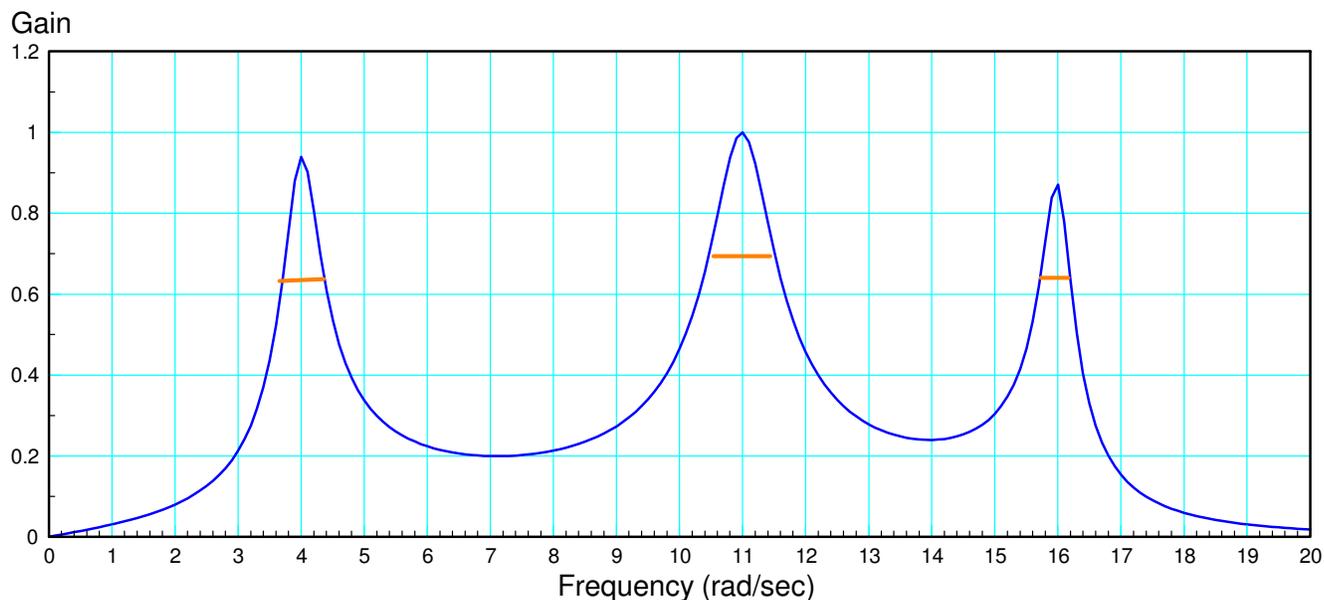


```
>> p1 = -0.25 + j*4;  
>> p2 = conj(p1);  
>> p3 = -0.5 + j*11;  
>> p4 = conj(p3);  
>> p5 = -0.25 + j*16;  
>> p6 = conj(p5);  
>> w = [0:0.01:20]';  
>> s = j*w;  
>> G = s ./ ( (s-p1) .* (s-p2) .* (s-p3) .* (s-p4) .* (s-p5) .* (s-p6) );  
>> max(G)
```

```
ans = 7.9059e-005 -4.3719e-006i
```

```
>> k = 1/abs(ans)
k = 1.2630e+004
>> G = k*s ./ ( (s-p1).(s-p2).(s-p3).(s-p4).(s-p5).(s-p6) );
>> plot(w,abs(G))
>>
```

Not exact, but close

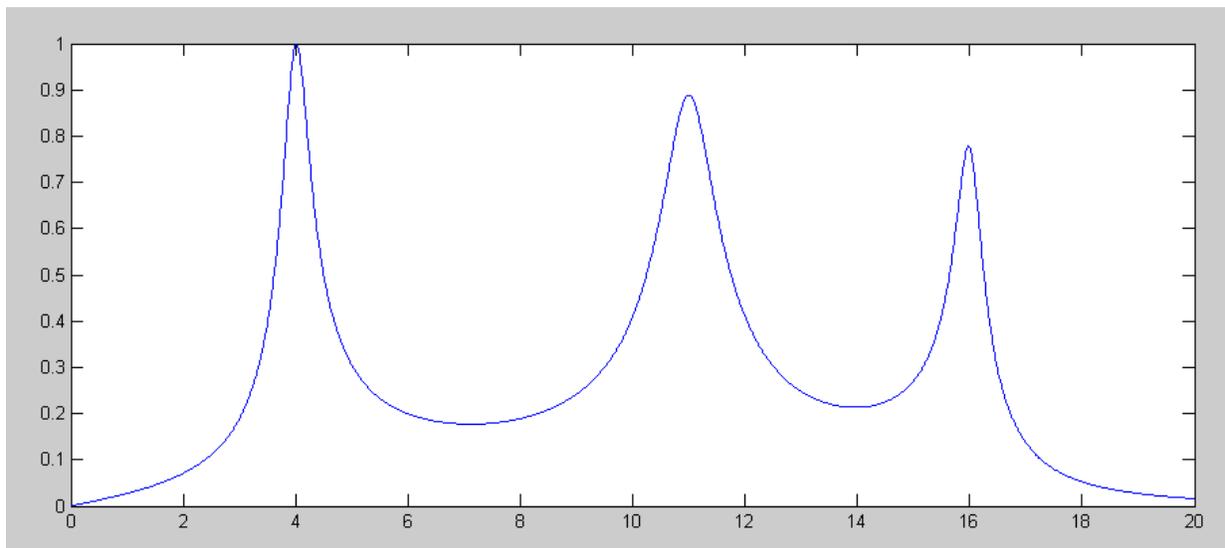


Filter Design using *fminsearch()*

5) Design a filter of the form

$$Y = \left(\frac{100a}{(s+b)(s^2+cs+d)(s^2+es+f)} \right) X$$

to give a gain vs. frequency as close to the following plot as possible over the range of (0, 10) rad/sec.

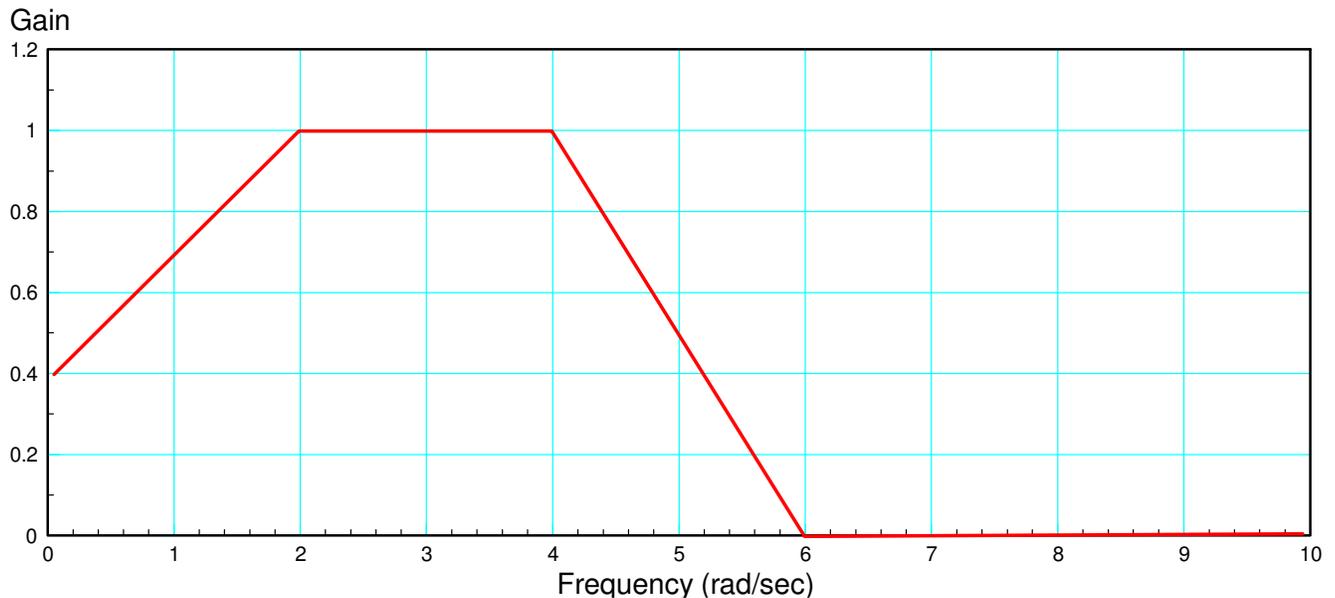Plot your filter's actual frequency response vs. its ideal response (red line).



First, create an m-file which


- Is passed your guess for {a..f},
- Computes G(s),
- Computes Gd(s), and
- Returns the sum-squared difference.

```
% ECE 321 Homework #3
% Cost function for a filter

function [ J ] = costF( z )
a = z(1);
b = z(2);
c = z(3);
d = z(4);
e = z(5);
f = z(6);
w = [0:0.01:9.9]' + 1e-6;
s = j*w;
Gideal = (0.3*w+0.4).* (w < 2) + 1.*(w>2).*(w<4) + (3-0.5*w).*(w>4).*(w<6);
G = 100*a ./ ( (s+b).*(s.^2 + c*s + d).*(s.^2 + e*s + f) );
e = abs(Gideal) - abs(G);
J = sum(e.^2);
plot(w,abs(Gideal), 'r', w, abs(G), 'b');
ylim([0,1.2]);
pause(0.01);
end
```

Check this from the command window:
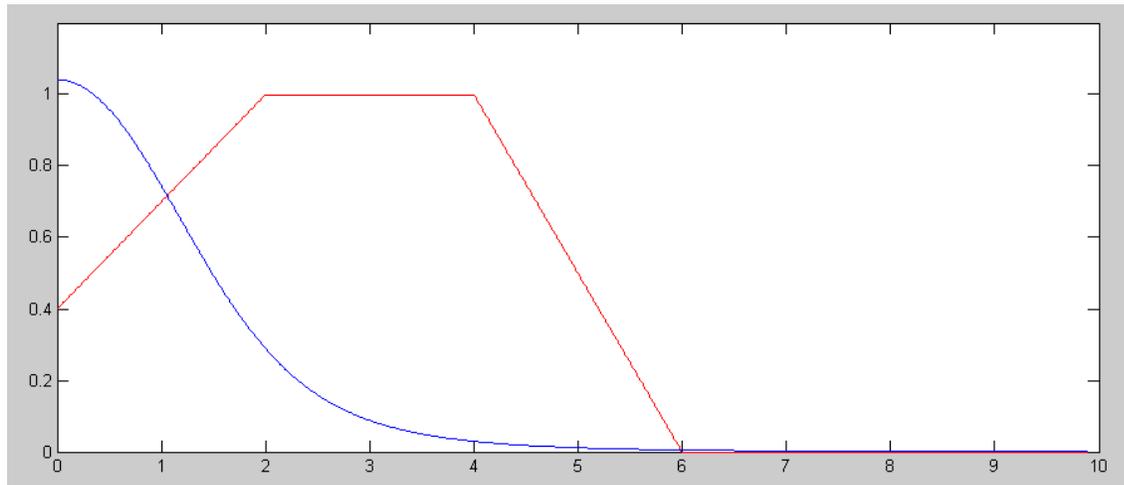
```
>> costF([0.5,2,3,4,5,6])  
ans =  
257.5852
```




Now let Matlab optimize the parameters:

```
>> [Z,e] = fminsearch('costF',[0.5,2,3,4,5,6])  
  
Z =      a      b      c      d      e      f  
    = 10.8526 14.2080 2.0776 6.8006 1.2423 19.5714  
e = 2.7239
```

Run again using the previous answer (just incase Matlab wasn't done yet)

```
>> [Z,e] = fminsearch('costF',Z)  
  
Z =      a      b      c      d      e      f  
    = 10.8526 14.2080 2.0776 6.8006 1.2423 19.5714  
e = 2.7239
```

This looks like the best matlab can do

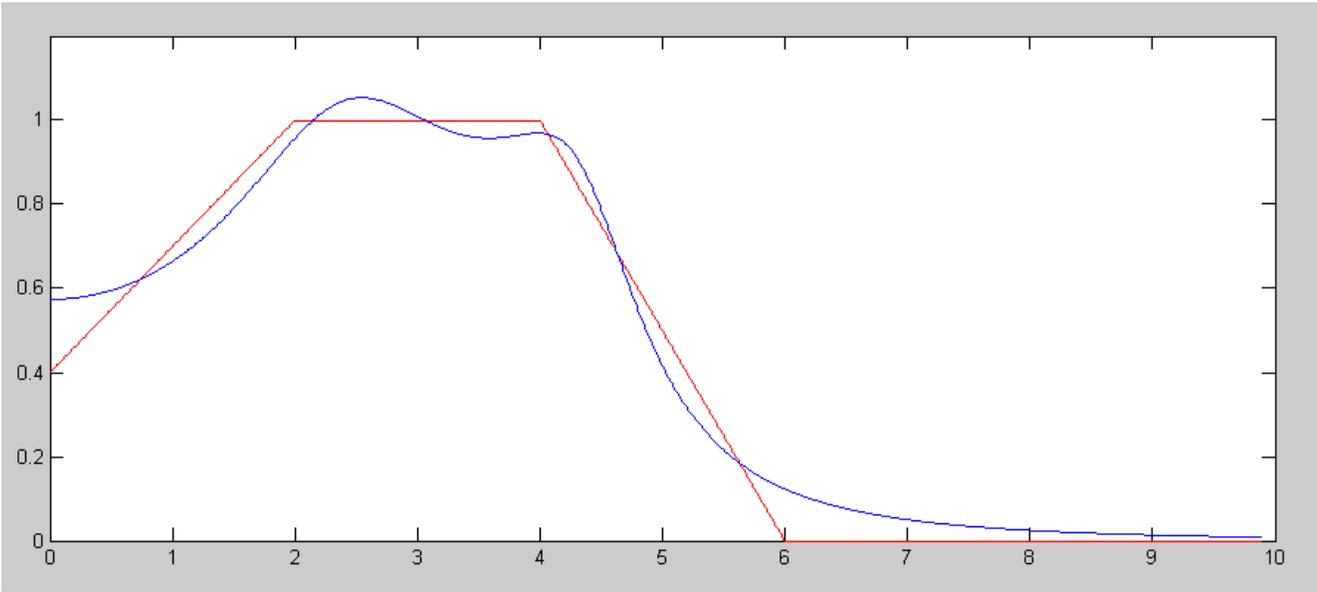

$$Y = \left(\frac{100a}{(s+b)(s^2+cs+d)(s^2+es+f)} \right) X$$

z = a b c d e f
 = 10.8526 14.2080 2.0776 6.8006 1.2423 19.5714

6) Design circuit to implement the filter you designed in problem #7

Do this in three stages

$$Y = \left(\frac{1085.26}{(s+14.2080)(s^2+2.0776s+6.8006)(s^2+1.2423s+19.5714)} \right) X$$

$$Y = \left(\frac{k_1}{s+14.2080} \right) \left(\frac{k_2}{s^2+2.0776s+6.8006} \right) \left(\frac{k_3}{s^2+1.2423s+19.5714} \right) X$$

$$Y = \left(\frac{k_1}{s+14.2080} \right) \left(\frac{k_2}{s+2.6078 \angle \pm 66.53^\circ} \right) \left(\frac{k_3}{s+4.424 \angle \pm 81.929^\circ} \right) X$$

Stage #1:

$$1/RC = 14.208$$

Stage #2


$$1/RC = 2.6078$$

$$k = 2.2035$$

Stage #3

$$1/RC = 4.424$$

$$k = 2.7192$$

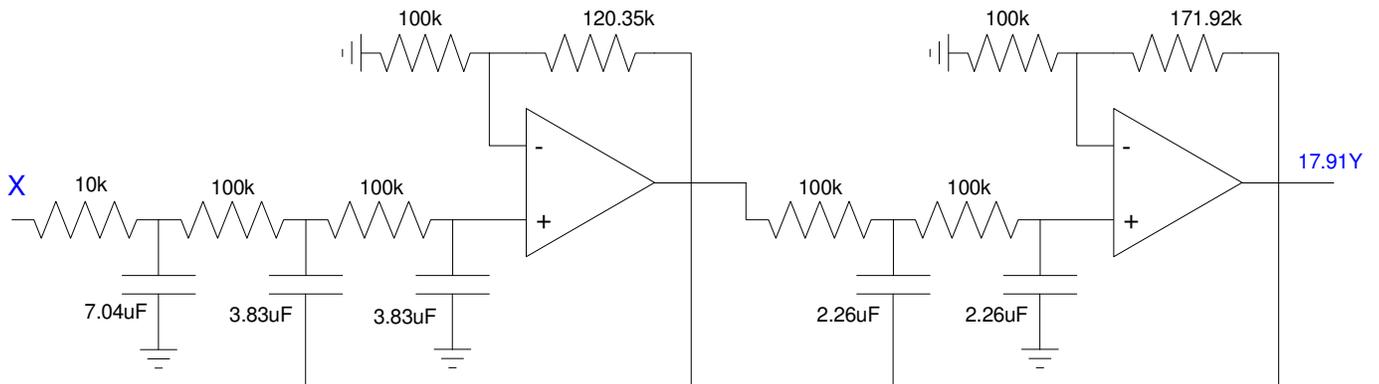

7) Check your filter using CircuitLab

Kind of hard to tell since the x-axis is on a log-scale. Sort of looks the same though...

