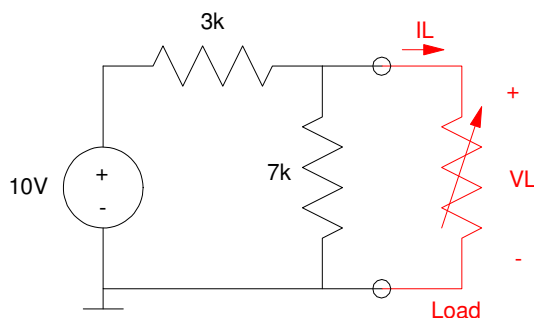


2-Port Models

Thevenin Equivalent:

Thevenin equivalents are a tool where you simplify a circuit to a voltage source and a resistance. The idea is that for any linear circuit, the output voltage/current relationship follows a straight line. For example, consider the following circuit:





Sample Circuit

Place a resistor across the load and vary it from zero to infinity. The voltage and current at the load will change in a linear fashion - with the result termed the load line.

Thevenin equivalents replace the circuit with a simple model which follows the same load line. The way you find the Thevenin terms are:

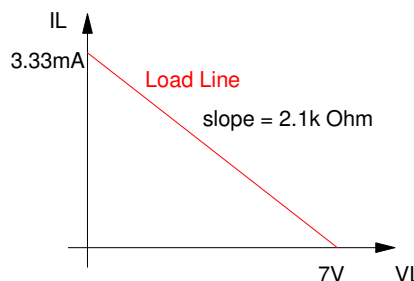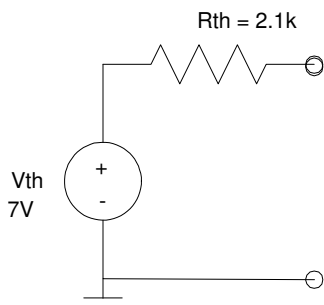
- V_{th} : The voltage at the load with $R_L = \text{infinity}$ (7V)
- R_{th} : The resistance looking in with sources turned off: $3k \parallel 7k = 2.1k$
- I_{short} : The current I_L when $R_L = 0$. $I_{short} = V_{th} / R_{th}$; $I_{short} = 10V / 3V = 3.33mA$



Thevenin Equivalent for Above Circuit along with its Load Line

2-Port Models

A 2-port model is a Thevenin equivalent for a circuit with an input and an output - such as an amplifier. Since the input can affect the output, the Thevenin voltage source at the output is replaced with a voltage controlled voltage source. Sometimes, the output can also affect the input. Likewise, the input has a like Thevenin equivalent: a Thevenin resistance along with a voltage-controlled voltage-source:

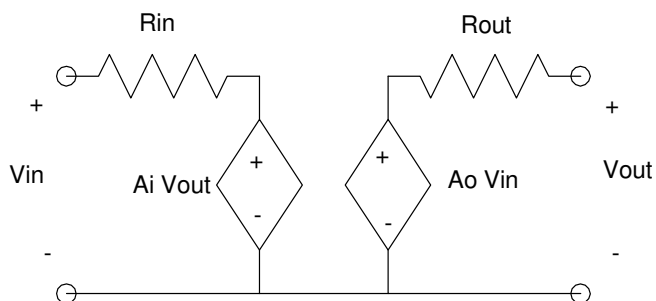

2-Port Model

Like a Thevenin equivalent, 2-Port models are tools which help with circuit analysis:

- Thevenin equivalents can make circuit analysis much simpler.
- 2-Port models can make multi-stage amplifier analysis much simpler


2-Port Parameters:

To determine each of the four 2-port model parameters, four tests are run:

- A_i : Set $V_{out} = 1V$ and measure V_{in} . $A_i = V_{in}$
- A_o : Set $V_{in} = 1V$ and measure V_{out} . $A_o = V_{out}$
- R_{in} : Set $V_{out} = 0V$ and measure the resistance seen at the input
- R_{out} : Set $V_{in} = 0V$ and measure the resistance seen at the output



Essentially, devise a test on the 2-port model to find a given parameter. Do the same with the circuit you are analyzing.

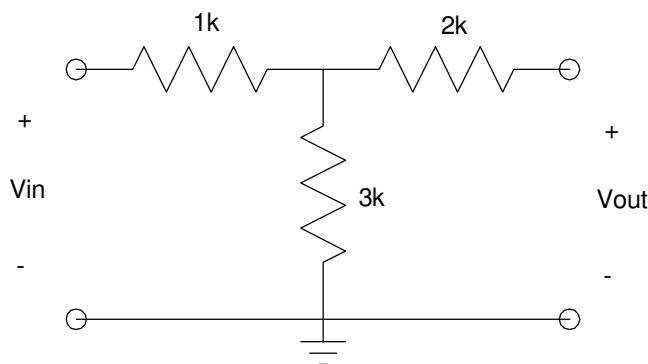Example: Determine the 2-port model for the following circuit:





Ai: Set $V_{out} = 1V$, measure the voltage at V_{in} . $A_i = V_{in}$

- $A_i = 0.6$

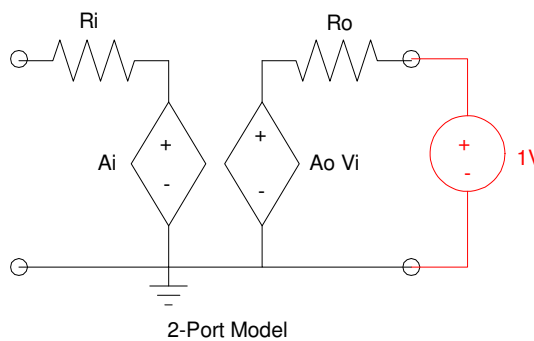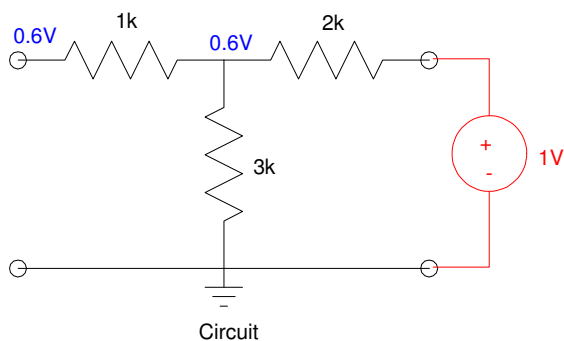



Ao: Set $V_{in} = 0V$, measure the voltage at V_{out} . $A_o = V_{out}$

- $A_o = 0.75$

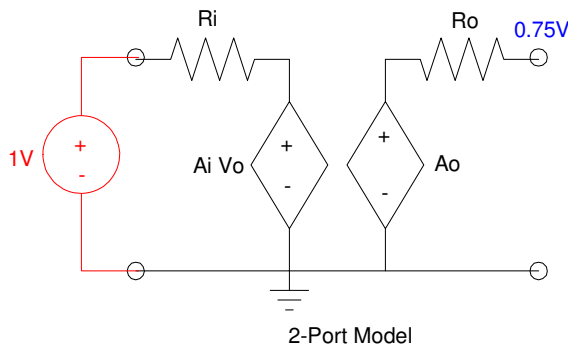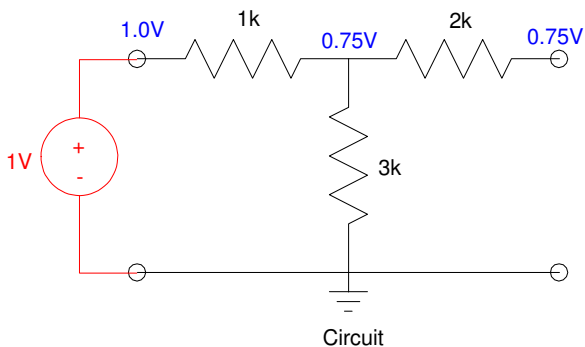


Rin: Set $V_{out} = 0V$, measure the resistance at V_{in} .

- $R_{in} = 1k + 3k || 2k = 2.2k\Omega$

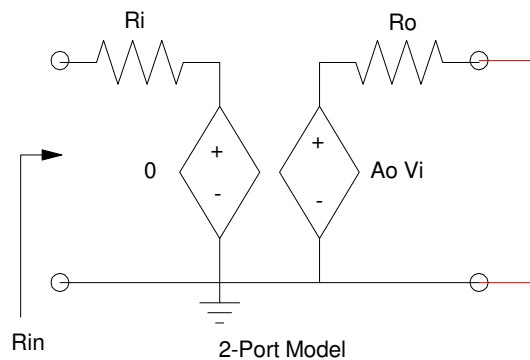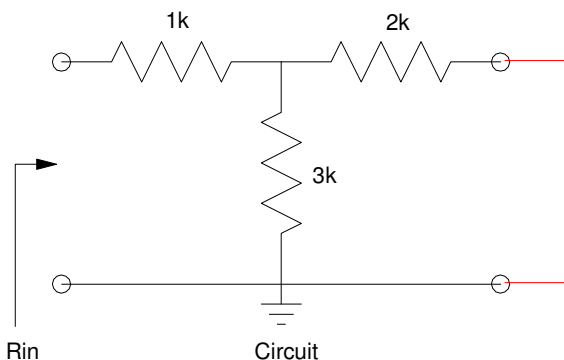


Rout: Set $V_{in} = 0V$, measure the resistance at V_{out}

- $R_{out} = 2k + 1k || 3k = 2750\Omega$

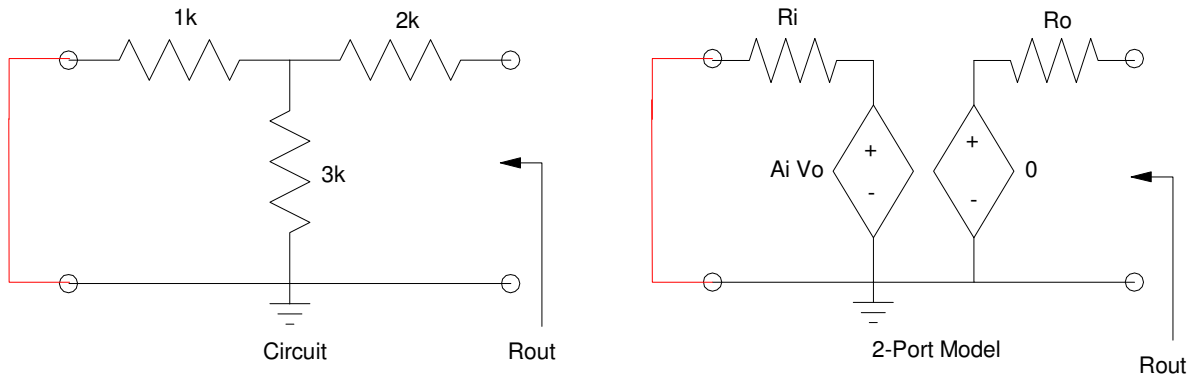


So, the 2-port model is:

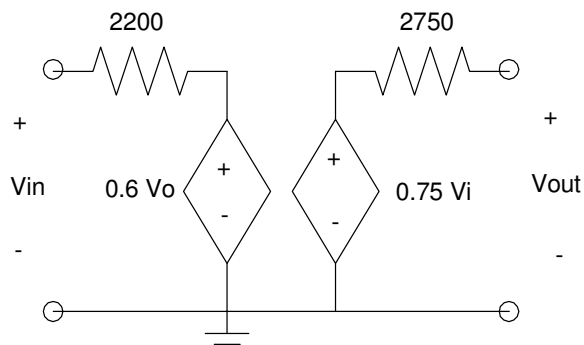


Sometimes the Thevenin resistance isn't so obvious. In this case, you might have to apply a test voltage, compute the resulting current, and compute resistance as $R = V/I$

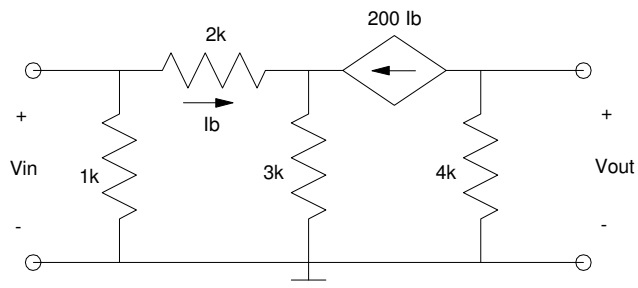Example 2: Find the 2-port model for the following circuit:



Ai: Set $V_{out} = 1V$, measure V_{in}

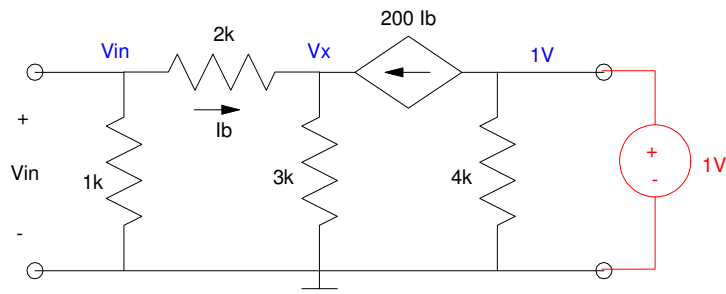


Compute V_x using voltage nodes:

$$\left(\frac{V_x}{1k+2k}\right) + \left(\frac{V_x}{3k}\right) - 200\left(\frac{0-V_x}{3k}\right) = 0$$

$$V_x = 0$$

So, **Ai = 0**

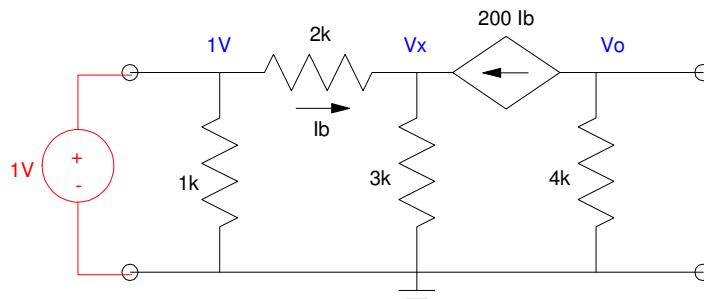Ao: Set $V_{in} = 1V$, measure the voltage at V_o



Find V_x using voltage nodes:

$$\left(\frac{V_x-1}{2k}\right) + \left(\frac{V_x}{3k}\right) - 200\left(\frac{1-V_x}{3k}\right) = 0$$


$$V_x = 0.9951V$$

$$I_b = \left(\frac{1-V_x}{2k}\right) = 2.469\mu A$$

$$V_o = -(200I_b)4k = 1.9753V$$

Ao = 1.9753

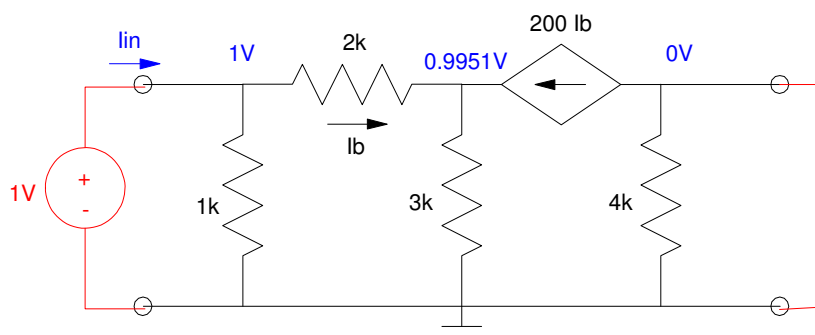Rin: Set $V_o = 0V$, measure the resistance at the input.




From the previous analysis, $V_x = 0.9951V$,

$$I_{in} = \left(\frac{1V-0.9951V}{2k}\right) + \left(\frac{1V}{1k}\right) = 1.0017mA$$

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{1V}{1.0017mA} = 998\Omega$$

Rout: Set $V_{in} = 0V$, measure the resistance at V_{out} .

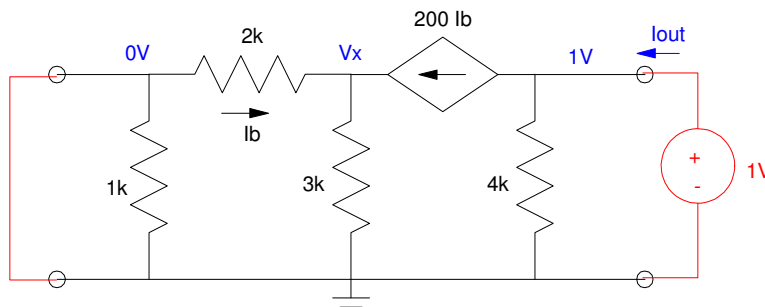This isn't obvious, so add a 1V source at the output and compute the resulting current



Solve for V_x :

$$\left(\frac{V_x-0}{2k}\right) + \left(\frac{V_x}{3k}\right) - 200\left(\frac{0-V_x}{2k}\right) = 0$$

$$V_x = 0$$

$$I_{out} = 0 + \left(\frac{1V}{4k}\right) = 250\mu A$$

so

$$R_{out} = \frac{V_{out}}{I_{out}} = \frac{1V}{250\mu A} = 4k\Omega$$

The resulting 2-port model is then:

