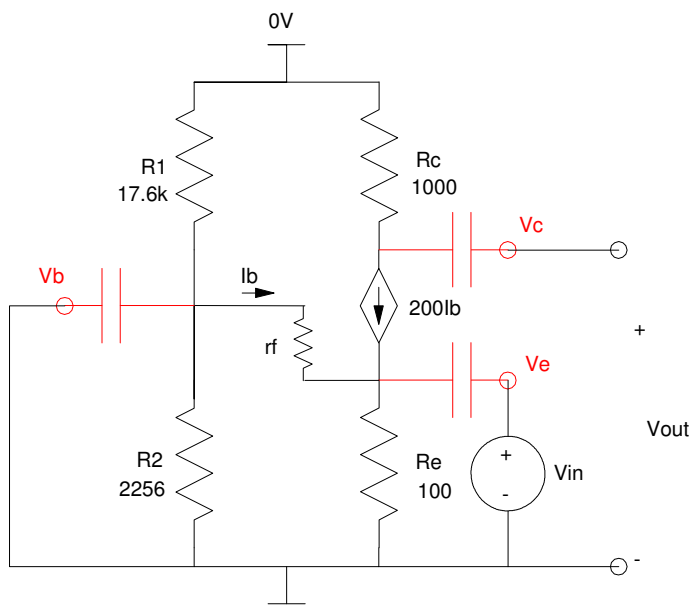



# Common Base, Common Collector Amplifiers.
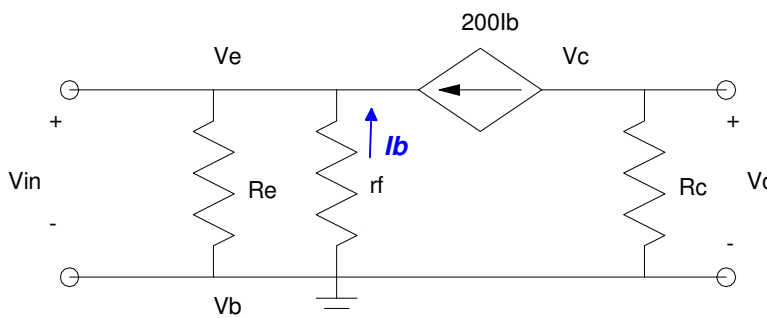
## Common Base Amplifier:

- Connect the base to ground
- Connect the input to  $V_e$
- Connect the output to  $V_c$ :



Now find the 2-port model. To do this, let's first redraw the circuit:



Now let's find the 2-port parameters:

Rin: Set  $V_o = 0V$  and measure the input resistance. In this case, it's not that obvious what the answer is. So, let's apply 1V to  $V_{in}$  and see how much current is drawn,  $1/I_{in}$  is the input resistance.

$$I_{in} = \frac{1V}{R_e} + \frac{1V}{r_f} + \beta I_b$$

$$I_{in} = \frac{1V}{R_e} + \frac{1V}{r_f} + \frac{\beta}{r_f}$$

so

$$R_{in} = \left( \frac{1}{R_e} + \frac{1}{r_f} + \frac{\beta}{r_f} \right)^{-1}$$

Note that this is also

$$R_{in} = R_e || r_f || \frac{r_f}{\beta}$$

$$R_{in} = 8\Omega$$

Ain: Set  $V_o = 1V$  and measure the voltage at the input. Again, this isn't obvious, but 0V works. If  $V_{in} = 0V$ ,  $I_b = 0$ ,  $\beta I_b = 0$ . So  $A_{in} = 0$ .

$$A_{in} = 0.$$

Rout: Set  $V_{in} = 0V$  and measure the resistance at the output. If  $V_{in} = 0V$ ,  $I_b = 0$ ,  $\beta I_b = 0$  and everything is turned off. The only thing you see at the output is  $R_c$ .

$$R_{out} = R_c.$$

Ao: Set  $V_{in} = 1V$  and measure the voltage at the output.


$$I_b = \frac{1}{r_f}$$

$$I_c = \beta I_b$$

$$A_o = V_o = -\frac{\beta R_c}{r_f}$$

$$A_o = -115$$

So, the 2-port model is then

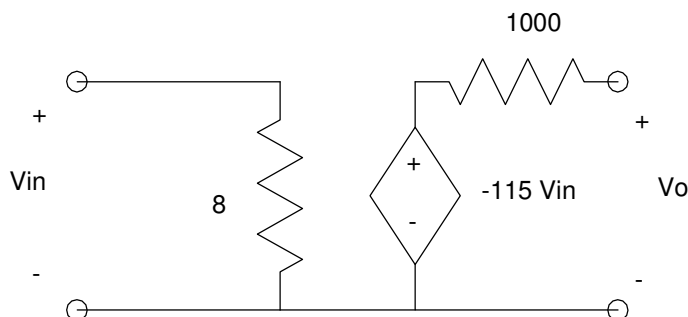


Note that the common-base amplifier has a low input impedance. It's used as the first stage in an amplifier where the sensor needs a low-impedance load, such as a phonograph (the current carries the signal.)


**Common Collector Amplifier:**

- Short the collector to ground
- Connect the input to the base

- Connect the output to the collector

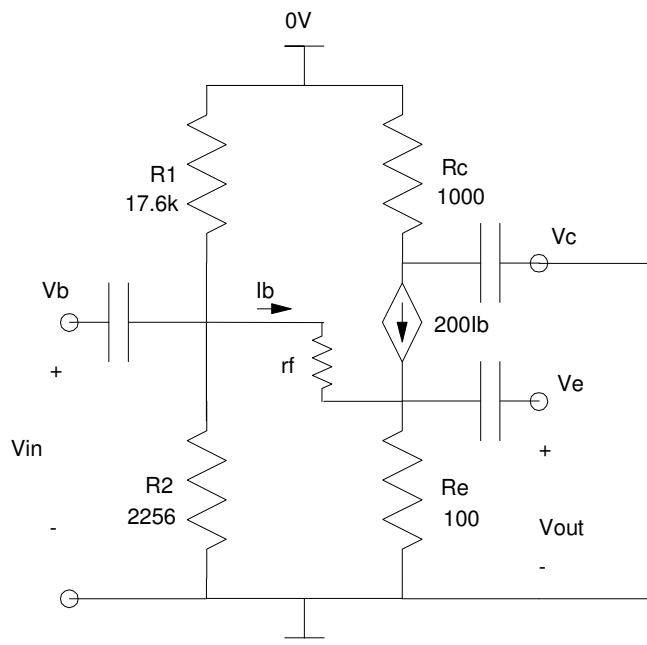

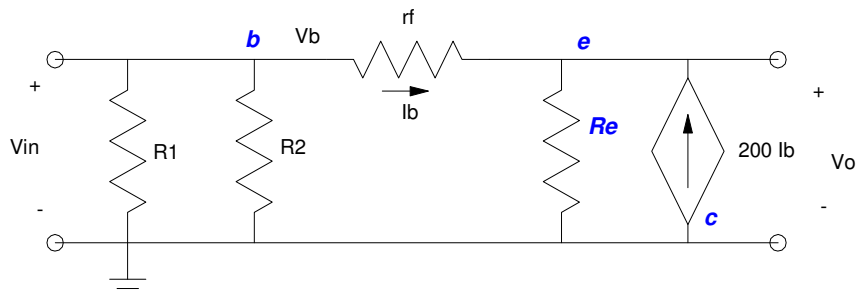To find the 2-port parameters, redraw the circuit:



Now, find the 2-port parameters:

Rin: Set  $V_o = 0V$  and measure the resistance at the input.

$$R_{in} = R_1 || R_2 || r_f$$

$$R_{in} = 928\Omega$$

Ain: Set  $V_o = 1V$  and measure the voltage at the input. By voltage division

$$A_{in} = \left( \frac{R_1 || R_2}{R_1 || R_2 + r_f} \right)$$

$$A_{in} = 0.5357$$

Rout: Set  $V_{in} = 0V$  and measure the resistance across  $V_o$ . Again, this isn't obvious, so let's apply a 1V source to  $V_o$  and measure the current drawn:

$$I = \frac{1}{r_f} + \frac{1}{R_e} - \beta(-I_b)$$

$$I = \frac{1}{r_f} + \frac{1}{R_e} + \frac{\beta}{r_f}$$

so

$$R_{out} = \left( \frac{1}{r_f} + \frac{1}{R_e} + \frac{\beta}{r_f} \right)^{-1}$$

which is also

$$R_{out} = r_f || R_e || \frac{r_f}{\beta}$$

$$R_{out} = 7.9\Omega$$

Ao: Set  $V_{in} = 1V$  and measure the voltage across the output. Using voltage node analysis:

$$\left( \frac{V_o - 1}{r_f} \right) + \left( \frac{V_o}{R_c} \right) - \beta I_b = 0$$

$$\left( \frac{V_o - 1}{r_f} \right) + \left( \frac{V_o}{R_c} \right) - \beta \left( \frac{1 - V_o}{r_f} \right) = 0$$

$$\left( \frac{1}{r_f} + \frac{1}{R_c} + \frac{\beta}{r_f} \right) V_o = - \left( \frac{\beta}{r_f} \right)$$


$$V_o = - \left( \frac{\beta}{r_f} \right) \left( \frac{1}{r_f} + \frac{1}{R_c} + \frac{\beta}{r_f} \right)^{-1}$$

or


$$A_o = \left( \frac{R_c || r_f || \frac{r_f}{\beta}}{r_f} \right) \beta$$

$$A_o = 0.9865$$

So the 2-port model is:

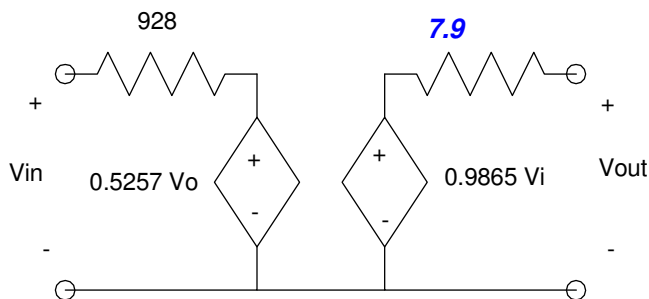

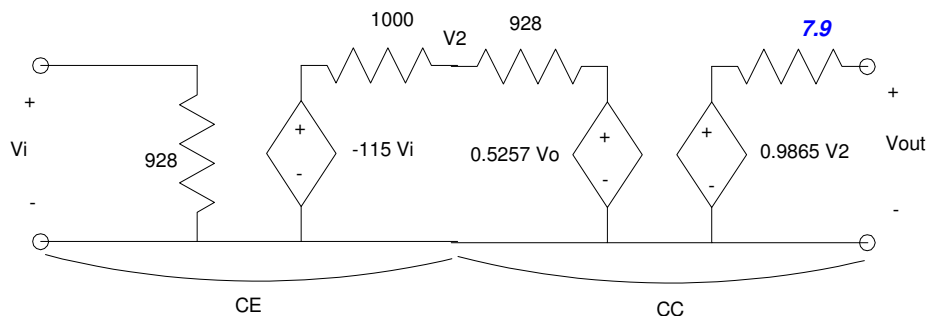It isn't really obvious what this is useful for. Typically, CC amplifiers are preceded by a CE amplifier:




Now the 2-port model becomes:

$R_{in} = 928 \text{ Ohms}$  by inspection

$A_i = 0$  by inspection

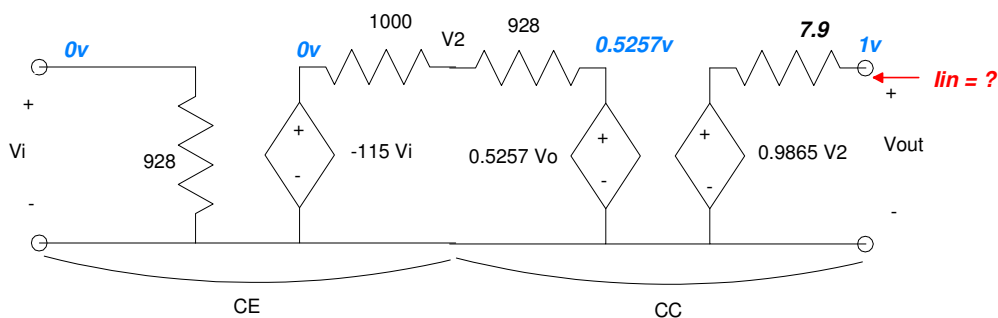$R_{out}$ : Set  $V_i = 0V$  and measure the resistance at the output. Apply a 1V source to  $V_{out}$  and see how much current you draw




$$V_2 = \left( \frac{1000}{1000+928} \right) (0.5257V) = 0.2727V$$

$$I = \left( \frac{1V-0.2727V}{7.9\Omega} \right) = 92.1mA$$

$$R_{out} = \frac{1V}{92.1mA} = 10.8\Omega$$

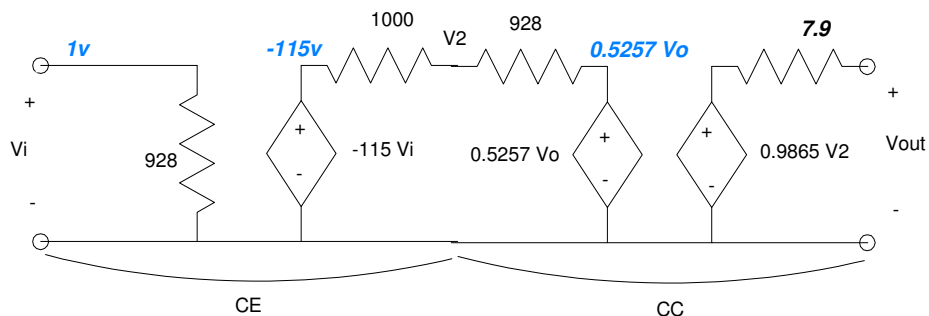Aout: Set  $V_i = 1V$  and measure the voltage at the output. Using voltage nodes, at  $V_2$ :



Solve for the voltage at  $V_2$ . Using voltage nodes:

$$\left(\frac{V_2-0}{1000}\right) + \left(\frac{V_2-0.5257V_o}{928}\right) = 0$$

$$V_o = 0.9865V_2$$

$$\left(\frac{V_2-(-115)}{1000}\right) + \left(\frac{V_2-0.5257 \cdot 0.9865 \cdot V_2}{928}\right) = 0$$


$$\left(\left(\frac{1}{1000}\right) + \left(\frac{1-0.5257 \cdot 0.9865}{928}\right)\right) V_2 = -\left(\frac{115}{1000}\right)$$

$$V_2 = -75.72V$$

$$V_o = 0.9865V_2$$

$$V_o = -74.69$$

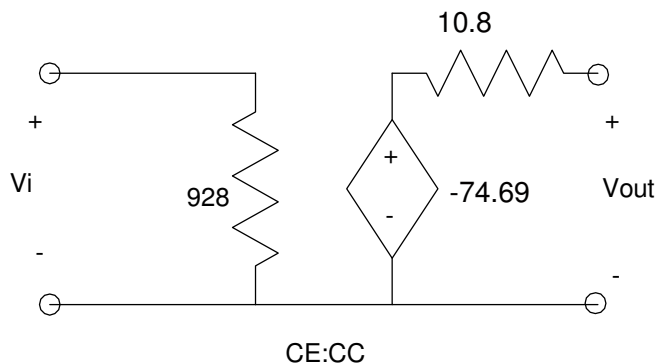So the 2-port model of a CE:CC amplifier is



Common collector amplifiers are used as the last stage for an amplifier when you need to drive a low-impedance load, such as an 8-Ohm speaker.

