

---

# **Push Pull Amplifiers**

## **ECE 321: Electronics II**

### **Lecture #3**

Please visit [Bison Academy](#) for corresponding lecture notes, homework sets, and solutions


---

---
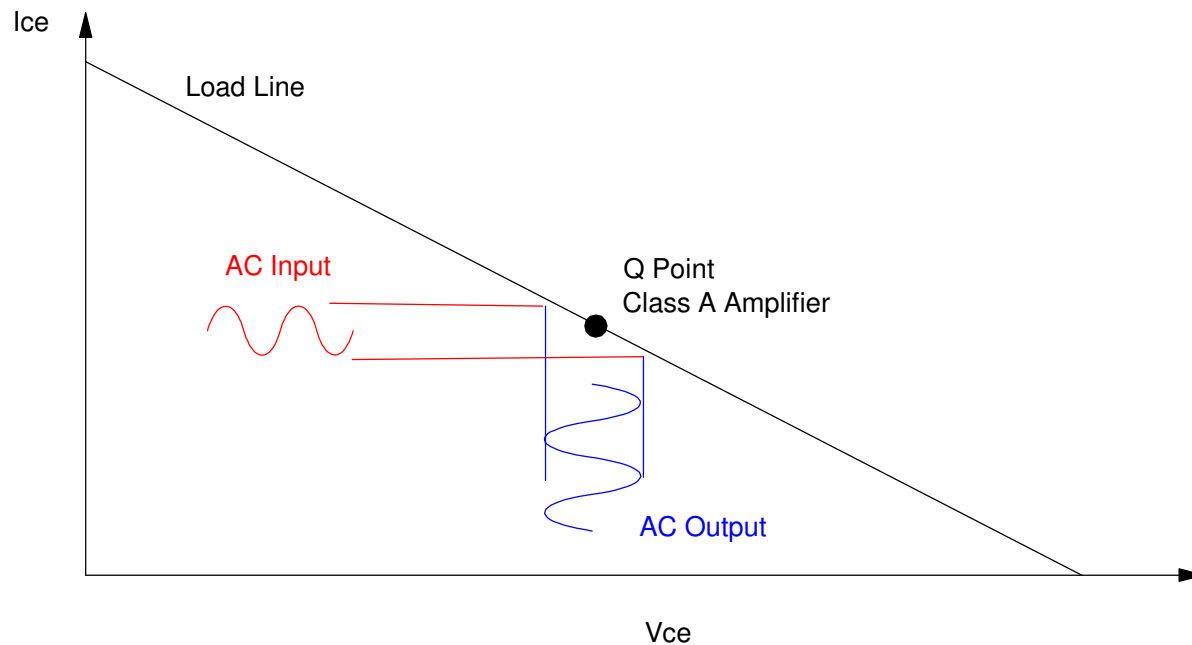
# Class-A Amplifiers

Bias the transistors in the active region


- Results in a large power drain even when there is no audio signal


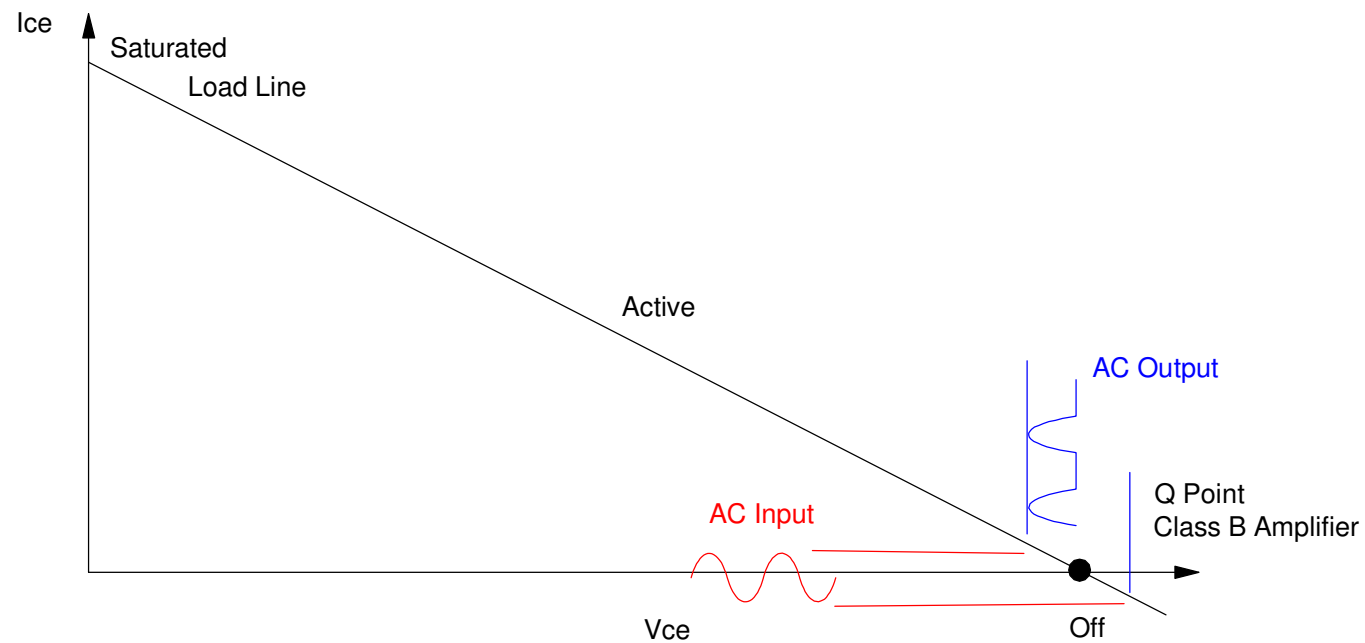
# Class-B Amplifiers (Push-Pull)

Biases the transistor so that it is off when there is no AC input.

- Less power consumption for small signals
- Results in clipping



## Example: Drive an 8-Ohm Speaker

### Input:

- 0..10V analog signal
- Capable of 20mA (i.e. a function generator)

### Output:

- 8 Ohm speaker

### Relationship:

- $Y = X$

### Option 1: Use an op-amp capable of 1.25A

- OPA2544: \$18 each
- AMT 30A8T: \$200 each

### Option 2: Use a push-pull amplifier

- TIP112 or 6411 (NPN)
- TIP117 (PNP)
- \$1 solution





## Solution (push):



- Use a transistor to amplify the current
- Place the load at the emitter
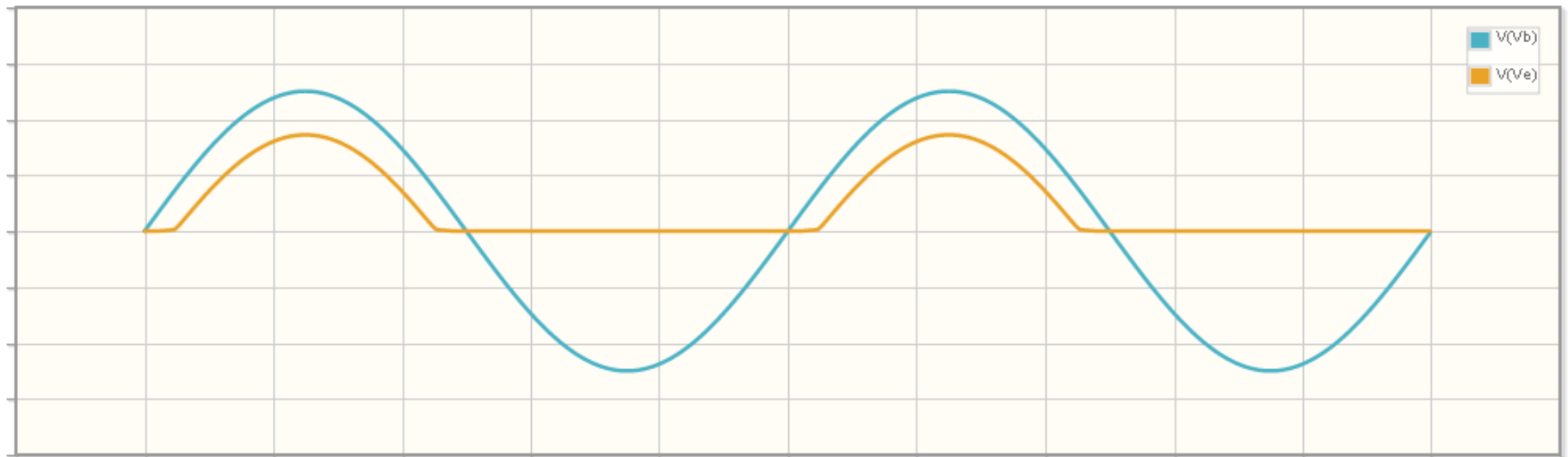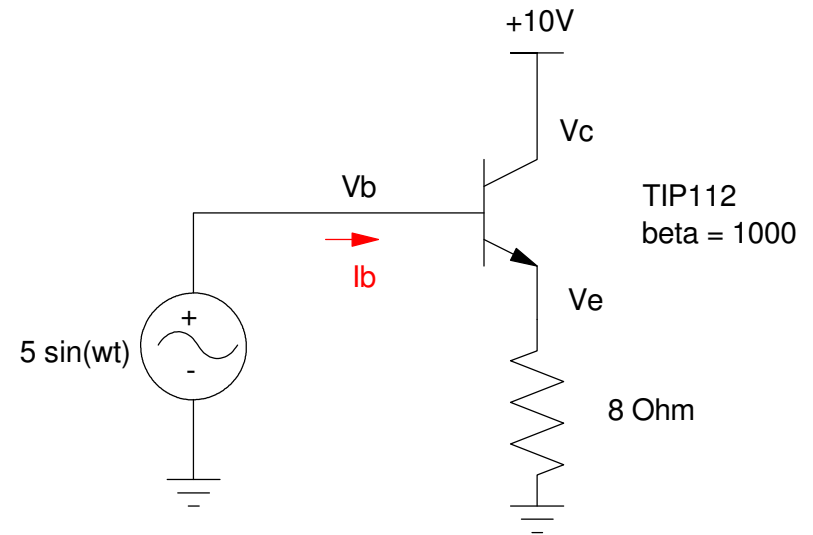
## What this does is



- When  $V_b > 0$ ,  $V_e$  follows  $V_b$
- When  $V_b < 0$ , the diode turns off and  $V_e = 0$ .



# Solution: Push-Pull

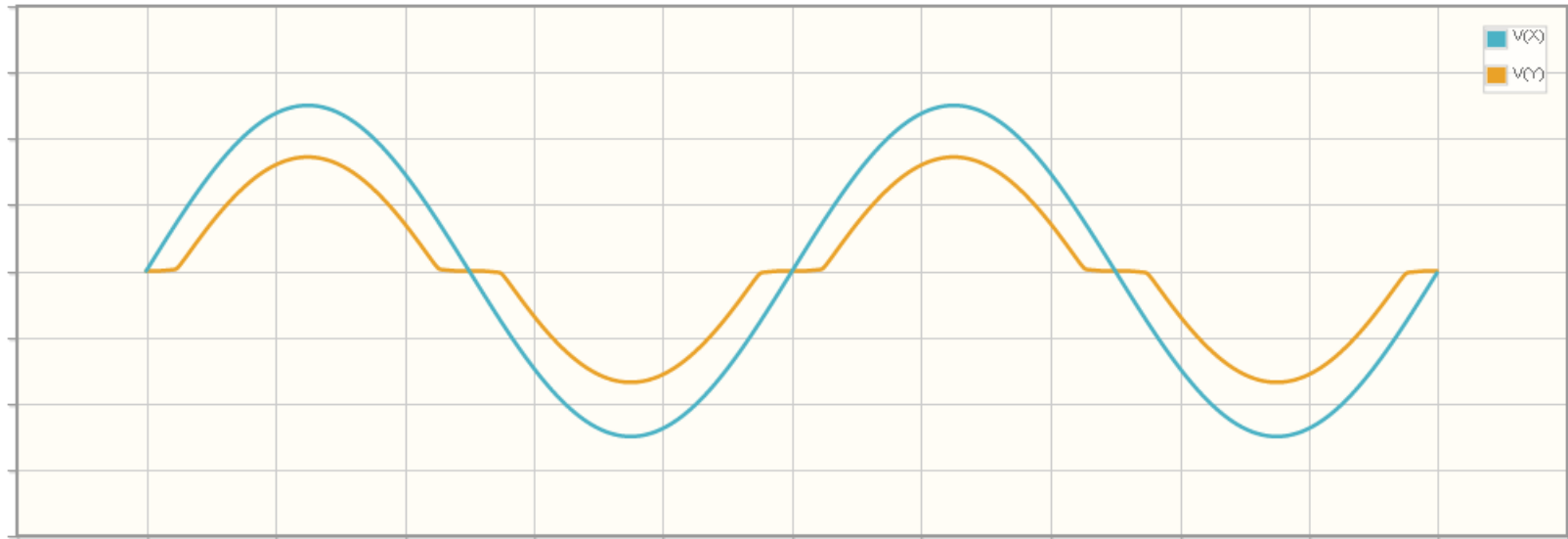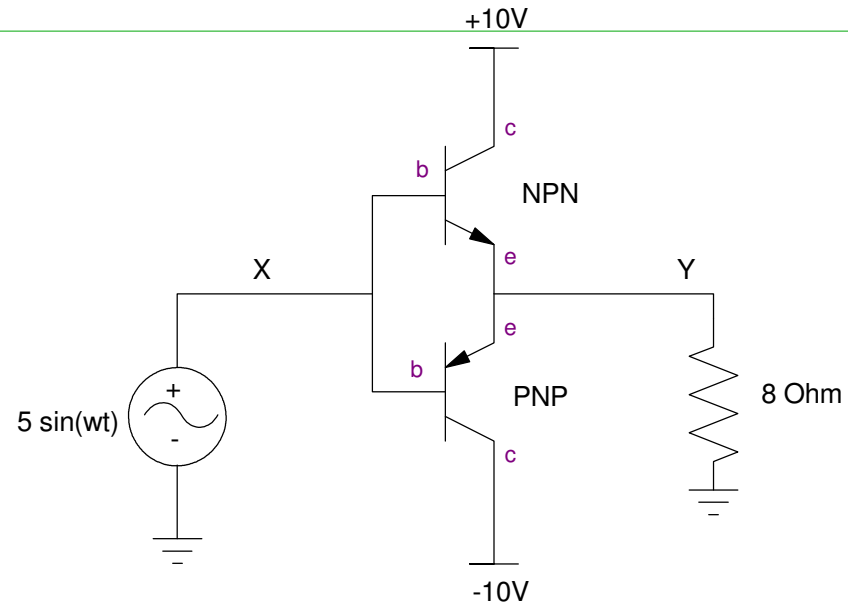
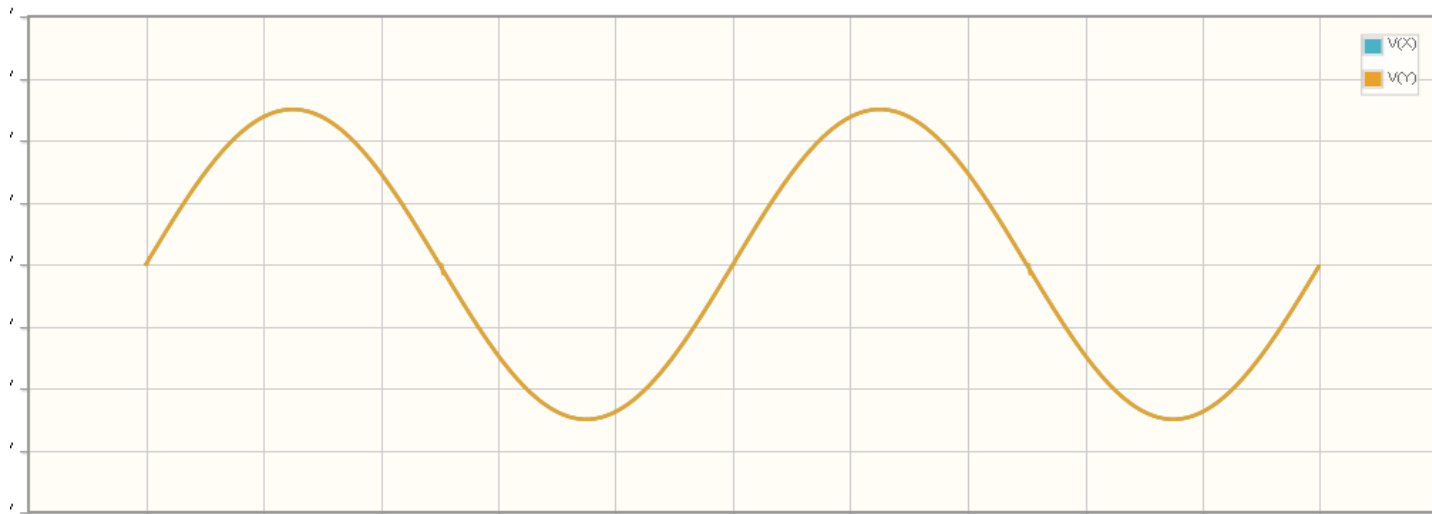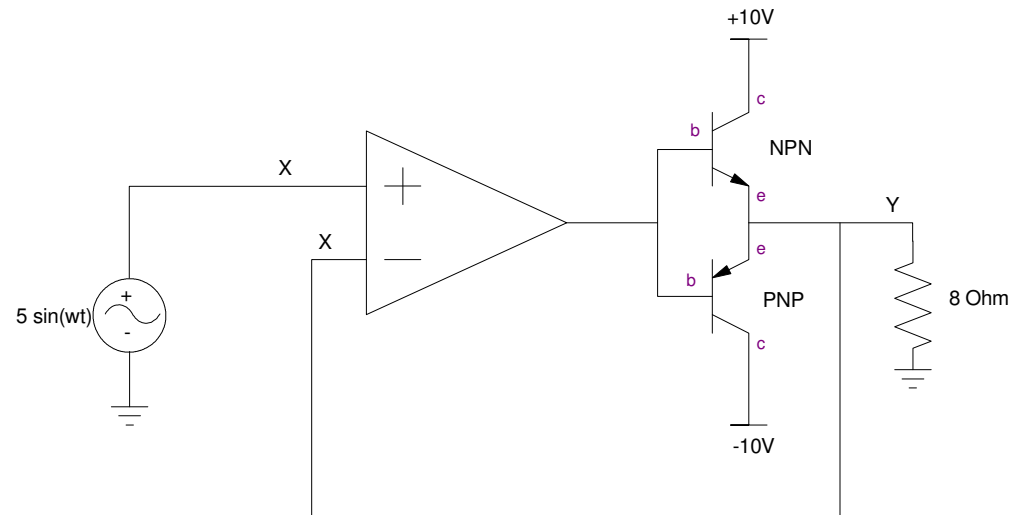
## Solution: Remove the cross-over distortion




# Result: Power Amplifier

Voltage: Assume  $X = 8V$

$$Y = X$$

Current:

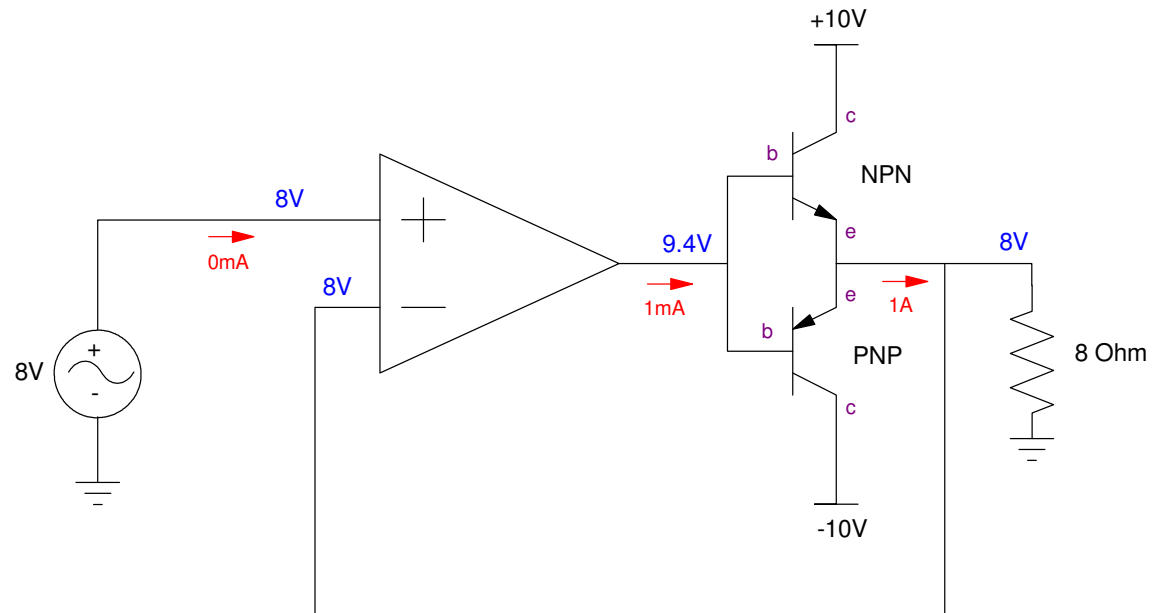- $I_3 = 1.00A$  (  $8V @ 8 Ohms$  )
- $I_2 = 1.00 mA$  (  $\beta = 1000$  )
- $I_1 = 0.00 mA$  ( ideal op amp )





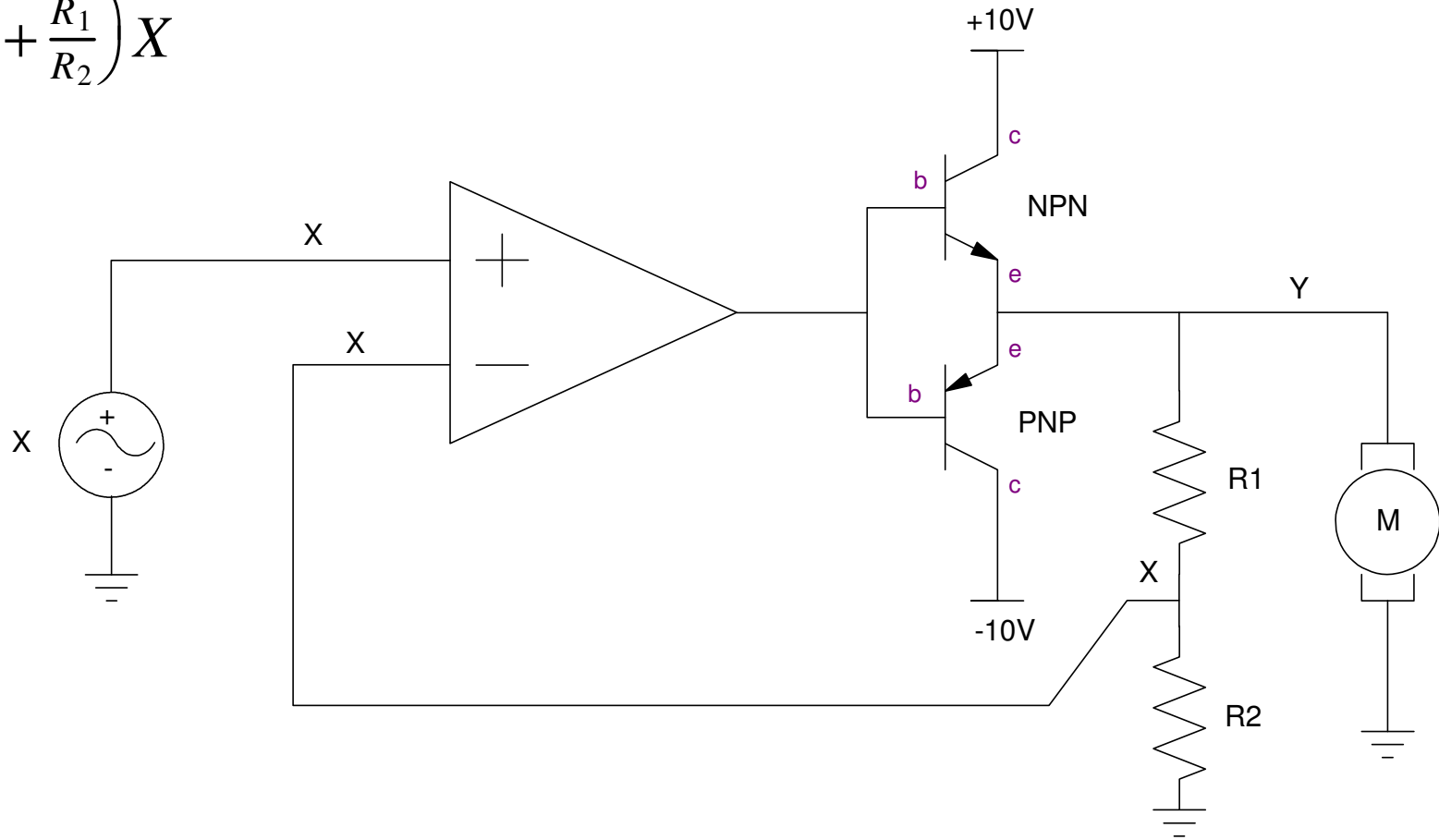
## Variation: Voltage Output


For DC motors, voltage is speed (approximately).

$$Y = \left(1 + \frac{R_1}{R_2}\right) X$$




## Handout: Determine the voltages and currents

- $|V_{be}| = 0.7V$
- $\beta = 300$

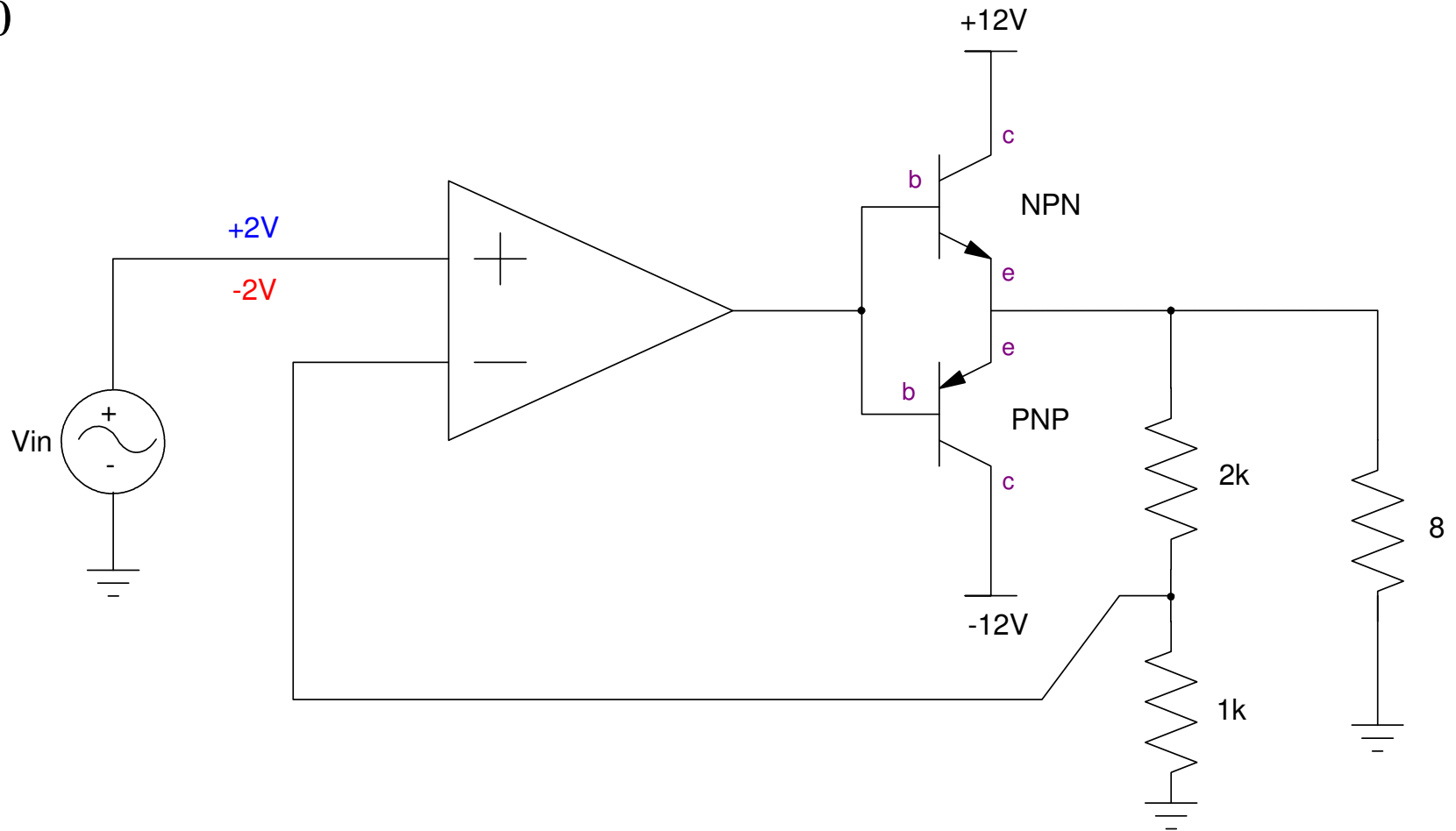

# Solution

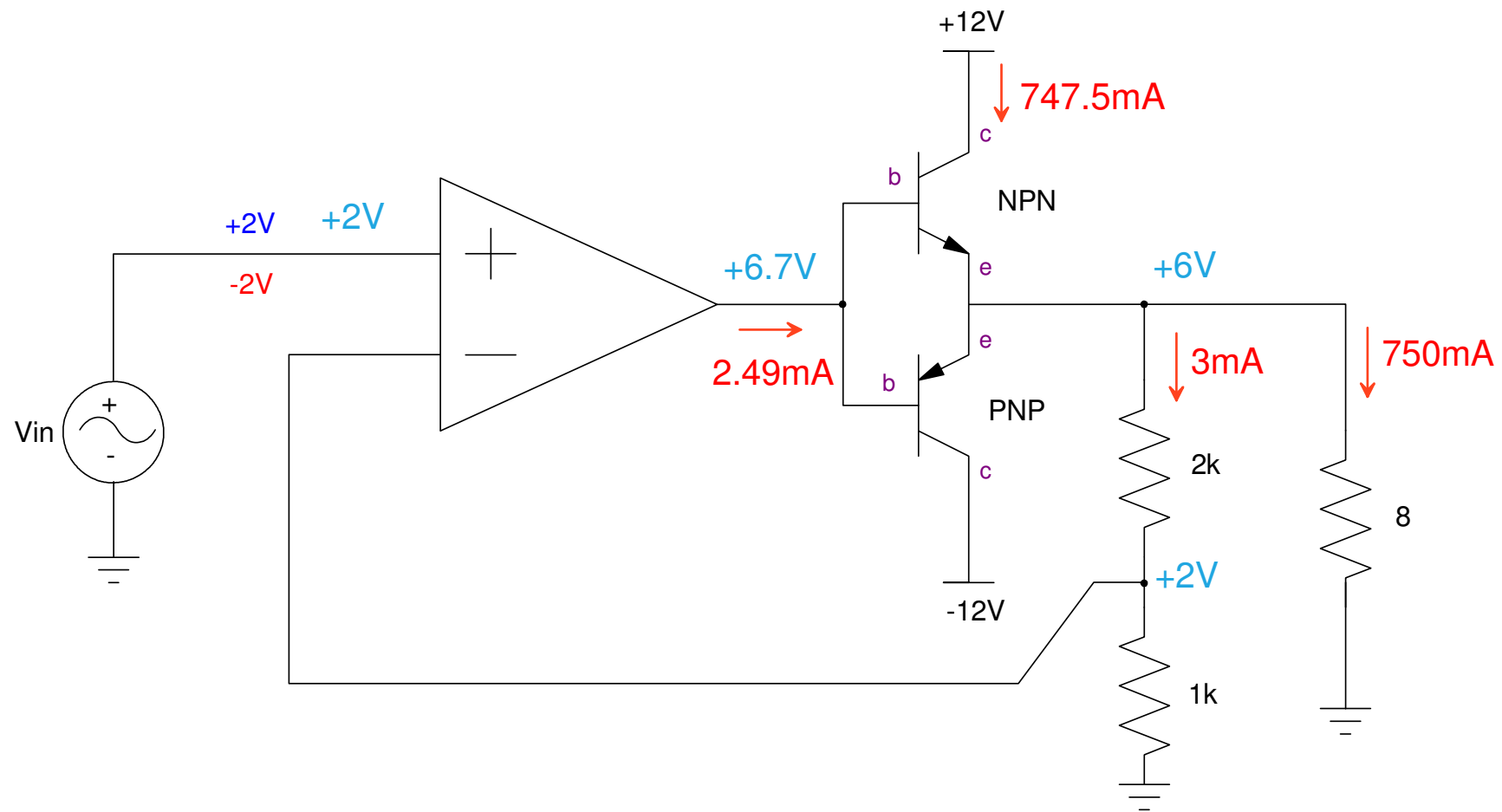


## Variation: Current Output


For DC motors, current is torque.


For LED's, current is brightness.

$$I_m = \frac{X}{1\Omega}$$

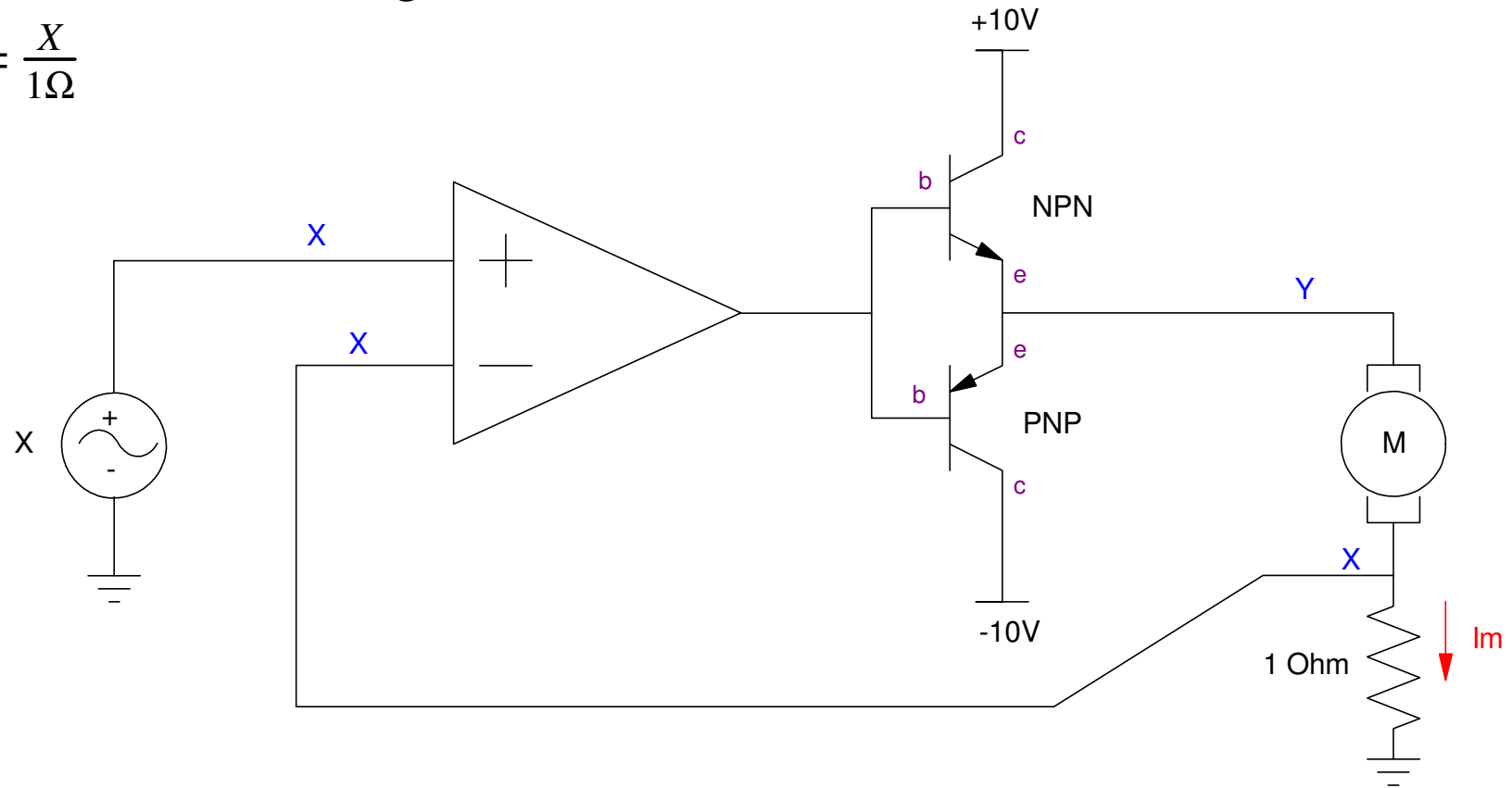
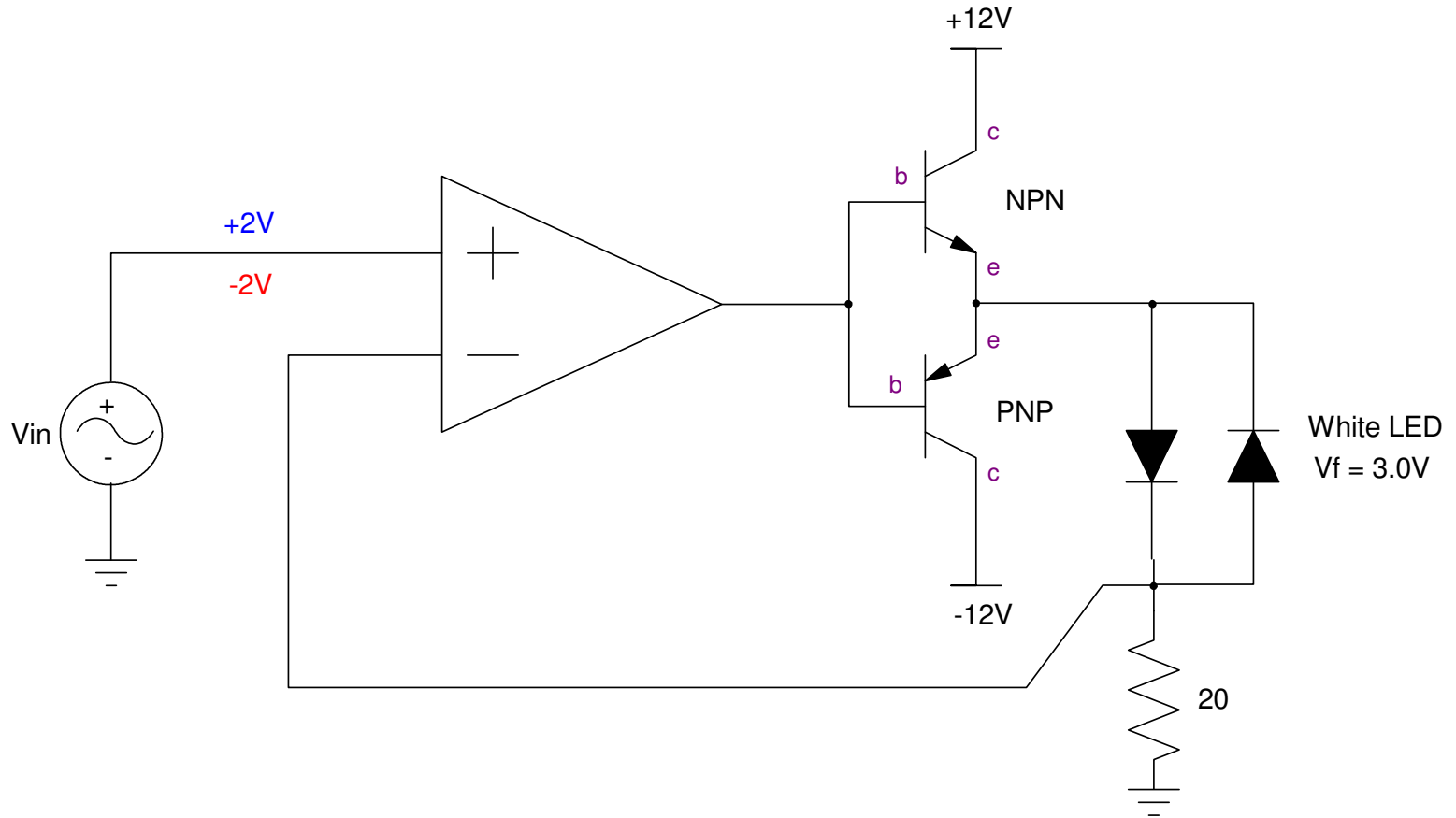
# Handout: Determine the voltages and currents




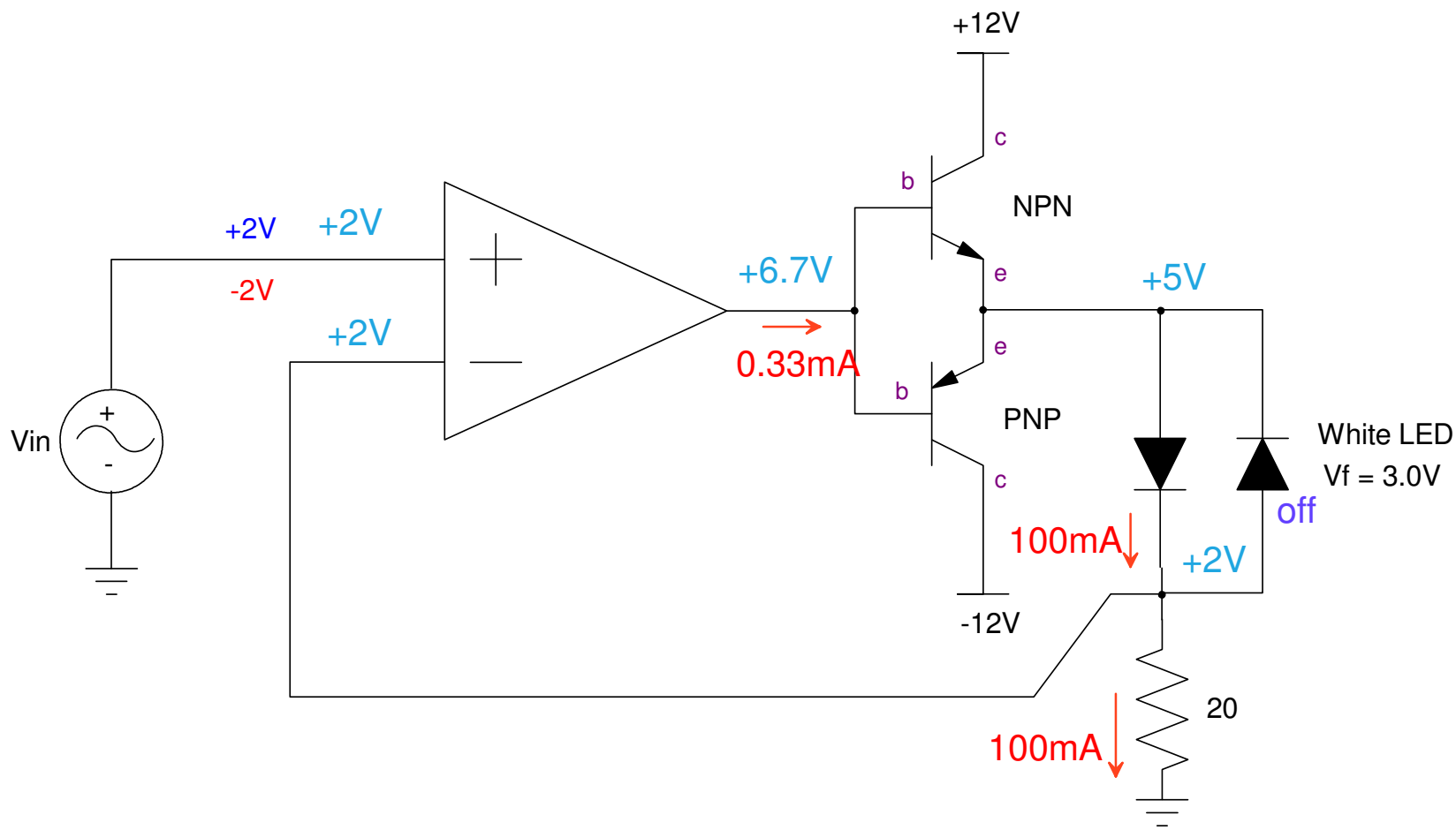

---


## Variation: Single Sided Supply

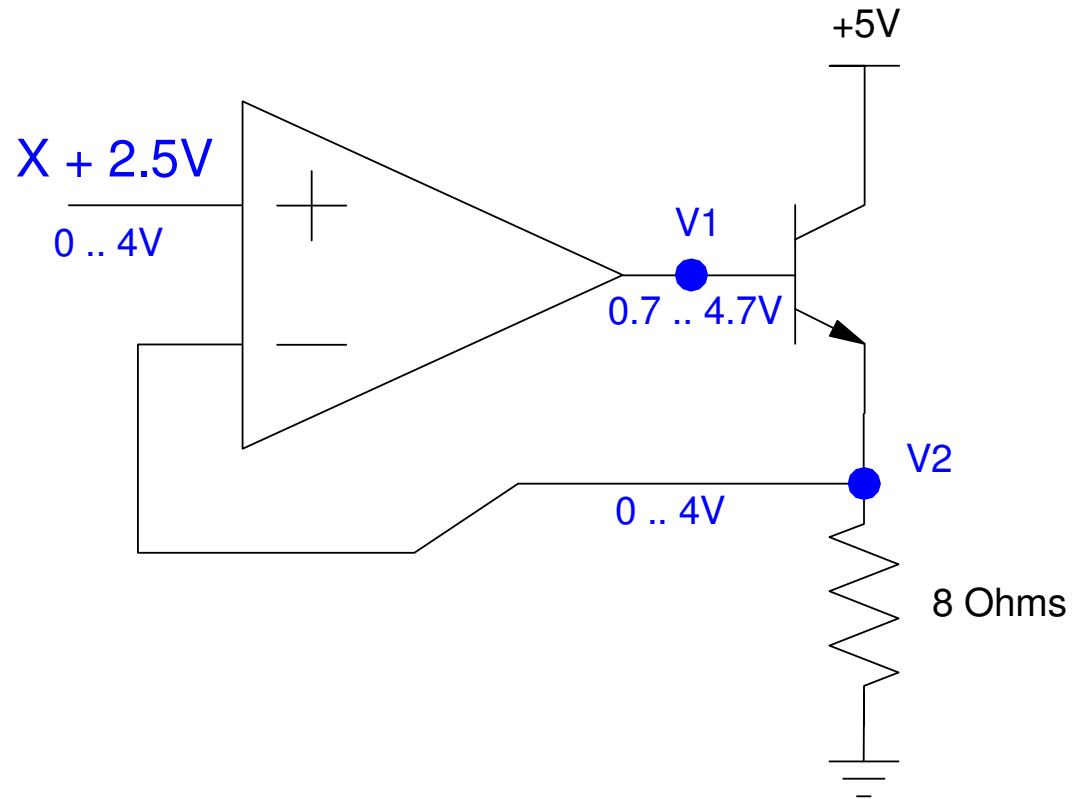- 0 .. +4V Out
- Class A Amplifier (inefficient)




# Handout: Determine the voltages and Currents

- $V1 = 2.8V$  ( circuit ground + 0.3V )

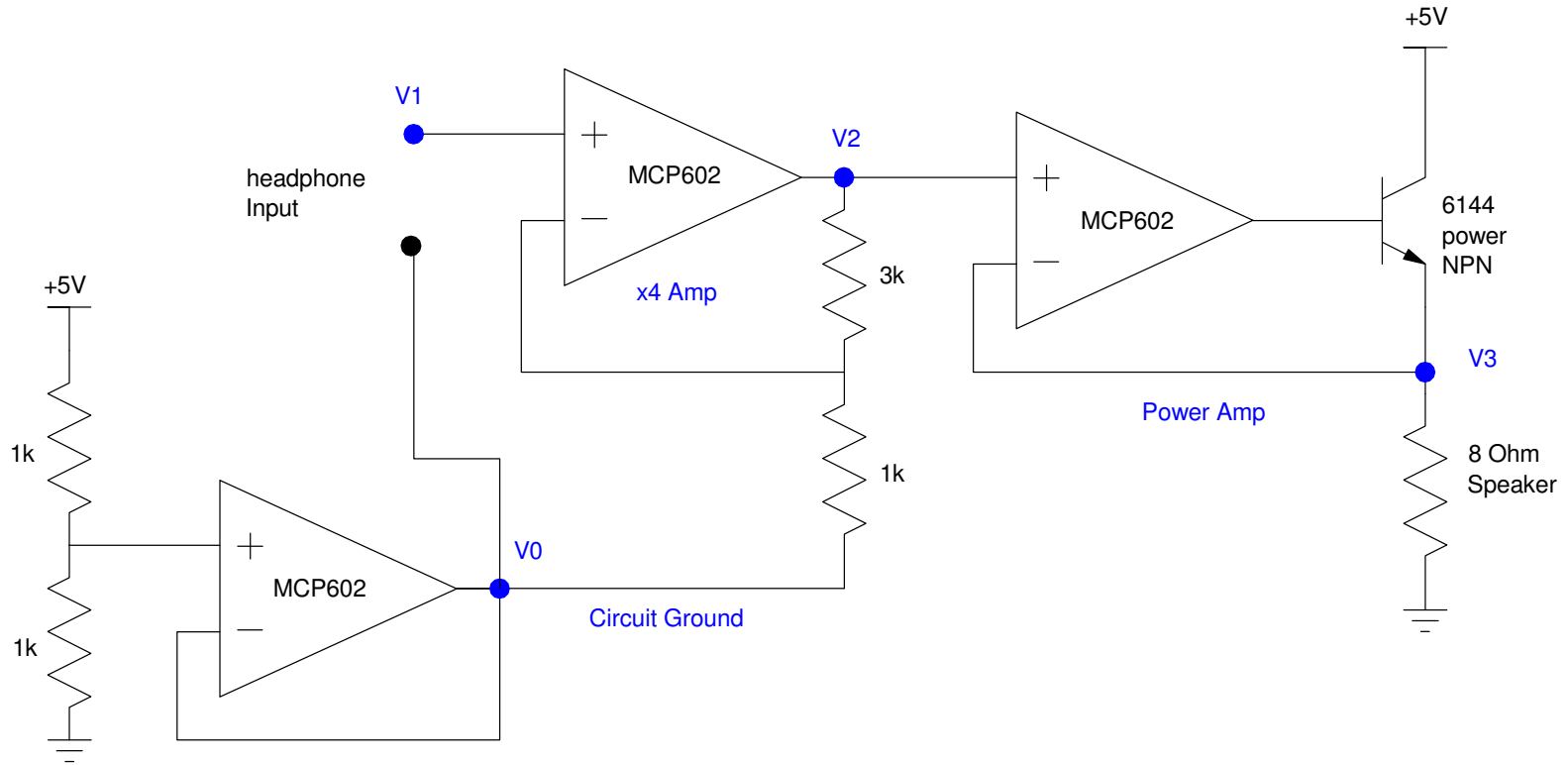




# Solution

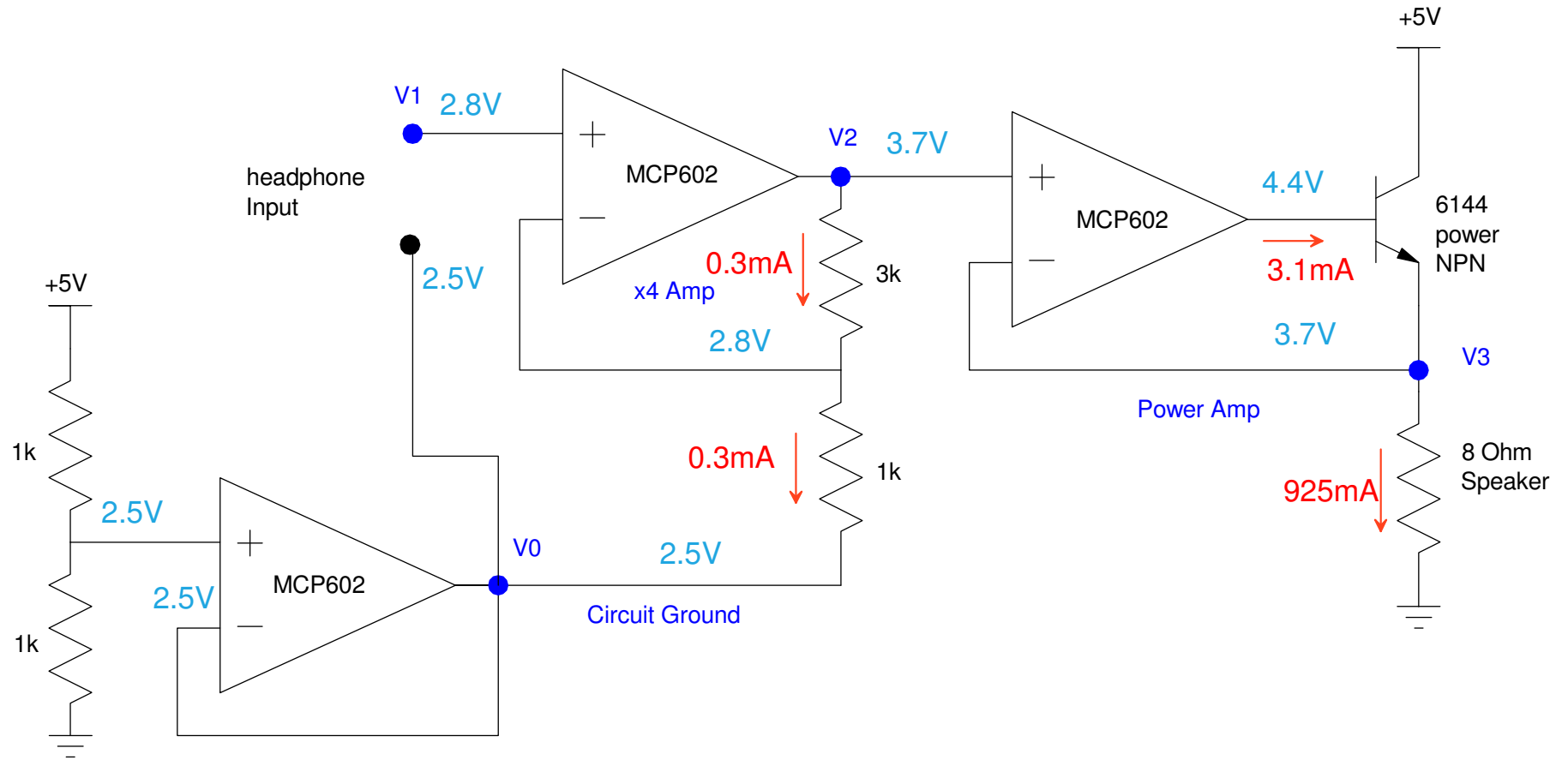

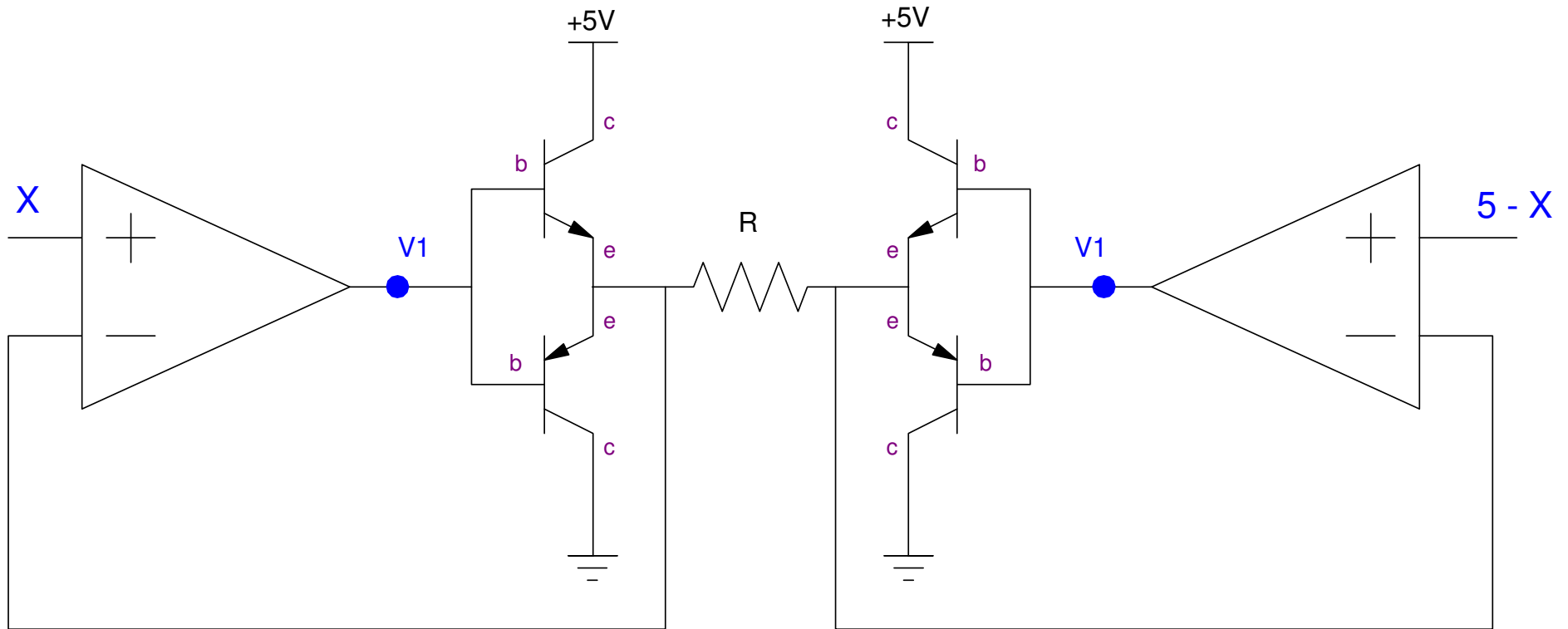
## Variation: Single-Sided Supply


- +3V .. -3V Out
- Class AB Amplifier (more efficient)



# +3V Out

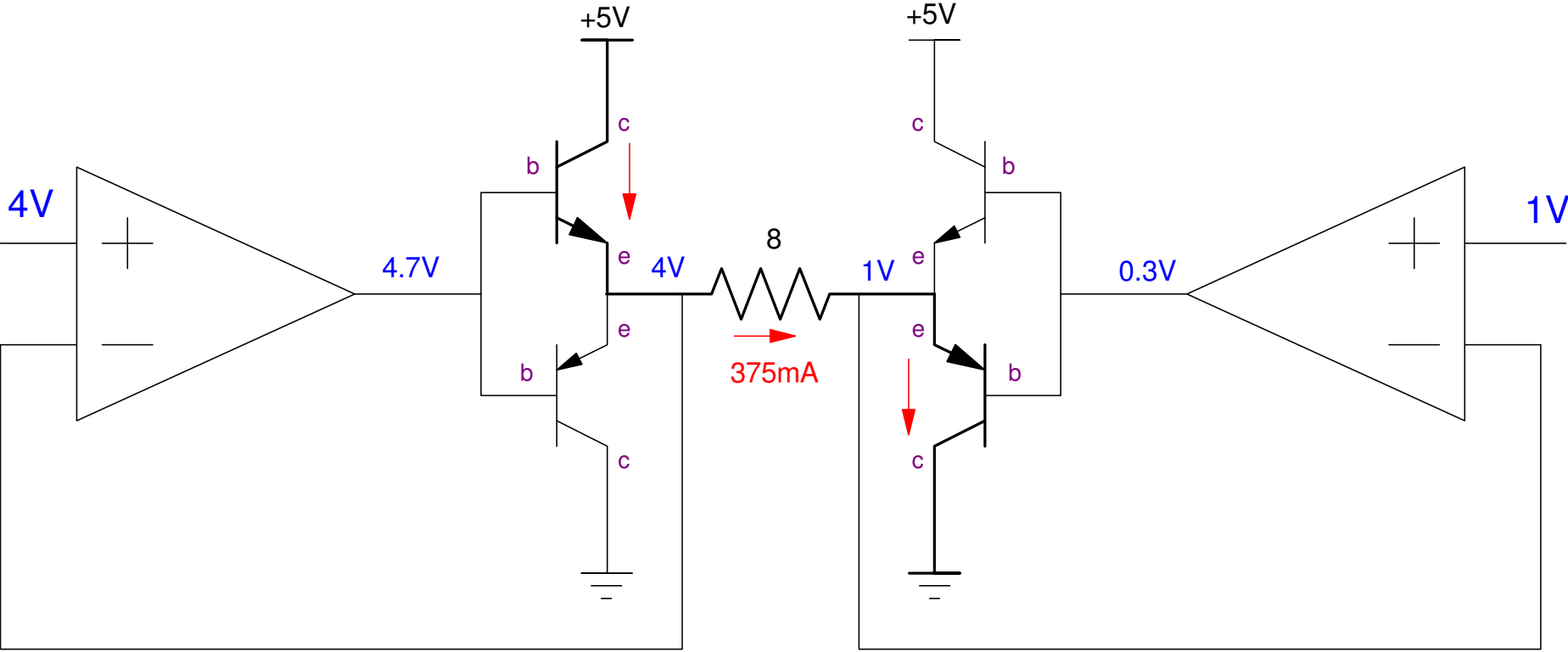

# -3V Out

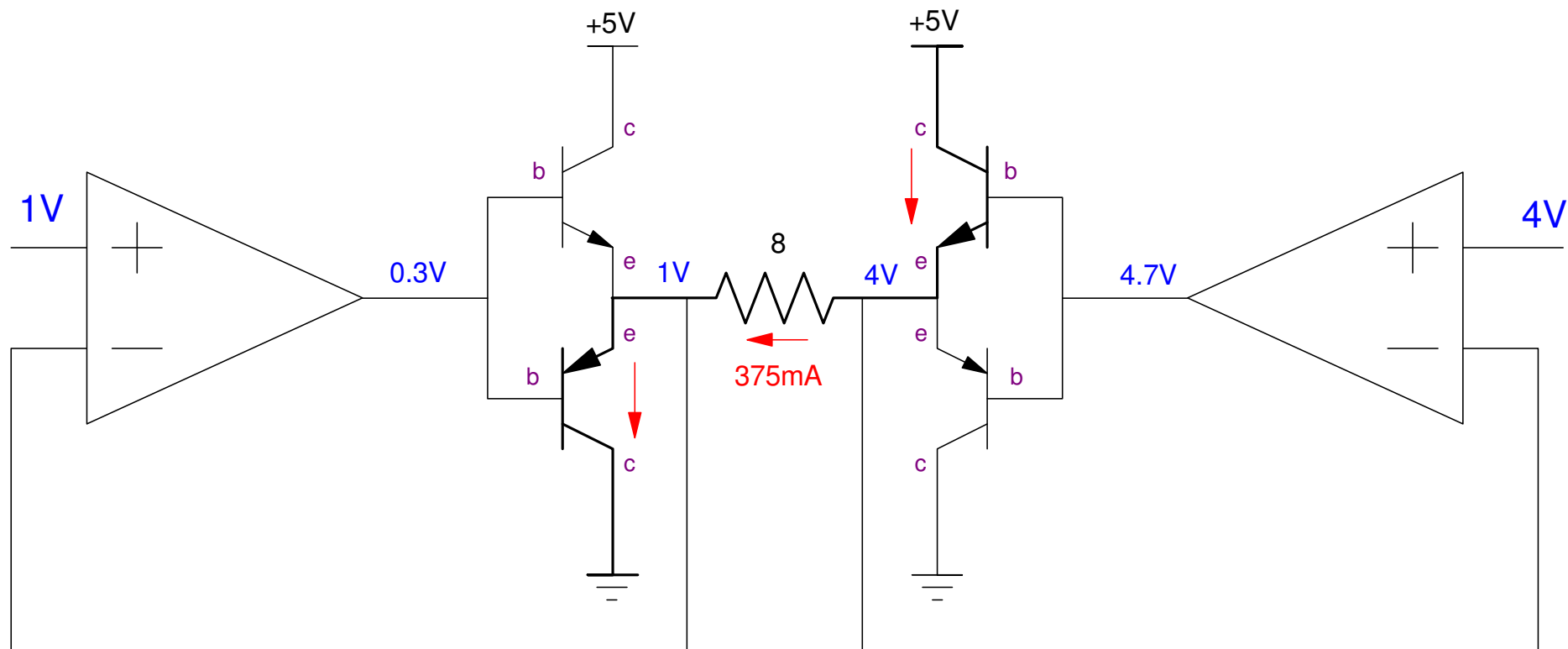

---

## Summary

A push-pull amplifier allows an op-amp circuit to drive a low-impedance load

- DC motor
- Speaker

Voltage Amplifier:

- Drive a speaker
- Control the speed of a DC motor

Current Amplifier

- Drive a power LED
  - Control the torque of a DC motor
-

