
Transistor Amplifiers: DC Analysis

Background:

Transistors can operate in three states:

- Off & Saturated: Used when operating as a switch
- Active: Used when operating as an amplifier.

In active mode, the collector current is

$$I_{CE} = \beta I_{BE}$$

subject to the constraint

$$V_{CE} > V_{CE:\min}$$

or

$$\beta I_{BE} < \max(I_{CE}).$$


For a transistor to act as an amplifier,

- You first have to bias the transistor to place it in the active region.
- Next, connect the base, collector, and emitter to the outside world with capacitors. This prevents the rest of the circuit from messing up the bias on the transistor.
- One of these three (base, emitter, collector) goes to the input, one goes to the output, and the third is grounded. This creates different types of amplifiers we'll discuss in a few days.


This lecture concentrates on biasing a transistor into the active region.

NPN Transistor Amplifier Circuit:

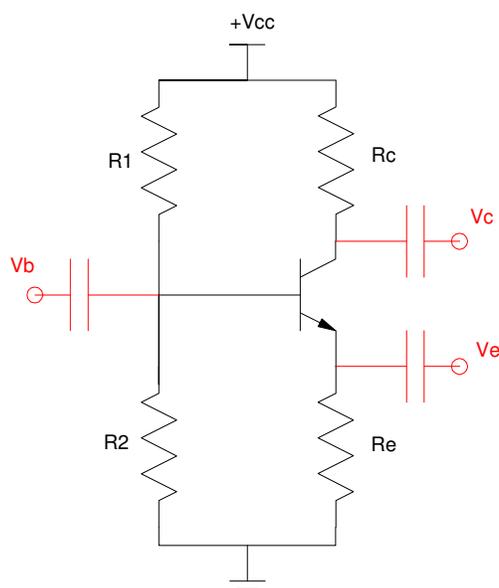The basic amplifier we'll be using is as follows. The capacitors will be added in lecture 21.



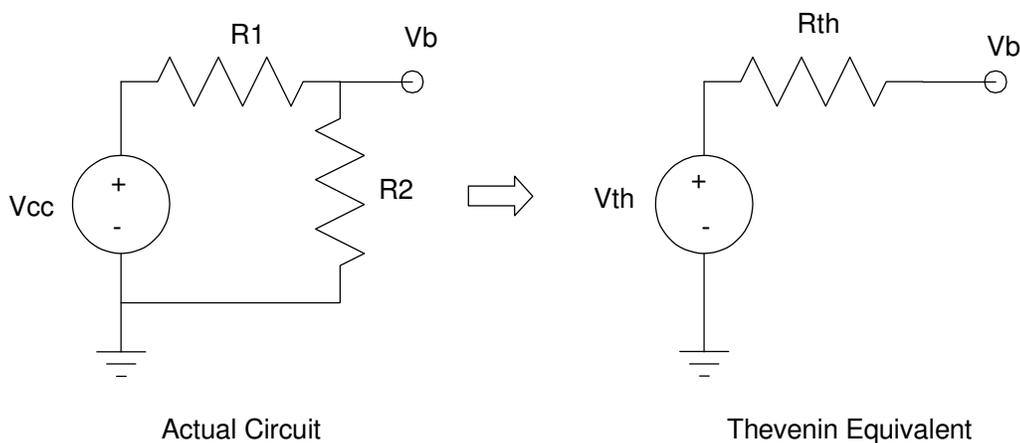To start, assume $R_e = 0$. Taking the Thevenin equivalent of R_1 and R_2 : (One theme in ECE 321 is the use of Thevenin equivalents. You don't have to do this, but if you get use to using Thevenin equivalents, problems in electronics become much simpler.)



The idea behind Thevenin equivalents is this is a linear circuit: meaning the VI characteristics are a straight line. Any circuit which has the same VI characteristic behaves the same as far as the output is concerned.

The simplest circuit to give a linear VI characteristic is a single voltage source and a single resistor. So, let's replace the more complex circuit with the simpler one. (If they behave the same, why not use the simpler one for analysis?)


First, let's find V_{th} . For the circuit on the right, you find V_{th} by leaving V_b open and measuring the voltage to ground. Doing the same test on the circuit to the left results in V_{th} :

$$V_b = \left(\frac{R_2}{R_1 + R_2} \right) V_{cc} = V_{th}$$

Next, measure R_{th} . To do this, turn off the power supply (set $V_{th}=0$) and measure the resistance from V_b to ground. Doing this to the circuit to the left results in R_1 and R_2 being in parallel, both connecting V_b to ground:


$$R_{th} = R_1 || R_2 = \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

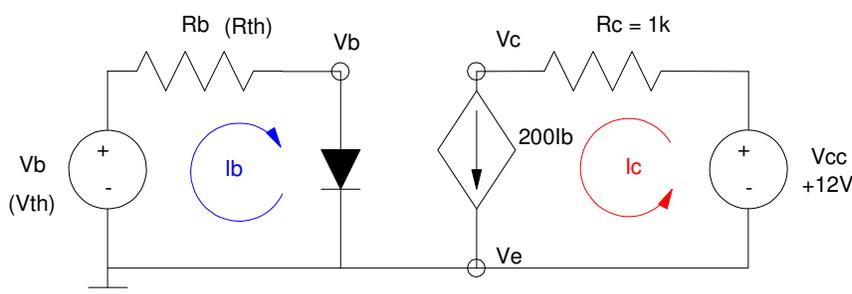Now, let's go back to the transistor circuit and replace R_1 and R_2 with their Thevenin equivalent. Also, let's replace the transistor with its model in the active mode: (sorry - my editor doesn't allow greek letters in figures. The current gain should be βI_b . Assume $\beta = 200$).



Let's look at the load line for I_c and V_{ce} .

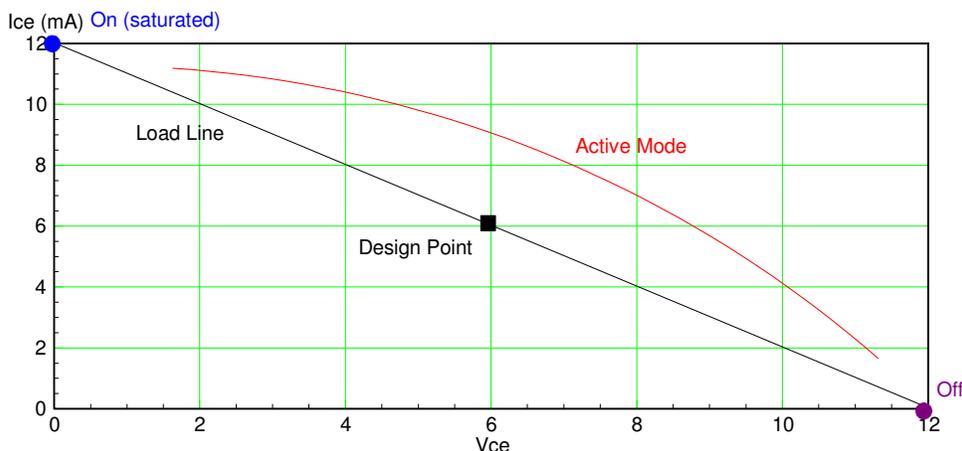- If $I_c = 0V$, $V_{ce} = +12V$.
- If $V_{ce} = 0V$, $I_c = 12mA$.
- This is a linear circuit, so the VI characteristics map a line:



Depending upon what I_c is, you can place V_{ce} anywhere you like on the load line.

- If you want the transistor to turn off, set $I_c = 0$ (meaning $I_b = 0$). The transistor is acting like a switch that's off.

- If you want the transistor to turn on, set $I_c > 12\text{mA}$ (meaning $I_b > 6\mu\text{A}$). The transistor is acting like a switch that's on.
- If you want the transistor to be in the active mode and behave like an amplifier, pick your operating point (termed the Q point) somewhere between $V_{ce}=0\text{V}$ and $V_{ce}=+12\text{V}$.

Shortly, we'll be adding an AC signal to this amplifier. This results in the design point swinging up and down. To allow maximum swing, let's pick the Q point to be (6V, 6mA).

Now, pick V_{th} and R_{th} to set the Q point to 6V and 6mA:

$$\beta I_b = I_c = 6\text{mA}$$

$$I_b = 30\mu\text{A}$$

and

$$I_b = \frac{V_b - 0.7\text{V}}{R_b} = 30\mu\text{A}$$

Here you have one equation for two unknowns. This lets you set one of the unknowns at will. Let $V_b = +12\text{V}$, resulting in

$$V_b = 12\text{V}$$

$$R_b = 377\text{k}\Omega$$

Converting back to R_1 and R_2 :


$$V_b = \left(\frac{R_2}{R_1 + R_2} \right) 12\text{V} = 12\text{V}$$

$$R_2 = \infty$$

$$R_b = R_1 || R_2 = 377\text{k}\Omega$$

$$R_1 = 377\text{k}\Omega$$

so your circuit is:

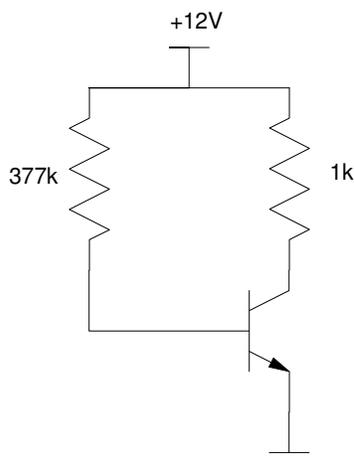

Q Point Stabilization

This circuit isn't very good to to variance in the gain, β . Transistors typically have a wide variance in gain. A 2n222 transistor, for example has a gain of 200 ± 100 . This results in the Q point being between:

If you compute the Q point as a function of β :

$$I_b = \left(\frac{12V - 0.7V}{377k} \right) = 30\mu A$$

$$I_c = \beta I_b$$


$$V_c = 12 - 1000I_c$$

or V_c is somewhere between 9V ($\beta = 100$) and 3V ($\beta = 300$).


ou can do a Monte-Carlo simulation of this circuit as well. For a Monte-Carlo simulation, you select random values for each component and compute the results for those values. Assuming 1% tolerance on the resistors and ± 100 for β results in:

```
for i=1:100
    Rb = 377000 * (1 + (rand()*2-1)*0.01);
    Rc = 1000 * (1 + (rand()*2-1)*0.01);
    Beta = 200 + 100*(rand()*2-1);
    Ib = (12-0.7)/Rb;
    Ic = Beta*Ib;
    Vc = 12-Ic*Rc;
    plot(Vc, Ic*1000, '.');
end
```

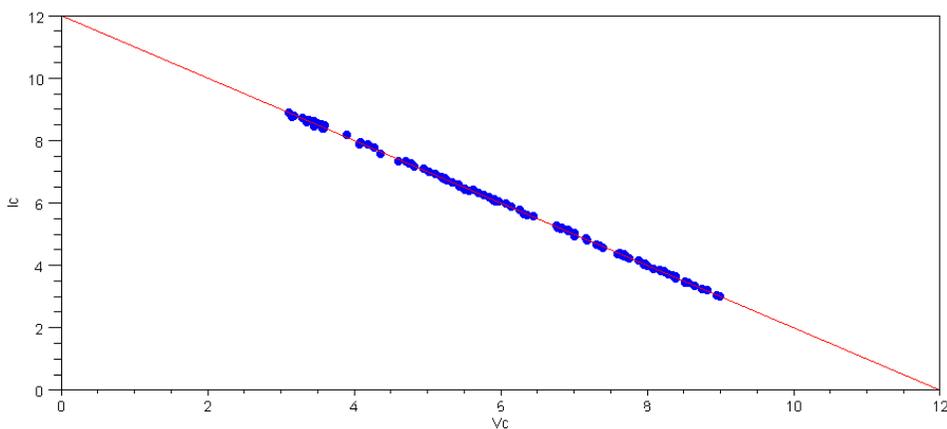A scattergram of the resulting Q point is shown below. Note that there is a lot of variation in where you are operating.



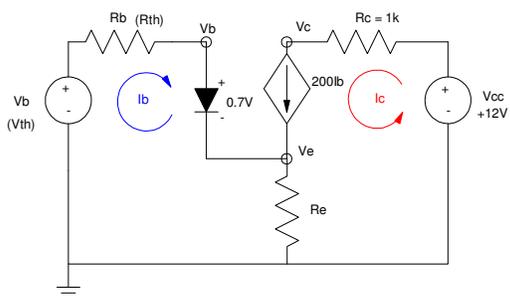To compensate for variations in β , add R_e .



Writing the loop equations:

$$I_c = \beta I_b$$

$$-V_b + R_b I_b + 0.7 + R_e (I_b + I_c) = 0$$

or


$$I_b = \left(\frac{V_b - 0.7}{R_b + (1 + \beta) R_e} \right)$$

To stabilize the voltage at V_c :

$$V_c = V_{cc} - R_c I_c$$

$$V_c = V_{cc} - \left(\frac{\beta R_c}{R_b + (1 + \beta) R_e} \right) (V_b - 0.7)$$

If

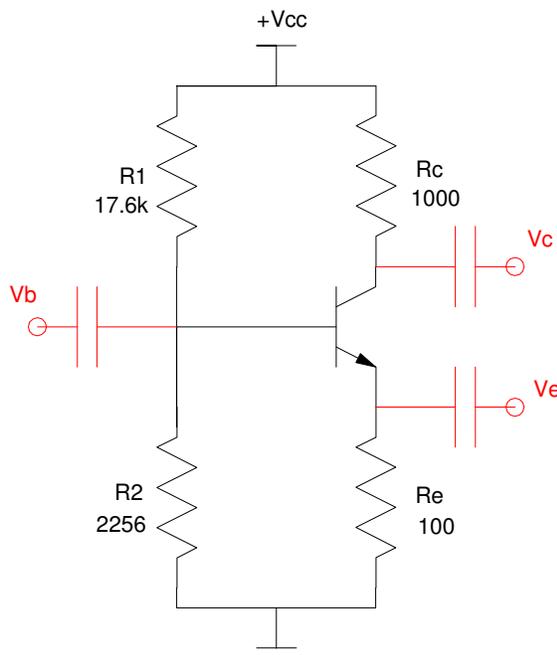

then

$$V_c \approx V_{cc} - \left(\frac{\beta R_c}{(1+\beta)R_e} \right) (V_b - 0.7)$$

For β large,

$$\left(\frac{\beta}{1+\beta} \right) \approx 1$$

so the voltage, V_c , is no longer affected by variations in β .

To stabilize the Q point, pick R_e such that

$$(1 + \beta)R_e \gg R_b$$

Going back to our original design, let's design for $V_c = 6V$. Ideally, I'd like $R_e = 0$ so that V_c can swing from $0V$ to $+12V$. $R_e = 0$ results in a Q point that's sensitive to variations in β , however. So, instead, let R_e be 1/10th of R_c (small to allow a large voltage swing but non-zero.)

$$R_e = 100\Omega$$

To stabilize the Q point

$$(1 + \beta)R_e \gg R_b$$

$$20, 100\Omega \gg R_b$$

Let

$$R_b = 2k\Omega$$

From before,

$$I_c = 6mA$$

$$I_b = 30\mu A$$

so

$$I_b = \left(\frac{V_b - 0.7}{R_b + (1+\beta)R_e} \right) = 30\mu A$$

$$V_b = 1.363V$$

This corresponds to R_1 and R_2 being:

$$\left(\frac{R_1 R_2}{R_1 + R_2} \right) = 2000$$

$$\left(\frac{R_2}{R_1 + R_2} \right) 12V = 1.363V$$

and


$$R_1 = 17.6k\Omega$$

$$R_2 = 2256\Omega$$

So your circuit is as shown to the right. If the gain, β , varies, the Q point varies as:

- $\beta = 100$: $V_c = 6.52V$
- $\beta = 200$: $V_c = 6.00V$
- $\beta = 300$: $V_c = 5.80V$
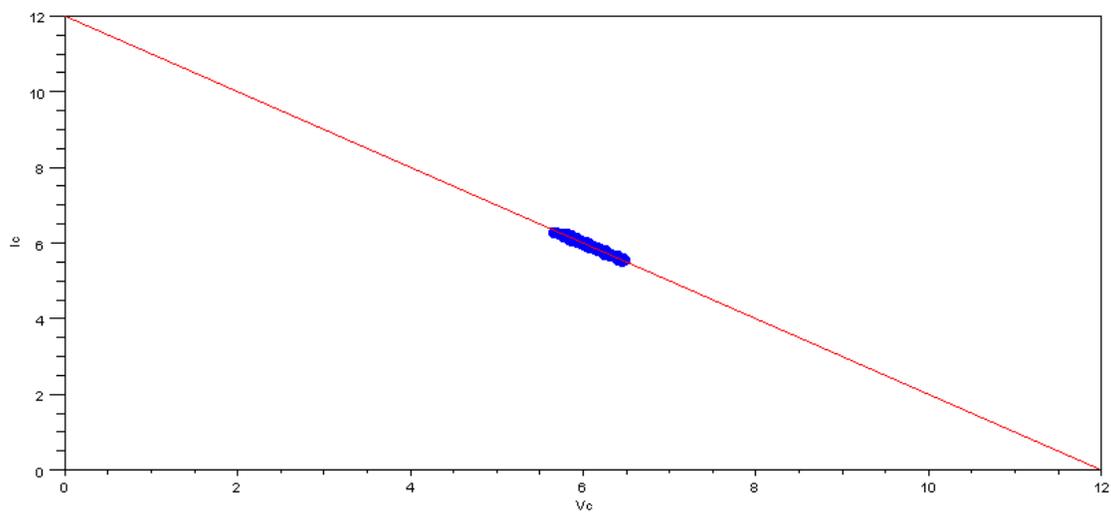
```
for i=1:100
R1 = 17600 * (1 + (rand()*2-1)*0.01);
R2 = 2256 * (1 + (rand()*2-1)*0.01);
Rc = 1000 * (1 + (rand()*2-1)*0.01);
Re = 100 * (1 + (rand()*2-1)*0.01);
Beta = 200 + 100*(rand()*2-1);
Vb = 12*(R2 / (R1+R2));
Rb = 1/(1/R1 + 1/R2);
Ib = (Vb-0.7) / (Rb + (1+Beta)*Re);
Ic = Beta*Ib;
Vc = 12 - Rc*Ic;
plot(Vc, Ic*1000, '.');
end
```



The Q point can still vary a bit - bit it's a lot better than before.