
2-Port Models

ECE 321: Electronics II

Lecture #13:
Jake Glower


Please visit Bison Academy for corresponding
lecture notes, homework sets, and solutions

2-Port Models

Generalized Thevenin Equivalent



Thevenin Equivalents

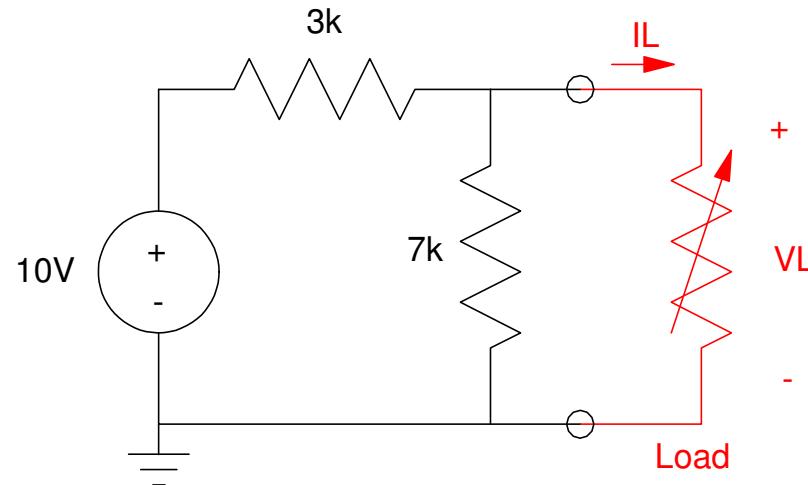- The output of a circuit follows a load line
- Any circuit with the same load line behaves the same
- The Thevenin Equivalent is the simplest circuit to obtain the same load line



Thevenin Example:

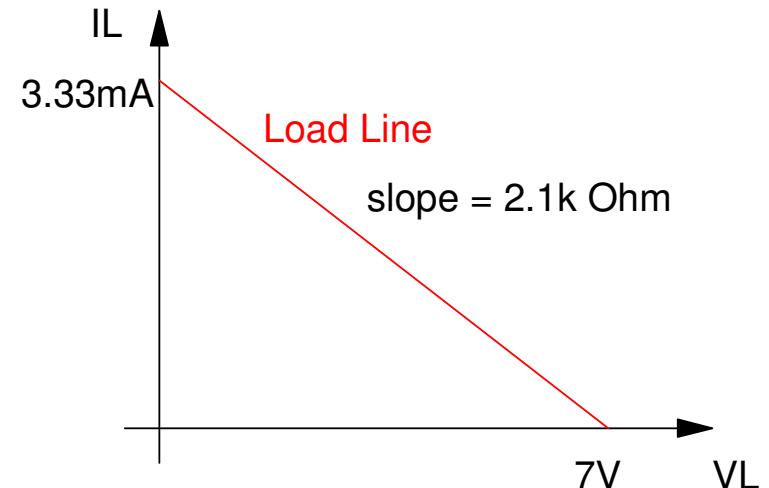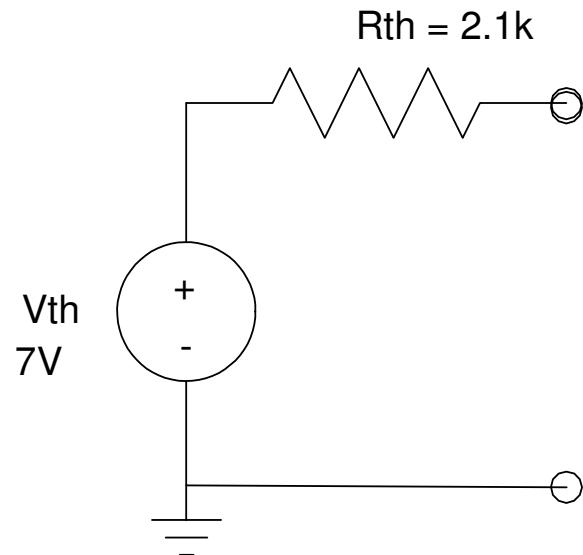- V_{th} : The voltage at the load with $R_L = \text{infinity}$ (7V)
- R_{th} : The resistance looking in with sources turned off: $3\text{k}\parallel 7\text{k} = 2.1\text{k}$
- I_{short} : The current I_L when $RL = 0$. $I_{short} = V_{th} / R_{th}$: $I_{short} = 10\text{V}/3\text{V} = 3.33\text{mA}$




Thevenin Equivalent for Previous Circuit along with its Load Line

2-Port Models

Thevenin equivalent for circuits with


- An input
- An output

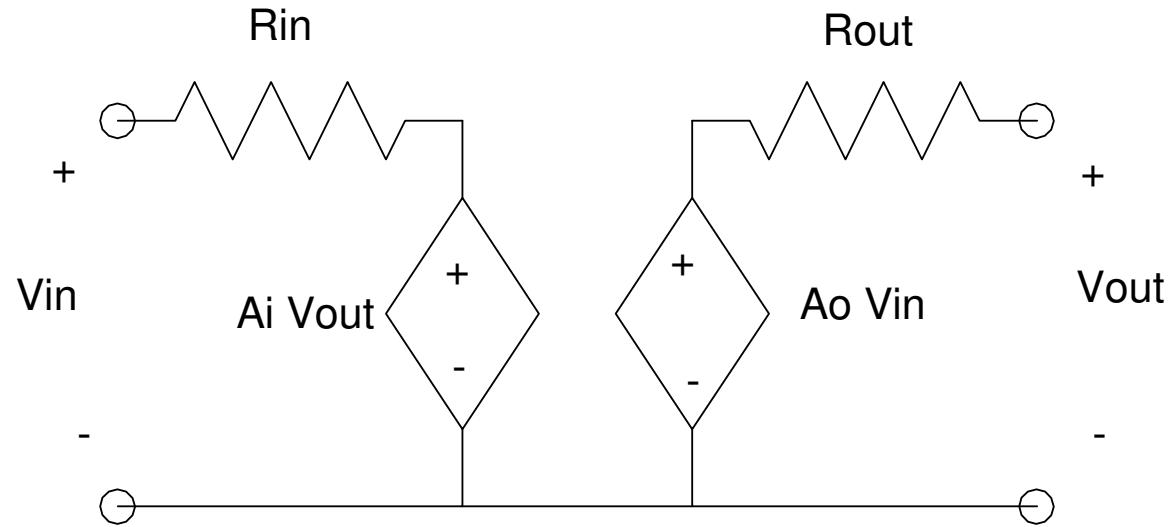


2-Port Parameters:

To determine each of the four 2-port model parameters, four tests are run:

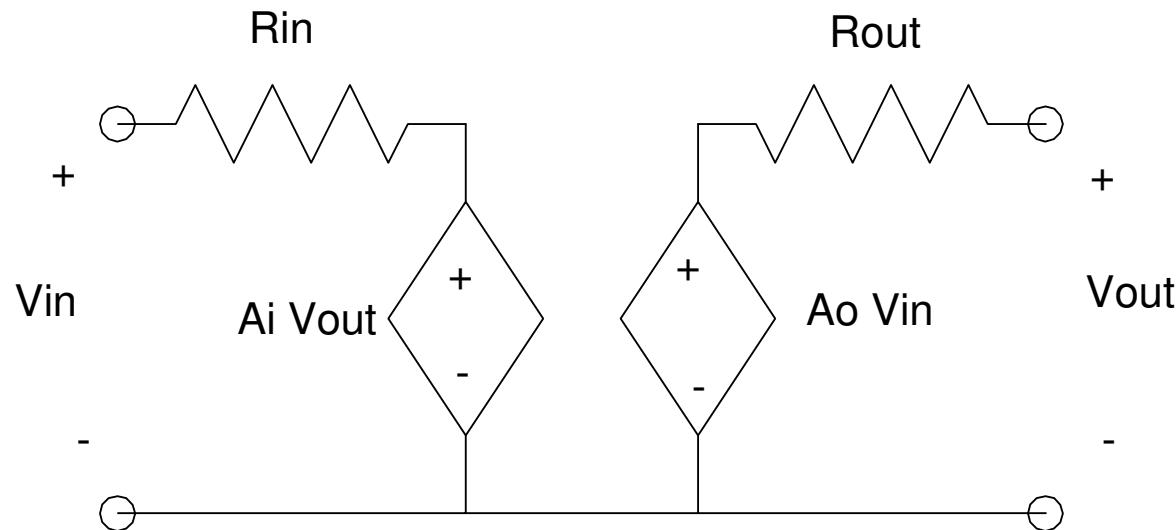- A_i : Set $V_{out} = 1V$ and measure V_{in} . $A_i = V_{in}$
- A_o : Set $V_{in} = 1V$ and measure V_{out} . $A_o = V_{out}$
- R_{in} : Set $V_{out} = 0V$ and measure the resistance seen at the input
- R_{out} : Set $V_{in} = 0V$ and measure the resistance seen at the output




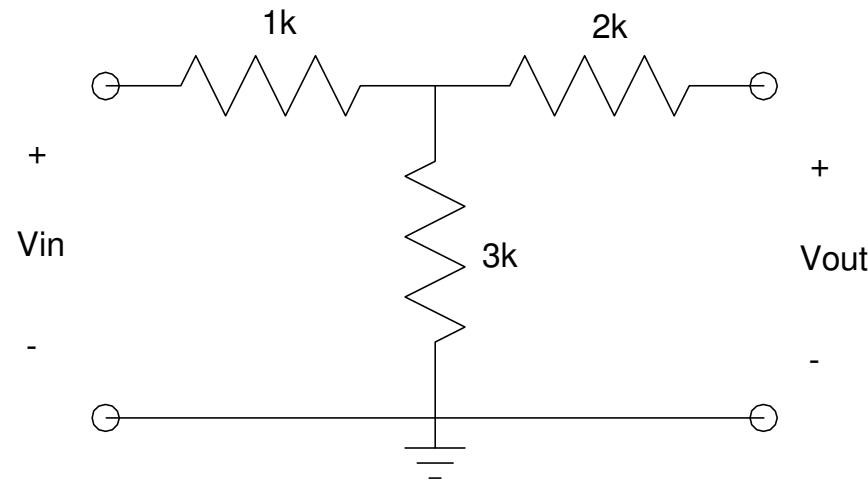Example: Determine the 2-port model for the following circuit:




Ai: Set $V_{out} = 1V$, measure the voltage at V_{in} . $A_i = V_{in}$

- $A_i = 0.6$

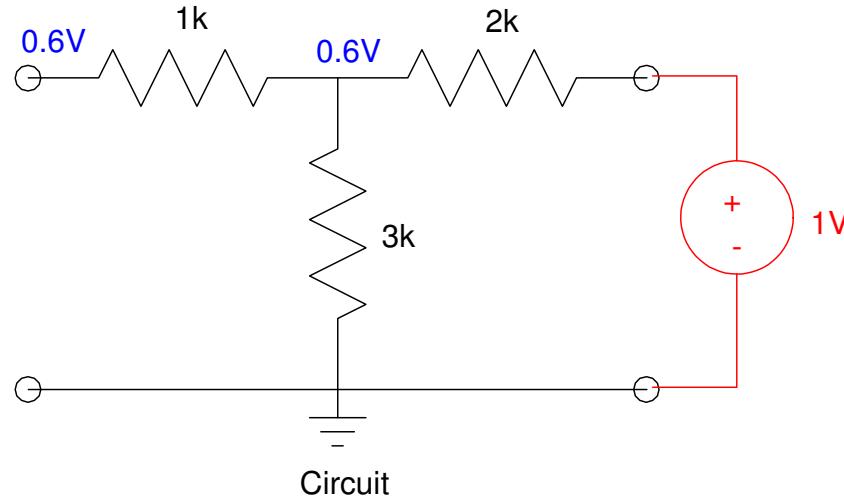



Circuit

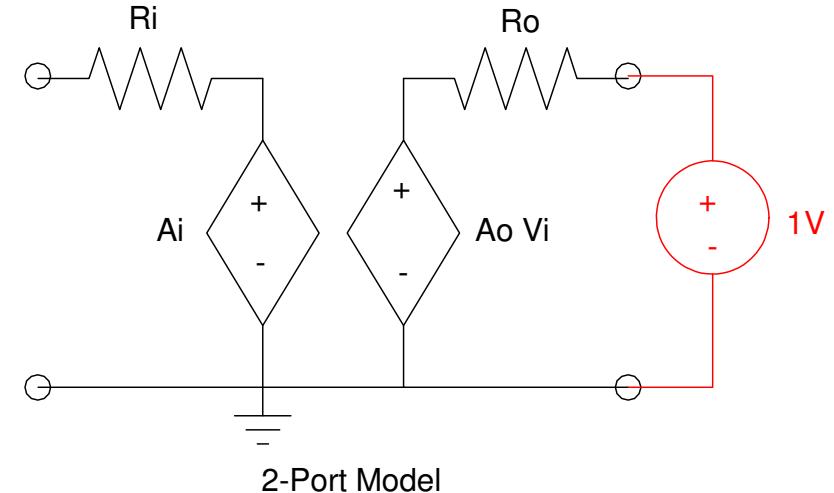

2-Port Model



Ao: Set $V_{in} = 0V$, measure the voltage at V_{out} . $A_o = V_{out}$

- $A_o = 0.75$

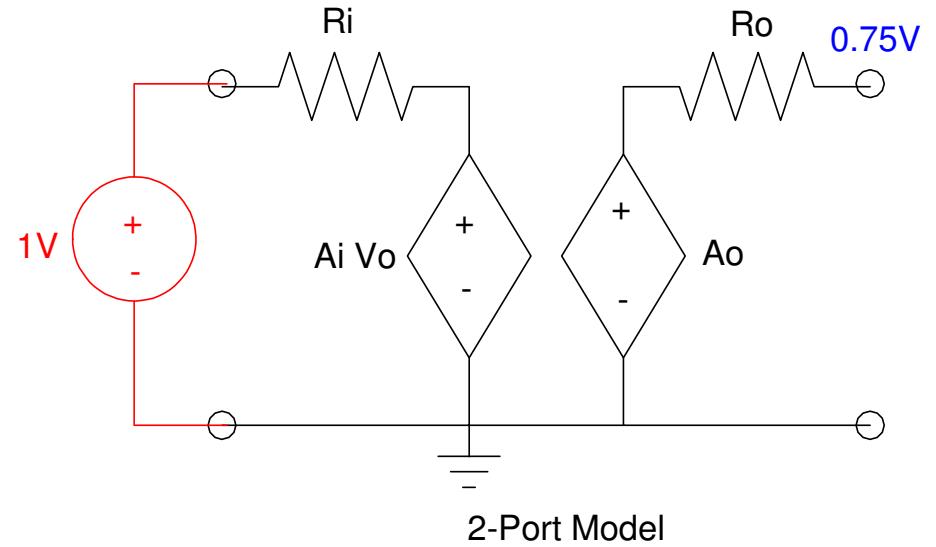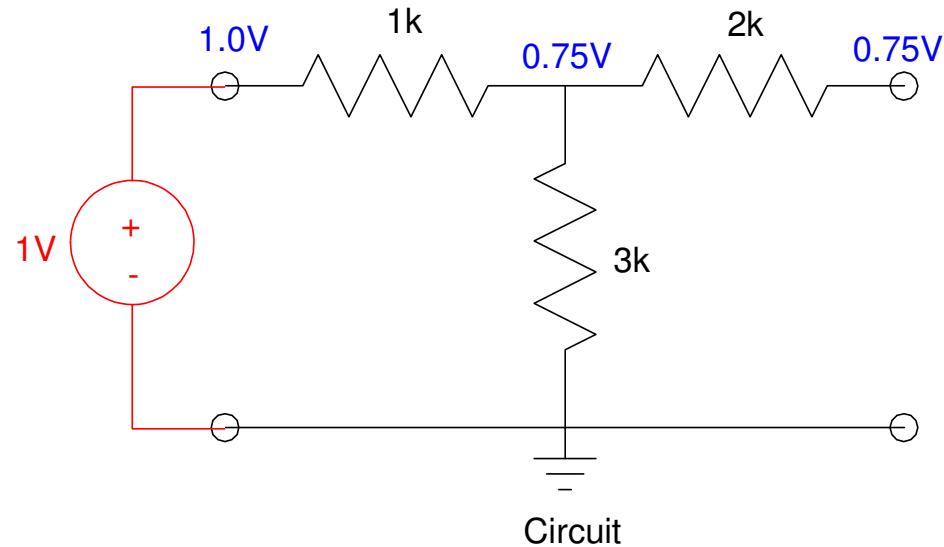



Rin: Set Vout = 0V, measure the resistance at Vin.

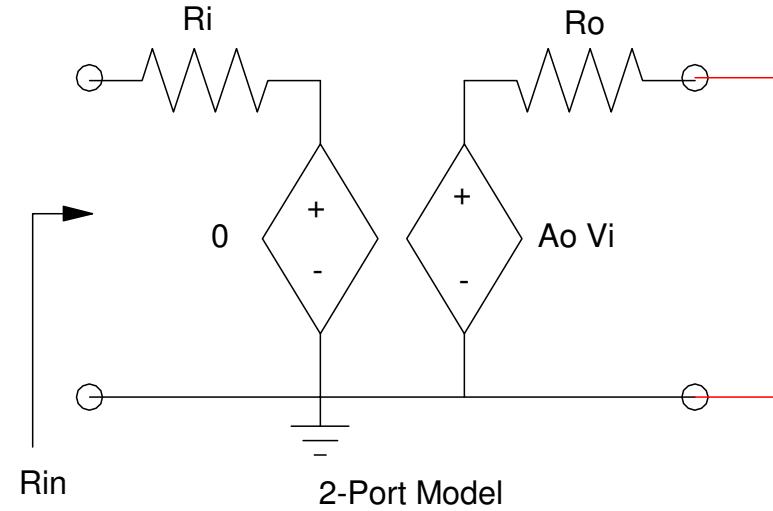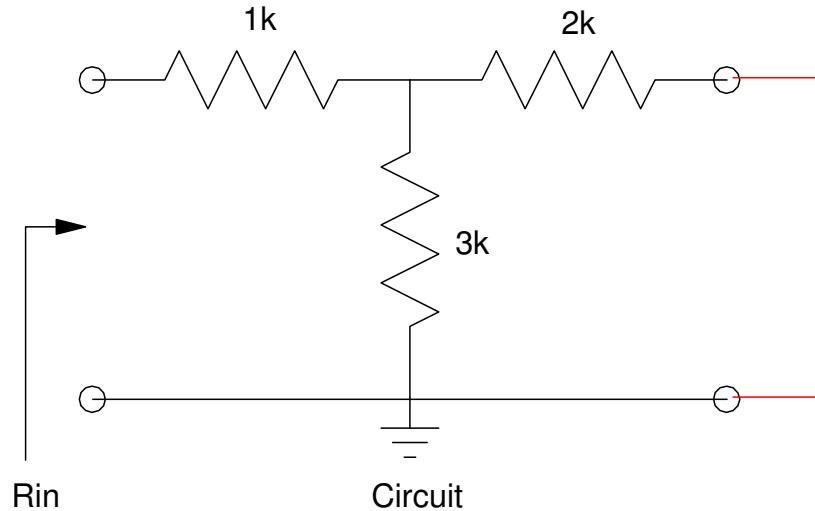- $R_{in} = 1k + 3k \parallel 2k = 2.2k\Omega$




R_{out}: Set V_{in} = 0V, measure the resistance at V_{out}

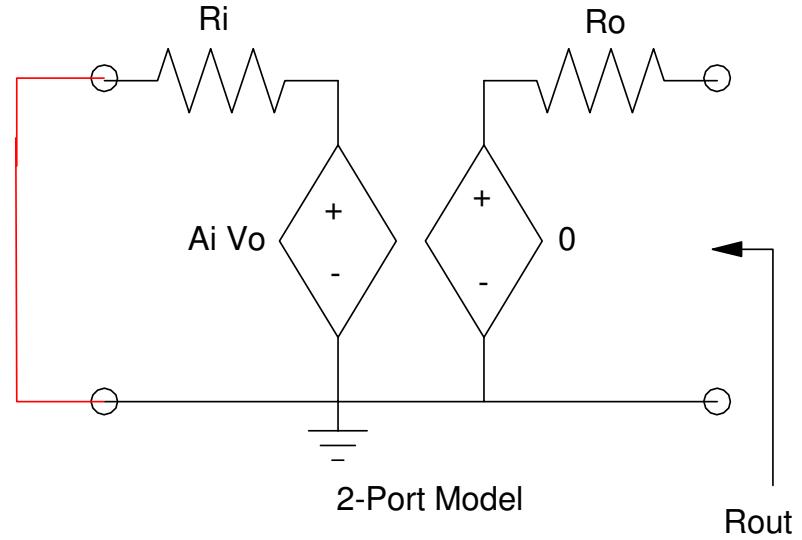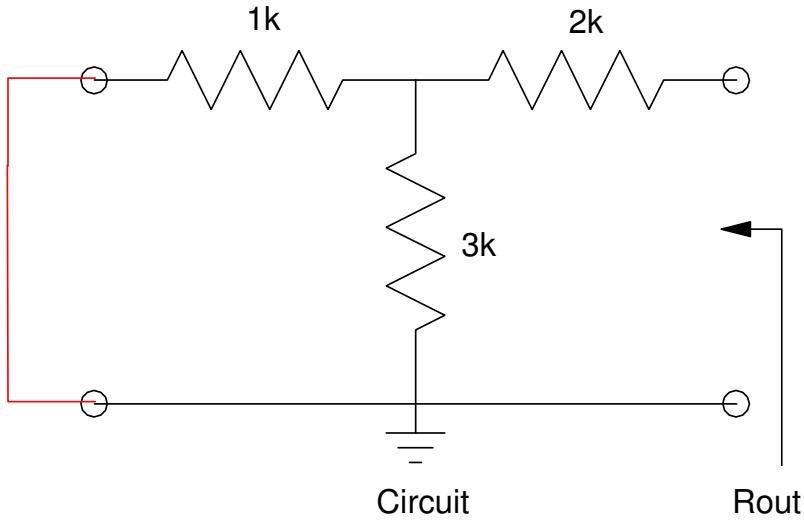- $R_{out} = 2k + 1k \parallel 3k = 2750\Omega$




So, the 2-port model is:

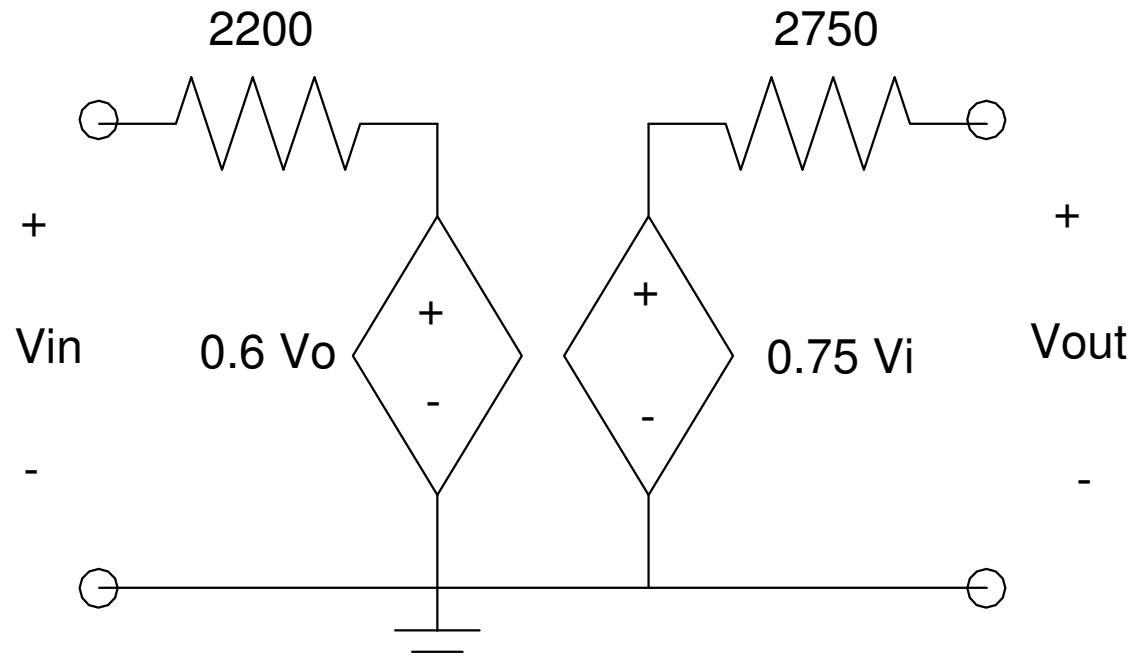


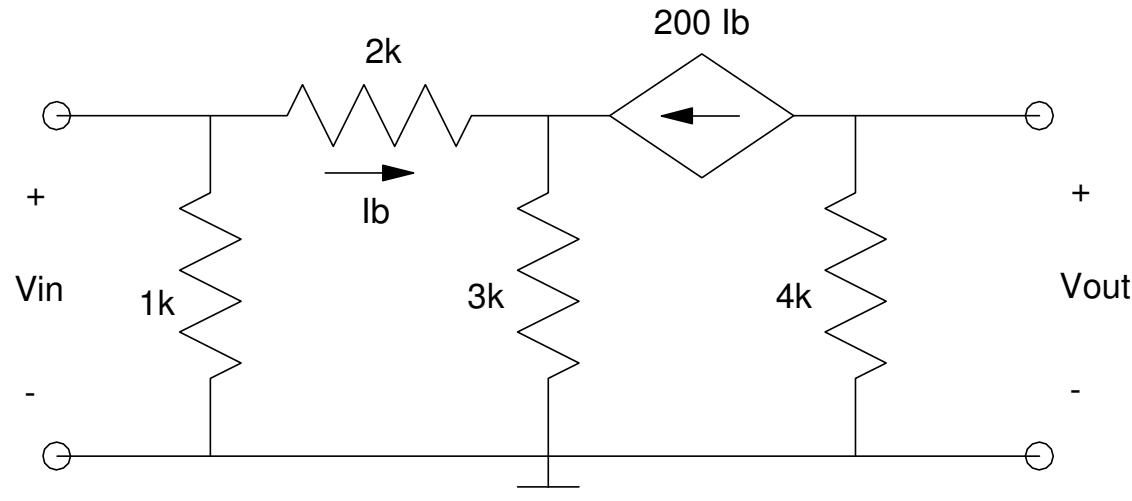Example 2: When R isn't obvious

- Apply a test voltage (1V typical)
- Compute the current draw
- $R = 1V / I$



Ai: Set $V_{out} = 1V$, measure V_{in}

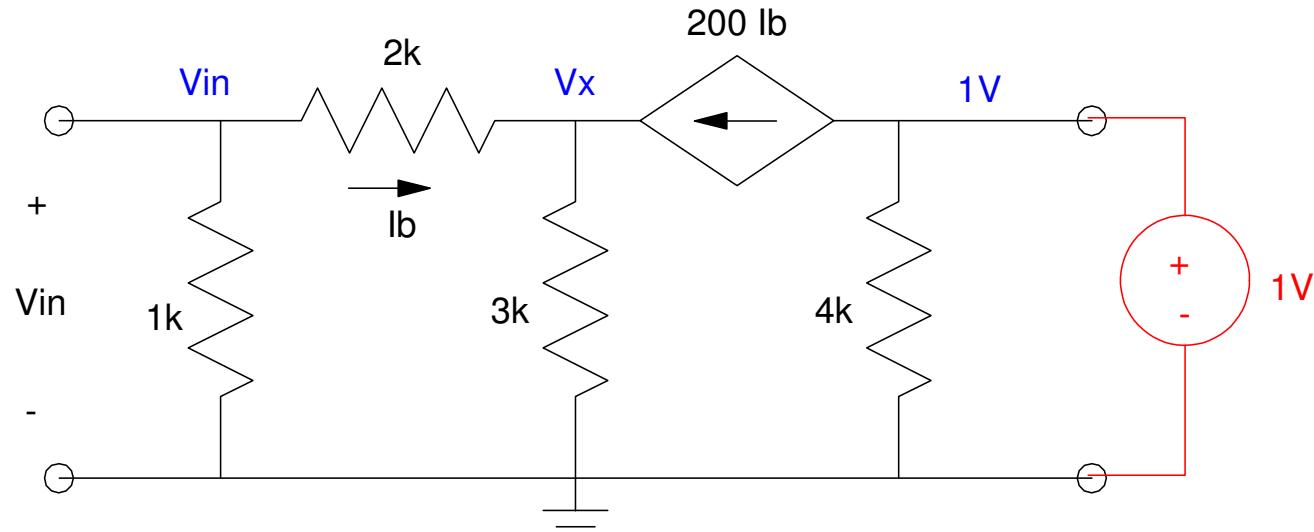

Compute V_x using voltage nodes:

$$\left(\frac{V_x}{1k+2k}\right) + \left(\frac{V_x}{3k}\right) - 200\left(\frac{0-V_x}{3k}\right) = 0$$

$$V_x = 0 \quad \Rightarrow \quad \mathbf{Ai} = \mathbf{0}$$

Ao: Set $V_{in} = 1V$, measure the voltage at V_o


Find V_x using voltage nodes:

$$\left(\frac{V_x - 1}{2k}\right) + \left(\frac{V_x}{3k}\right) - 200\left(\frac{1 - V_x}{2k}\right) = 0$$

$$V_x = 0.9951V$$


$$I_b = \left(\frac{1 - V_x}{2k}\right) = 2.469\mu A$$

$$V_o = -(200I_b)4k = 1.9753V$$

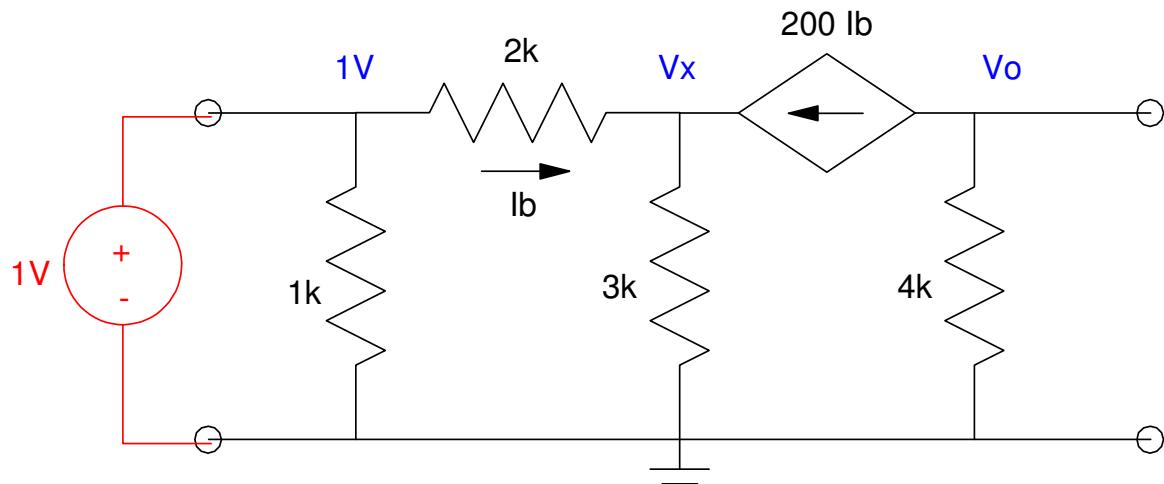

Ao = 1.9753

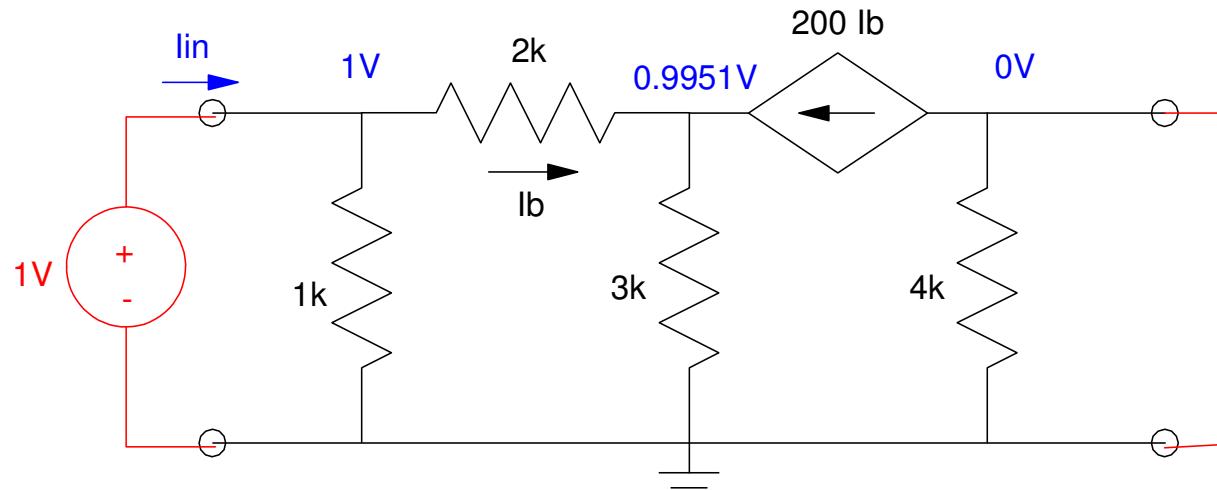Rin: Set $V_o = 0V$, measure the resistance at the input.



From the previous analysis, $V_x = 0.9951V$,

$$I_{in} = \left(\frac{1V - 0.9951V}{2k} \right) + \left(\frac{1V}{1k} \right) = 1.0017mA$$

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{1V}{1.0017mA} = 998\Omega$$

R_{out}: Set V_{in} = 0V, measure the resistance at V_{out}.

This isn't obvious, so add a 1V source at the output and compute the resulting current

Solve for V_x:

$$\left(\frac{V_x - 0}{2k}\right) + \left(\frac{V_x}{3k}\right) - 200\left(\frac{0 - V_x}{2k}\right) = 0$$

$$V_x = 0$$

$$I_{out} = 0 + \left(\frac{1V}{4k}\right) = 250\mu A$$

so

$$R_{out} = \frac{V_{out}}{I_{out}} = \frac{1V}{250\mu A} = 4k\Omega$$

