

Circuit Analysis with Forcing Functions

Background

Last lecture covered circuit analysis with LaPlace transforms when there are

- Initial conditions, and
- No input.

Today, let's look at circuit analysis when you have

- Zero initial conditions, and
- A non-zero input.

This is equivalent to having an in put which is zero for $t < 0$

$$v_{in}(t) = f(t)u(t)$$


Since the input is zero for $t < 0$, at $t = 0$, the states should all be zero.

Again, let's use state-space. It's also easier to explain through examples.

Example 1: 2-Stage RC Filter.

Find $y(t)$ assuming a step input:

$$v_0(t) = u(t)$$

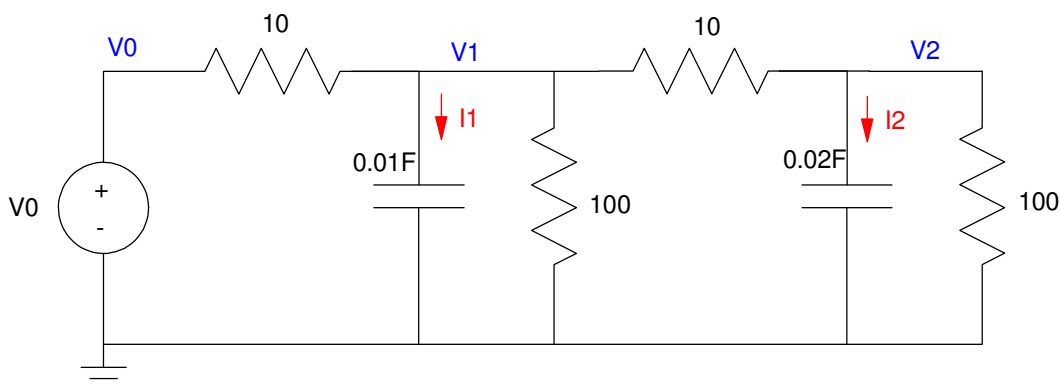

2-Stage RC Filter with an input, V_0

The procedure is almost identical to the previous solution, only now with

- Initial conditions are zero, and
- There is an input, V_0

Step 1: Define the system states.

This is the voltage across the capacitors and the current through inductors. This defines the energy in the system.

$$X = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Step 2: Define the change in energy in terms of the input and the system states

$$I_1 = 0.01 \cdot sV_1 = \left(\frac{V_0 - V_1}{10} \right) + \left(\frac{V_2 - V_1}{10} \right) + \left(\frac{0 - V_1}{100} \right)$$

$$I_2 = 0.02 \cdot sV_2 = \left(\frac{0 - V_2}{100} \right) + \left(\frac{V_1 - V_2}{10} \right)$$

Group terms:

$$sV_1 = -21V_1 + 10V_2 + 10V_0$$

$$sV_2 = 5V_1 - 5.5V_2$$

Step 3: Place in matrix (state-space) form

$$s \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -21 & 10 \\ 5 & -5.5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \begin{bmatrix} 10 \\ 0 \end{bmatrix} V_0$$

$$Y = V_2 = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + [0]$$

Solve for the transfer function from V0 to Y in Matlanb:

$$A = [-21, 10 ; 5, -5.5]$$

$$\begin{array}{cc} -21.0000 & 10.0000 \\ 5.0000 & -5.5000 \end{array}$$

$$B = [10 ; 0]$$

$$\begin{array}{c} 10 \\ 0 \end{array}$$

$$C = [0, 1];$$

$$D = 0;$$

$$G = ss(A, B, C, D);$$

$$G(s) = \frac{50}{(s+23.74)(s+2.759)}$$

At this point you can solve for $Y(s)$:


$$Y(s) = G(s) \cdot V_0(s)$$

If the input is a unit step:

$$Y(s) = \left(\frac{10(s+26)}{(s+2.759)(s+23.74)} \right) \left(\frac{1}{s} \right)$$

In Matlab, you can solve using the *step* function
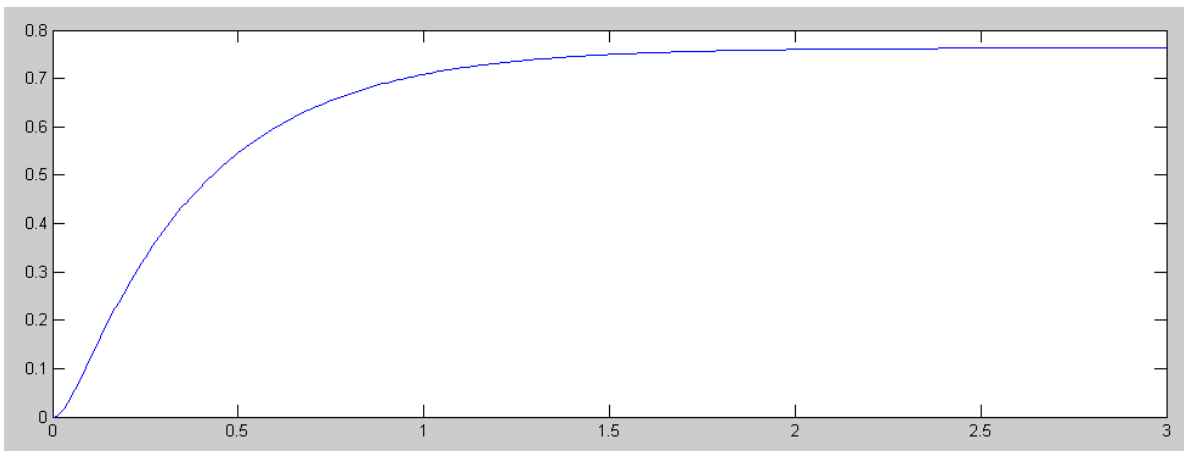
```
>> t = [0:0.01:3]';
>> y = step(G, t);
>> plot(t, y);
```



$y(t)$ for $v_0(t) = u(t)$. Note that $y(t) = 0$ for $t < 0$

You can also find the output for other inputs, but Matlab doesn't have those functions built in (like the step function). If you have a different input, you need to find $Y(s)$ and use the *impulse* command.

Example: Find the response for

$$v_0(t) = \sin(4t)u(t)$$

Solution: Find the LaPlace transfer for $v_0(t)$. From http://tutorial.math.lamar.edu/pdf/Laplace_Table.pdf

$$\sin(at) \leftrightarrow \left(\frac{a}{s^2+a^2} \right)$$

$$\cos(at) \leftrightarrow \left(\frac{s}{s^2+a^2} \right)$$

This gives

$$V_0(s) = \left(\frac{4}{s^2+16} \right)$$

$Y(s)$ is then

$$Y(s) = G(s) \cdot V_0(s)$$

$$Y(s) = \left(\frac{10(s+26)}{(s+2.759)(s+23.74)} \right) \left(\frac{4}{s^2+16} \right)$$

Find $Y(s)$

```
Vo = tf(4, [1,0,16])
```

$$V_0(s) = \frac{4}{s^2 + 16}$$


```
Y = G * Vo;
```

```
zpk(Y)
```

$$Y(s) = \frac{200}{(s+23.74)(s+2.759)(s^2 + 16)}$$

```
t = [0:0.01:5]';
y = impulse(Y,t);
```

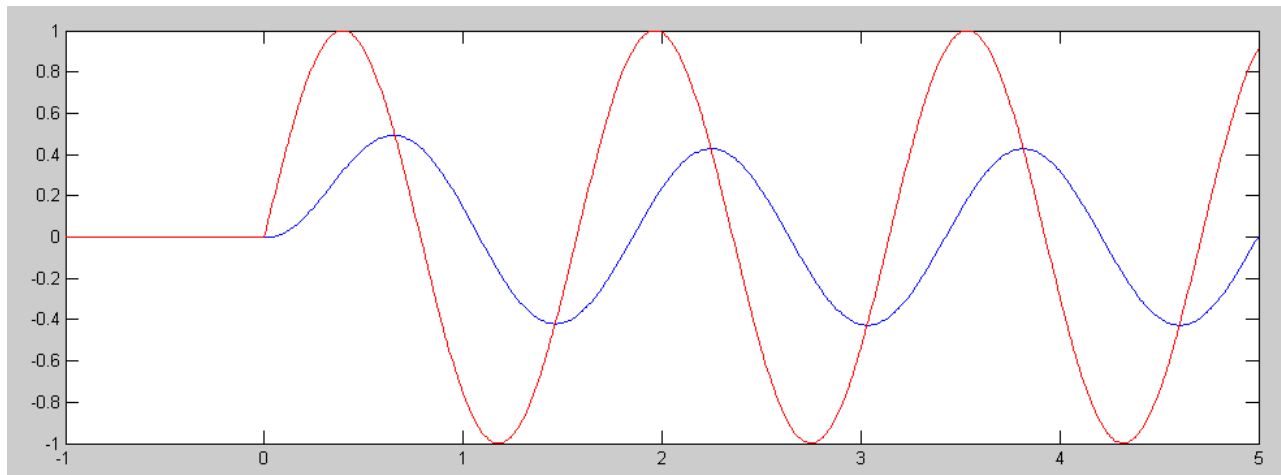
```
t1 = [-1:0.01:5]';
Vo = sin(4*t1) .* (t1>0);
plot(t,y,'b',t1,Vo,'r')
```



$y(t)$ (blue) and $v_o(t)$ (red) for a 4 rad/sec sine wave input.
Note that $y(t) = 0$ for $t < 0$.

Example 2: 5-stage RC filter.

Find $V_5(t)$ assuming $v_0(t) = u(t)$

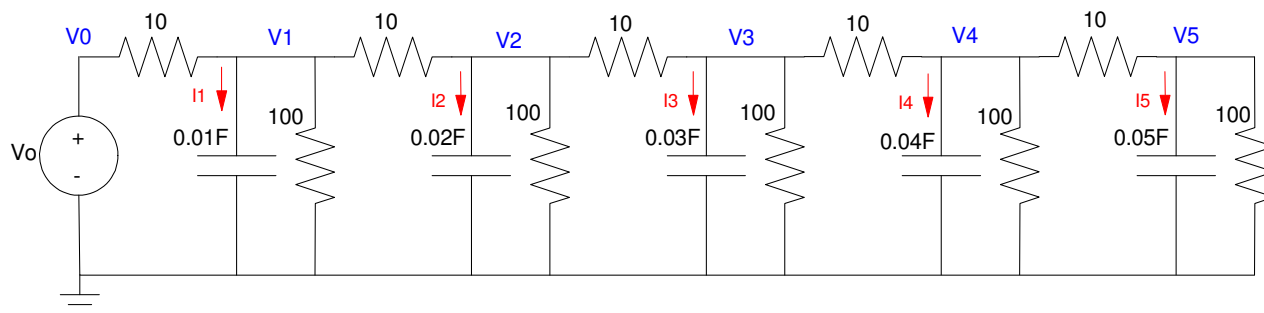

Again, this follows the previous analysis fairly closely - except that now you have

- No initial conditions, and
- Input V_0 .

Step 1: Define the state variables. The energy in the system is defined by

$$X = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix}$$

Step 2: Define the change in the state variables in terms of the other states

$$I_1 = 0.01sV_1 = \left(\frac{V_0 - V_1}{10} \right) + \left(\frac{0 - V_1}{100} \right) + \left(\frac{V_2 - V_1}{10} \right)$$

$$I_2 = 0.02sV_2 = \left(\frac{V_1 - V_2}{10} \right) + \left(\frac{0 - V_2}{100} \right) + \left(\frac{V_3 - V_2}{10} \right)$$

$$I_3 = 0.03sV_3 = \left(\frac{V_2 - V_3}{10} \right) + \left(\frac{0 - V_3}{100} \right) + \left(\frac{V_4 - V_3}{10} \right)$$

$$I_4 = 0.04sV_4 = \left(\frac{V_3 - V_4}{10} \right) + \left(\frac{0 - V_4}{100} \right) + \left(\frac{V_5 - V_4}{10} \right)$$

$$I_5 = 0.05sV_5 = \left(\frac{V_4 - V_5}{10} \right) + \left(\frac{0 - V_5}{100} \right)$$

Group terms and solve for the derivative

$$sV_1 = -21V_1 + 10V_2 + 10V_0$$

$$sV_2 = 5V_1 - 10.5V_2 + 5V_3$$

$$sV_3 = 3.33V_2 - 7V_3 + 3.33V_4$$

$$sV_4 = 2.5V_3 - 5.25V_4 + 2.5V_5$$

$$sV_5 = 2V_4 - 2.2V_5$$

Place in matrix form

$$s \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} = \begin{bmatrix} -21 & 10 & 0 & 0 & 0 \\ 5 & -10.5 & 5 & 0 & 0 \\ 0 & 3.33 & -7 & 3.33 & 0 \\ 0 & 0 & 2.5 & -5.25 & 2.5 \\ 0 & 0 & 0 & 2 & -2.2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} + \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} V_0$$

$$Y = V_5 = \begin{bmatrix} 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} + [0]$$

Step 3: Find the transfer function from V0 to Y:

$$A = [-21, 10, 0, 0, 0 ; 5, -10.5, 5, 0, 0 ; 0, 3.333, -7, 3.333, 0 ; 0, 0, 2.5, -5.25, 2.5 ; 0, 0, 0, 2, -2.2]$$

$$\begin{bmatrix} -21.0000 & 10.0000 & 0 & 0 & 0 \\ 5.0000 & -10.5000 & 5.0000 & 0 & 0 \\ 0 & 3.3330 & -7.0000 & 3.3330 & 0 \\ 0 & 0 & 2.5000 & -5.2500 & 2.5000 \\ 0 & 0 & 0 & 2.0000 & -2.2000 \end{bmatrix}$$

$$B = [10; 0; 0; 0; 0]$$

$$\begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$C = [0, 0, 0, 0, 1];$$

$$D = 0;$$


$$G = ss(A, B, C, D);$$

zpk(G)

$$G(s) = \frac{833.25}{(s+24.76)(s+11.31)(s+6.601)(s+2.822)(s+0.4601)}$$

Step 4: Find $y(t)$ for $V_o(t) = u(t)$. This is the *step* command in Matlab:
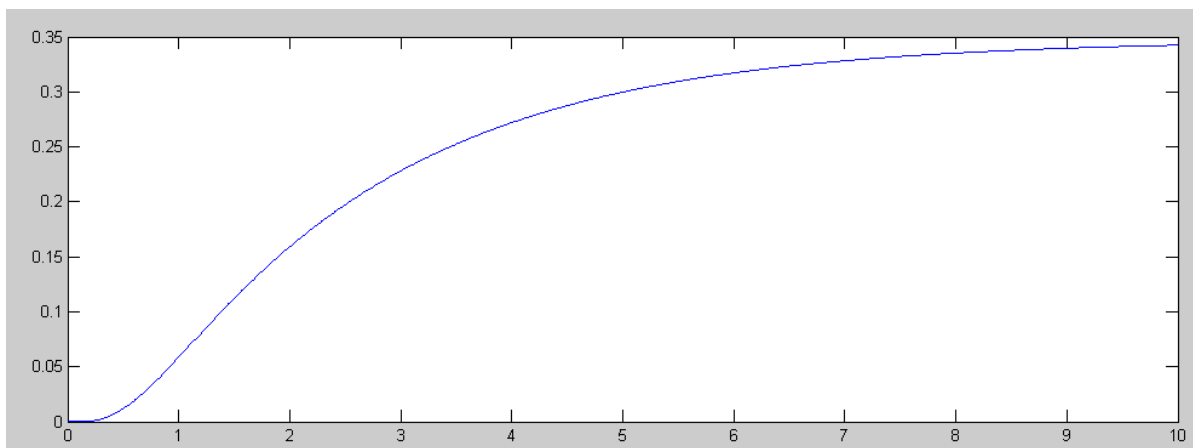
```
t = [0:0.01:10]';
y = step(G,t);
plot(t,y);
```



Response for a step input: $v_o(t) = u(t)$

Repeat for

$$v_o(t) = \cos(t)u(t)$$

Take the LaPlace transform of v_o :

$$V_o(s) = \left(\frac{s}{s^2+1} \right)$$

$Y(s)$ is then

$$Y(s) = G(s) \cdot V_o(s)$$


```
>> Vo = tf([1,0],[1,0,1])
```

$$V_o(s) = \frac{s}{s^2 + 1}$$

```
>> Y = G * Vo;
>> zpk(Y)
```

$$Y(s) = \frac{833.25 s}{(s+24.76)(s+11.31)(s+6.601)(s+2.822)(s+0.4601)(s^2 + 1)}$$

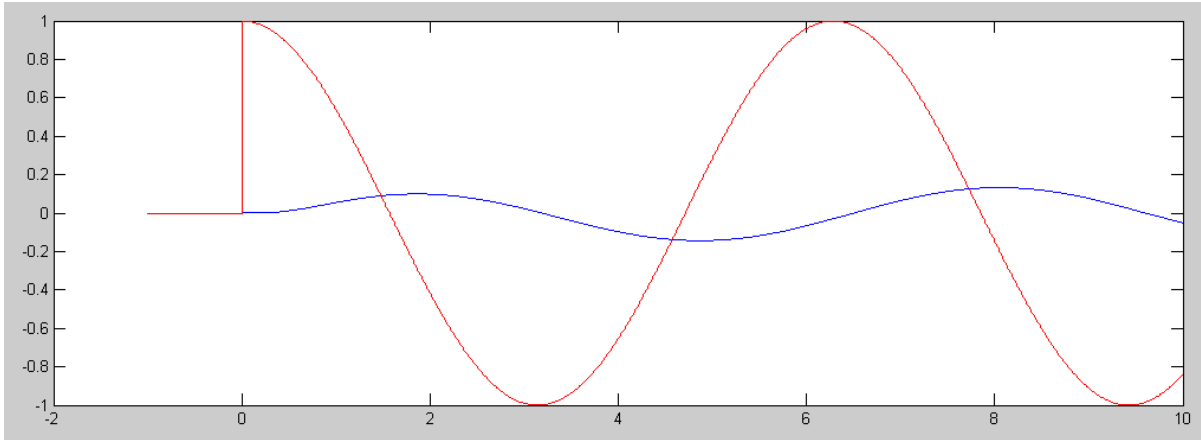
```
y = impulse(Y, t);  
t1 = [-1:0.01:10]';  
vo = cos(t1) .* (t1>0);  
plot(t,y,'b',t1,vo,'r')
```



$y(t)$ and $v_o(t)$ for $v_o(t) = \cos(t) u(t)$

Example 3: RLC Circuit

Find $V_4(t)$ assuming $v_0(t) = u(t)$

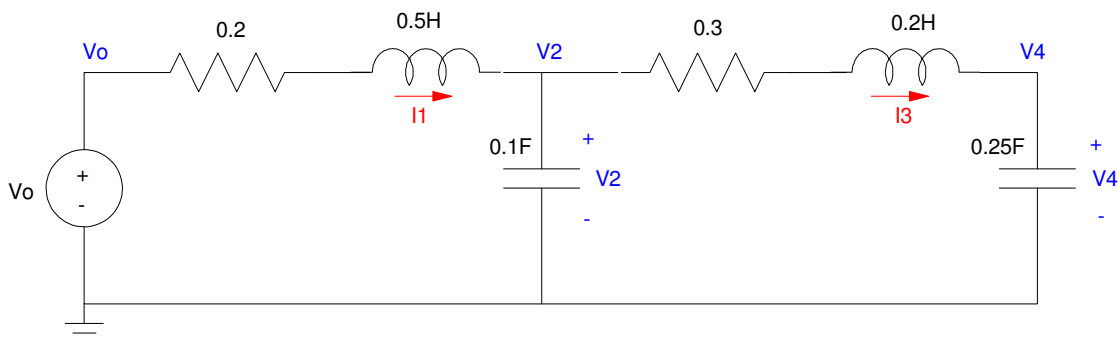

Solution: Follow the same procedure as before but with

- No initial conditions, and
- An input, V_0

Step 1: Define the state variables. These define the energy in the system

$$X = \begin{bmatrix} I_1 \\ V_2 \\ I_3 \\ V_4 \end{bmatrix}$$

Step 2: Define the change in the states.

$$v_1 = 0.5sI_1 = (V_0 - 0.2I_1) - V_2$$

$$i_2 = 0.1sV_2 = I_1 - I_3$$

$$v_3 = 0.2sI_3 = V_2 - 0.3I_3 - V_4$$

$$i_4 = 0.25sV_4 = I_3$$

Step 3: Rewrite these equations as

$$sI_1 = -0.4I_1 - 2V_2 + 2V_0$$

$$sV_2 = 10I_1 - 10I_3$$

$$sI_3 = 5V_2 - 1.5I_3 - 5V_4$$

$$sV_4 = 4I_3$$

Place in matrix form

$$s \begin{bmatrix} I_1 \\ V_2 \\ I_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} -0.4 & -2 & 0 & 0 \\ 10 & 0 & -10 & 0 \\ 0 & 5 & -1.5 & -5 \\ 0 & 0 & 4 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \\ I_3 \\ V_4 \end{bmatrix} + \begin{bmatrix} 2 \\ 0 \\ 0 \\ 0 \end{bmatrix} V_0$$

$$Y = V_4 = \begin{bmatrix} 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \\ I_3 \\ V_4 \end{bmatrix} + [0]$$

Solve in Matlab

$$A = [-0.4, -2, 0, 0 ; 10, 0, -10, 0 ; 0, 5, -1.5, -5 ; 0, 0, 4, 0]$$

$$\begin{array}{cccc} -0.4000 & -2.0000 & 0 & 0 \\ 10.0000 & 0 & -10.0000 & 0 \\ 0 & 5.0000 & -1.5000 & -5.0000 \\ 0 & 0 & 4.0000 & 0 \end{array}$$

$$B = [2 ; 0 ; 0 ; 0]$$

$$\begin{array}{c} 2 \\ 0 \\ 0 \\ 0 \end{array}$$

$$\gg C = [0, 0, 0, 1];$$

$$\gg D = 0;$$

$$\gg G = ss(A, B, C, D);$$

$$\gg zpk(G)$$


$$G(s) = \frac{400}{(s^2 + 0.6102s + 4.7) (s^2 + 1.29s + 85.11)}$$

Find the step response ($v_o(t) = u(t)$)

$$t = [0:0.01:10]';$$

$$y = \text{step}(G, t);$$

$$\text{plot}(t, y)$$

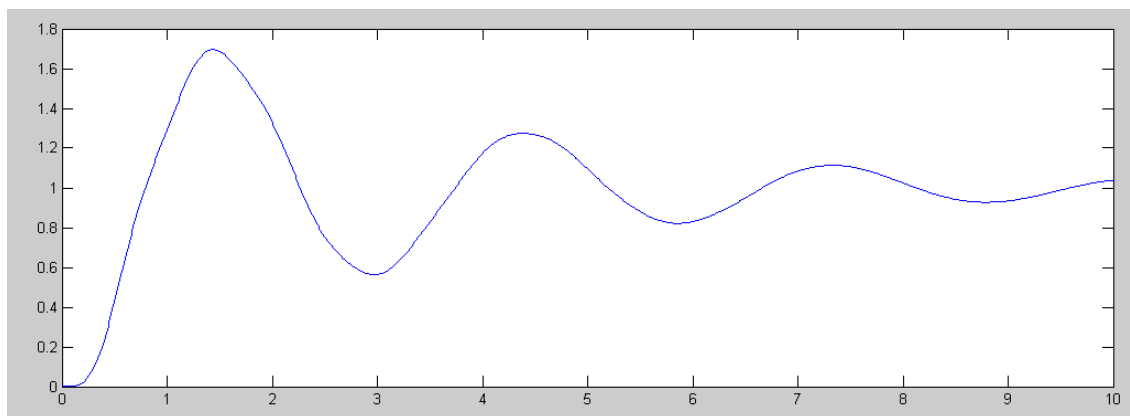Step Response: $v_o(t) = u(t)$

Repeat for


$$v_0(t) = 3 \cos(4t)$$

$$V_0(s) = \left(\frac{3s}{s^2+16} \right)$$

```
>> V0 = tf([3,0],[1,0,4])
```

$$V_0 = \frac{3s}{s^2 + 4}$$

```
>> Y = G * V0;
>> y = impulse(Y,t);
>> t1 = [-2:0.01:10]';
>> vo = 3 * cos(2*t1) .* (t1>0);
>> plot(t,y,'b',t1,vo,'r')
```

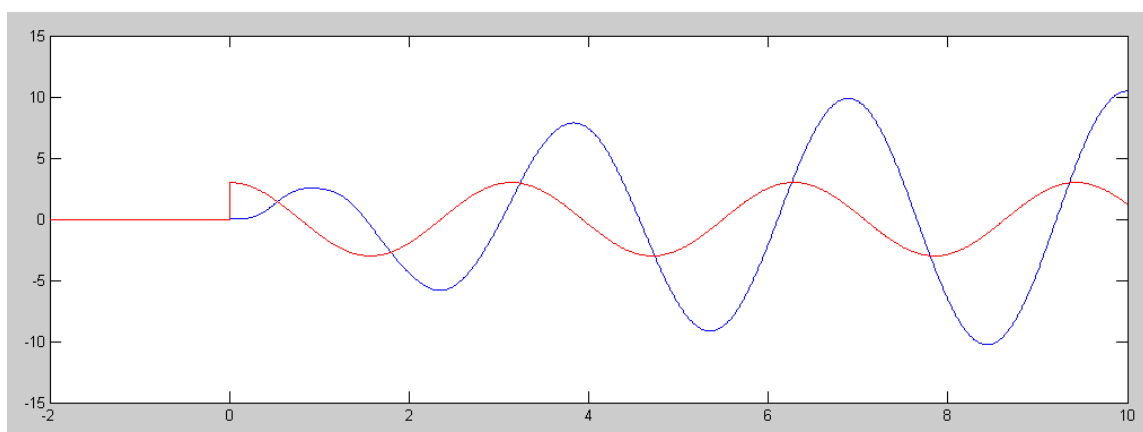
 $y(t)$ (blue) and $v_o(t)$ (red) for $v_o(t) = 3 \cos(2t) u(t)$