


# ECE 111 - Homework #10

ECE 311 Circuits II - Heat Equation

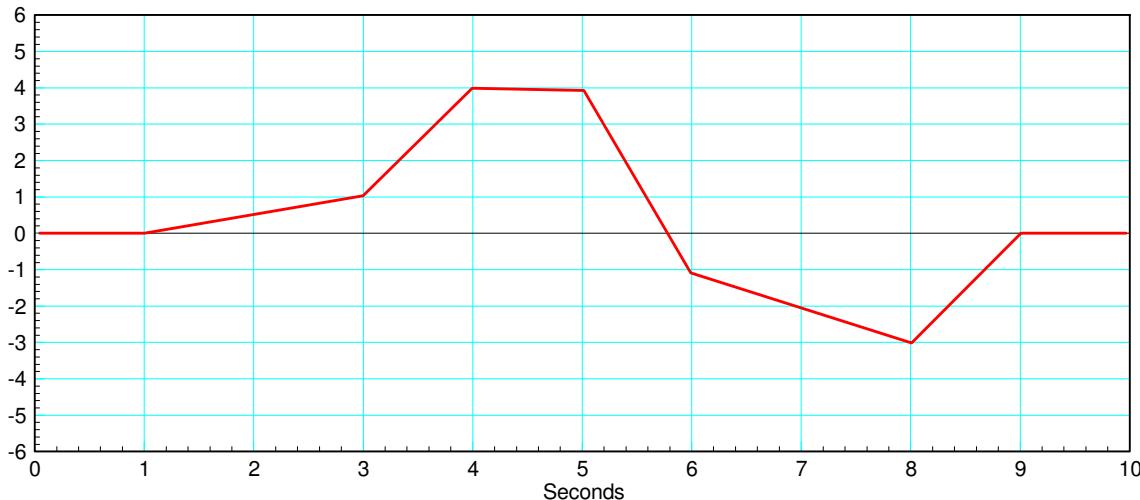
- 1) Assume the current flowing through a one Farad capacitor is shown below. Sketch the voltage. Assume  $V(0) = 0$ . The voltage is the integral of the current (capacitors are integrators)

$$V = \frac{1}{C} \int I \cdot dt$$

Assume the initial voltage on the capacitor is -5V.



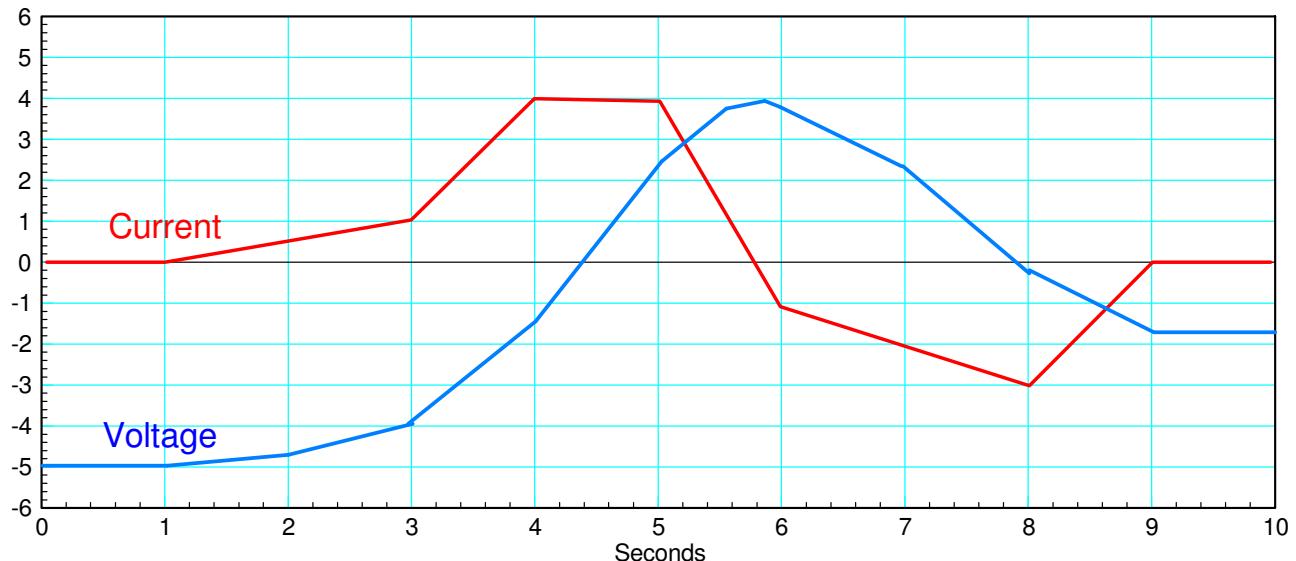
Capacitor are integrators: the voltage is the integral of the current (the area under the curve)



### 1-Stage RC filter:

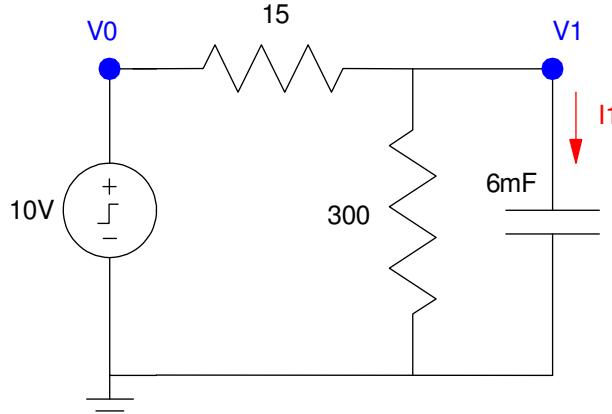2) Write the differential equation that describe this circuit. Note:

$$I_1 = C \frac{dV_1}{dt} = \sum(\text{current to node } V_1)$$



$$I_1 = 0.006 \cdot \frac{dV_1}{dt} = \left( \frac{V_0 - V_1}{15} \right) - \left( \frac{V_1}{300} \right)$$

$$\frac{dV_1}{dt} = 11.11V_0 - 11.6676V_1$$

3) Find and plot  $V_1(t)$  for one second using Matlab.

Matlab Code


```
V1 = 0;
t = 0;
dt = 0.01;
y = [];
V0 = 10;

while(t < 1)
    dV1 = 11.11*V0 - 11.667*V1;



    V1 = V1 + dV1*dt;
    t = t + dt;

    y = [y ; V1];
end

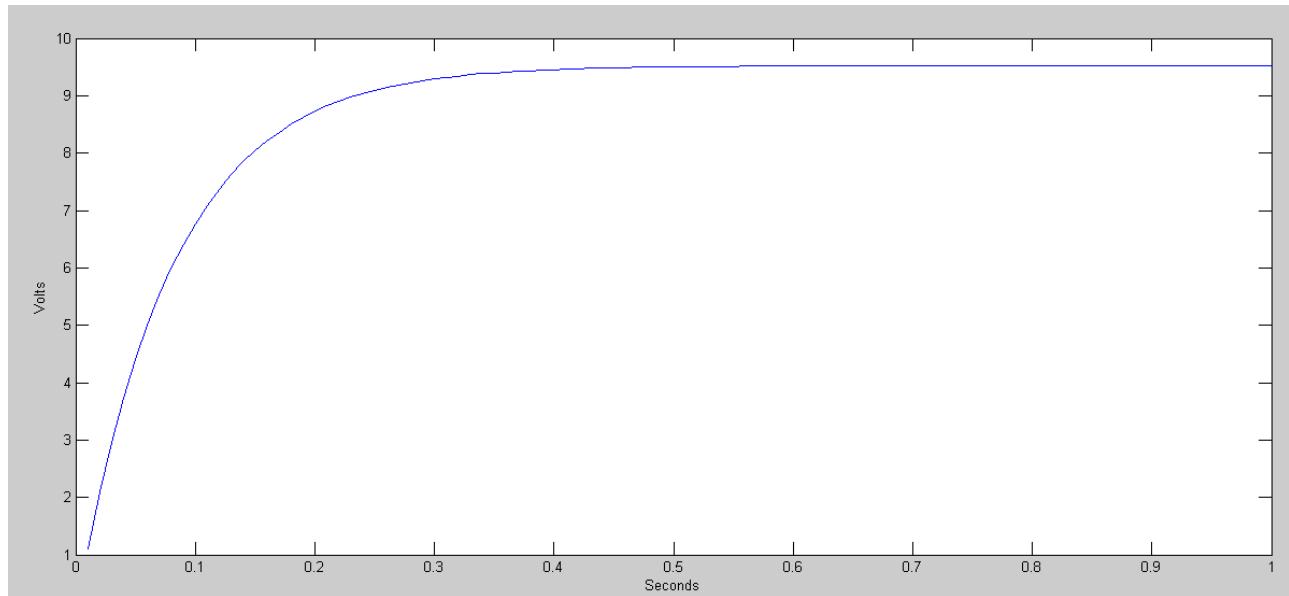t = [1:length(y)]' * dt;
plot(t,y);
xlabel('Seconds');
ylabel('Volts');
```



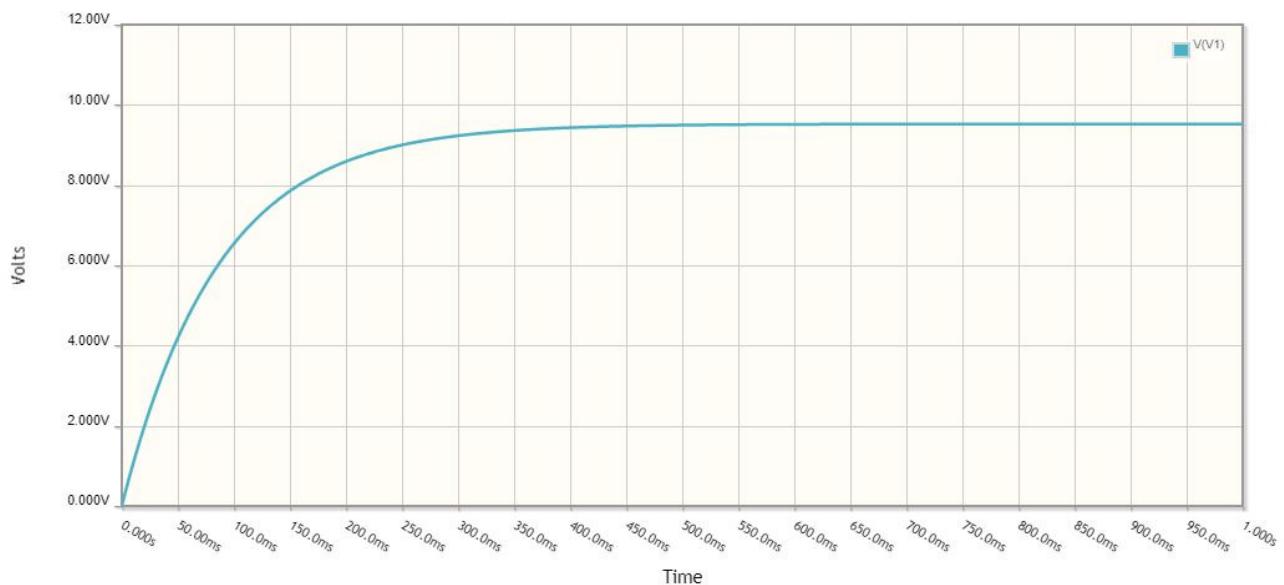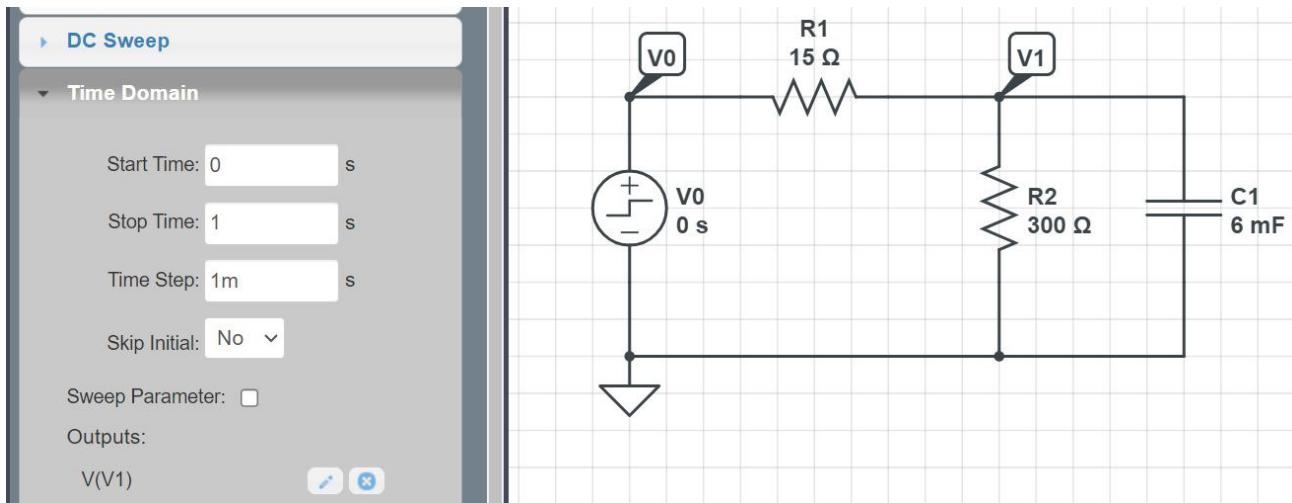4) Find and plot  $V_1(t)$  for one seconds using CircuitLab




Note: This is the same result we got with Matlab

## 10-Stage RC Filter

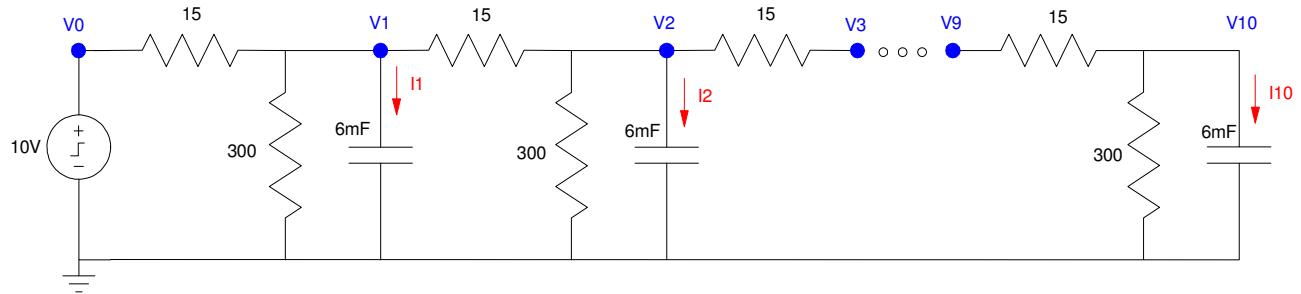5) Write the dynamics for this system as a set of ten coupled differential equations:

$$I_1 = C \frac{dV_1}{dt} = \sum(\text{current to node } V_1)$$



At node V1:

$$C \cdot \frac{dV_1}{dt} = \left( \frac{V_0 - V_1}{15} \right) + \left( \frac{V_2 - V_1}{15} \right) - \left( \frac{V_1}{300} \right)$$

Simplifying

$$\frac{dV_1}{dt} = \left( \frac{1}{15C} \right) V_0 - \left( \frac{1}{15C} + \frac{1}{15C} + \frac{1}{300C} \right) V_1 + \left( \frac{1}{15C} \right) V_2$$

$$\frac{dV_1}{dt} = 11.111V_0 - 22.778V_1 + 11.111V_2$$

The same pattern holds for nodes 2..9

$$\frac{dV_2}{dt} = 11.111V_1 - 22.778V_2 + 11.111V_3$$

$\vdots$

$$\frac{dV_9}{dt} = 11.111V_8 - 22.778V_9 + 11.111V_{10}$$

The last node is a little different since there is only a single 15 ohm resistor connected


$$\frac{dV_{10}}{dt} = \left( \frac{1}{15C} \right) V_9 - \left( \frac{1}{15C} + \frac{1}{300C} \right) V_{10}$$

$$\frac{dV_{10}}{dt} = 11.111V_9 - 11.667V_{10}$$


## Forced Response for a 10-Node RC Filter (heat.m):

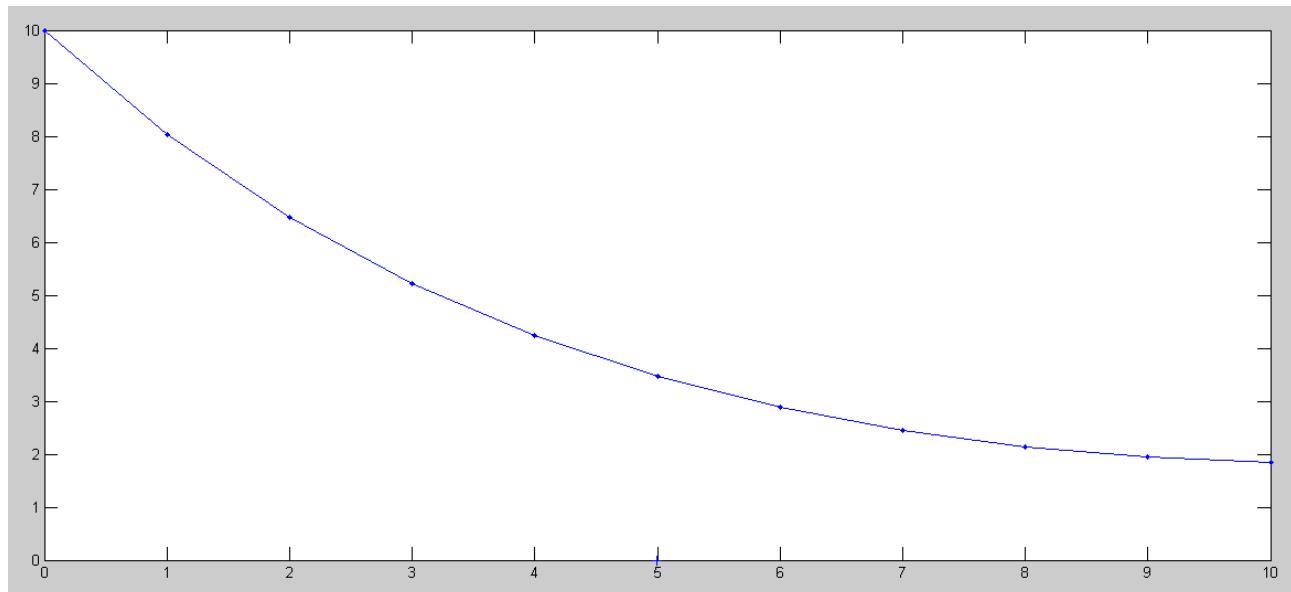6) Using Matlab, solve these ten differential equations for  $0 < t < 5$  s assuming

- The initial voltages are zero, and
- $V_0 = 10V$ .



Voltages at  $t = 5$  seconds

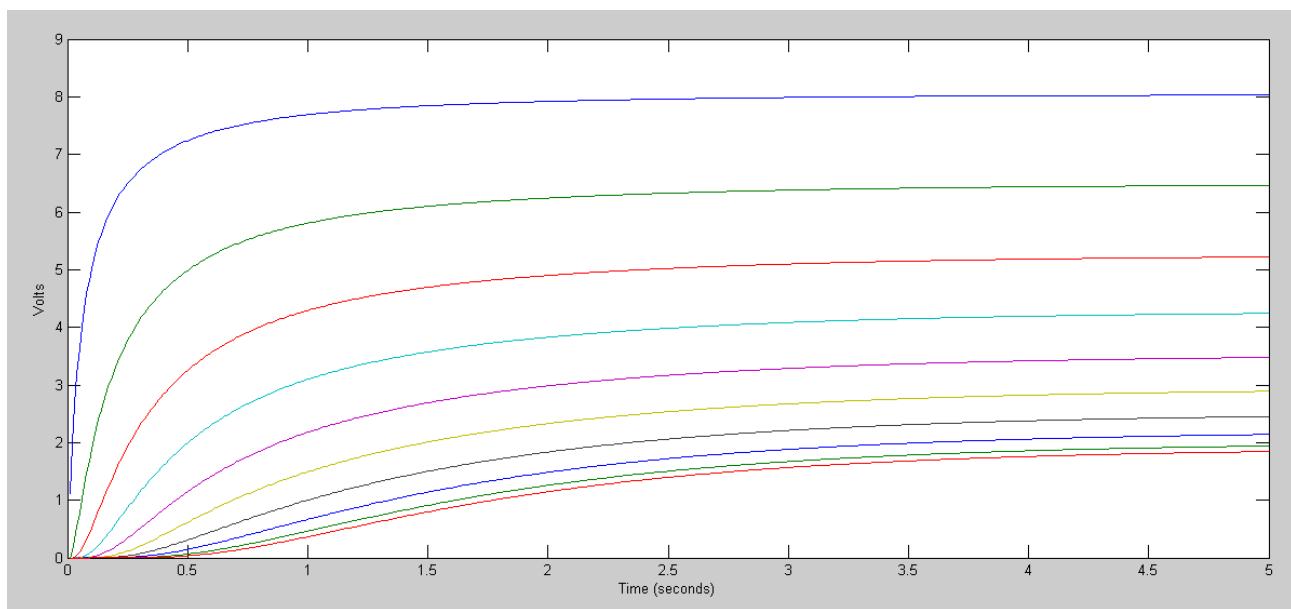

Voltages vs. Time

**Code:**

```
% 10-stage RC Filter

V = zeros(10,1);

V = zeros(10,1);

dV = zeros(10,1);
V0 = 10;
dt = 0.01;
t = 0;
i = 0;

y = [];

while(t < 4.99)

dV(1) = 11.111*V0 - 22.778*V(1) + 11.111*V(2);
dV(2) = 11.111*V(1) - 22.778*V(2) + 11.111*V(3);
dV(3) = 11.111*V(2) - 22.778*V(3) + 11.111*V(4);
dV(4) = 11.111*V(3) - 22.778*V(4) + 11.111*V(5);
dV(5) = 11.111*V(4) - 22.778*V(5) + 11.111*V(6);
dV(6) = 11.111*V(5) - 22.778*V(6) + 11.111*V(7);
dV(7) = 11.111*V(6) - 22.778*V(7) + 11.111*V(8);
dV(8) = 11.111*V(7) - 22.778*V(8) + 11.111*V(9);
dV(9) = 11.111*V(8) - 22.778*V(9) + 11.111*V(10);
dV(10) = 11.111*V(9) - 11.667*V(10);

V = V + dV*dt;
t = t + dt;

y = [y ; V'];

plot([0:10], [V0;V], '.-', t, 0, 'b+');
xlim([0,10]);
ylim([0,10]);
pause(0.01);



end

pause(5);

t = [1:length(y)]' * dt;
plot(t,y);
xlabel('Time (seconds)');
ylabel('Volts');
```

7) Using CircuitLab, find the response of this circuit to a 10V step input. *note: It's OK if you only build this circuit to 3 nodes...*

Running with six nodes:

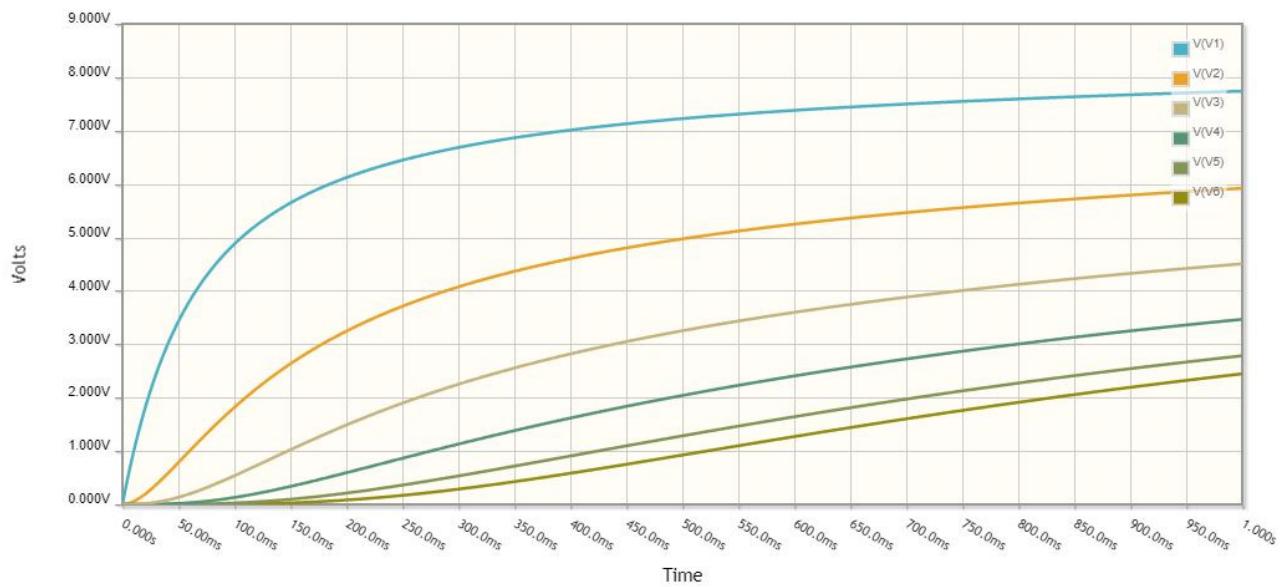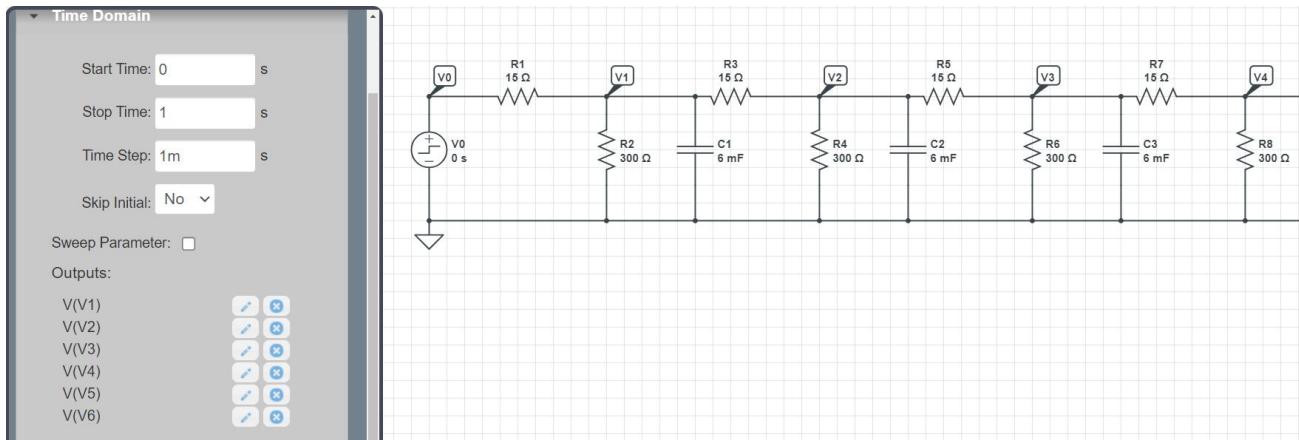

The response is essentially what we got with Matlab (only with six nodes instead of 10)

## Natural Response: Eigenvectors and Eigenvalues

8) Assume V0 = 0V. Determine the initial conditions of V1..V10 so that

- The maximum voltage is 10V and
- The voltages go to zero as slow as possible
- The voltages go to zero as fast as possible.

Simulate the response for these initial conditions in Matlab.

This is an eigenvalue / eigenvector probem. Expressing the dynamics in matrix form:

```
>> A = zeros(10,10);
>> for i=1:9
A(i,i) = -22.778;
A(i+1,i) = 11.111;
A(i,i+1) = 11.111;
end
>> A(10,10) = -11.667

A =
-22.7780    11.1110      0      0      0      0      0      0      0      0
 11.1110   -22.7780   11.1110      0      0      0      0      0      0      0
      0    11.1110   -22.7780   11.1110      0      0      0      0      0      0
      0      0    11.1110   -22.7780   11.1110      0      0      0      0      0
      0      0      0    11.1110   -22.7780   11.1110      0      0      0      0
      0      0      0      0    11.1110   -22.7780   11.1110      0      0      0
      0      0      0      0      0    11.1110   -22.7780   11.1110      0      0
      0      0      0      0      0      0    11.1110   -22.7780   11.1110      0
      0      0      0      0      0      0      0    11.1110   -22.7780   11.1110
      0      0      0      0      0      0      0      0    11.1110   -11.6670

>> [M,V] = eig(A)

M =
fast mode                                         slow mode
-0.1286    -0.2459    0.3412    0.4063    0.4352    0.4255    0.3780    0.2969   -0.1894    0.0650
 0.2459     0.4063   -0.4255   -0.2969   -0.0650    0.1894    0.3780    0.4352   -0.3412    0.1286
-0.3412    -0.4255    0.1894   -0.1894   -0.4255   -0.3412    0.0000    0.3412   -0.4255    0.1894
 0.4063     0.2969    0.1894    0.4352    0.1286   -0.3412   -0.3780    0.0650   -0.4255    0.2459
-0.4352    -0.0650   -0.4255   -0.1286    0.4063    0.1894   -0.3780   -0.2459   -0.3412    0.2969
 0.4255    -0.1894    0.3412   -0.3412   -0.1894    0.4255   -0.0000   -0.4255   -0.1894    0.3412
-0.3780     0.3780     0.0000    0.3780   -0.3780   -0.0000    0.3780   -0.3780     0.0000    0.3780
 0.2969    -0.4352   -0.3412    0.0650    0.2459   -0.4255    0.3780   -0.1286    0.1894    0.4063
-0.1894     0.3412    0.4255   -0.4255    0.3412   -0.1894    0.0000    0.1894    0.3412    0.4255
 0.0650    -0.1286   -0.1894    0.2459   -0.2969    0.3412   -0.3780    0.4063    0.4255    0.4352

>> eig(A)'

-44.0127   -41.1387   -36.6332   -30.8966   -24.4387   -17.8331   -11.6670   -6.4881   -2.7567   -0.8042
```

Eigenvalues tell you how the system behaves

- Something decays as  $\exp(-44.0127t)$  *fast mode*
- Something decays as  $\exp(-0.8042t)$  *slow mode*

Eigenvectors tell you what behaves that way

Fast Mode: Make the initial condition proportional to the fast eigenvector

Code:


```
% 10-stage RC Filter
```

```
v = 20 * M(:,1);
```

```
dV = zeros(10,1);  
V0 = 0;  
dt = 0.001;  
t = 0;  
i = 0;
```

```
y = [];
```

```
while(t < 0.99)  
(etc)
```

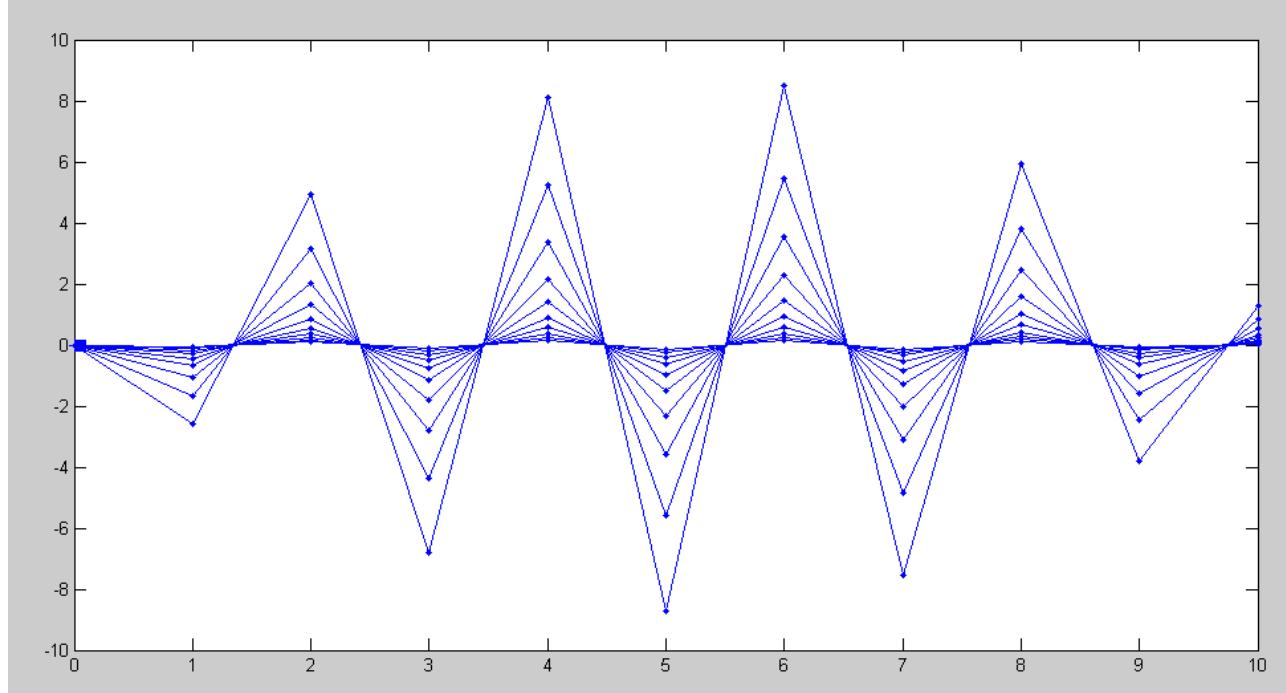


Fast Mode: Voltage plotted every 10ms

Note:

- The shape remains the same (the eigenvector)
- The amplitude decays quickly (the fast eigenvalue)

Slow Mode:

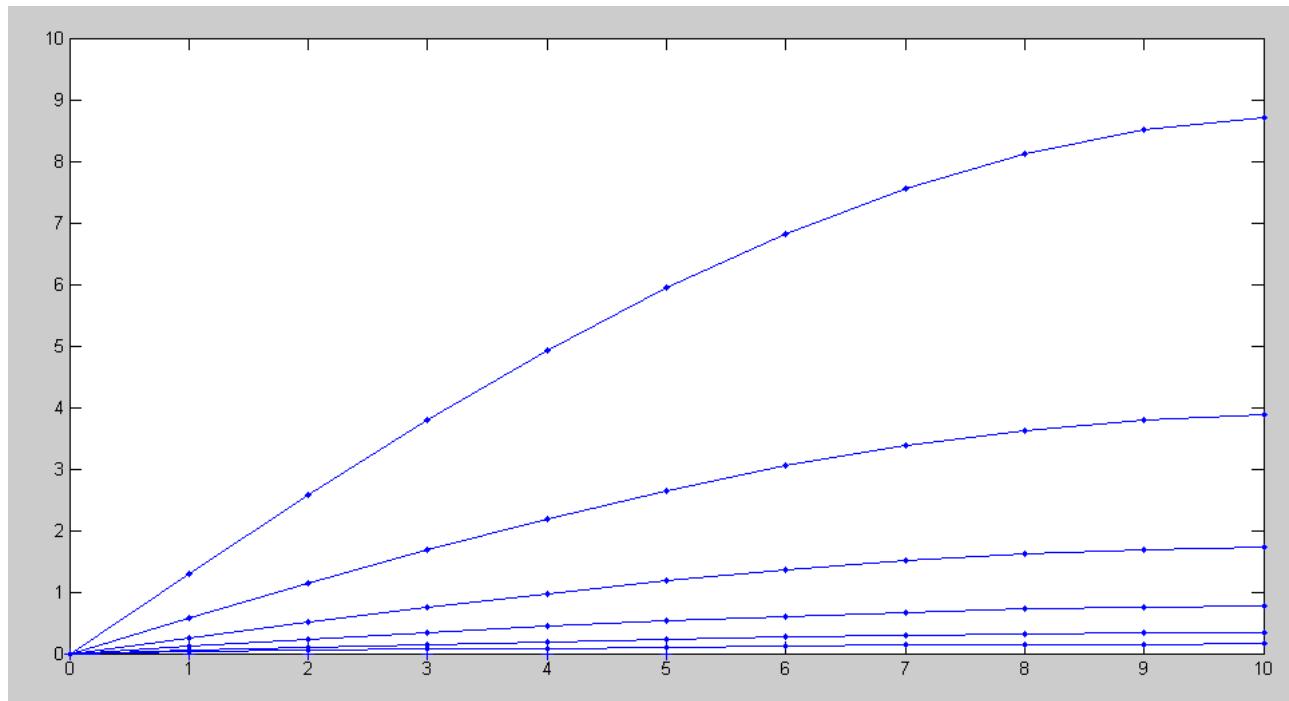

Voltages plotted every 1.000 second.

Note that the shape remains the same

- the eigenvector


The amplitude decays slowly

- the eigenvalue
-

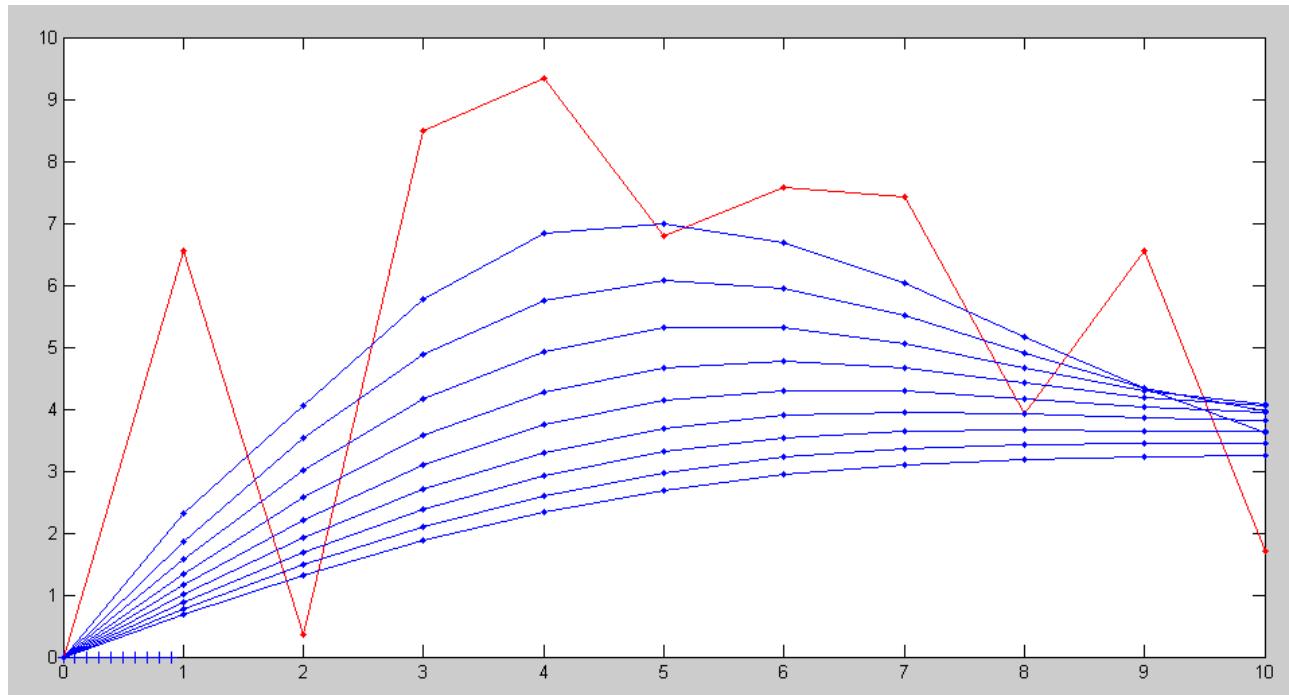9) Assume  $V_{in} = 0V$ . Pick random voltages for  $V_1 \dots V_{10}$  in the range of (0V, 10V):

```
V = 10 * rand(10,1)
```

Plot the voltages at  $t = 2$ . Which eigenvector does it look like?



Voltages plotted every 100ms with a random initial condition (red)

Note:

- The initial voltage includes all ten eigenvectors
- The fast modes decay quickly
- Leaving the slow mode

After 2 seconds, what you see is the slow eigenvector