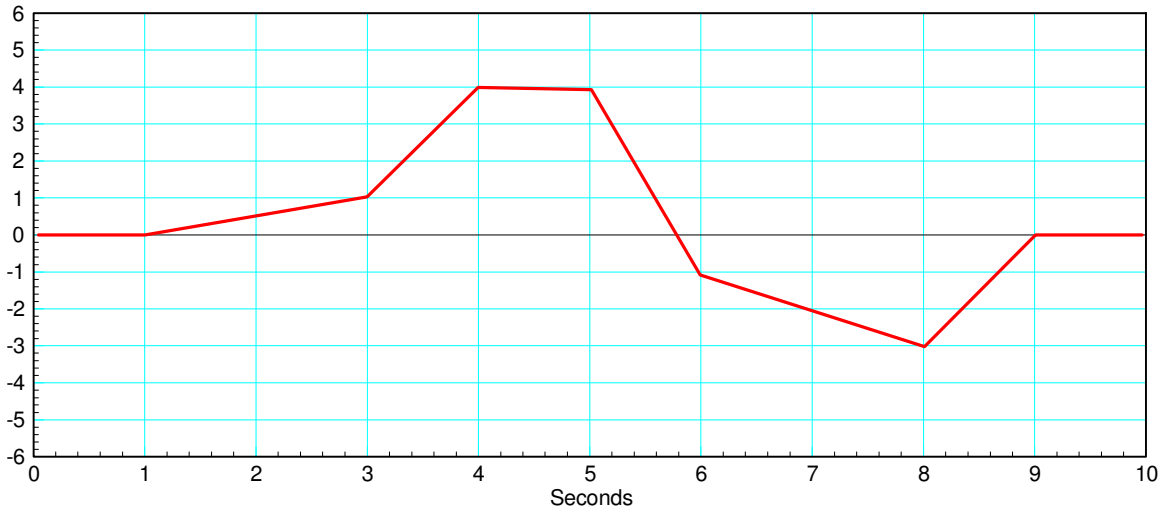


# ECE 111 - Homework #11

ECE 351 Electromagnetics - Wave Equation


1) Assume the current flowing through a one Henry inductor is shown below. Sketch the voltage.

$$V = L \frac{dI}{dt}$$




Inductors are differentiators: the voltage is the derivative of the current

Sketching the derivative (slope) gives V

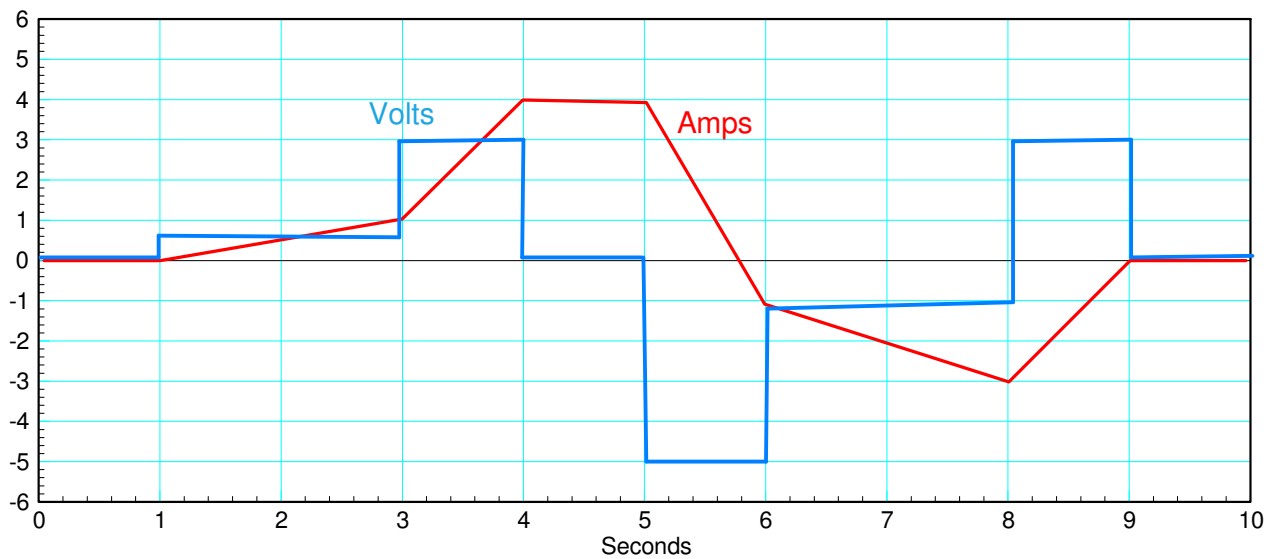

## 4-Node RLC Circuit

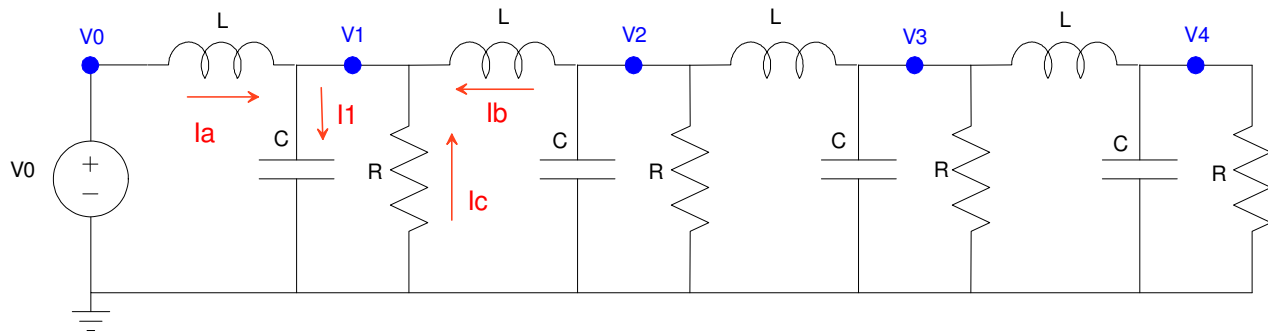

$R = 220\Omega$ ,  $C = 0.15F$ ,  $L = 0.22H$ . Repeat for 30 nodes for problems 4-6

2) Write the dynamic equations for the following 4-stage RLC circuit. (i.e. write the node equations)

This is kind of tricky. One way to do this is to use conservation of current

$$I_1 = I_a + I_b + I_c$$

The inductor and capacitor equations are

$$I_1 = C \cdot V_1'$$

$$V_0 - V_1 = L \cdot I_a'$$

$$V_2 - V_1 = L \cdot I_b'$$

and

$$I_c = -\frac{1}{R}V_1$$

Substitute for  $I_1$  and  $I_c$

$$C \cdot V_1' = I_a + I_b - \frac{1}{R}V_1$$

Differentiate

$$C \cdot V_1'' = I_a' + I_b' - \frac{1}{R}V_1'$$

Substitute for  $I'$

$$C \cdot V_1'' = \left(\frac{V_0 - V_1}{L}\right)' + \left(\frac{V_2 - V_1}{L}\right)' - \frac{1}{R}V_1'$$

Group terms and solve for  $V''$

$$V_1'' = \left(\frac{1}{LC}\right)V_0 - \left(\frac{2}{LC}\right)V_1 + \left(\frac{1}{LC}\right)V_2 - \left(\frac{1}{RC}\right)V_1'$$

Plugging in numbers

$$V_1'' = \left(\frac{1}{LC}\right) V_0 - \left(\frac{2}{LC}\right) V_1 + \left(\frac{1}{LC}\right) V_2 - \left(\frac{1}{RC}\right) V_1'$$

$$V_1'' = 30.30V_0 - 60.60V_1 + 30.30V_2 - 0.03V_1'$$

Same holds for nodes 2 and 3

$$V_2'' = 30.30V_1 - 60.60V_2 + 30.30V_3 - 0.03V_2'$$

$$V_3'' = 30.30V_2 - 60.60V_3 + 30.30V_4 - 0.03V_3'$$


Node 4 is a little different due to only one inductor being attached

$$V_4'' = \left(\frac{1}{LC}\right) V_3 - \left(\frac{1}{LC}\right) V_4 - \left(\frac{1}{RC}\right) V_4'$$

$$V_4'' = 30.30V_3 - 30.30V_4 - 0.03V_4'$$

3) Assume  $V_{in} = 10V$  and the initial conditions are zero ( $V_1 = V_2 = V_3 = V_4 = 0$ ). Solve for the voltages at  $t = 3$  seconds. *Hint: Solve numerically using Matlab*

Voltages vs time

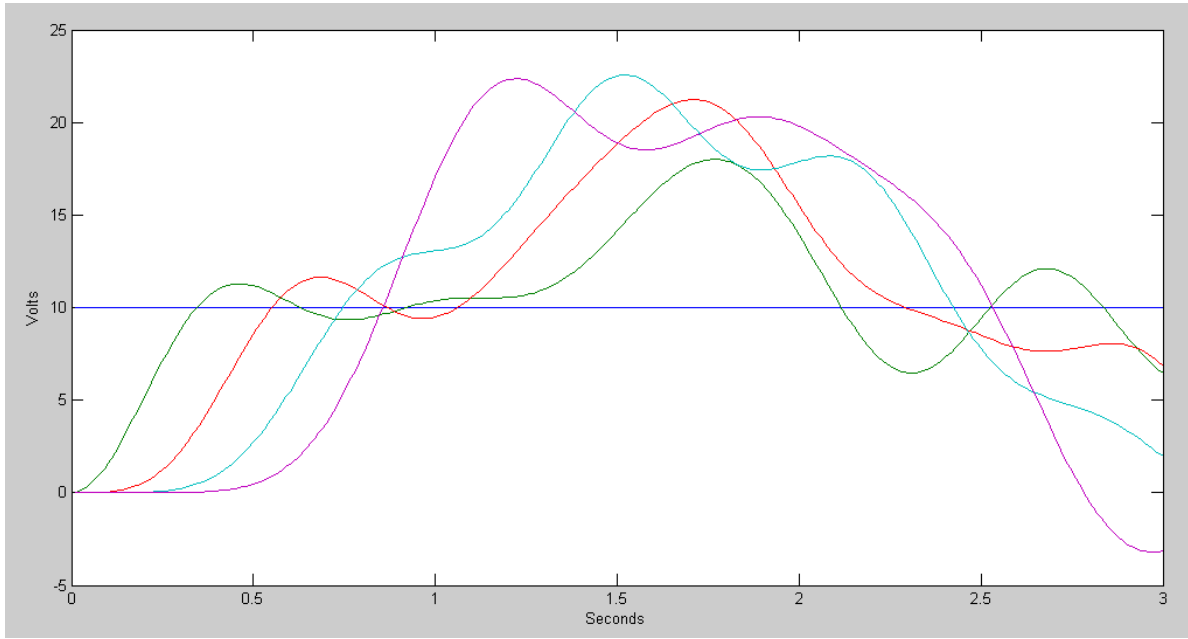

Note:

- The wave equation behaves very differently than the heat equation (last week)

## Code:

```
V0 = 10;
V1 = 0;
V2 = 0;
V3 = 0;
V4 = 0;

dV1 = 0;
dV2 = 0;
dV3 = 0;
dV4 = 0;

V = [];

t = 0;
dt = 0.01;

while(t < 2.99)

    ddV1 = 30.3*V0 - 60.6*V1 + 30.3*V2 - 0.03*dV1;
    ddV2 = 30.3*V1 - 60.6*V2 + 30.3*V3 - 0.03*dV2;
    ddV3 = 30.3*V2 - 60.6*V3 + 30.3*V4 - 0.03*dV3;
    ddV4 = 30.3*V3 - 30.3*V4 - 0.03*dV4;

    dV1 = dV1 + ddV1*dt;
    dV2 = dV2 + ddV2*dt;
    dV3 = dV3 + ddV3*dt;
    dV4 = dV4 + ddV4*dt;

    V1 = V1 + dV1*dt;
    V2 = V2 + dV2*dt;
    V3 = V3 + dV3*dt;
    V4 = V4 + dV4*dt;

    t = t + dt;

    plot([0,1,2,3,4],[V0,V1,V2,V3,V4],'.-');
    ylim([-20,20]);
    pause(0.01);


    V = [V ; [V0,V1,V2,V3,V4]];

end


pause(2)
t = [1:length(V)]' * dt;
plot(t,V)
```

### 30-Node RLC Circuit ( hint: modify the program Wave.m )

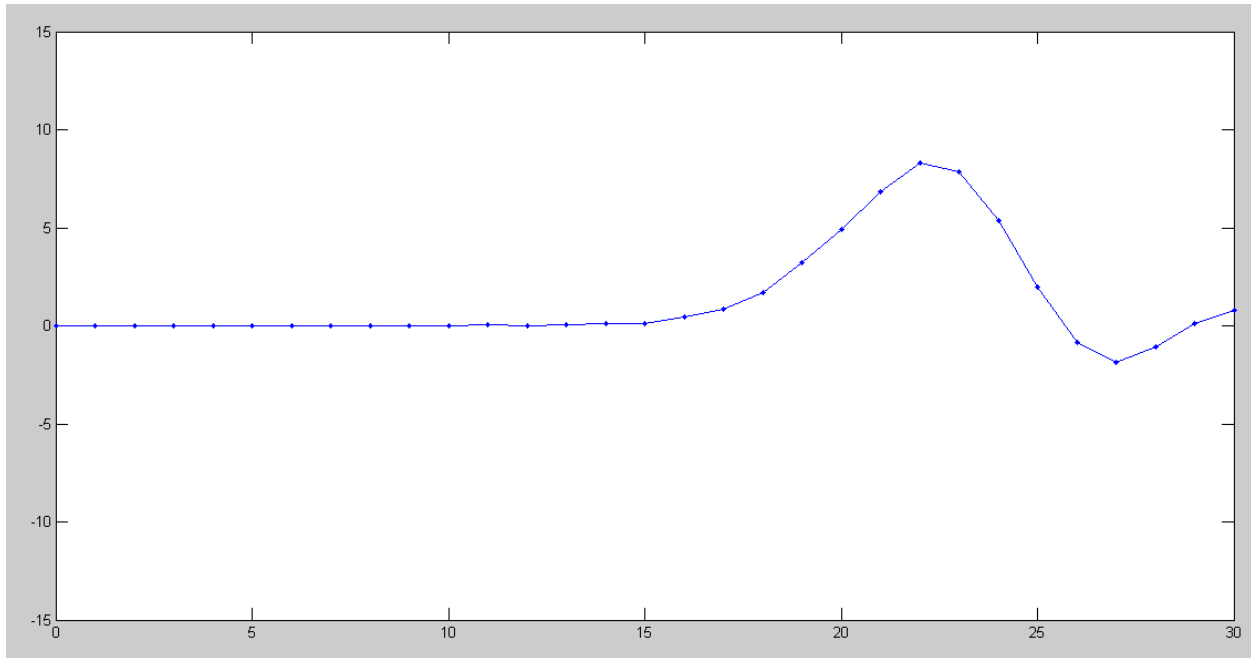4) Expand the RLC circuit from problem #2 to 30 nodes. Plot the voltage at  $t = 8$  seconds (just after the reflection) for  $1 / R_{30}C = 0.01$



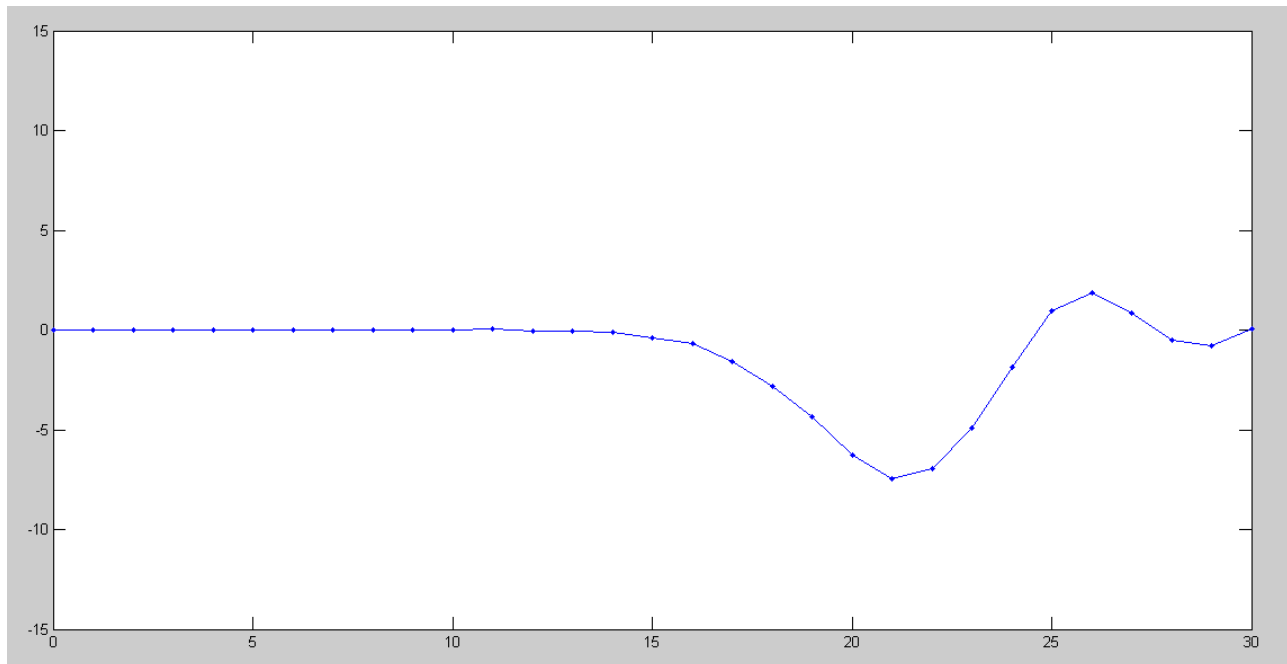5) Plot the voltage at  $t = 8$  seconds for  $1 / R_{30}C = 100$




6) Determine experimentally  $R_{30}$  so that the reflection is almost zero

$$\left(\frac{1}{R_{30}C}\right) = 5.5$$

$$R_{30} = 1.21\Omega$$

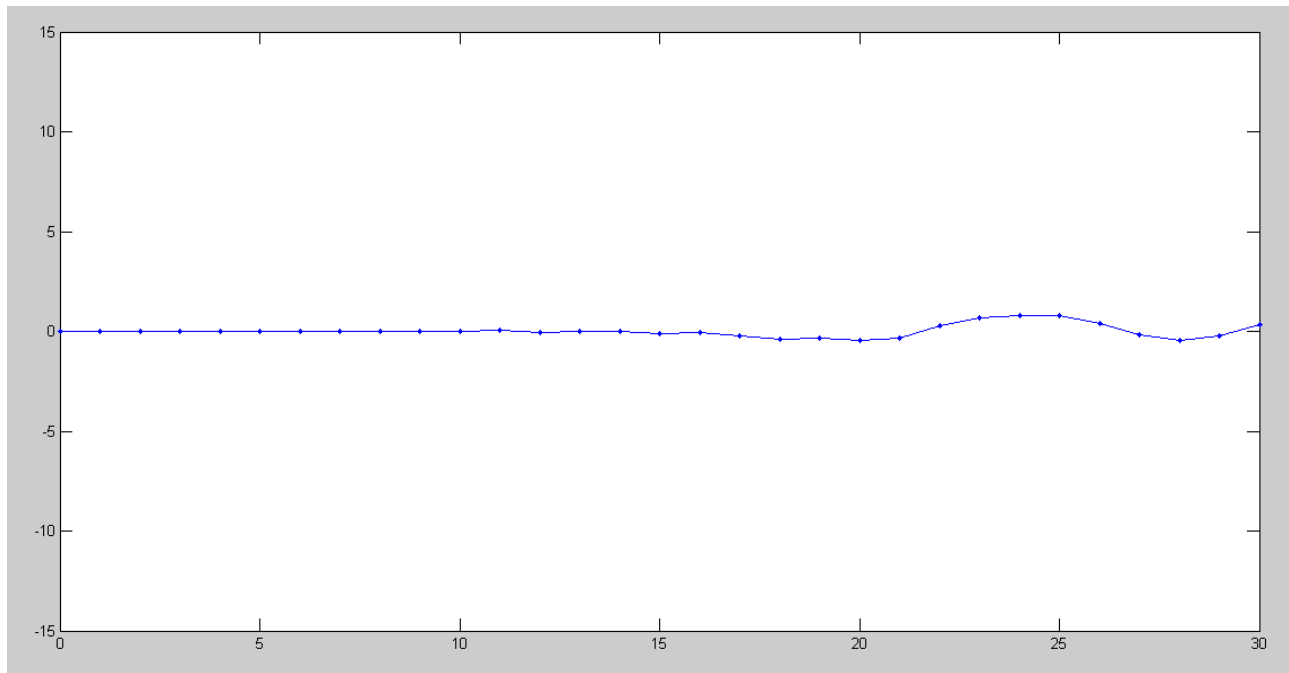Add a 1.21 Ohm resistor at the right endpoint and you'll remove almost all reflections



Voltage at  $t = 8$  seconds for  $1/RC = 5.5$  at the right endpoint