


ECE 111 - Homework #13

ECE 311 Circuits II - Phasors

Phasor Voltages

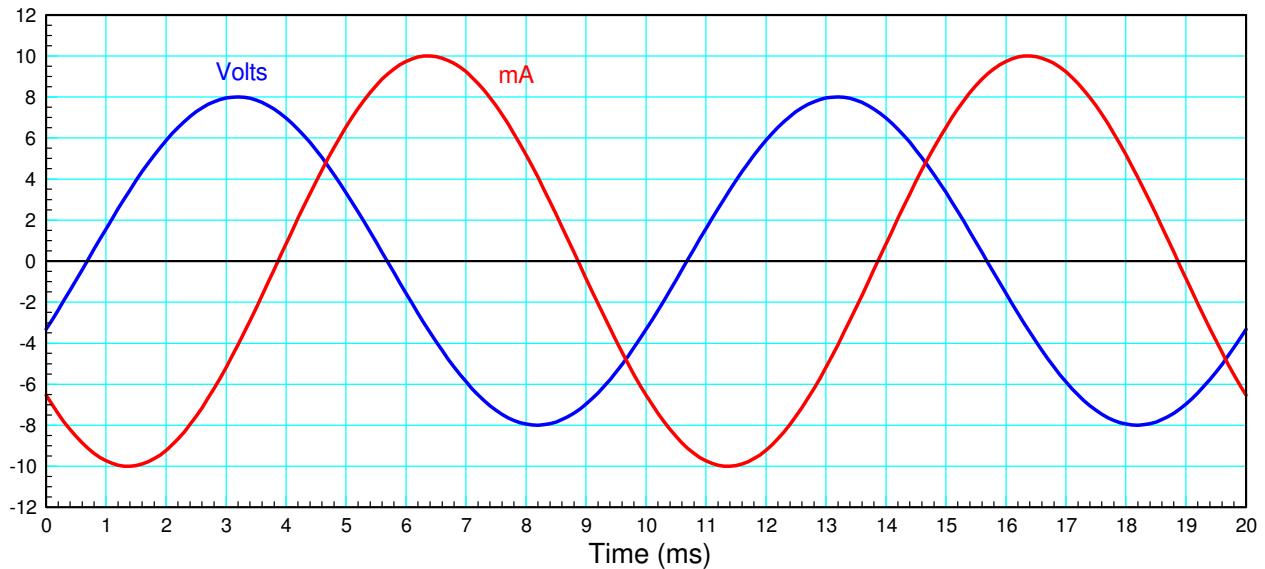1) Express V and I as phasors (i.e. as complex numbers)

- From this, determine the impedance, $Z = V/I$



Polar mode is easiest

Volts:

$$|V| = 8.00 \text{V} \text{ (peak)}, \quad \text{period} = 10\text{ms}. \quad \text{delay} = 3.2\text{ms}$$

$$\theta = -\left(\frac{3.2\text{ms}}{10\text{ms}}\right)360^0 = -115.2^0$$

$$V = 8.00\angle -115.2^0$$

Current

$$|I| = 10\text{ms}, \quad \text{period} = 10\text{ms}, \quad \text{delay} = 6.3\text{ms}$$

$$\theta = -\left(\frac{6.3\text{ms}}{10\text{ms}}\right)360^0 = -226.8^0$$


$$I = 10.00\angle -226.8^0 \text{ mA}$$

Impedance

$$Z = \left(\frac{V}{I}\right) = \left(\frac{8.00\angle -115.2^0}{10.00\angle -226.8^0}\right) = 0.80\angle 111.6^0$$

Phasor Impedances


2) Determine the impedance, Z_{ab}

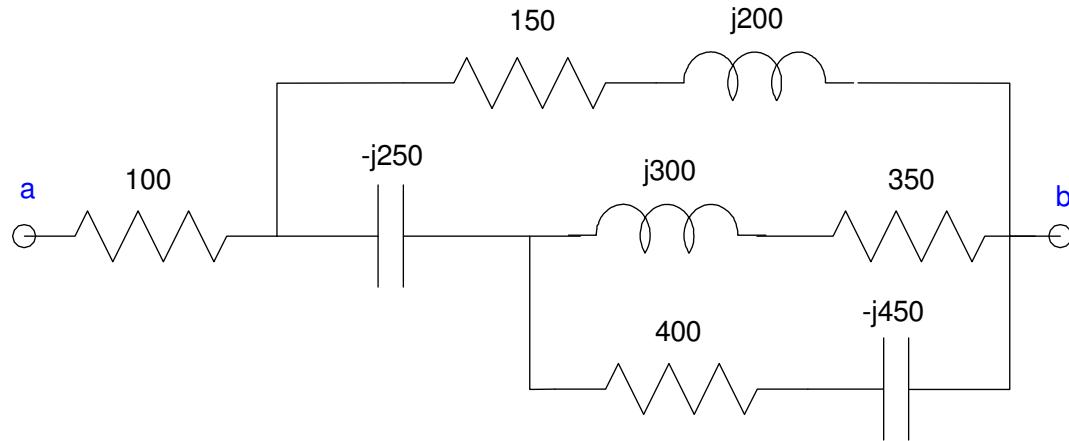


HP Prime: (RPN mode)

- Settings - Entry - RPN
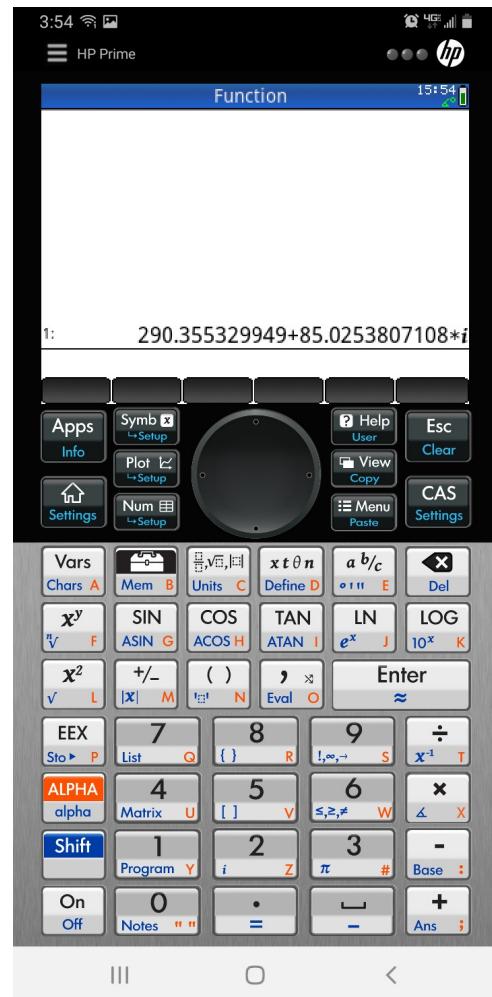
```
350i300
enter
x-1
400i-450
x-1
+
x-1
0i-250
+
x-1
150i200
x-1
+
x-1
100
+
```



3) Determine the impedance, Z_{ab}

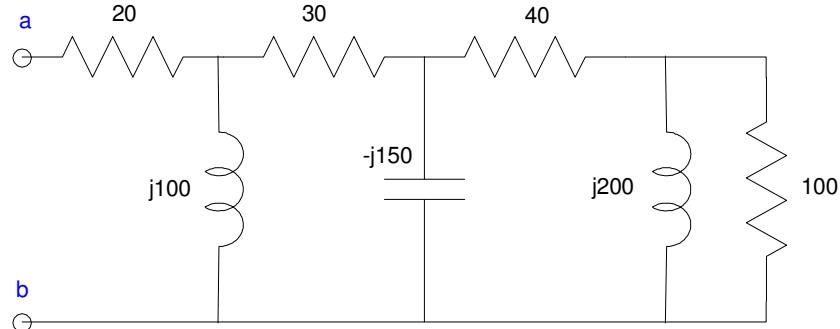


$$Z_{ab} = 88.415 + j77.488$$


HP Prime (RPN mode)

- Settings - Entry - RPN
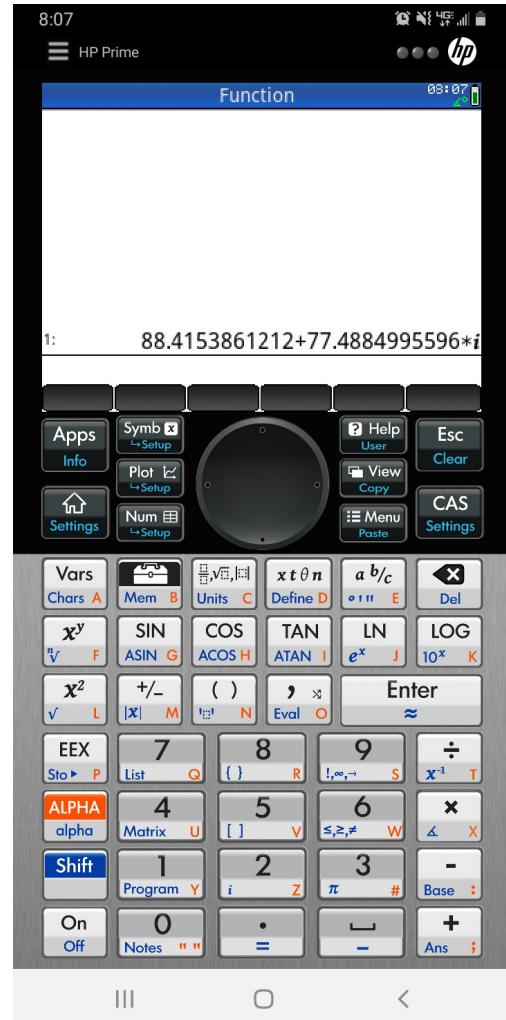
```
100
enter
x-1
0i200
x-1
+
x-1
40
+
x-1
0i-150
x-1
+
x-1
30
+
x-1
0i100
x-1
+
x-1
20
+
```



Voltage Nodes with Phasors

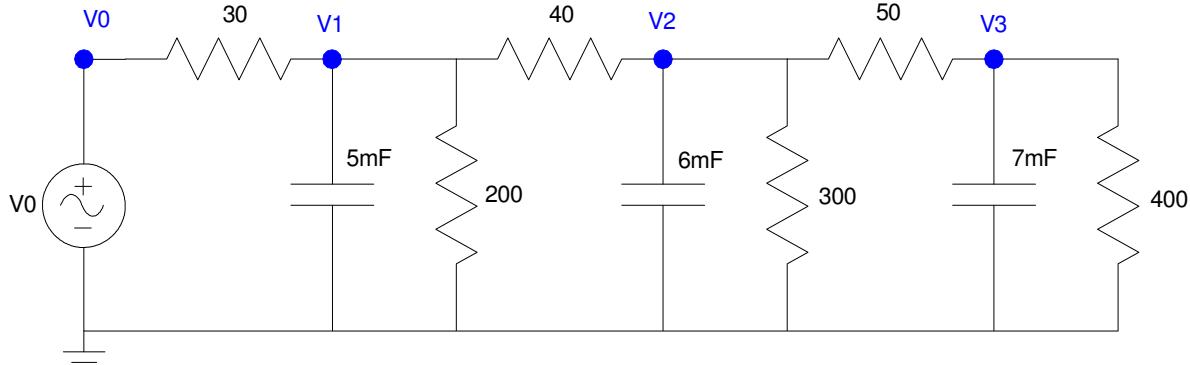

4) Assume $V_0 = 10$.

a) Determine the impedances of each element at 0 rad/sec

$$C \rightarrow \frac{1}{j\omega C} = \infty$$

$$I_c = 0$$

you can ignore capacitors at DC: the current is zero

b) Write the voltage node equations

$$V_0 = 10$$

$$\left(\frac{V_1-V_0}{30}\right) + \left(\frac{V_1}{200}\right) + \left(\frac{V_1-V_2}{40}\right) = 0$$

$$\left(\frac{V_2-V_1}{40}\right) + \left(\frac{V_2}{300}\right) + \left(\frac{V_2-V_3}{50}\right) = 0$$

$$\left(\frac{V_3-V_2}{50}\right) + \left(\frac{V_3}{400}\right) = 0$$

c) Solve for V_1 , V_2 , and V_3 .

Group terms

$$V_0 = 10$$

$$-\left(\frac{1}{30}\right)V_0 + \left(\frac{1}{30} + \frac{1}{200} + \frac{1}{40}\right)V_1 - \left(\frac{1}{40}\right)V_2 = 0$$

$$-\left(\frac{1}{40}\right)V_1 + \left(\frac{1}{40} + \frac{1}{300} + \frac{1}{50}\right)V_2 - \left(\frac{1}{50}\right)V_3 = 0$$

$$-\left(\frac{1}{50}\right)V_2 + \left(\frac{1}{50} + \frac{1}{400}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{30}\right) \left(\frac{1}{30} + \frac{1}{200} + \frac{1}{40}\right) & \left(\frac{-1}{40}\right) & 0 & 0 \\ 0 & \left(\frac{-1}{40}\right) & \left(\frac{1}{40} + \frac{1}{300} + \frac{1}{50}\right) & \left(\frac{-1}{50}\right) \\ 0 & 0 & \left(\frac{-1}{50}\right) & \left(\frac{1}{50} + \frac{1}{400}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve using Matlab

```

>> b1 = [1,0,0,0];
>> b2 = [-1/30,1/30+1/200+1/40,-1/40,0];
>> b3 = [0,-1/40,1/40+1/300+1/50,-1/50];
>> b4 = [0,0,-1/50,1/50+1/400];
>> B = [b1;b2;b3;b4]

1.0000      0      0      0
-0.0333    0.0633   -0.0250    0
      0   -0.0250    0.0483   -0.0200
      0        0   -0.0200    0.0225

>> A = [10;0;0;0]

10
0
0
0

>> V = inv(B)*A

v0 10.0000
v1 7.7739
v2 6.3604
v3 5.6537

>>

```

5) Check your results in CircuitLab




The results are the same

V0 10.0000

V1 7.7739


V2 6.3604

V3 5.6537

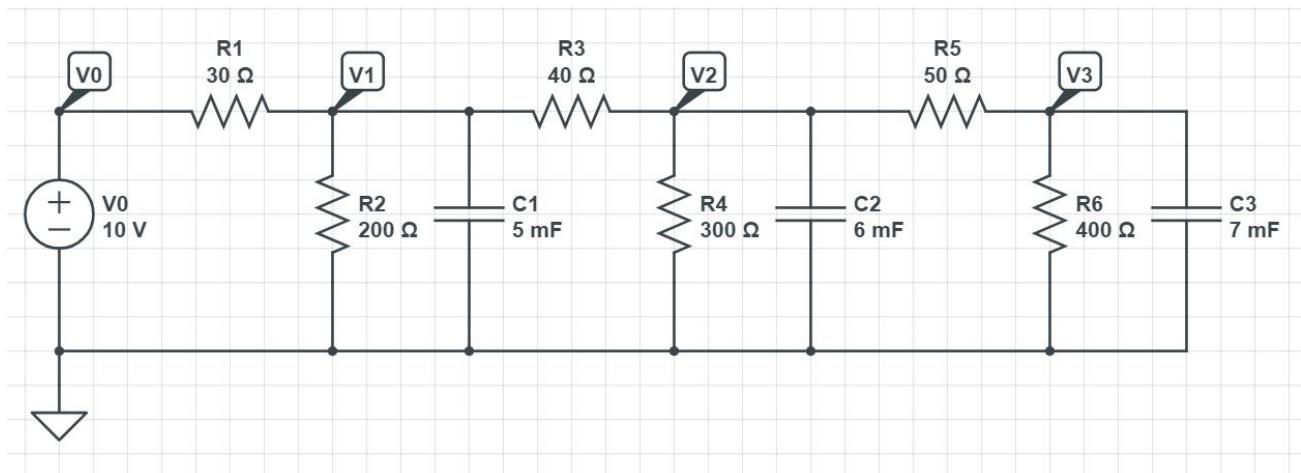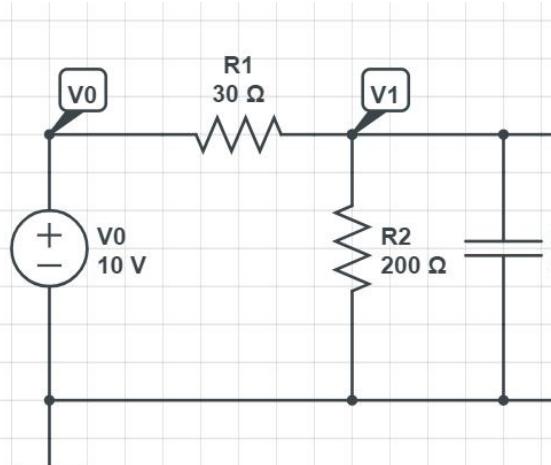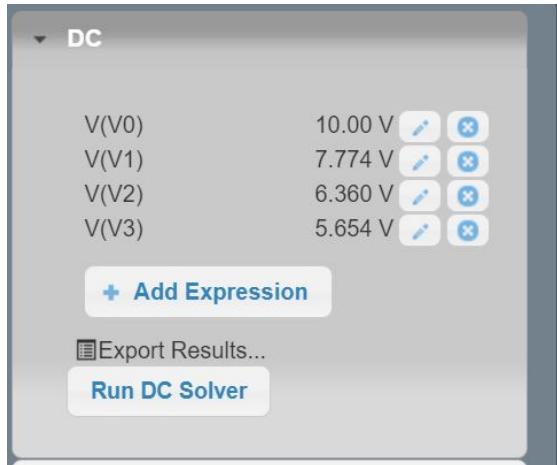

6) Assume $V_0 = 10 \sin(3t)$ $10V, 3 \text{ rad/sec sine wave (}0.478\text{Hz)}$

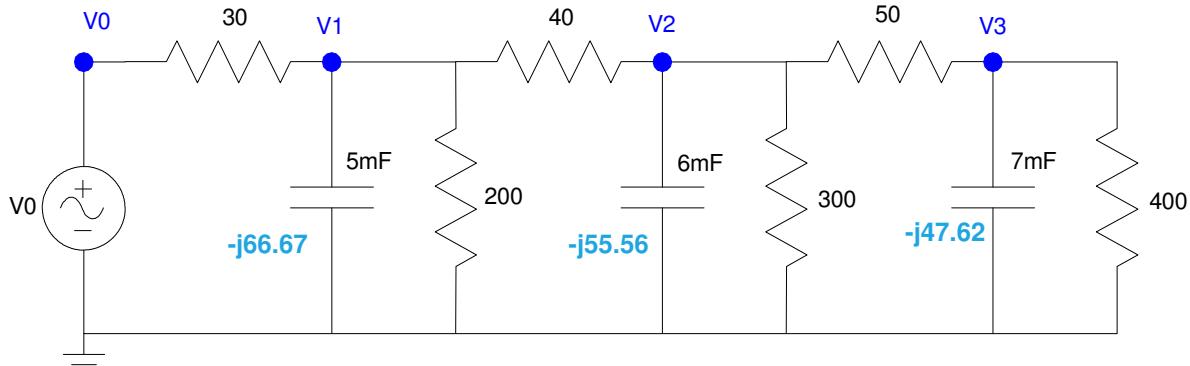a) Determine the impedances of each element at 3 rad/sec



$$C_1 \rightarrow \frac{1}{j\omega C} = \frac{1}{j(3)(0.005)} = -j66.67\Omega$$

$$C_2 \rightarrow \frac{1}{j\omega C} = \frac{1}{j(3)(0.006)} = -j55.56\Omega$$

$$C_3 \rightarrow \frac{1}{j\omega C} = \frac{1}{j(3)(0.007)} = -j47.62\Omega$$

b) Write the voltage node equations

$$V_0 = 0 - j10$$

$$\left(\frac{V_1 - V_0}{30}\right) + \left(\frac{V_1}{200}\right) + \left(\frac{V_1 - V_2}{-j66.67}\right) + \left(\frac{V_1 - V_2}{40}\right) = 0$$

$$\left(\frac{V_2 - V_1}{40}\right) + \left(\frac{V_2}{300}\right) + \left(\frac{V_2 - V_3}{-j55.56}\right) + \left(\frac{V_2 - V_3}{50}\right) = 0$$

$$\left(\frac{V_3 - V_2}{50}\right) + \left(\frac{V_3}{400}\right) + \left(\frac{V_3 - V_0}{-j47.62}\right) = 0$$

c) Solve for V_1 , V_2 , and V_3 as complex numbers

Group terms

$$V_0 = 0 - j10$$

$$-\left(\frac{1}{30}\right)V_0 + \left(\frac{1}{30} + \frac{1}{200} + \frac{1}{40} + \frac{1}{-j66.67}\right)V_1 - \left(\frac{1}{40}\right)V_2 = 0$$

$$-\left(\frac{1}{40}\right)V_1 + \left(\frac{1}{40} + \frac{1}{300} + \frac{1}{50} + \frac{1}{-j55.56}\right)V_2 - \left(\frac{1}{50}\right)V_3 = 0$$

$$-\left(\frac{1}{50}\right)V_2 + \left(\frac{1}{50} + \frac{1}{400} + \frac{1}{-j47.62}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{30}\right) \left(\frac{1}{30} + \frac{1}{200} + \frac{1}{40} + \frac{1}{-j66.67}\right) & \left(\frac{-1}{40}\right) & 0 & 0 \\ 0 & \left(\frac{-1}{40}\right) & \left(\frac{1}{40} + \frac{1}{300} + \frac{1}{50} + \frac{1}{-j55.56}\right) & \left(\frac{-1}{50}\right) \\ 0 & 0 & \left(\frac{-1}{50}\right) & \left(\frac{1}{50} + \frac{1}{400} + \frac{1}{-j47.62}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve in Matlab

```
>> b1 = [1,0,0,0];
>> b2 = [-1/30,1/30+1/200+1/40+1/(-j*66.67),-1/40,0];
>> b3 = [0,-1/40,1/40+1/300+1/50+1/(-j*55.56),-1/50];
>> b4 = [0,0,-1/50,1/50+1/400+1/(-j*47.62)];
>> B = [b1;b2;b3;b4]

1.0000      0      0      0
-0.0333    0.0633 + 0.0150i -0.0250      0
  0      -0.0250      0.0483 + 0.0180i -0.0200
  0          0      -0.0200      0.0225 + 0.0210i

>> A = [0-j*10;0;0;0]

      0  -10.0000i
      0
      0
      0

>> V = inv(B)*A

v0      0  -10.0000i
v1  -2.3048 - 5.3654i
v2  -2.6197 - 1.6418i
v3  -1.9725 + 0.3816i
```

d) Express V1, V2, and V3 in terms of sine and cosine function:

```
v0 = 10.0000 sin(3t)
v1 = -2.3048 cos(3t) + 5.3654 sin(3t)
v2 = -2.6197 cos(3t) + 1.6418 sin(3t)
v3 = -1.9725 cos(3t) - 0.3816 sin(3t)
```

7) Check your results in CircuitLab using a transient simulation for 5 seconds (time step = 5ms).

Note: Polar form works better

>> abs (V)

```
V0    10.0000
V1    5.8395
V2    3.0916
V3    2.0090
```

The magnitude of each voltage from CircuitLab matches calculations (move cursor over waveforms)

```
V0    10.000
V1    5.836
V2    3.122
V3    1.938
```

