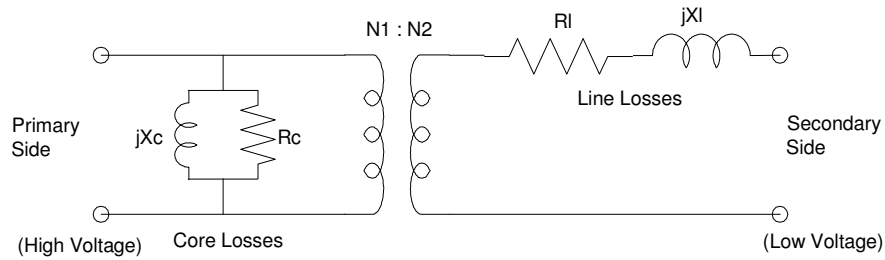


# ECE 111: Homework 16

ECE 331 Energy Conversion

1) Determine the circuit model for a 13.2kV : 240V transformer is tested with the following test results:



Transformer Model

	V	Power	pf
Open-Circuit Test	V1 = 13.2kV	60 W	0.02
Short-Circuit Test	V2 = 40V	15 W	0.99

Equations: Open-Circuit Test (code model)

$$P = V \cdot I \cdot pf$$

$$60W = 13.2kV \cdot I \cdot 0.02$$

$$I = 0.2273$$

$$Z = \left( \frac{V}{I} \right) \angle \theta$$

$$\theta = \arccos(0.02) = 88.854^\circ$$

$$Z = \left( \frac{13.2kV}{0.2273A} \right) \angle 88.854^\circ$$

$$Z = 1161.6 + j58068$$

To get the parallel model

$$\frac{1}{Z} = \frac{1}{R_c} + \frac{1}{jX_c} = 3.4435e-007 - 1.7214e-005i$$

$$R_c = \frac{1}{3.4435e-007} = 2.9040e+006$$

$$X_c = \frac{1}{1.7214e-005i} = 5.8092e+004$$

## In Matlab

```
>> V = 13.2e3;
>> P = 60;
>> pf = 0.02;
>> I = P / (V*pf)

I =    0.2273

>> q = acos(0.02)

q =    1.5508    radians

>> Z = (V/I) * exp(j*q)

Z =    1.1616e+003 +5.8068e+004i    series model

>> 1/Z

ans =    3.4435e-007 -1.7214e-005i

>> Rc = 1/real(1/Z)


Rc =    2.9040e+006

>> Xc = -1/imag(1/Z)

Xc =    5.8092e+004
```
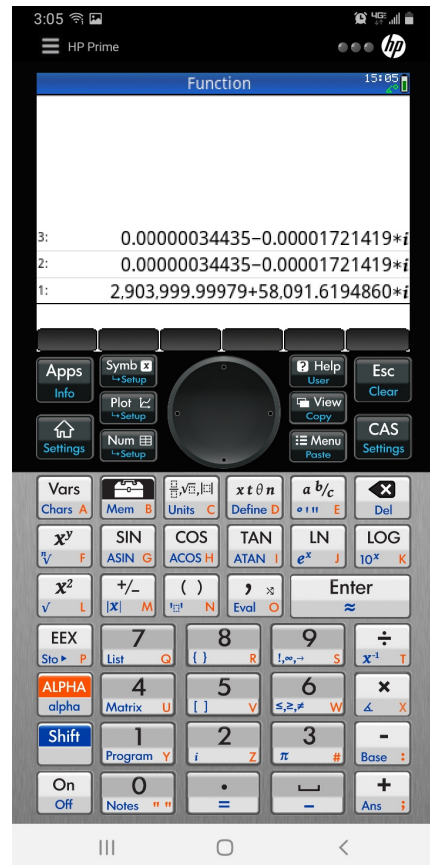
## HP Prime

```
60
enter
13200
/
0.02
/    the current, I
x-1
13200
*    impedance, Z
0.02
ACOS    angle in degrees
180
/
pi
*    angle in radians
0i1
*
e^x
*    series model
x^-1
enter
enter
Mem - Arithmetic - complex - Real Part
x^-1    Rc
(grab the stack for 1/series model)
Mem - Arithmetic - complex - Imaginary Part
x^-1    Xc
+/-
0i1
*
+    Rc + jXc
```



## Line Model

$$P = V \cdot I \cdot pf$$

$$I = \left( \frac{15W}{40V \cdot 0.99} \right) = 0.3788A$$

$$\theta = \arccos(0.99) = 8.11^\circ$$

$$Z = \left( \frac{V}{I} \right) \angle \theta$$

$$Z = \left( \frac{40V}{0.3788A} \right) \angle 8.11^\circ$$

$$Z = R_L + jX_L = 104.54 + j14.897$$

## In Matlab

```
>> P = 15;
>> V = 40;
>> pf = 0.99;
>> I = P / (V*pf)

I =      0.3788          amps

>> q = acos(pf)

q =      0.1415          radians

>> Z = (V/I) * exp(j*q)


Z = 1.0454e+002 +1.4897e+001i

>> RL = real(Z)
RL = 104.5440

>> XL = imag(Z)
XL = 14.8967
```

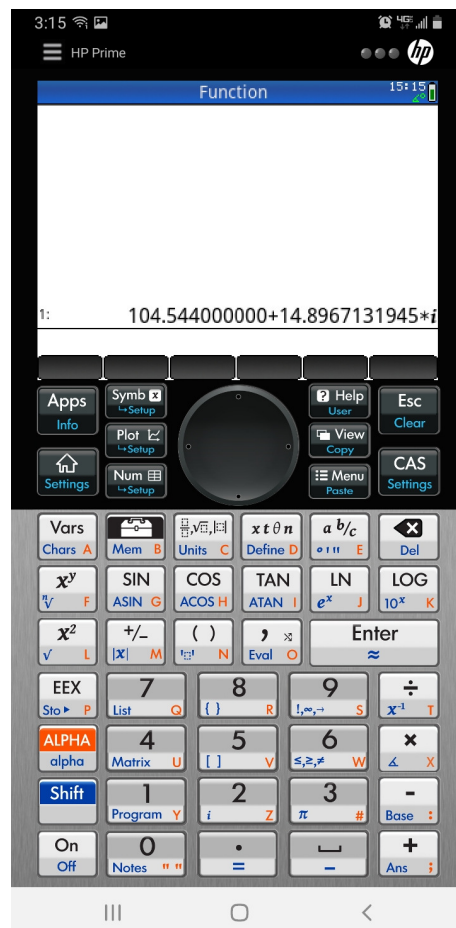
## HP Prime

```
15
enter
40
/
0.99
/          current, I
x-1
40
*          impedance Z
0.99
ACOS
180
/
pi
*
0i1
*
ex
*
```



For the utility grid on the back of the page....

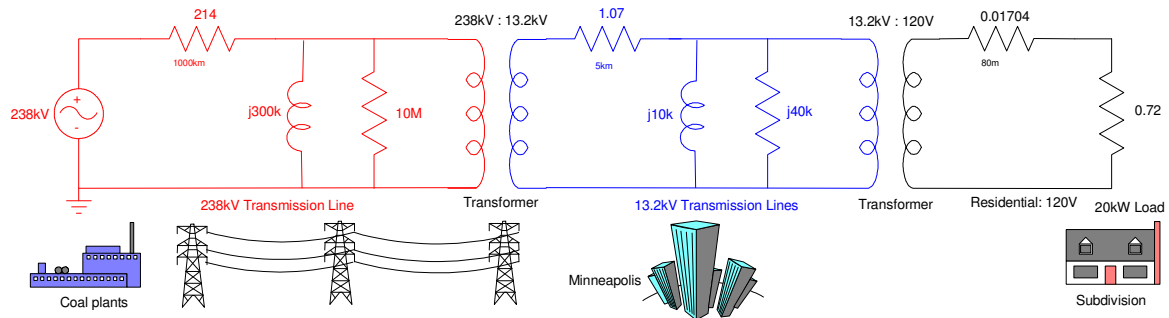2) Convert the voltages and impedances to the 120V node (right side)



Voltages convert as the turns-ratio

$$238kV \left( \frac{13.2kV}{238kV} \right) \left( \frac{120V}{13.2kV} \right) = 120V$$

Impedances convert as the turn-ratio squared

$$\gg R01 = 214 * (120/238e3)^2$$

$$R01 = 5.4403e-005$$

$$\gg R1 = 10e6 * (120/238e3)^2$$

$$R1 = 2.5422$$

$$\gg X1 = j*300e3 * (120/238e3)^2$$

$$X1 = 0 + 0.0763i$$

$$\gg R12 = 1.07 * (120/13.2e3)^2$$

$$R12 = 8.8430e-005$$

$$\gg R2 = 40e3 * (120/13.2e3)^2$$

$$R2 = 3.3058$$


$$\gg X2 = j*10e3 * (120/13.2e3)^2$$

$$X2 = 0 + 0.8264i$$

$$\gg R23 = 0.01704;$$

$$\gg R3 = 0.72;$$

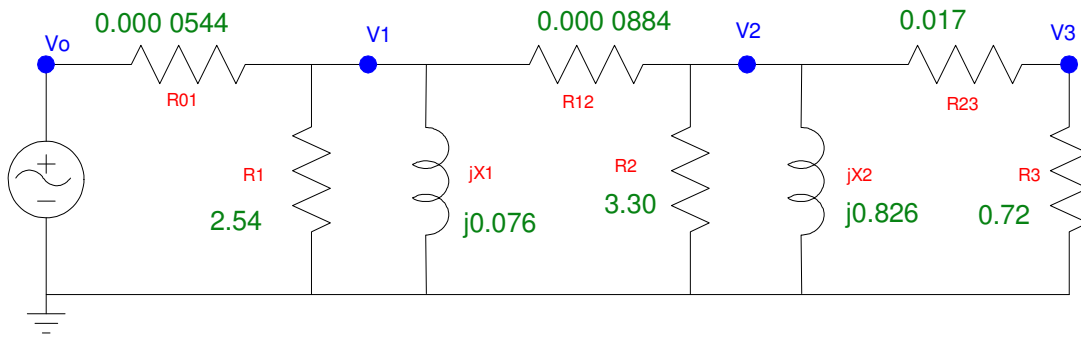3) Write the voltage node equations for this circuit (with transformers removed)



$$V_0 = 120$$

$$\left( \frac{V_1 - V_0}{R_{01}} \right) + \left( \frac{V_1}{R_1} \right) + \left( \frac{V_1}{jX_1} \right) + \left( \frac{V_1 - V_2}{R_{12}} \right) = 0$$

$$\left( \frac{V_2 - V_1}{R_{12}} \right) + \left( \frac{V_2}{R_2} \right) + \left( \frac{V_2}{jX_2} \right) + \left( \frac{V_2 - V_3}{R_{23}} \right) = 0$$

$$\left( \frac{V_3 - V_2}{R_{23}} \right) + \left( \frac{V_3}{R_3} \right) = 0$$

4) Determine the voltages at each node

Group terms

$$V_0 = 120$$

$$-\left(\frac{1}{R_{01}}\right)V_0 + \left(\frac{1}{R_{01}} + \frac{1}{R_1} + \frac{1}{jX_1} + \frac{1}{R_{12}}\right)V_1 - \left(\frac{1}{R_{12}}\right)V_2 = 0$$

$$-\left(\frac{1}{R_{12}}\right)V_1 + \left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{jX_2} + \frac{1}{R_{23}}\right)V_2 - \left(\frac{1}{R_{23}}\right)V_3 = 0$$

$$-\left(\frac{1}{R_{23}}\right)V_2 + \left(\frac{1}{R_{23}} + \frac{1}{R_3}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{R_{01}}\right) & \left(\frac{1}{R_{01}} + \frac{1}{R_1} + \frac{1}{jX_1} + \frac{1}{R_{12}}\right) & \left(\frac{-1}{R_{12}}\right) & 0 \\ 0 & \left(\frac{-1}{R_{12}}\right) & \left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{jX_2} + \frac{1}{R_{23}}\right) & \left(\frac{-1}{R_{23}}\right) \\ 0 & 0 & \left(\frac{-1}{R_{23}}\right) & \left(\frac{1}{R_{23}} + \frac{1}{R_3}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 120 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve in Matlab

```
R01 = 214 * (120/238e3)^2;
R1 = 10e6 * (120/238e3)^2;
X1 = j*300e3 * (120/238e3)^2;
R12 = 1.07 * (120/13.2e3)^2;
R2 = 40e3 * (120/13.2e3)^2;
X2 = j*10e3 * (120/13.2e3)^2;
R23 = 0.01704;
R3 = 0.72;
```

```
b1 = [1, 0, 0, 0];
b2 = [-1/R01, 1/R01+1/R1+1/X1+1/R12, -1/R12, 0];
b3 = [0, -1/R12, 1/R12+1/R2+1/X2+1/R23, -1/R23];
b4 = [0, 0, -1/R23, 1/R23+1/R3];
B = [b1;b2;b3;b4]
A = [120;0;0;0]
V = inv(B)*A
```

```
B =
1.0e+004 *
    0.0001                0                0                0
   -1.8381             2.9690 - 0.0013i    -1.1308                0
                0             -1.1308             1.1367 - 0.0001i    -0.0059
                0                0             -0.0059             0.0060
```

A =

```
120
  0
  0
  0
```

V =


**1.0e+002 \***

```
V0  1.2000 + 0.0000i
V1  1.1999 + 0.0009i
V2  1.1997 + 0.0011i
V3  1.1720 + 0.0010i
```

>> abs(V)

```
V0  120.0000
V1  119.9866
V2  119.9690
V3  117.1953
```

>>

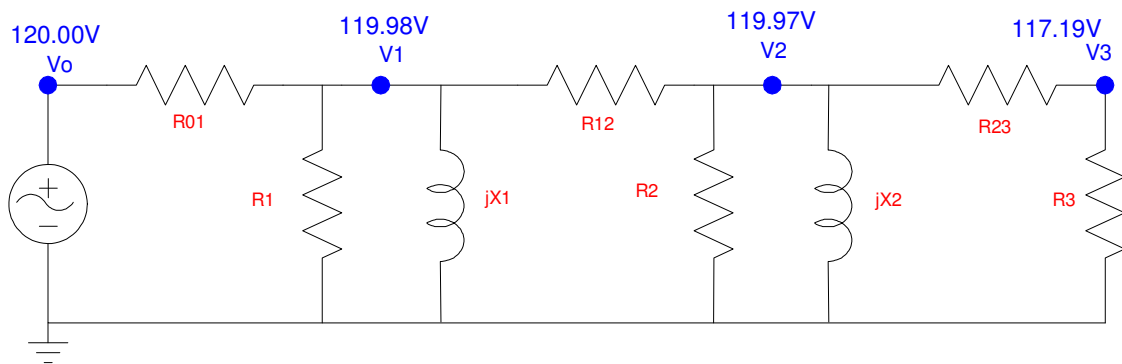

5) Determine the efficiency of this system

- Ignoring the core losses
  - Assumes a large number of customers share these losses
- Including the core losses
  - Assumes a single customer

$$\begin{aligned}V_0 &= V(1); \\V_1 &= V(2); \\V_2 &= V(3); \\V_3 &= V(4); \end{aligned}$$

$$\begin{aligned}P_{01} &= \text{abs}(V_0 - V_1)^2 / R_{01} \\P_1 &= \text{abs}(V_1)^2 / R_1 \\P_{12} &= \text{abs}(V_1 - V_2)^2 / R_{12} \\P_2 &= \text{abs}(V_2)^2 / R_2 \\P_{23} &= \text{abs}(V_2 - V_3)^2 / R_{23} \\P_3 &= \text{abs}(V_3)^2 / R_3 \end{aligned}$$

$$\text{eff} = P_3 / (P_1 + P_{12} + P_2 + P_{23} + P_3)$$

$$\text{eff} = P_3 / (P_{12} + P_{23} + P_3)$$

$$P_{01} = 163.9477$$

$$P_1 = 5.6631e+003$$

$$P_{12} = 5.3675$$

$$P_2 = 4.3537e+003$$

$$P_{23} = 451.4662$$

$$P_3 = 1.9076e+004$$

$$\text{eff} = 0.6456$$

$$\text{eff} = 0.9766$$


**The efficiency including the core losses is 64.56%**

The efficiency is you only have one customer

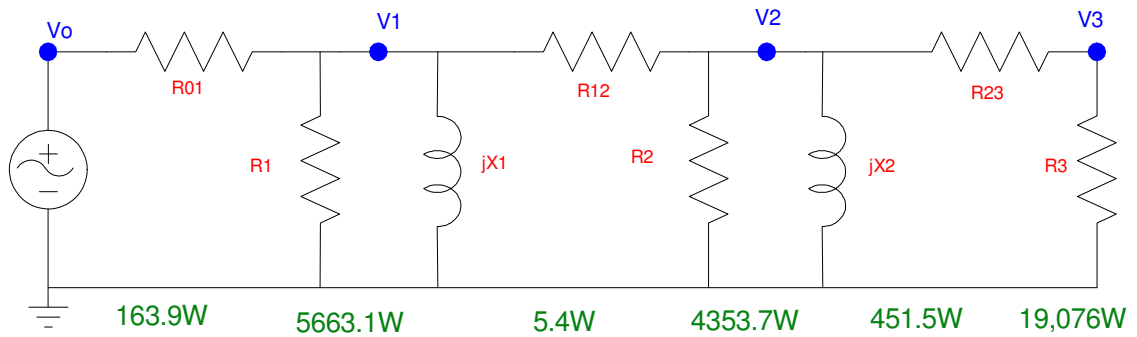**The efficiency excluding the core losses is 97.66%**

The efficiency if you have many customers





### Power Dissipated by Each Resistor

$$P_{01} = 163.9477$$

$$P_1 = 5.6631\text{e}+003$$

$$P_{12} = 5.3675$$

$$P_2 = 4.3537\text{e}+003$$

$$P_{23} = 451.4662$$

$$P_3 = 1.9076\text{e}+004$$

### Efficiency Including Core Losses

$$\text{eff} = 0.6456$$

### Efficiency Excluding Core Losses

$$\text{eff} = 0.9766$$