

# ECE 111 - Make-Up Homework #8

EE 206 Circuits I

$$V = IR, P = VI$$


1) A resistor has the following volts / amps / resistance / power. Determine the missing parameters:

Volts	Amps	Ohms	Watts
15V	3.0A		
15V		8	
	6.0A		120W
15V			60W

## Resistor Color Codes


2) Determine the value of the following resistors

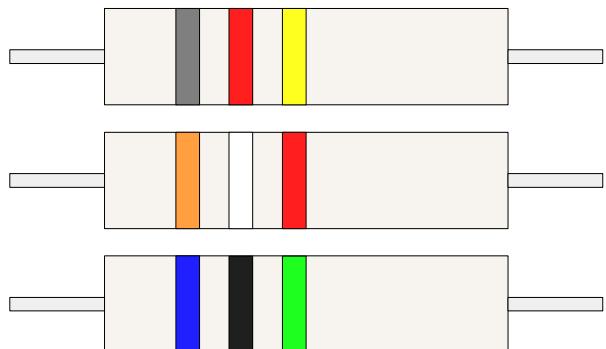- a) Grey - Red - Yellow
- b) Orange - White - Red
- c) Blue- Black - Green




## Kirchoff's Laws:

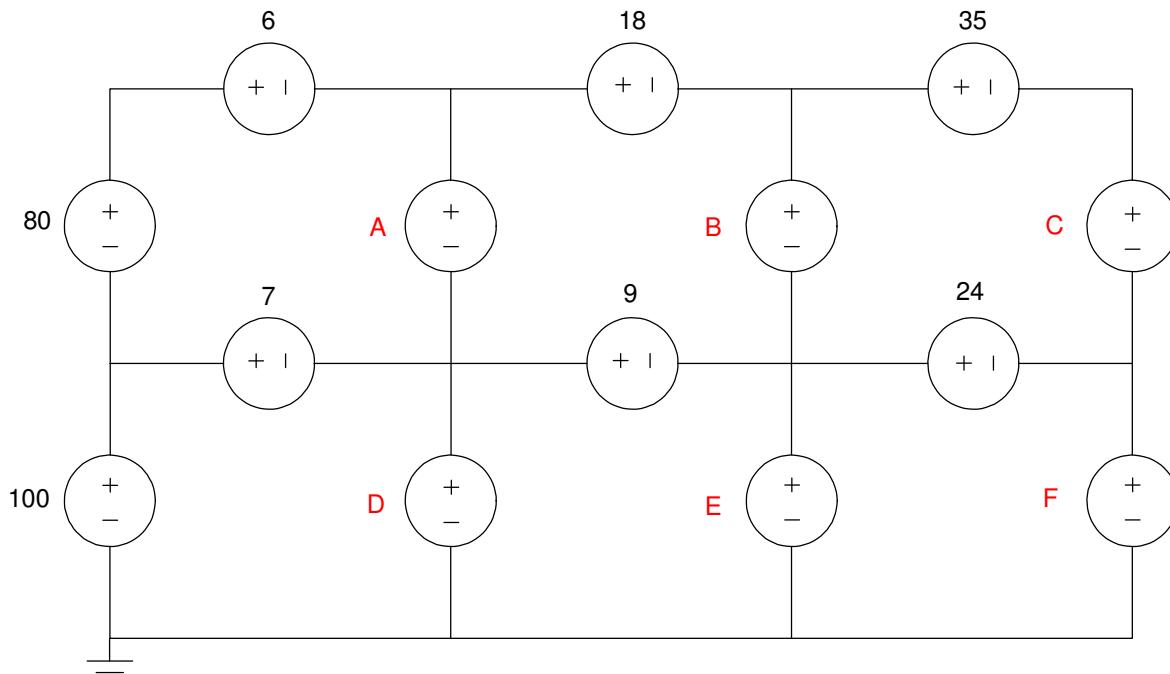- 3) Use conservation of voltage to determine the unknown voltages



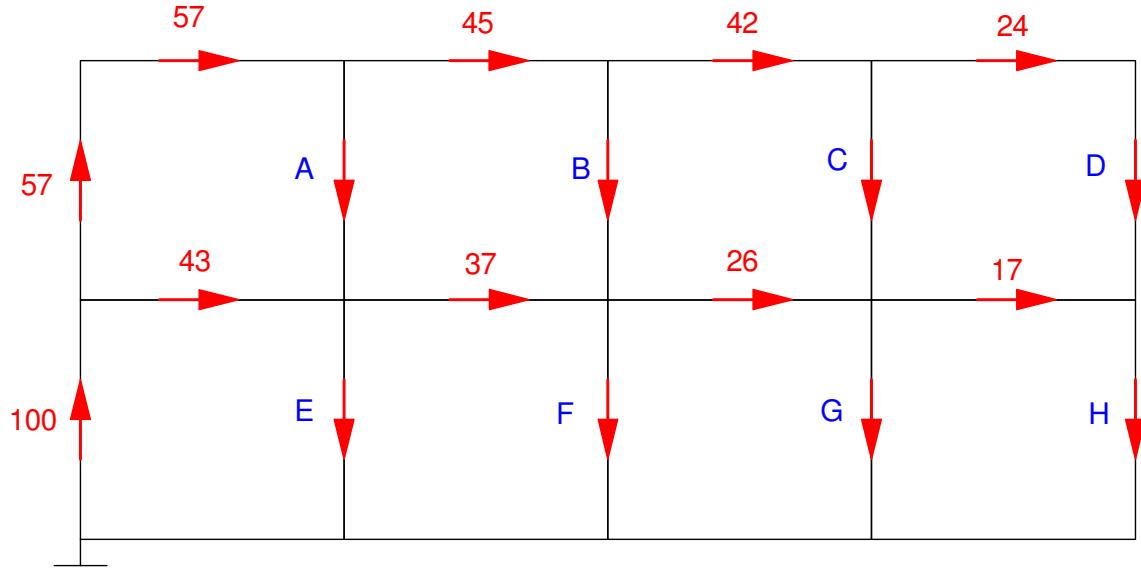- 4) Use conservation of current to determine the unknown currents




## Resistors in Series and Parallel

5) Compute the total resistance  $R_{ab}$  by hand (i.e. using Matlab or a calculator)

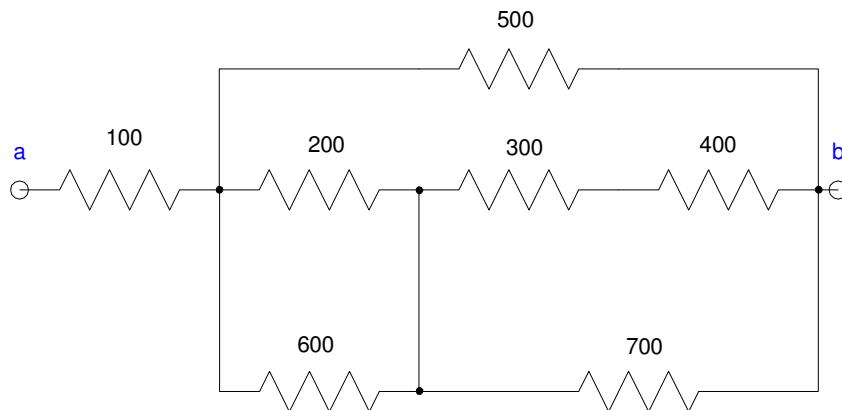6) Find the total resistance  $R_{ab}$  using CircuitLab

- Apply a 10V source to a and b.
- Determine the current draw from the 10V source
- Calculate the net resistance from  $V = IR$




Problem 5 & 6

7) Compute the total resistance  $R_{ab}$  by hand (i.e. using Matlab or a calculator)

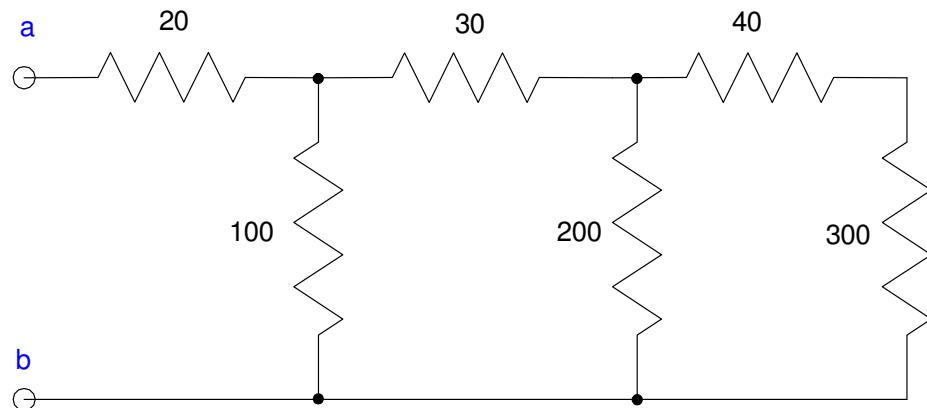8) Find the total resistance,  $R_{ab}$ , using CircuitLab

- Apply a 10V source to a and b.
- Determine the current draw from the 10V source
- Calculate the net resistance from  $V = IR$




Problem 7 & 8

## Voltage Division

9) Use voltage division to find V<sub>1</sub>, V<sub>2</sub>, and V<sub>3</sub>.

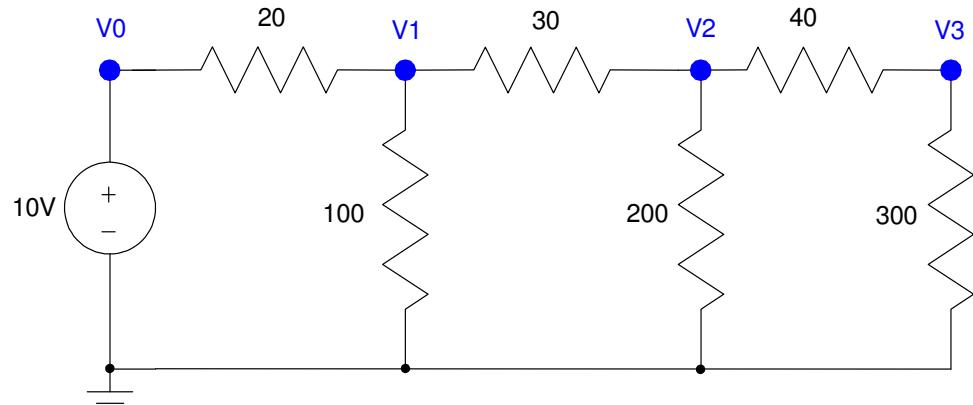10) Use CircuitLab to find V<sub>1</sub>, V<sub>2</sub>, V<sub>3</sub>.



Problem 9 & 10