


ECE 111 - Homework #10

ECE 311 Circuits II - Capacitors & the Heat Equation
Due Monday, March 31st. Please submit via email or on BlackBoard

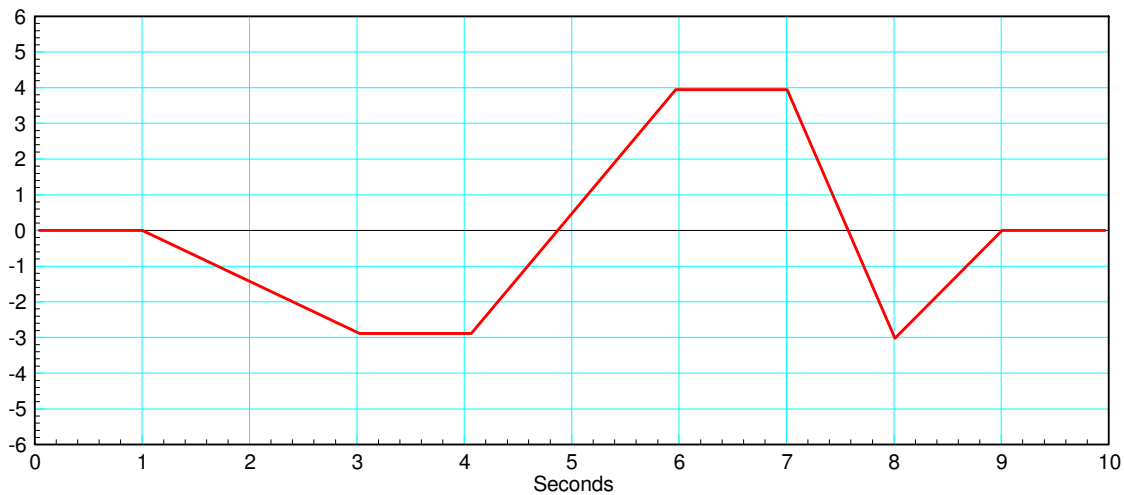
1) Assume the current flowing through a one Farad capacitor is shown below. Sketch the voltage. Assume $V(0) = 0$. The voltage is the integral of the current (capacitors are integrators)

$$V = \frac{1}{C} \int I \cdot dt$$

Assume the initial voltage on the capacitor is +2V.



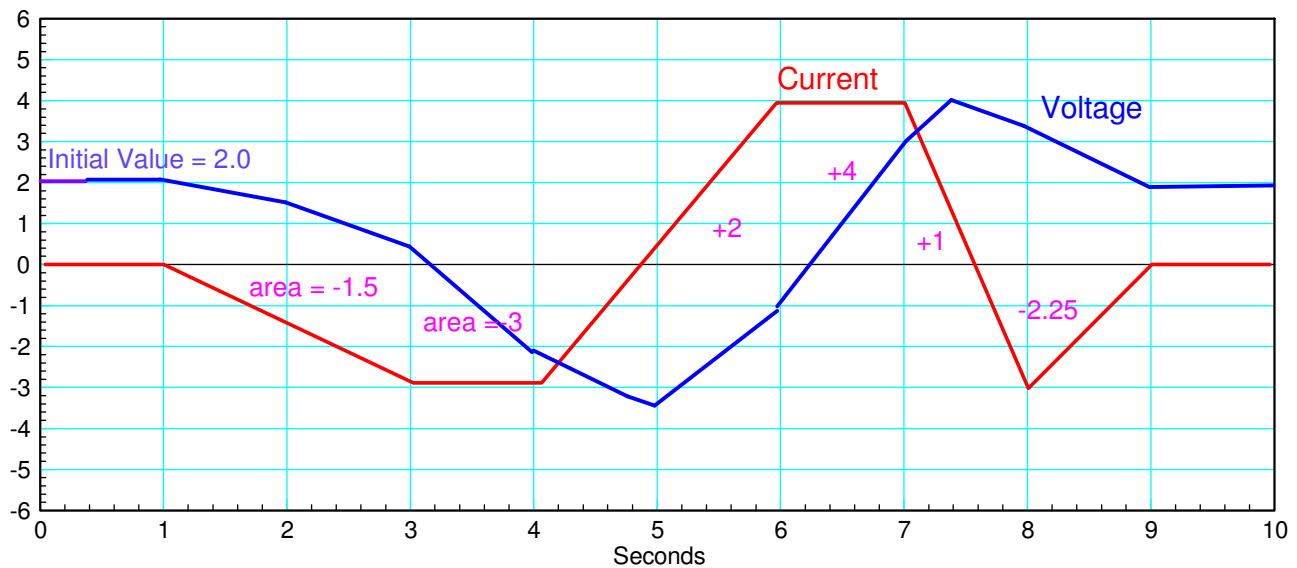
Capacitors integrate. The answer is the same as homework set #7



1-Stage RC filter:

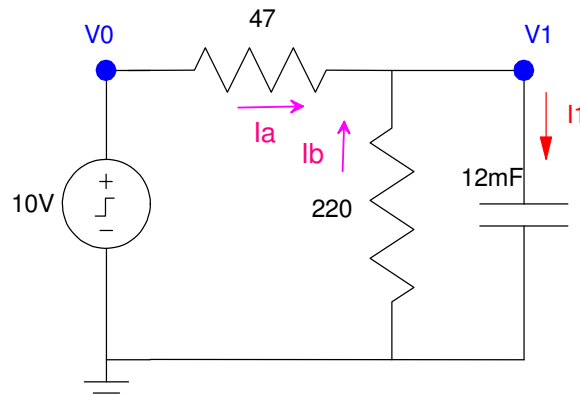2) Write the differential equation that describe this circuit. Note:

$$I_1 = C \frac{dV_1}{dt} = \sum (\text{current to node } V_1)$$



Current In = Current Out

$$I_1 = I_a + I_b$$

$$I_1 = 0.012 \frac{dV_1}{dt} = \left(\frac{V_0 - V_1}{47} \right) + \left(\frac{0 - V_1}{220} \right)$$

Simplifying

$$\frac{dV_1}{dt} = 1.773V_0 - 2.190V_1$$

Comment:

- Writing the differential equations is fairly easy: just use conservation of current
current in = current out
- Solving these differential equations by hand is something you'll do in Calculus III

For this course, we'll use Matlab to solve using numerical methods

- Once you get the differential equation, you pretty much have the program

3) Find and plot $V_1(t)$ for two seconds using Matlab.

Solve

$$\frac{dV_1}{dt} = 1.773V_0 - 2.190V_1$$

with the initial condition:


$$V_1(0) = 0$$

(Since $V_0 = 0$ for time less than infinity, all voltages will be zero at $t=0$)

Write a Matlab program to simulate for 2 seconds.

- Set the integration step size to 2ms for 1000 points on the plot


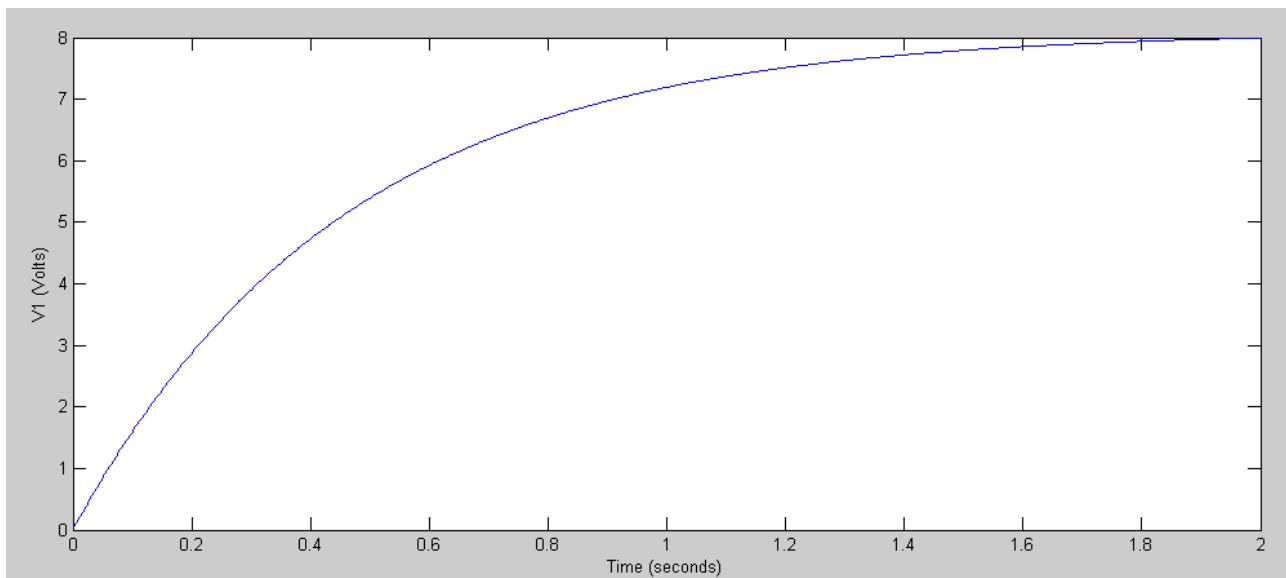
```
dt = 0.002;  
t = 0;  
V0 = 10;  
V1 = 0;  
  
x = [];  
y = [];  
  
while(t < 2)  
    dV1 = 1.773*V0 - 2.190*V1;  
    V1 = V1 + dV1 * dt;  
    t = t + dt;  
    x = [x; t];  
    y = [y ; V1];  
end  
  
plot(x,y);  
xlabel('Time (seconds)');  
ylabel('V1 (Volts)')
```



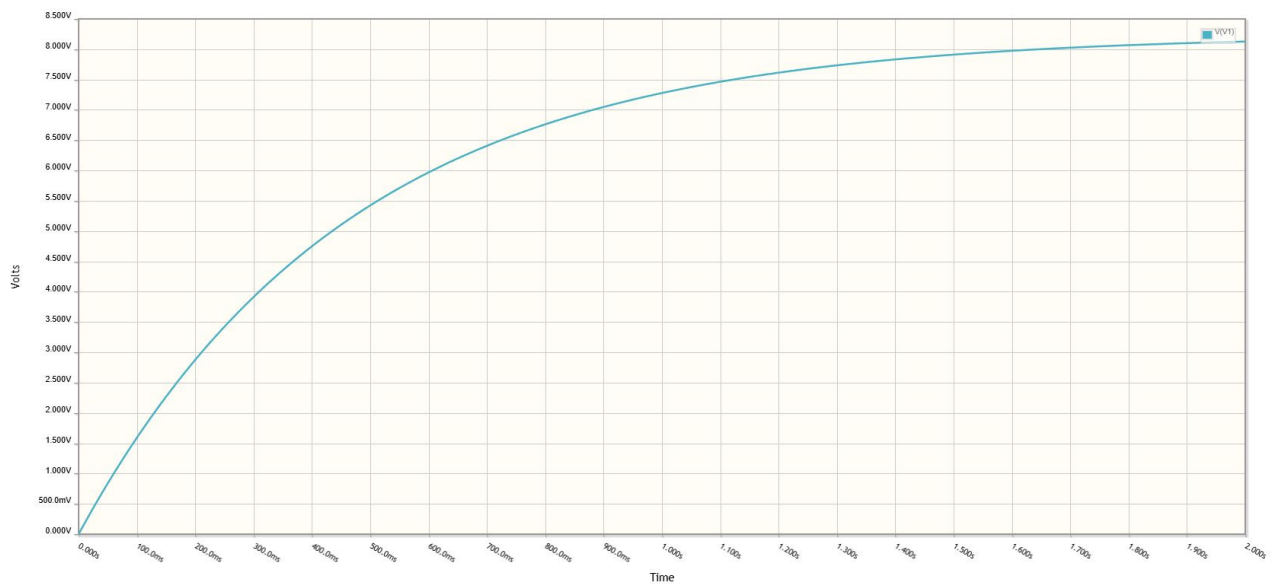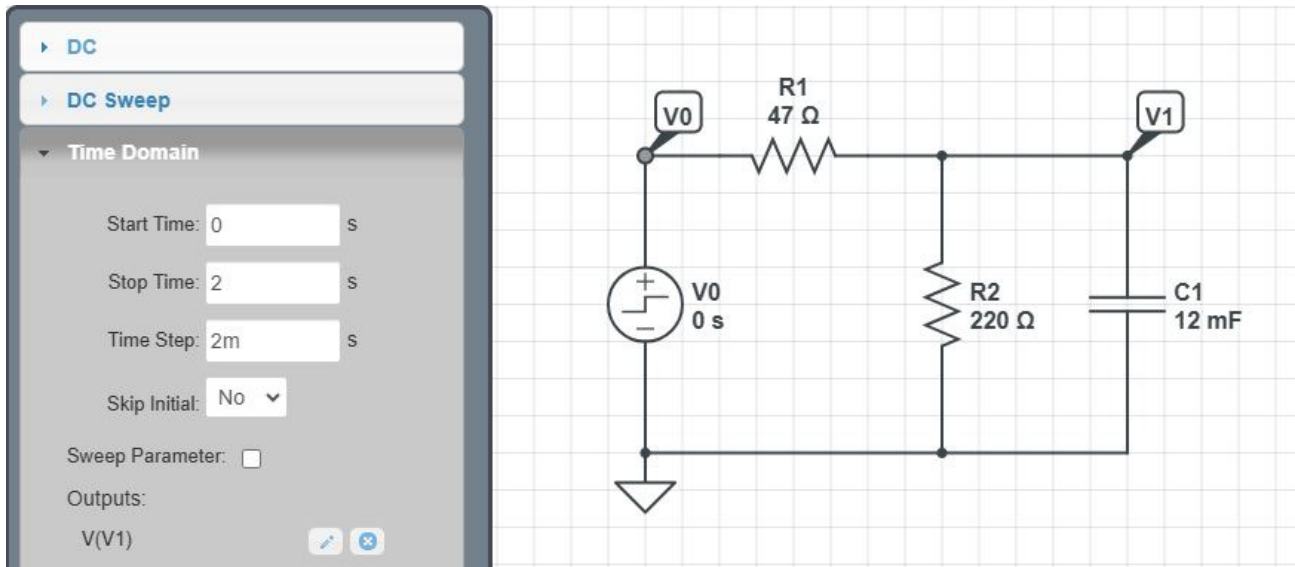4) Find and plot $V_1(t)$ for two seconds using CircuitLab

- Set the simulating time to 2 seconds
- Set the simulation step size to 2ms (1000 points on the plot)


The graph is pretty much the same as we calculated in Matlab



85010-Stage RC Filter

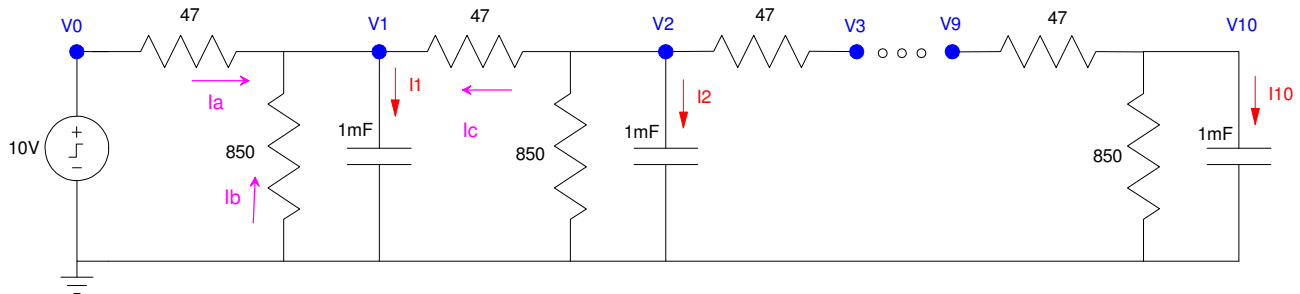5) Write the dynamics for this system as a set of ten coupled differential equations:

$$I_1 = C \frac{dV_1}{dt} = \sum (\text{current to node } V_1)$$



Now, solve ten coupled 1st-order differential equations

- easy in Matlab
- hard by hand

First, write the differential equations. At node V1

$$I_1 = I_a + I_b + I_c$$

$$I_1 = 0.001 \frac{dV_1}{dt} = \left(\frac{V_0 - V_1}{47} \right) + \left(\frac{0 - V_1}{850} \right) + \left(\frac{V_2 - V_1}{47} \right)$$

Simplifying

$$\frac{dV_1}{dt} = 21.277V_0 - 43.73V_1 + 21.277V_2$$

By symmetry, nodes 2..9 are all similar

$$\frac{dV_2}{dt} = 21.277V_1 - 43.73V_2 + 21.277V_3$$

$$\frac{dV_3}{dt} = 21.277V_2 - 43.73V_3 + 21.277V_4$$

$$\frac{dV_4}{dt} = 21.277V_3 - 43.73V_4 + 21.277V_5$$

⋮

The odd-ball is node #10 since there is no current I_c

$$I_{10} = I_a + I_b$$

$$I_{10} = 0.001 \frac{dV_{10}}{dt} = \left(\frac{V_9 - V_{10}}{47} \right) + \left(\frac{0 - V_{10}}{850} \right)$$

$$\frac{dV_{10}}{dt} = 21.277V_9 - 22.453V_{10}$$

Forced Response for a 10-Node RC Filter (heat.m):

6) Using Matlab, solve these ten differential equations for $0 < t < 5$ s assuming

- The initial voltages are zero, and
- $V_0 = 10$ V.

Matlab Code:

```
V = zeros(10,1);
dV = 0*V;

dt = 0.01;
t = 0;
V0 = 10;

DATA = [];


while(t < 5)

    dV(1) = 21.277*V0 - 43.73*V(1) + 21.277*V(2);
    dV(2) = 21.277*V(1) - 43.73*V(2) + 21.277*V(3);
    dV(3) = 21.277*V(2) - 43.73*V(3) + 21.277*V(4);
    dV(4) = 21.277*V(3) - 43.73*V(4) + 21.277*V(5);
    dV(5) = 21.277*V(4) - 43.73*V(5) + 21.277*V(6);
    dV(6) = 21.277*V(5) - 43.73*V(6) + 21.277*V(7);
    dV(7) = 21.277*V(6) - 43.73*V(7) + 21.277*V(8);
    dV(8) = 21.277*V(7) - 43.73*V(8) + 21.277*V(9);
    dV(9) = 21.277*V(8) - 43.73*V(9) + 21.277*V(10);
    dV(10) = 21.277*V(9) - 22.453*V(10);


    V = V + dV * dt;
    t = t + dt;

    plot([0:10], [V0;V], 'b.-');
    ylim([0,12]);
    xlim([0,10]);
    pause(0.01);
    DATA = [DATA ; V'];
end

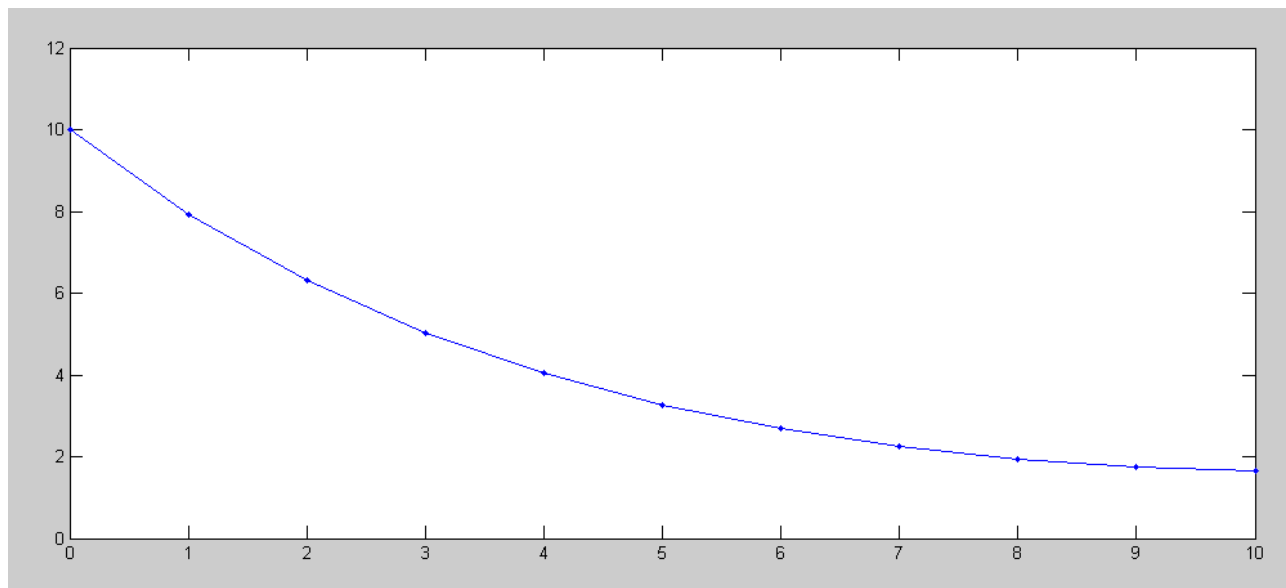pause(2);
t = [1:length(DATA)]' * dt;
plot(t,DATA)
```






Node voltages at $t = 5$ seconds

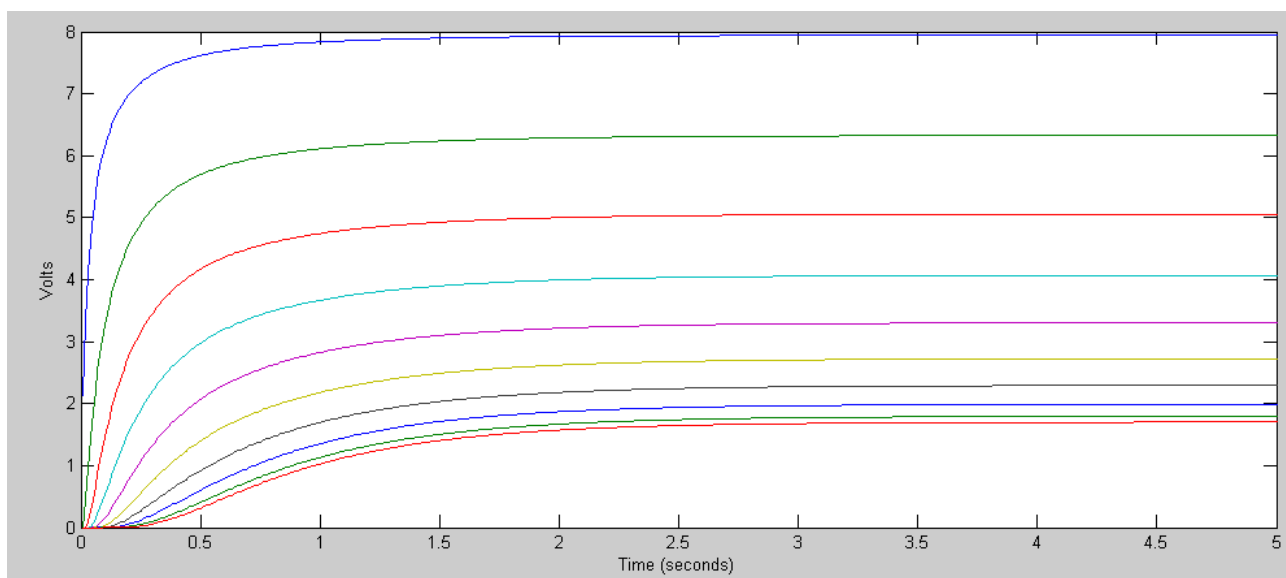

Voltages vs time

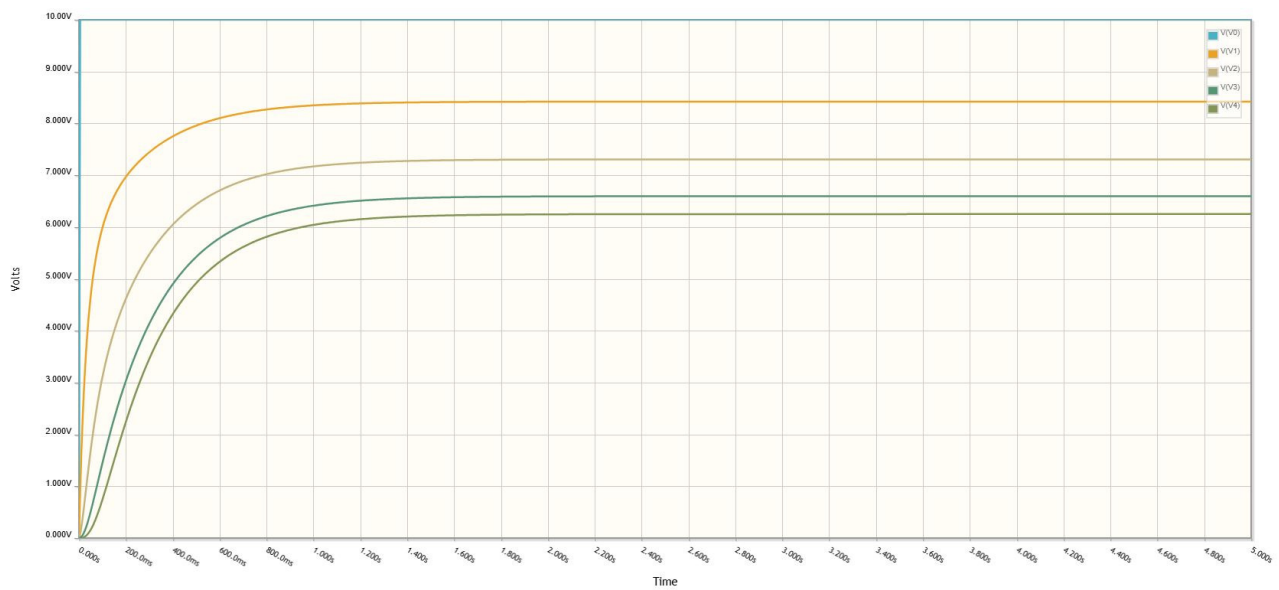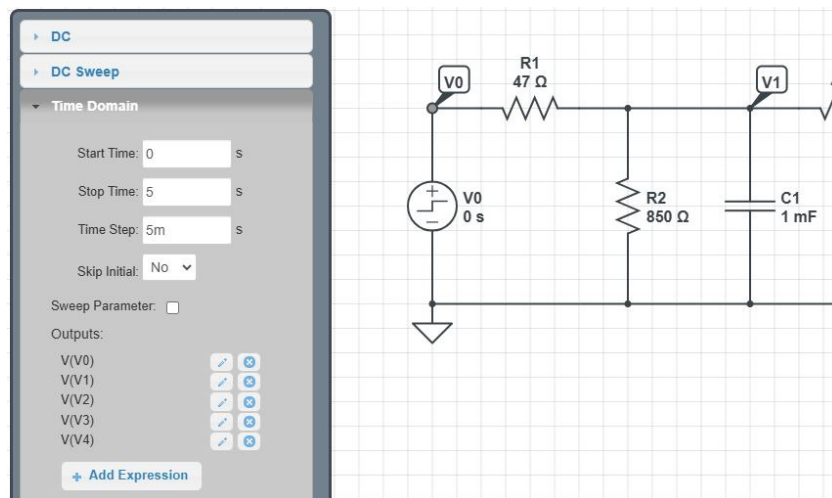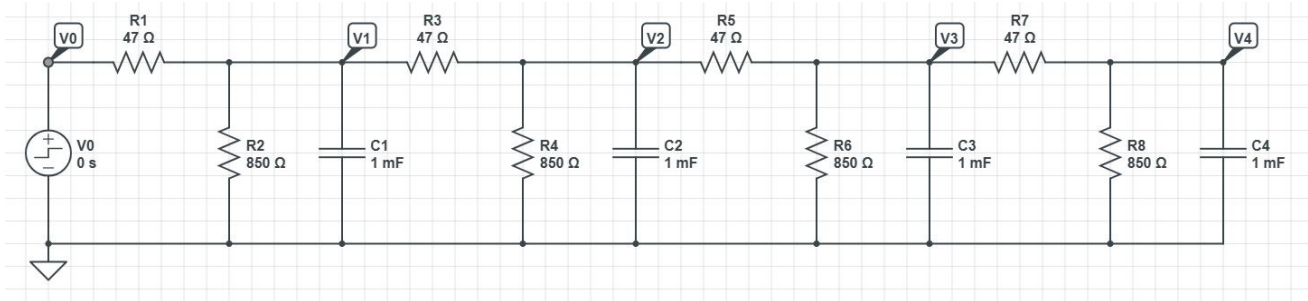7) Using CircuitLab, find the response of this circuit to a 10V step input. *note: It's OK if you only build this circuit to 3 nodes...*



Natural Response: Eigenvectors and Eigenvalues

8) Assume $V_0 = 0V$. Determine the initial conditions of $V_1..V_{10}$ so that

- The maximum voltage is 10V and
- 5a) The voltages go to zero as slow as possible
- 5b) The voltages go to zero as fast as possible.

Simulate the response for these initial conditions in Matlab.

This is an eigenvector problem. Express the dynamics in matrix form

$$\frac{dV}{dt} = AV$$

From before

$$\begin{aligned} dV(1) &= 21.277*V_0 - 43.73*V(1) + 21.277*V(2); \\ dV(2) &= 21.277*V(1) - 43.73*V(2) + 21.277*V(3); \\ dV(3) &= 21.277*V(2) - 43.73*V(3) + 21.277*V(4); \\ dV(4) &= 21.277*V(3) - 43.73*V(4) + 21.277*V(5); \\ dV(5) &= 21.277*V(4) - 43.73*V(5) + 21.277*V(6); \\ dV(6) &= 21.277*V(5) - 43.73*V(6) + 21.277*V(7); \\ dV(7) &= 21.277*V(6) - 43.73*V(7) + 21.277*V(8); \\ dV(8) &= 21.277*V(7) - 43.73*V(8) + 21.277*V(9); \\ dV(9) &= 21.277*V(8) - 43.73*V(9) + 21.277*V(10); \\ dV(10) &= 21.277*V(9) - 22.453*V(10); \end{aligned}$$

In matrix form

$$dV = \begin{bmatrix} -43.73 & 21.28 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 21.28 & -43.73 & 21.28 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 21.28 & -43.73 & 21.28 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 21.28 & -43.73 & 21.28 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 21.28 & -43.73 & 21.28 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 21.28 & -43.73 & 21.28 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 21.28 & -43.73 & 21.28 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 21.28 & -43.73 & 21.28 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 21.28 & -43.73 & 21.28 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 21.28 & -22.453 \end{bmatrix} V$$

This is a 10x10 matrix. It has

- Ten eigenvalues, and
- Ten eigenvectors

(something you'll cover when you take Math 129). With Matlab, you can calculate what these are:

In Matlab, input the 10x10 matrix. Since all terms repeat along the diagonal,

- Start with a 10x10 matrix of zeros (most terms are zero),
- Change the terms along the diagonal

A(10,10) is the odd-ball and is input by itself at the end

```
>> A = zeros(10,10);
>> for i = 1:9
    A(i,i) = -43.73;
    A(i+1,i) = 21.28;
    A(i,i+1) = 21.28;
end
>> A(10,10) = -22.453
```

```
-43.7300    21.2800         0         0         0         0         0         0         0         0
 21.2800   -43.7300    21.2800         0         0         0         0         0         0         0
         0    21.2800   -43.7300    21.2800         0         0         0         0         0         0
         0         0    21.2800   -43.7300    21.2800         0         0         0         0         0
         0         0         0    21.2800   -43.7300    21.2800         0         0         0         0
         0         0         0         0    21.2800   -43.7300    21.2800    21.2800         0         0
         0         0         0         0         0    21.2800   -43.7300    21.2800    21.2800         0
         0         0         0         0         0         0    21.2800   -43.7300    21.2800    21.2800
         0         0         0         0         0         0         0    21.2800   -43.7300    21.2800
         0         0         0         0         0         0         0         0    21.2800   -22.4530
```

Now that A is in Matlab, find the eigenvalues and eivenctors

```
>> [M,V] = eig(A)
```

Eigenvectors

	fast									slow
-0.1286	-0.2459	0.3412	0.4063	0.4352	0.4255	0.3780	0.2969	-0.1894	0.0651	0.0651
0.2459	0.4063	-0.4255	-0.2969	-0.0651	0.1894	0.3780	0.4352	-0.3412	0.1287	0.1287
-0.3412	-0.4255	0.1894	-0.1894	-0.4255	-0.3412	-0.0000	0.3412	-0.4255	0.1894	0.1894
0.4063	0.2969	0.1894	0.4352	0.1287	-0.3412	-0.3780	0.0650	-0.4255	0.2459	0.2459
-0.4352	-0.0651	-0.4255	-0.1287	0.4063	0.1894	-0.3779	-0.2459	-0.3412	0.2969	0.2969
0.4255	-0.1894	0.3412	-0.3412	-0.1894	0.4255	0.0000	-0.4255	-0.1893	0.3413	0.3413
-0.3780	0.3780	-0.0000	0.3780	-0.3780	-0.0000	0.3780	-0.3779	0.0001	0.3780	0.3780
0.2969	-0.4352	-0.3412	0.0650	0.2459	-0.4255	0.3779	-0.1286	0.1894	0.4063	0.4063
-0.1894	0.3412	0.4255	-0.4255	0.3412	-0.1893	-0.0000	0.1894	0.3413	0.4254	0.4254
0.0651	-0.1287	-0.1894	0.2459	-0.2969	0.3412	-0.3780	0.4063	0.4255	0.4351	0.4351

Eigenvalues

```
-84.3992   -78.8948   -70.2658   -59.2791   -46.9108   -34.2599   -22.4504   -12.5318    -5.3853    -1.6459
```

Eigenvalues tell you *how* the system behaves.

- This is a 10th-order system
- It has 10 energy states
- The fast mode decays as $\exp(-84.399t)$
- The slow mode decays as $\exp(-1.645t)$

Eigenvectors tell you *what* behaves that way


- If you make the initial conditions the fast eigenvector, the states decay as $\exp(-84.399t)$
- If you make the initial conditions the slow eigenvector, the states decay as $\exp(-1.64t)$

Try this in Matlab

Fast Mode:

```
V = 20*M(:,1);  
dV = 0*V;  
  
dt = 0.001;  
t = 0;  
V0 = 0;  
  
DATA = [];  
  
while(t < 0.5)  
  
    dV(1) = 21.277*V0 - 43.73*V(1) + 21.277*V(2);  
    dV(2) = 21.277*V(1) - 43.73*V(2) + 21.277*V(3);
```

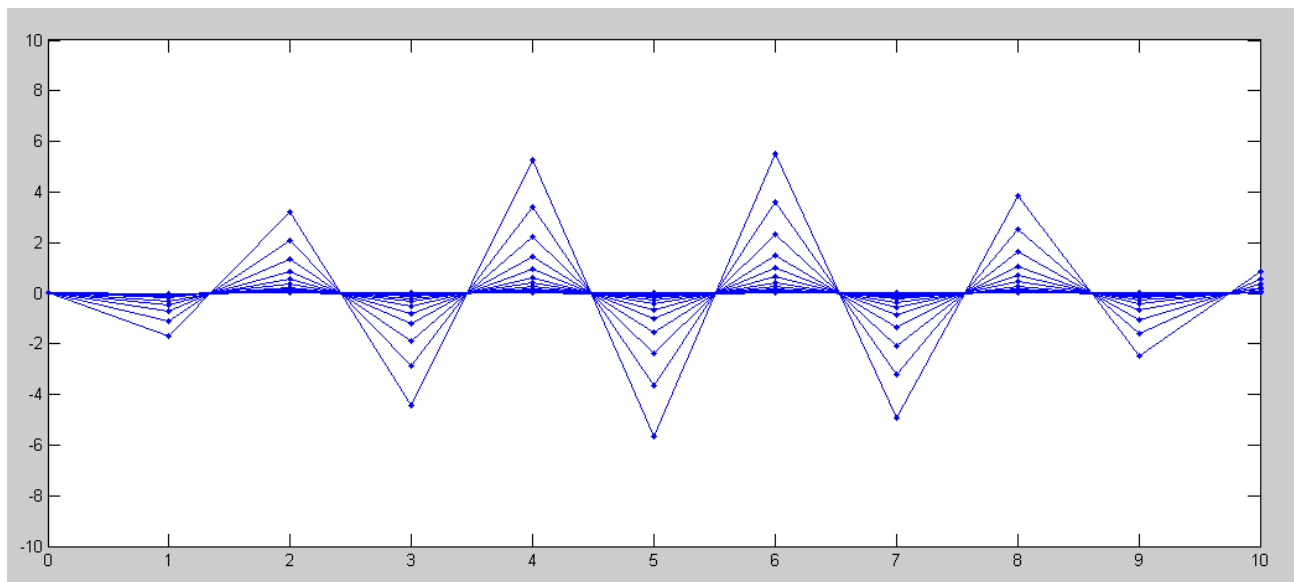This is the fast mode - it decays as $\exp(-84.39t)$



The shape as it decays (show up better in the video)

- The shape remains the same (the shape is the eigenvector)


The amplitude decays as $\exp(-83.39t)$

- The amplitude is the eigenvalue

Slow Mode

```
v = 20*M(:,10);  
dV = 0*v;  
  
dt = 0.01;  
t = 0;  
v0 = 0;  
  
DATA = [];  
  
while(t < 0.5)  
    dV(1) = 21.277*v0 - 43.73*v(1) + 21.277*v(2);  
    dV(2) = 21.277*v(1) - 43.73*v(2) + 21.277*v(3);  
    :  
end
```

This decays as $\exp(-1.64t)$

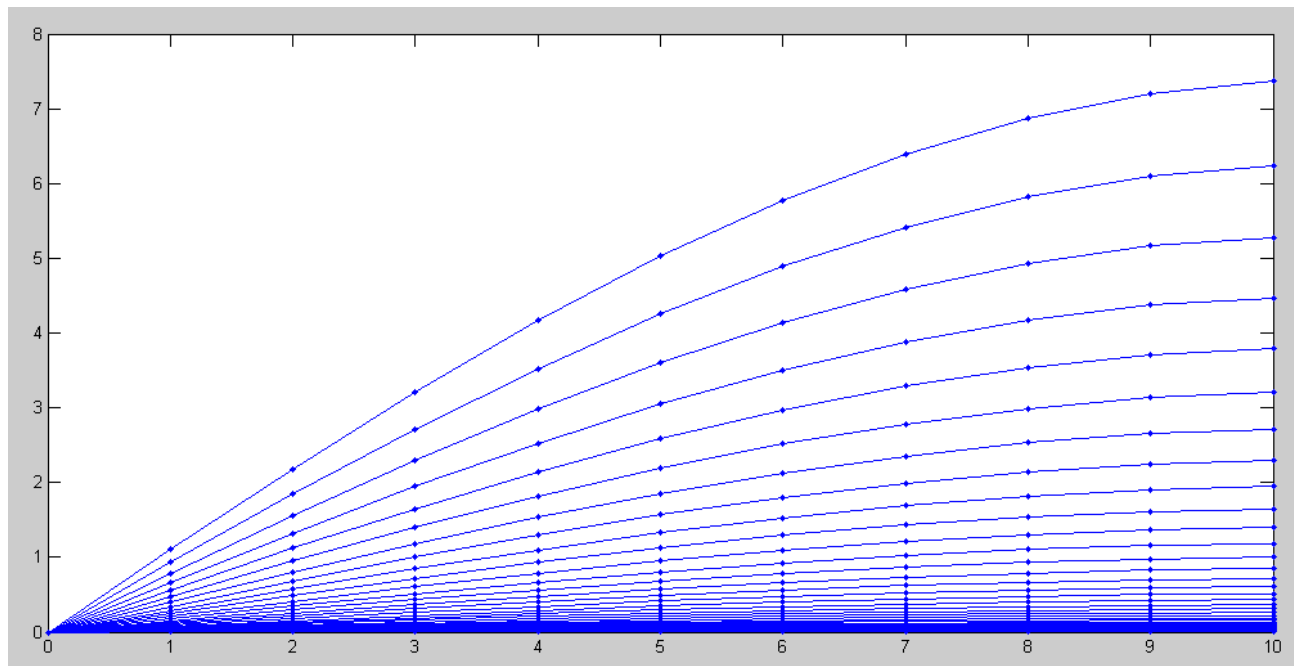

Note the shape remains the same as it runs

- The shape is the eigenvector


The amplitude decays as $\exp(-1.64t)$

- The amplitude is the eigenvalue

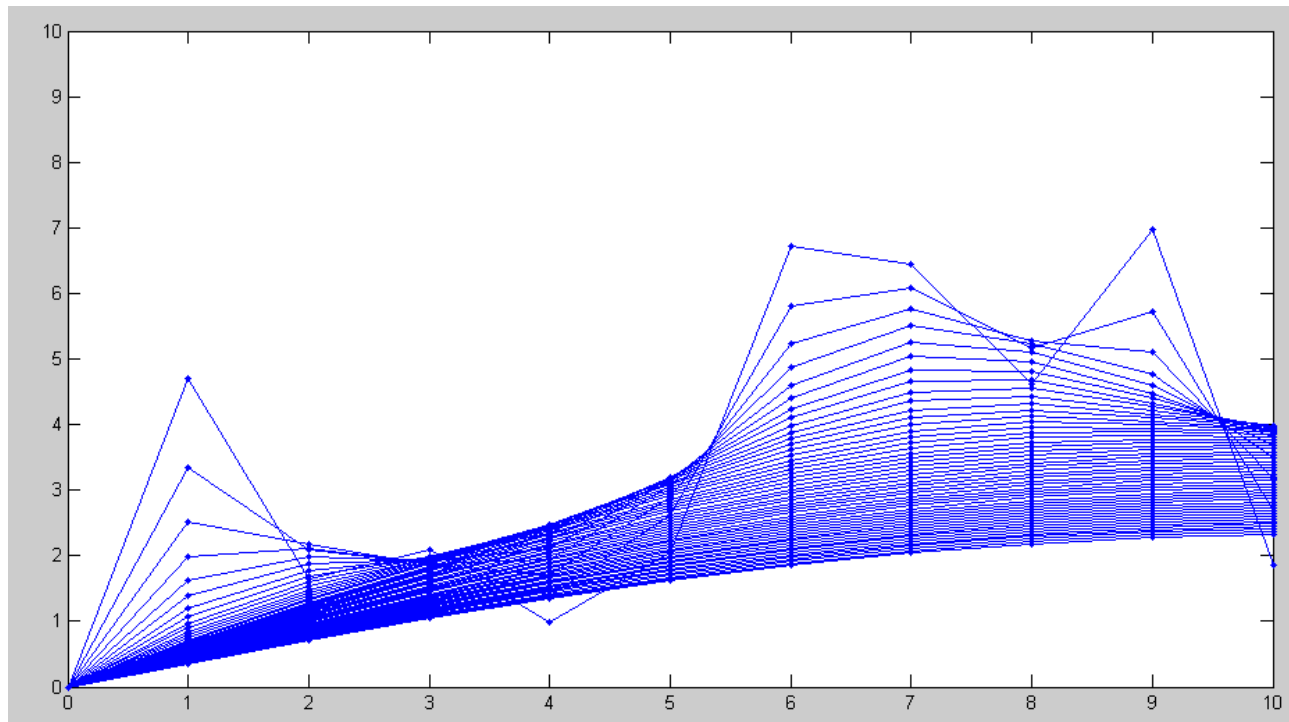9) Assume $V_{in} = 0V$. Pick random voltages for $V_1 \dots V_{10}$ in the range of (0V, 10V):

```
V = 10 * rand(10,1)
```

Plot the voltages at $t = 2$. Which eigenvector does it look like?



Voltages plotted every 10ms

Random initial conditions excite all ten eigenvectors

- The fast modes decay quickly
- Leaving the slow (dominant) mode

After 2 seconds, all that's left is the slow eigenvector

Comment: Very few people understand eigenvalues. Even fewer understand eigenvectors.

It helps to have something concrete to refer to when trying to understand a difficult concept.

When you take Linear Algebra, you'll cover eigenvalues and eigenvectors - and most of the class will be lost. When you get to Linear Algebra, think about this problem and the heat equation. Just remember:

- *Eigenvalues tell you how a system behaves (how each mode behaves)*
- *Eigenvectors tell you what behaves that way (the shape of the modes)*

If you make the initial conditions an eigenvector, only that one mode is excited

If you make the initial conditions something random, all of the modes get excited

- *The fast modes decay quickly, the slow modes decay slowly*

When you get to Linear Algebra and need to find eigenvalues and eigenvectors, think Matlab.