


ECE 111 - Homework #13

ECE 311 Circuits II - Phasors
Due Monday, April 21st. Please submit via email or on BlackBoard

Phasor Voltages

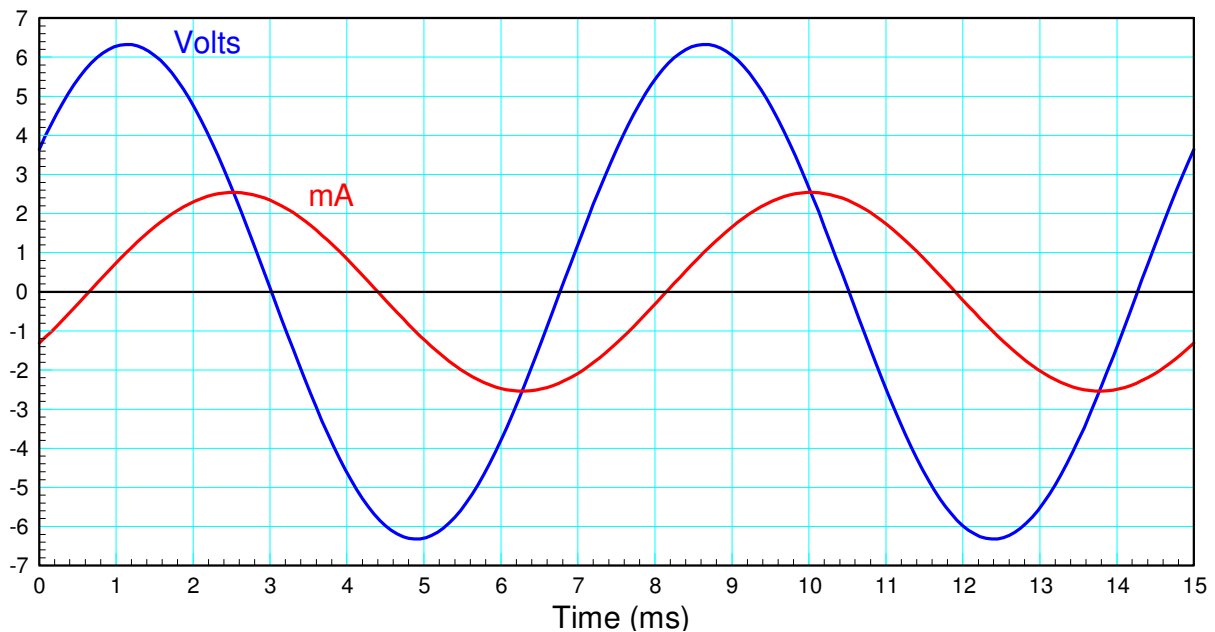1) Express V and I as phasors (i.e. as complex numbers)

- From this, determine the impedance, $Z = V/I$



Voltage:

- Peak = 6.2
- Delay = 1.2ms
- Period = 7.5ms

$$\theta = -\left(\frac{1.2\text{ms}}{7.5\text{ms}}\right) 360^\circ = -57.6^\circ$$

$$V = 6.2 \angle -57.6^\circ \text{ Volts}$$

Current

- Peak = 2.5mA
- Delay = 2.5ms
- Period = 7.5ms

$$\theta = -\left(\frac{2.5\text{ms}}{7.5\text{ms}}\right) 360^\circ = -120^\circ$$

$$I = 2.5 \angle -120^\circ \text{ mA}$$

The impedance is then

$$Z = \frac{V}{I}$$

$$Z = \left(\frac{6.2 \angle -57.6^\circ}{0.0025 \angle -120^\circ} \right)$$


$$Z = 2680 \angle 62.4^\circ$$

or if you prefer rectangular form

$$Z = 1241.63 + j2375.02$$

Phasor Impedances

2) Determine the impedance, Z_{ab}

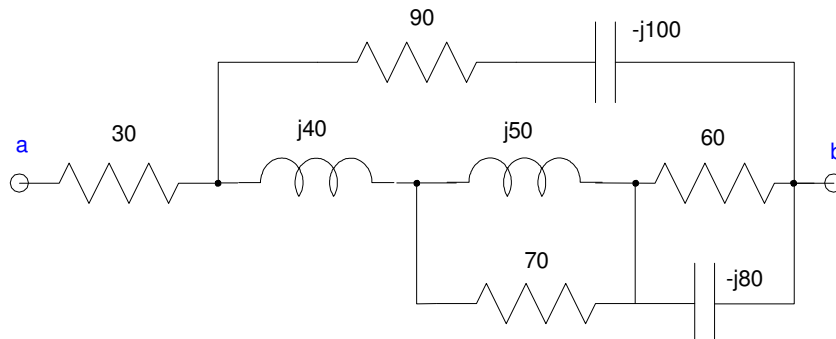


In Matlab

```
>> Z1 = 1 / (1/60 + 1/(-80i))  
Z1 = 38.4000 -28.8000i  
  
>> Z2 = 1 / (1/(50i) + 1/70)  
Z2 = 23.6486 +33.1081i  
  
>> Z3 = Z1 + Z2  
Z3 = 62.0486 + 4.3081i  
  
>> Z4 = Z3 + 40i  
Z4 = 62.0486 +44.3081i  
  
>> Z5 = 1 / (1/Z4 + 1/(90-100i))  
Z5 = 62.7860 + 8.4153i  
  
>> Z6 = Z5 + 30  
Z6 = 92.7860 + 8.4153i
```

With a Free42 calculator

60	0
1/x	enter
0	40
enter	complex
-80	+
complex	1/x
1/x	90
+	enter
1/x	-100
70	complex
1/x	1/x
0	+
enter	1/x
50	30
complex	+
1/x	
+	
1/x	

3) Determine the impedance, Z_{ab}

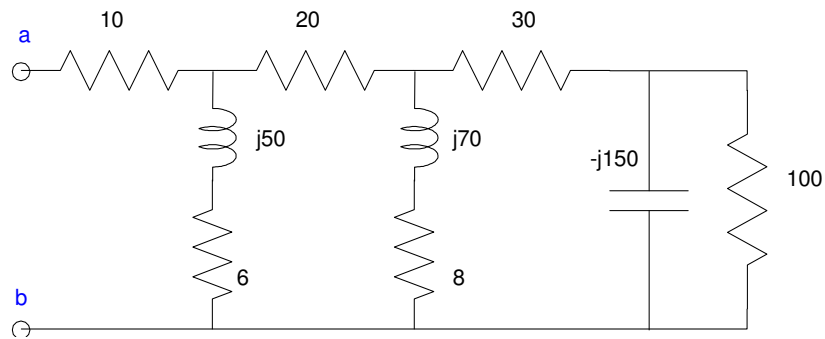

In Matlab

```
>> Za = 1 / (1/100+ 1/(-150i))
Za = 69.2308 -46.1538i

>> Zb = Za + 30
Zb = 99.2308 -46.1538i

>> Zc = 1 / ( 1/Zb + 1/(8+70i) )
Zc = 48.7605 +50.4908i

>> Zd = 20 + Zc
Zd = 68.7605 +50.4908i


>> Ze = 1 / ( 1/Zd + 1/(6+50i) )
Ze = 13.8990 +31.3568i

>> Zab = Ze + 10
Zab = 23.8990 +31.3568i
```

With a Free42 Calculator

100	20
1/x	+
0	1/x
enter	6+50i
-150	1/x
complex	+
1/x	1/x
+	10
1/x	+
30	
+	
1/x	
8	
enter	
70	
complex	
1/x	
+	
1/x	

Voltage Nodes with Phasors

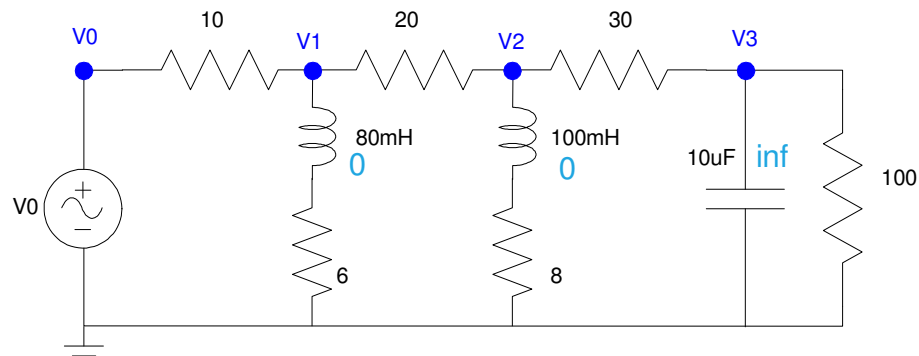

4) Assume $V_0 = 10$.

a) Determine the impedances of each element at 0 rad/sec

- Inductors are zero Ohms at DC
- Capacitors are infinite Ohms at DC

b) Write the voltage node equations

$$V_0 = 10$$

$$\left(\frac{V_1 - V_0}{10} \right) + \left(\frac{V_1}{6} \right) + \left(\frac{V_1 - V_2}{20} \right) = 0$$

$$\left(\frac{V_2 - V_1}{20} \right) + \left(\frac{V_2}{8} \right) + \left(\frac{V_2 - V_3}{30} \right) = 0$$

$$\left(\frac{V_3 - V_2}{30} \right) + \left(\frac{V_3}{\infty} \right) + \left(\frac{V_3}{100} \right) = 0$$

you can leave out the term that divides by infinity. This current is zero.

c) Solve for V_1 , V_2 , and V_3 .

Group terms

$$V_0 = 10$$

$$-\left(\frac{1}{10} \right) V_0 + \left(\frac{1}{10} + \frac{1}{6} + \frac{1}{20} \right) V_1 - \left(\frac{1}{20} \right) V_2 = 0$$

$$-\left(\frac{1}{20} \right) V_1 + \left(\frac{1}{20} + \frac{1}{8} + \frac{1}{30} \right) V_2 - \left(\frac{1}{30} \right) V_3 = 0$$

$$-\left(\frac{1}{30} \right) V_2 + \left(\frac{1}{30} + \frac{1}{100} \right) V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{10}\right) & \left(\frac{1}{10} + \frac{1}{6} + \frac{1}{20}\right) & \left(\frac{-1}{20}\right) & 0 \\ 0 & \left(\frac{-1}{20}\right) & \left(\frac{1}{20} + \frac{1}{8} + \frac{1}{30}\right) & \left(\frac{-1}{30}\right) \\ 0 & 0 & \left(\frac{-1}{30}\right) & \left(\frac{1}{30} + \frac{1}{100}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve using Matlab

```
>> a1= [1,0,0,0];
>> a2 = [-1/10, 1/10+1/6+1/20,-1/20,0];
>> a3 = [0,-1/20,1/20+1/8+1/30,-1/30];
>> a4 = [0,0,-1/30,1/30+1/100];
>> A = [a1;a2;a3;a4]
```

```
    1.0000         0         0         0
   -0.1000    0.3167   -0.0500         0
         0   -0.0500    0.2083   -0.0333
         0         0   -0.0333    0.0433
```

```
>> B = [10;0;0;0]
```



```
    10
     0
     0
     0
```

```
>> V = inv(A)*B
```

```
v0    10.0000
v1     3.3005
v2     0.9033
v3     0.6948
```

Note: Hand calculators work pretty well when dealing with one equation and one unknown. They really struggle when dealing with N equations and N unknowns. That's where Matlab shines.

5) Check your results in CircuitLab

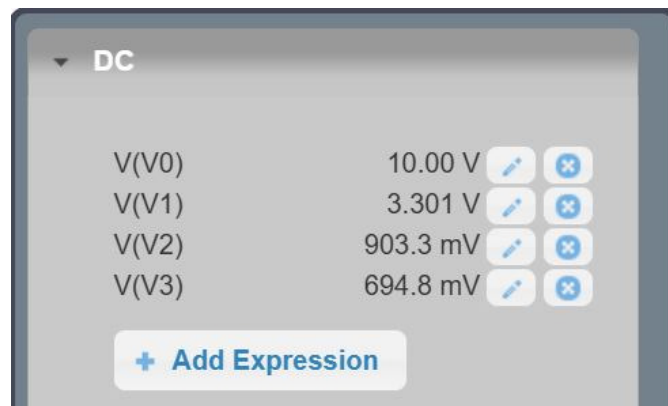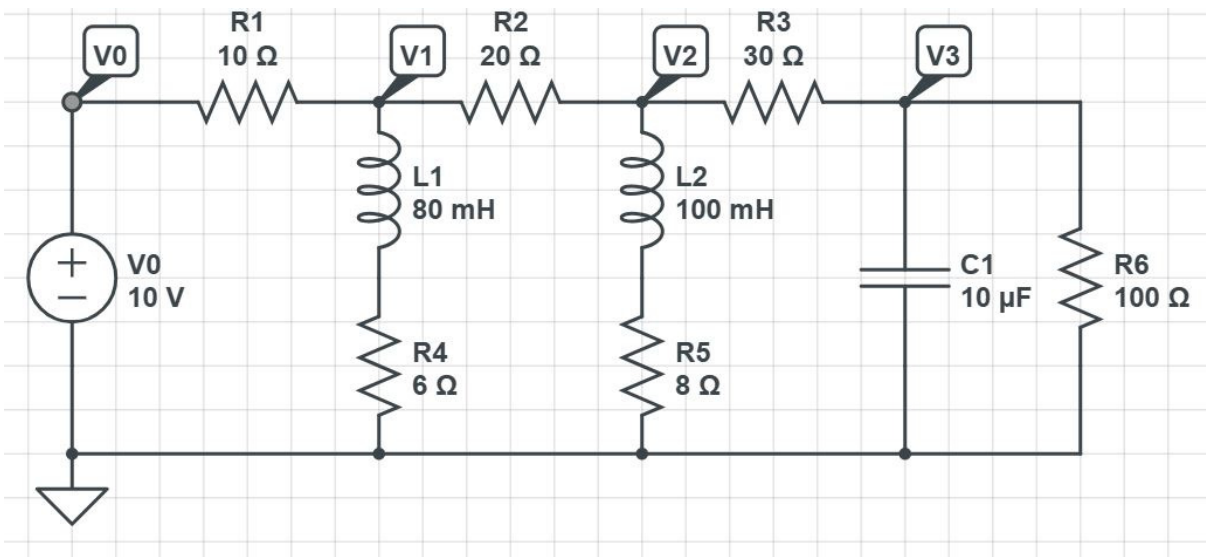


This matches previous calculations

```
>> V = inv(A) * B
```

v0	10.0000
v1	3.3005
v2	0.9033
v3	0.6948

6) Assume $V_0 = 10 \sin(628t)$

10V, 628 rad/sec sine wave (100Hz)

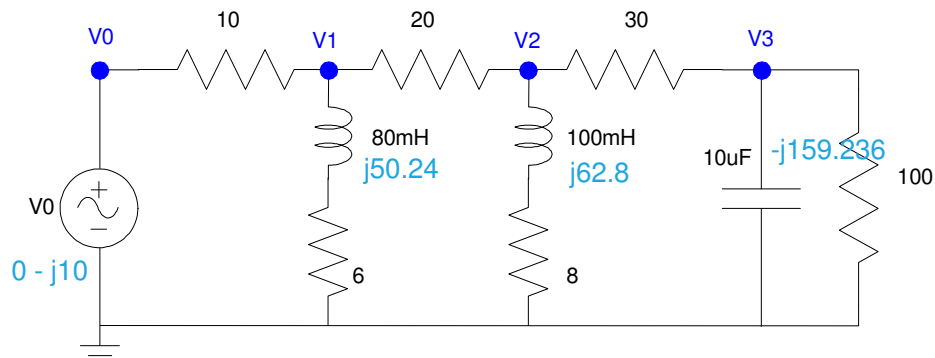

a) Determine the impedances of each element at 628 rad/sec

80mH:

$$Z = j\omega L = j \cdot 628 \cdot 0.08$$

$$Z = j50.24\Omega$$

100mH

$$Z = j\omega L = j62.8\Omega$$

10uF

$$Z = \frac{1}{j\omega C} = -j159.236\Omega$$

V0

$$V = 0 - j10$$

real = cosine

-imag = sine

b) Write the voltage node equations

same as we had at DC, only now with complex numbers

$$V_0 = 0 - j10$$

$$\left(\frac{V_1 - V_0}{10} \right) + \left(\frac{V_1}{6 + j50.24} \right) + \left(\frac{V_1 - V_2}{20} \right) = 0$$

$$\left(\frac{V_2 - V_1}{20} \right) + \left(\frac{V_2}{8 + j62.8} \right) + \left(\frac{V_2 - V_3}{30} \right) = 0$$

$$\left(\frac{V_3 - V_2}{30} \right) + \left(\frac{V_3}{-j159.236} \right) + \left(\frac{V_3}{100} \right) = 0$$

c) Solve for V1, V2, and V3 as complex numbers

Group terms

$$V_0 = -j10$$

$$-\left(\frac{1}{10}\right)V_0 + \left(\frac{1}{10} + \frac{1}{6+j50.24} + \frac{1}{20}\right)V_1 - \left(\frac{1}{20}\right)V_2 = 0$$

$$-\left(\frac{1}{20}\right)V_1 + \left(\frac{1}{20} + \frac{1}{8+j62.8} + \frac{1}{30}\right)V_2 - \left(\frac{1}{30}\right)V_3 = 0$$

$$-\left(\frac{1}{30}\right)V_2 + \left(\frac{1}{30} + \frac{1}{100} + \frac{1}{-j159.236}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{10}\right) & \left(\frac{1}{10} + \frac{1}{6+j50.24} + \frac{1}{20}\right) & \left(\frac{-1}{20}\right) & 0 \\ 0 & \left(\frac{-1}{20}\right) & \left(\frac{1}{20} + \frac{1}{8+j62.8} + \frac{1}{30}\right) & \left(\frac{-1}{30}\right) \\ 0 & 0 & \left(\frac{-1}{30}\right) & \left(\frac{1}{30} + \frac{1}{100} + \frac{1}{-j159.236}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -j10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve using Matlab

```
a1= [1,0,0,0];
a2 = [-1/10, 1/10+1/(6+50.24i)+1/20,-1/20,0];
a3 = [0,-1/20,1/20+1/(8+62.8i)+1/30,-1/30];
a4 = [0,0,-1/30,1/30+1/100+1/(-159.236i)];
```

```
A = [a1;a2;a3;a4]
```

```
1.0000      0      0      0
-0.1000    0.1523 - 0.0196i -0.0500      0
      0    -0.0500    0.0853 - 0.0157i -0.0333
      0      0    -0.0333    0.0433 + 0.0063i
```

```
>> B = [-10i;0;0;0]
```

```
0 -10.0000i
0
0
0
```

```
>> V = inv(A)*B
```

```
V0      0 -10.0000i
V1    2.0597 - 8.3895i
V2    2.9829 - 6.3703i
V3    1.5518 - 5.1251i
```

d) Express V1, V2, and V3 in terms of sine and cosine function:



$$\begin{aligned}V_0 &= 0 \cos(628t) + 10.0000 \sin(628t) \\V_1 &= 2.0597 \cos(628t) + 8.3895 \sin(628t) \\V_2 &= 2.9829 \cos(628t) + 6.3703 \sin(628t) \\V_3 &= 1.5518 \cos(628t) + 5.1251 \sin(628t)\end{aligned}$$

Note: Hand calculators struggle when dealing with N equations and N unknowns with real numbers. They *really* struggle when dealing with N equations and N unknowns with complex numbers. This is where Matlab *really* shines. Matlab has no problem dealing with complex numbers. Matlab has no problem dealing with N equations and N unknowns.

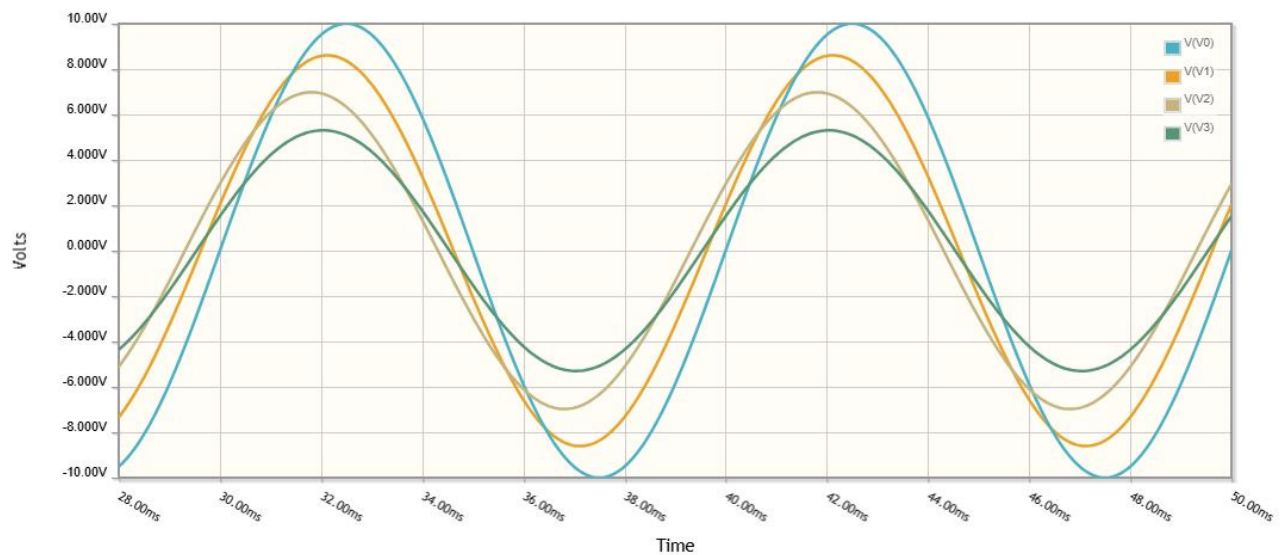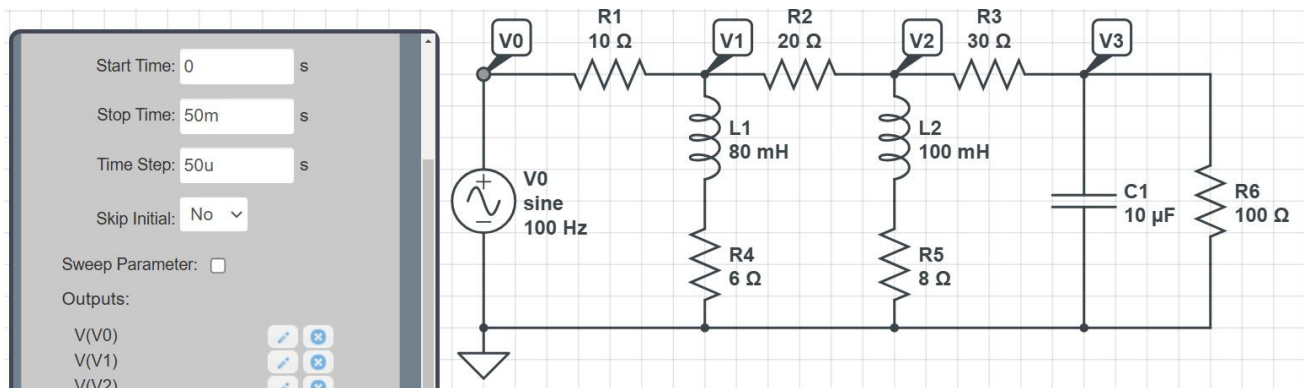7) Check your results in CircuitLab using a transient simulation for 50ms (time step = 50us).

The amplitude matches calculations

```
>> abs(V)
V0 10.0000
V1 8.6387
V2 7.0341
V3 5.3549
```



The CircuitLab results match calculations from Matlab

Peak Voltage	V0	V1	V2	V3
Matlab	10.000	8.6387	7.0341	5.3549
CircuitLab	10.000	8.545	6.922	5.326