

# Diodes, & Transistors

## Introduction

In ECE 401, you can choose from a dozen different circuits to build. Regardless of which one you select, your overall design:

- Must operate at 5VDC
- Must have LEDs operating at 20mA +/- 5mA
- Must have one NPN and one PNP transistor (or more), capable of driving a 100mA load
- Must have at least one IC (Raspberry Pi Pico, MCP602 op-amp, 555 timer)

This lecture covers:

- Analysis and design of LED circuits, and
- Analysis and design of NPN and PNP electronic switches,


Transistors can also be used as amplifiers in analog circuits, but this is left for ECE 320.

## Diodes

A diode is a semiconductor device made up of a pn junction (covered in ECE 320 Electronics I). Diodes act as valves:

- Current can flow from the anode to the cathode,
- Current is blocked if it tries to flow from the cathode to the anode.

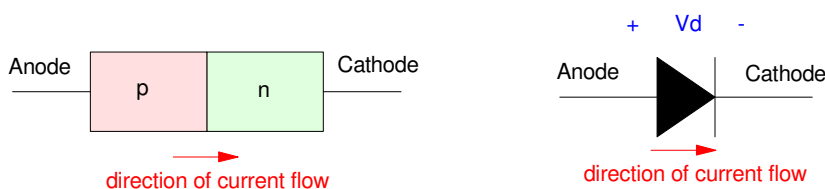Because of this, the symbol for a diode looks like an arrow: this arrow serves as a reminder for which way the current can flow.




Symbol for a diode: Diodes only allow current to flow from the anode to the cathode

The VI characteristics of diodes are highly nonlinear. This makes analysis of diode circuits very difficult. To simplify circuit analysis, *ideal diode* models are usually used. This model approximates the nonlinear characteristic with two linear models:

- $I_d = 0$  when  $V_d < V_f$
- $V_d = V_f$  when  $I_d > 0$

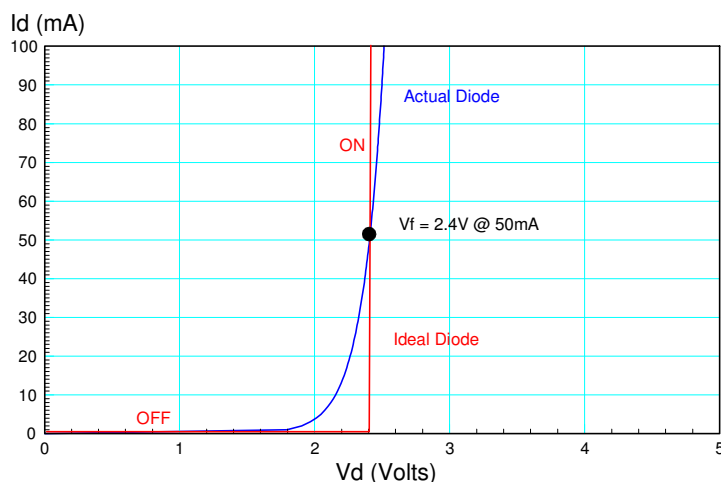While not perfect, the ideal diode model usually gives results which are close enough for most purposes. For more accurate results, nonlinear circuit simulators, such as CircuitLab, can be used.



To simplify circuit analysis, the nonlinear diode VI characteristics (blue) are replaced with an ideal diode model (red)

$V_f$  acts like a turn-on voltage:

- If you try to apply more than  $V_f$  volts across the diode, it turns on.
- If you apply less than  $V_f$  volts across the diode, it turns off.

The value of  $V_f$  depends upon the diode. Some typical values are:


- Germanium Diode:  $V_f = 0.3V$
- Silicon Diode:  $V_f = 0.7V$
- Red LED:  $V_f = 1.9V$
- Yellow LED:  $V_f = 2.0V$
- Green LED:  $V_f = 2.0V$  (sometimes  $3.0V$  - depends upon the LED)

For example, take the following circuit: a source driving a  $1k$  resistor through a diode.

In CircuitLab, you can build this circuit through drag and drop.

- R rotates the element
- Double Click to change values
- k = 1000
- M = million
- m = milli
- u = micro

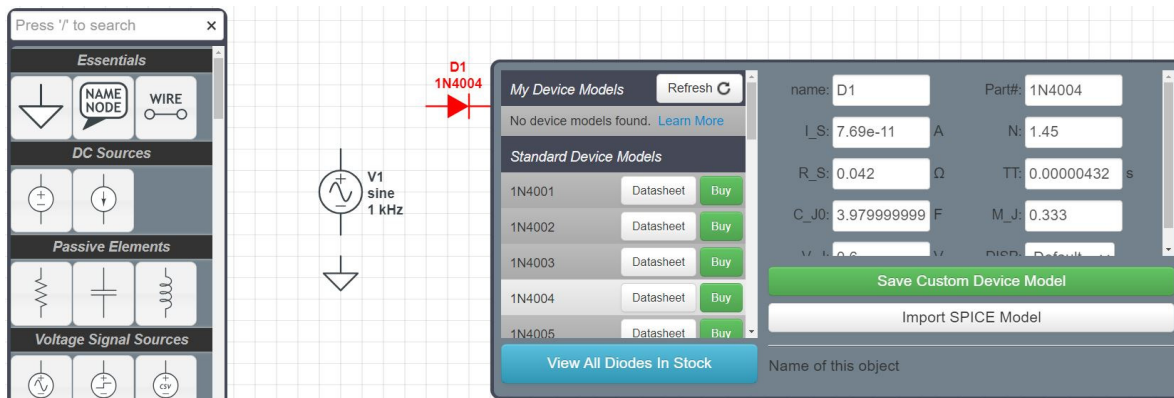
Make sure you have a ground (CircuitLab insists on this)



CircuitLab: Double Click to change a component


Once completed, you can determine the voltages and currents by

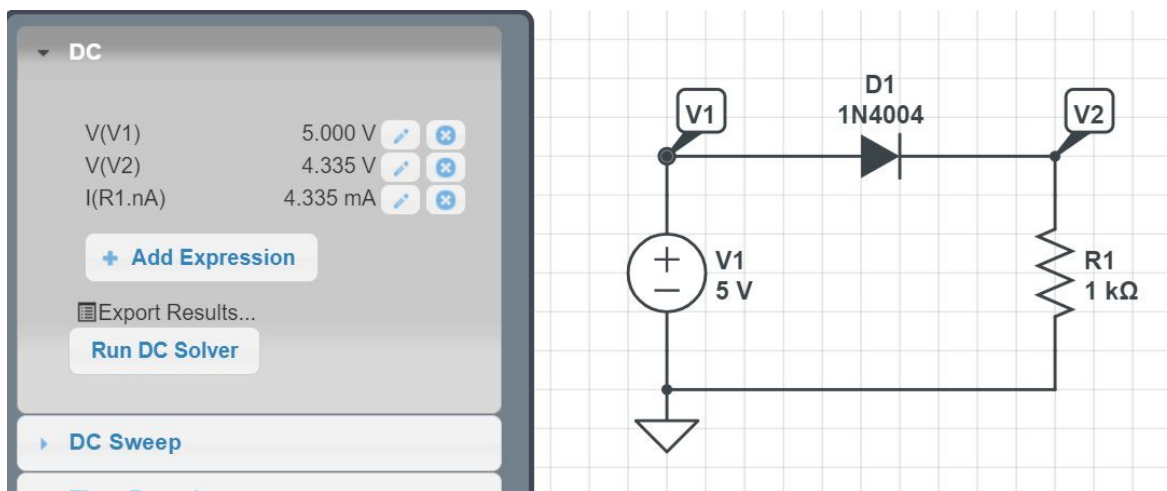- Clicking on Add Expression and then click on the voltage node to see that voltage
- Click on one side of a resistor to see the current through that resistor:



DC Analysis in CircuitLab: Diode D1 turns on and has a 0.7V drop across it (roughly).

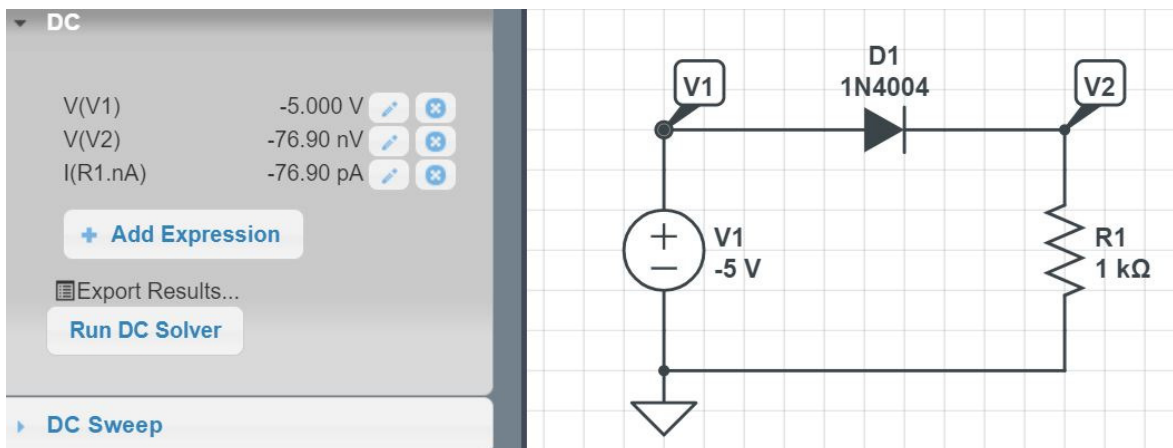As expected, the diode is turned on with a 0.7V drop across it (approximately). If you apply -5V instead, the diode turns off and the current is approximately zero:



The diode turns off when you try to push current backwards through the diode


Note that when V1 is less than 0.7V,

- The diode turns off
- V2 = 0V (approximately), and
- I = 0 (approximately).

Diodes *do* allow some current when reverse biased, 76.9pA in this case. In this class were we deal with mA, that current is negligible.


Another way to see diodes acting like a valve is to make V1 a 5Vp sine wave. In CircuitLab, if you run an AC transient simulation, you can see the voltage at V2 (similar to what you'd see on an oscilloscope). To do this

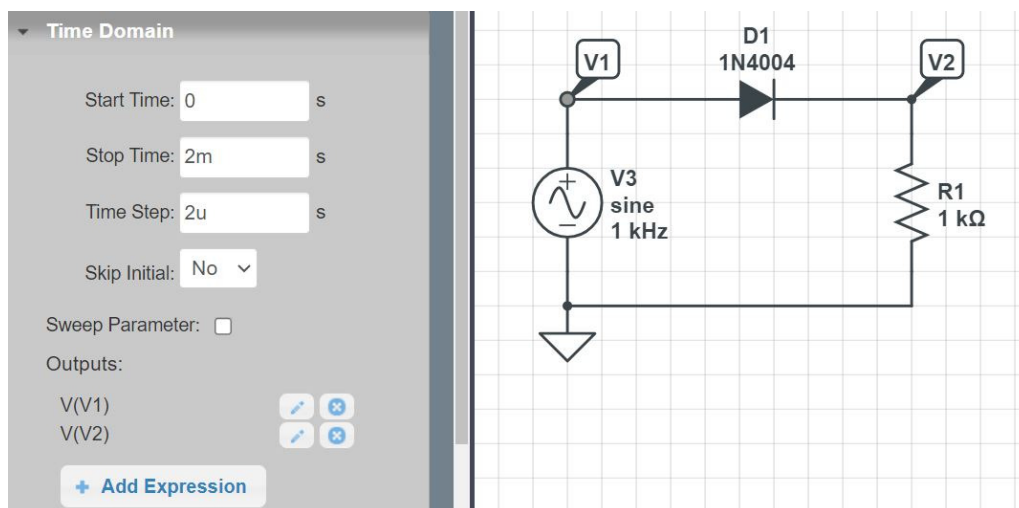- Specify the start and stop time. For a 1kHz sine wave, 2ms cover two cycles
- Specify the time step. I usually make this 1000x smaller than the stop time, giving 1000 points



Time-Domain Simulation in CircuitLab

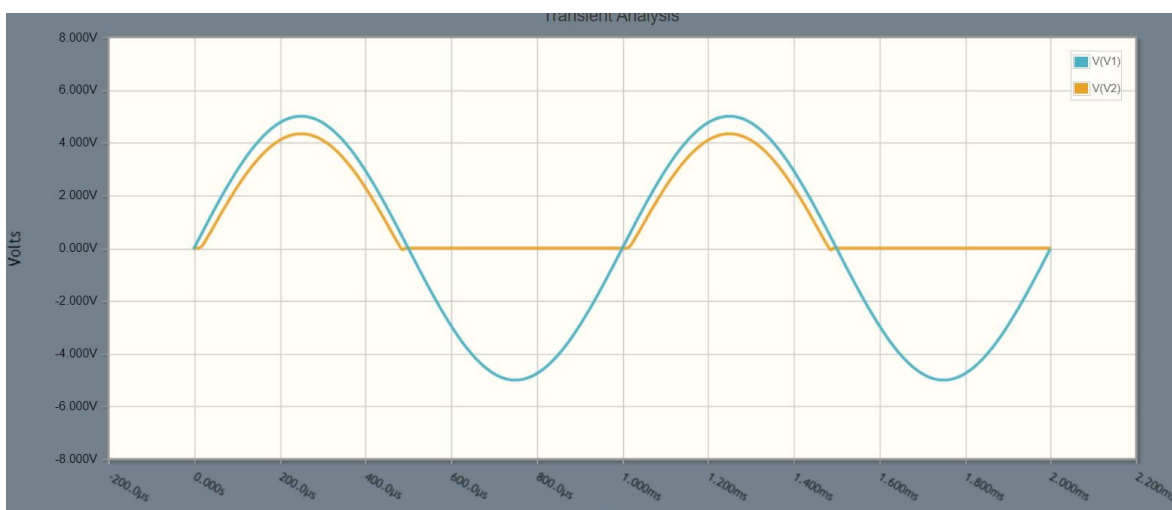When you press Run Time-Domain Simulation, a graph appears showing the voltages:



Result of a Time-Domain Simulation

Note:


- There is a lot more information in a graph than a number (oscilloscopes tell you more than multimeters)
- When  $V1 > 0.7V$  (ish), the diode turns on and  $V2 = V1 - 0.7$
- When  $V1 < 0.7V$ , the diode turns off and  $V2 = 0$  (ish)

The diode is acting like a valve.

**Diode Circuit Analysis:** To analyze a circuit with a diode, you first have to determine whether the diode is on or off. This can be a bit of guesswork. If you guess correctly, the circuit will work, meaning

- Diodes which are on have  $I_d > 0$ , and
- Diodes which are off have  $V_d < V_f$

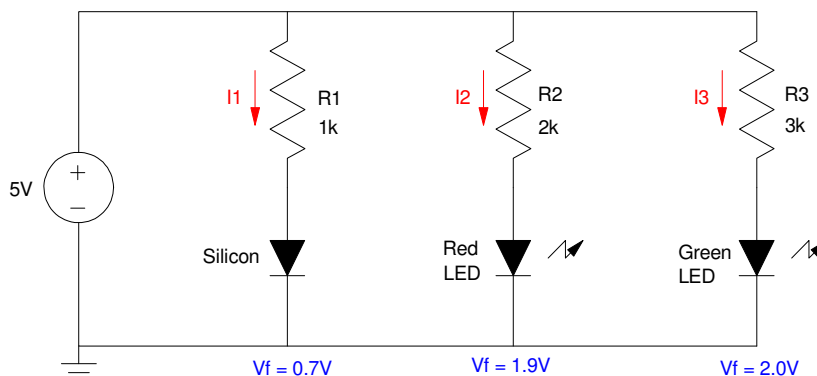For example, determine the current through each diode for the following circuit:



Diode Circuit: Determine the current in each diode

In this case, the diodes have to be on since  $5V > V_f$  for each diode. So, assume they are on.

The current can then be found as

$$I_1 = \left( \frac{5V - 0.7V}{1k} \right) = 4.3mA$$

$$I_2 = \left( \frac{5V - 1.9V}{2k} \right) = 1.55mA$$


$$I_3 = \left( \frac{5V - 2.0V}{3k} \right) = 1.00mA$$

**Diode Circuit Design:** If you want to change the current through the diodes, change the resistor connected to it. For example, to set all three currents to 20mA

$$R_1 = \left( \frac{5V - 0.7V}{20mA} \right) = 215\Omega$$

$$R_2 = \left( \frac{5V - 1.9V}{20mA} \right) = 155\Omega$$
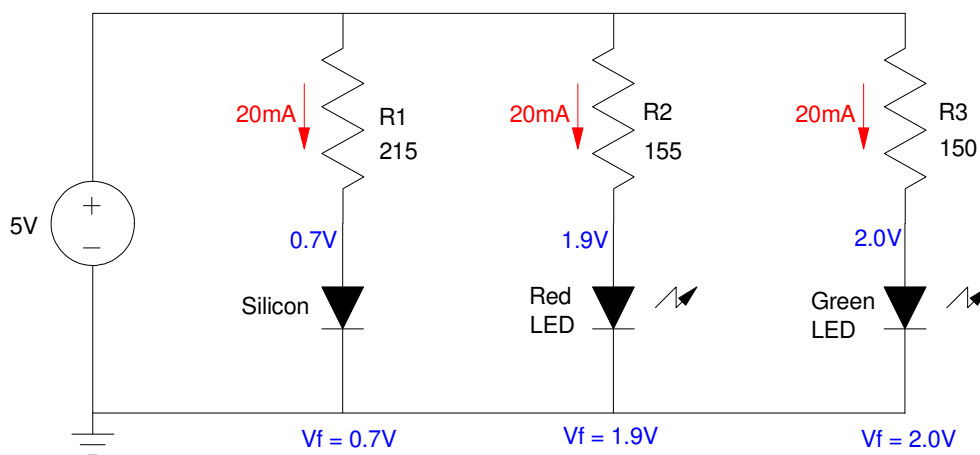
$$R_3 = \left( \frac{5V - 2.0V}{20mA} \right) = 150\Omega$$



Resistors adjusted so that 20mA flows through each diode

## Light Emitting Diodes (LEDs)

LEDs are nothing more than diodes - except that they produce light proportional to the current flowing through them. As diodes, they can be approximated with an ideal-diode model:

- $I_d = 0$  if  $V_d < V_f$
- $V_d = V_f$  if  $I_d > 0$

The on-voltage ( $V_f$ ) depends upon the diode and is usually specified in the diode's data sheets:

| LED    | $V_f$       | mcd           | Wavelength | Cost   | Digikey PN  |
|--------|-------------|---------------|------------|--------|-------------|
| Red    | 1.9V @ 20mA | 30mcd @ 20mA  | 645nm      | \$0.13 | 732-5016-ND |
| Yellow | 2.0V @ 20mA | 450mcd @ 20mA | 592nm      | \$0.18 | 732-5018-ND |
| Green  | 2.1V @ 20mA | 140mcd @ 20mA | 572nm      | \$0.21 | 732-5017-ND |

Example of diode spec. These parameters vary with each LED (green LEDs can have  $V_f = 3.0V$  for example)

The brightness of an LED is proportional to the current flowing through the diode: if you halve the current, you halve the brightness. For example, the following soldering kit from Amazon varies the current (and brightness) of each diode by varying the resistor connected to the diode



LED Soldering Kit from Amazon

Assuming a 9V source (the kit assume you're using a 9V battery). the current and brightness of the first diode (330 Ohms) is:

$$I = \left( \frac{9V - 2.0V}{330\Omega} \right) = 21.21mA$$

The brightness is then proportional to this current where 20mA = 450mcd:

$$\left( \frac{21.21mA}{20mA} \right) 450mcd = 477.2mcd$$

## Diodes & Voltage Regulation

In ECE 401,

- Power to your PCB comes from a 9V battery, while
- Your components on your PCB operate off of 5VDC.

This creates a problem: how to generate 5VDC, capable of driving 100mA, using a 9V battery.

There are several ways to convert 9VDC to 5VDC. You could use

- A 7805SR Buck Converter: (\$13, >90% efficient), or
- An LM7805 Voltage Regulator (\$1.19, 55% efficient), or
- Many other IC's.

For ECE 401, we'll be using an LM7805 because they work, they're fairly inexpensive, and the power used in the circuits in this class are low enough that we don't worry too much about being only 55% efficient.




Image shown is a representation only. Exact specifications should be obtained from the product data sheet.

### LM7805CT

**105,263 In Stock**

|                                    |  |
|------------------------------------|--|
| <b>Digi-Key Part Number</b>        | 2156-LM7805CT-ND   |
| <b>Manufacturer</b>                | Fairchild Semiconductor  |
| <b>Manufacturer Product Number</b> | LM7805CT   |
| <b>Description</b>                 | IC REG LINEAR FIXED POS STD REG  |
| <b>Detailed Description</b>        | Linear Voltage Regulator IC Positive Fixed 1 Output 1.5A TO-220-3                            |
| <b>Customer Reference</b>          | <input style="width: 100%; border: 1px solid gray;" type="text" value="Customer Reference"/> |
| <b>Datasheet</b>                   | <a href="#">Datasheet</a>  |
| <b>EDA/CAD Models</b>              | <a href="#">LM7805CT Models</a>  |

| <b>Bulk</b> |            |
|-------------|------------|
| QTY         | UNIT PRICE |
| 253         | \$1.19000  |

LM7805 Voltage Regulator from Digikey. These ICs are fairly inexpensive and available.

If you look at the data sheets for a LM7805, you can pull out the limits of this IC:


- Output Voltage: 4.80V to 5.20V with 1A load
- Peak Current: 2.2A
- Max continuous current: 1A
- Input voltage range: 7V to 36V
- Quiescent Current: < 8mA

What this tells you is

- The LM7805 will operate just fine with a 9V battery,
- It needs less than 8mA to operate, and
- It can drive a 5V load with up to 1A of current



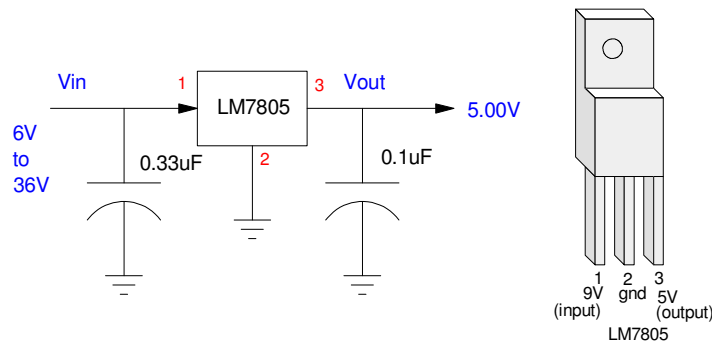The recommended configuration for a LM7805 is to connect a capacitor at the input (9V) and output (5V). Other than that, they're pretty easy to get to work.



Wiring for an LM7805 Voltage Regulator

For example, suppose you want to

- Convert 9V down to 5V, and
- Drive an LED at 10mA from the 5V source


Assuming the LED has a 1.9V drop across it (ideal red LED), the resistor should be 310 Ohms

$$R = \left( \frac{5V - 1.9V}{10mA} \right) = 310\Omega$$

Checking in CircuitLab:

- V2 = 5V (close), meaning the 7805 is doing its job
- V3 = 1.9V (close), meaning the red LED is on, and
- I3 = 10mA (close), meaning R2 is correct

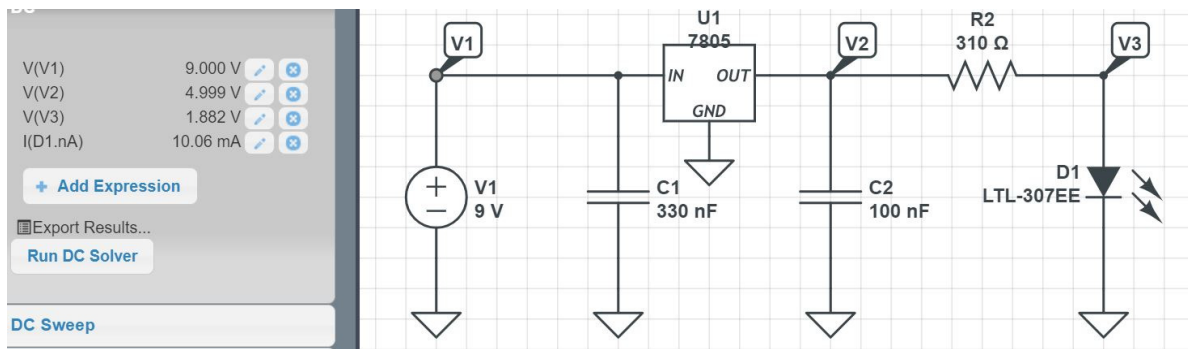You could find tune R2 if you really want 10.00mA exactly.



Converting 9V to 5V using a LM7805 in CircuitLab

A limitation of the LM7805 is its efficiency

- The input current is the same as the output current, plus 8mA to operate the LM7805

- The way the LM7805 works is it dumps voltage. If the input is 9V, the 7805 will dump 4V to produce a 5V output.

This means, assuming the load draws 100mA

- The output power is 500mW (5V \* 100mA)
- The input power is 900mW (9V \* 100mA)

The efficiency is then

$$\eta = \left( \frac{\text{output power}}{\text{input power}} \right) = \left( \frac{500mW}{900mW} \right) = 55\%$$

It's actually a little less than this since the LM7805 draws some current for its own operation (less than 8mA).

You can buy voltage regulators with higher efficiencies, such as a 7805SR Buck Converter, but these are \$13 each.


### Reverse Polarity Protection & Overcurrent Protection

Another requirement for your PCB in ECE 401 is to add

- Reverse polarity protection (connecting 9V to your PCB backwards will not fry your PCB), and
- Overcurrent protection (if your circuit draws too much current, a fuse blows).

There are several ways to do this.

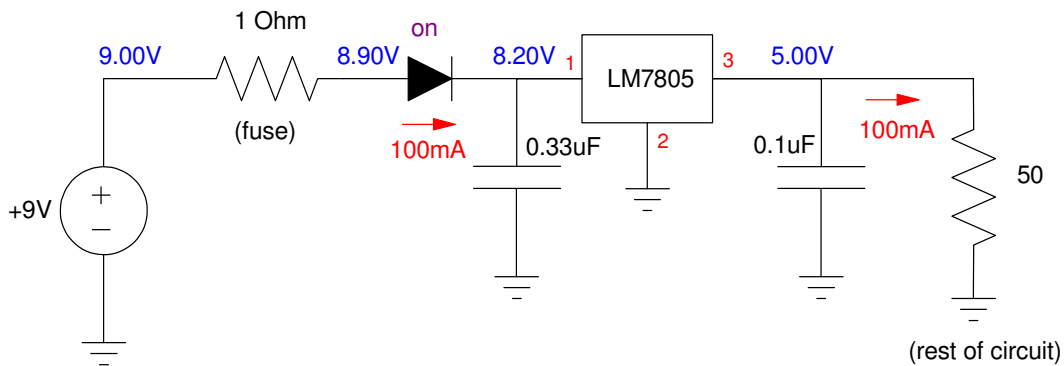**Method #1: Diode + Fuse.** Diodes do not allow current to flow backwards. If you place a diode in series with your 9V battery, the diode will turn off if the 9V battery is inserted backwards.



One method of providing reverse polarity protection: add a diode in series with the 9V power supply.  
 note: The 50 Ohm resistor models the rest of your circuit - it isn't included in your actual design.

A disadvantage of this approach is you lose 0.7V through the diode. That's not a major issue here since you're going to dump 4V somewhere to bring 9V down to 5V. The diode just means the LM7805 now only has to dump 3.3V.


Adding a fuse in series with the 9V supply also protects your circuit from overcurrent: if your circuit tries to draw too much current, the fuse will blow.

In ECE 401, we use a 1 Ohm resistor instead of a fuse since they cost less than 2 cents each.

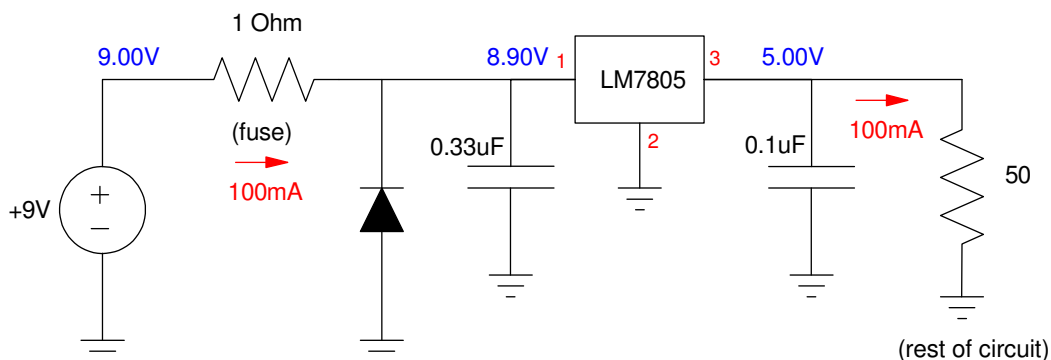**Method #2: Fuse + Diode.**

A second approach is to use a fuse along with a diode.

- If the 9V battery is connected correctly, the diode remains off. The circuit operates as normal.
- If the 9V battery is reversed,
  - The diode turns on, limiting the voltage to the LM7805 to -0.7V,
  - The current through the fuse becomes large (9A), blowing the fuse.



A second method of providing reverse polarity protection and overcurrent protection.

Either circuit works for our application. In ECE 401, you can use either one.

*note: The 50 Ohm resistor models the rest of your circuit in ECE 401, assuming your overall circuit draws 100mA. When you build your breadboard and PCB, replace the 50 Ohm resistor with your actual circuit.*

## BJT Transistors

Many of the electronic devices we use in ECE 401 have current outputs which are limited. This includes

- Raspberry Pi Pico (12mA max current out)
- 555 timers (50mA)
- MCP602 op-amps (25mA)
- LM833 op-amps (40mA)

What this means is

- If you are driving a load which needs less than 25mA, you can connect that load directly to these devices using a resistor.
- If, however, you need more than 25mA, you need to use a buffer circuit which amplifies the current. A BJT transistor is one way to do this.

BJT transistors act as

- Electronic switches (you can turn a device on and off using 0V & 5V),
- Which amplify current (1mA can turn on and off a device which draws 100mA)

The current amplification and the maximum current a given BJT transistor can handle depends upon which transistor you're using. The specs for the ones used in ECE 401 are as follows:


| Spec               | 3904 NPN | 3906 PNP |
|--------------------|----------|----------|
| Current Gain (min) | 100      | 100      |
| Max Current        | 200mA    | 200mA    |
| Vbe  (on)          | 0.7V     | 0.7V     |
| Vce  (sat)         | 0.2V     | 0.2V     |
| Cost (ea)          | \$0.11   | \$0.11   |

Typical parameters for 3904 and 3906 transistors.

Two types of BJT transistors exist:

- PNP: an electronic switch which connects your device to +5V, or
- NPN: an electronic switch which connects your device to ground.

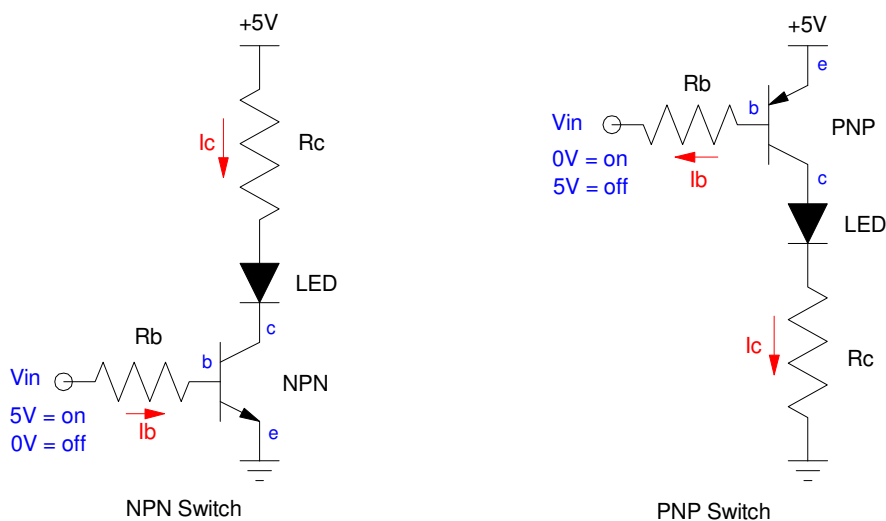The basic circuit for each of these are as follows:



BJT Switch: Either NPN or PNP transistors can be used.  
 NPN transistors act as a switch to ground, PNP transistors act as a switch to power

With the transistors, the arrow going between the base and the emitter is all important:

- The arrow represents a diode (a pn junction), telling you which way the current can flow
- The base current controls the current from the collector to the emitter.

Due to the way the transistor is made, the transistor tries to set  $I_c$  according to  $I_b$  by the current gain:

$$I_c = \beta I_b = 100 I_b$$

The transistor does this by dumping whatever voltage is necessary to set the current.

A good way to see how a transistor switch operates is to look at the load line for the transistor. Assume that  $R_c$  is selected so that  $I_c = 20\text{mA}$  when  $V_{ce} = 0\text{V}$ . Then, the load line will look like the following:


- When  $I_c = 0\text{mA}$ ,  $V_{ce} = 5\text{V}$  (the x-axis intercept)
- When  $V_{ce} = 0\text{V}$ ,  $I_c = 20\text{mA}$  (the y-axis intercept)
- The line connecting these two points is called *the load line*.

Any solution has to be on the load line somewhere.

When  $I_b = 0$  (there is no current through the diode connecting the base and the emitter)

- $I_c = 0$
- $V_{ce} = 5\text{V}$ , and
- The transistor is off.

With no current flow, the diode is off.

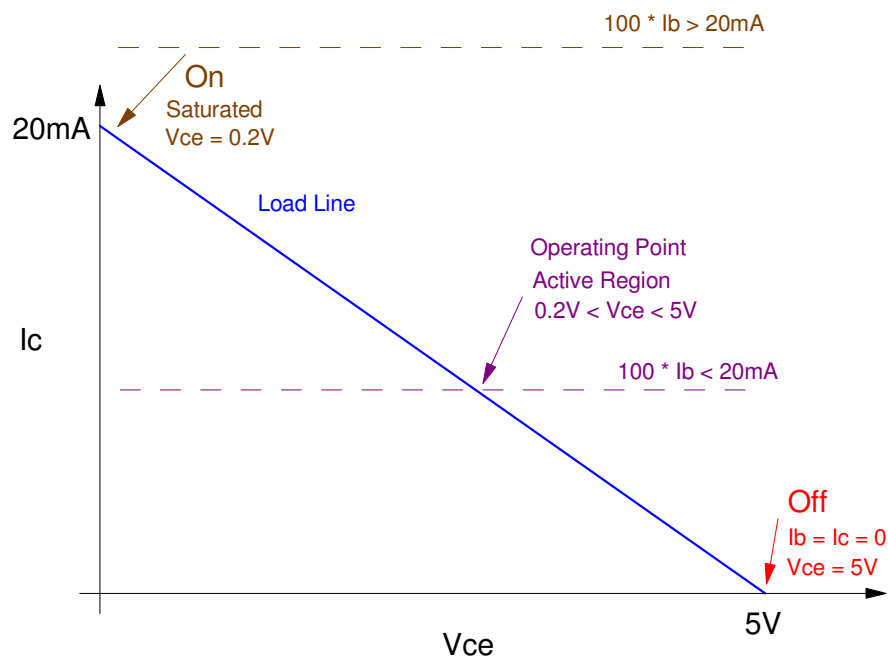

Load Line for an NPN transistor switch  
 You want to operate either in the Off state or the On state (saturated)

As  $I_b$  increases,


- $I_c$  increases according to the current gain ( $I_c = 100 I_b$ ),
- $V_{ce}$  drops from 5V down to 0.2V, and
- The transistor gets hot ( $P = V \cdot I$ )

The way the transistor sets the current  $I_c$  is by dumping voltage ( $V_{ce}$ ). This places the transistor in the active region - and the transistor gets hot ( $P = V \cdot I > 0$ ). You want to avoid this when using a transistor as a switch.

If  $I_b$  is large enough that  $100 I_b > 20mA$ , the transistor saturates:

- $V_{ce}$  saturates at its minimum value (0.2V), and
- $I_c$  saturated at its maximum value (a little less than 20mA).
- The transistor is in the On state (saturated)

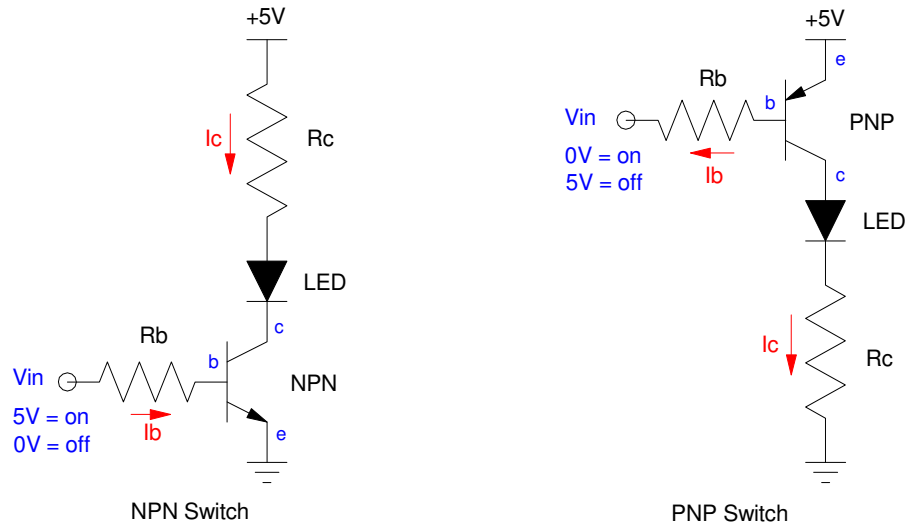**Analysis of Transistor Switches:** In terms of analysis, the currents and voltages are as follows (same equations for both PNP and NPN):



Analysis: Find the voltages and currents

The off state is kind of a gimme: the currents are zero.

For the on-state, assume the transistor is saturated

$$V_{ce} = 200mV$$

$$I_c = \left( \frac{5V - V_f - V_{ce}}{R_c} \right)$$

$$I_b = \left( \frac{5V - 0.7V}{R_b} \right)$$

The check to see that the transistor is saturated is the current you allow ( $100 I_b$ ) must be more than the current you need ( $I_c$ )

$$\beta I_b > I_c$$

$$I_b > \left( \frac{I_c}{100} \right)$$

Note that diodes and transistors are not ideal - meaning that the measured values will be slightly different from what you calculated. This show up in CircuitLab as well as in hardware.

For example, assume


- $R_c = 50 \text{ Ohms}$
- $R_b = 1k \text{ Ohms}$
- $V_f = 1.9V$  (red LED)
- 3904 NPN transistor with a current gain of 100

What you expect when  $V_{in} = 5V$  is

- $V_b = 0.7V$  *the drop across a silicon diode*
- $V_c = 0.2V$  *saturated*
- $I_c = 58.0mA$

$$I_c = \left( \frac{5V - 1.9V - 0.2V}{50\Omega} \right) = 58.0mA$$

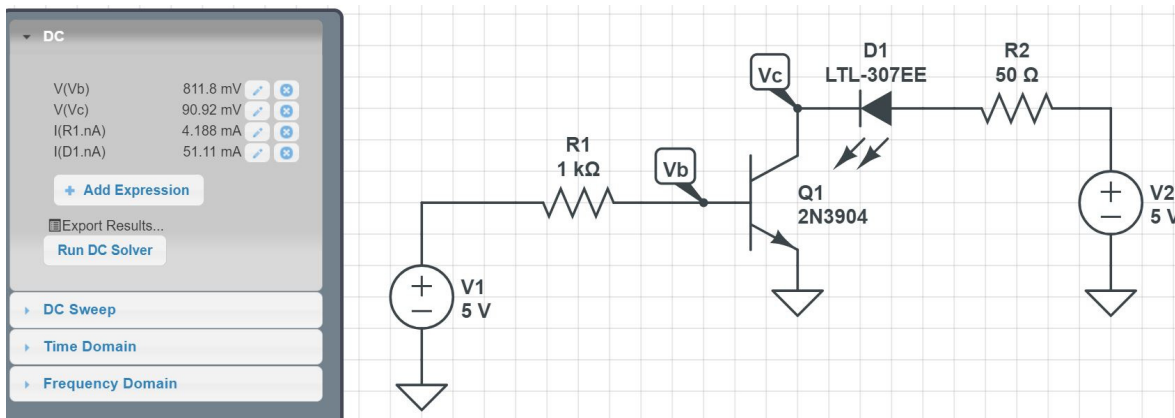In CircuitLab, what you get is close but slightly different:



NPN Switch Simulation in CircuitLab

What these numbers tell you is:

- $V_b = 0.8118V$ : Q1 is a silicon transistor with  $V_f = 0.7V$  (ish)
- $V_c = 0.0909V$ : Q1 is saturated with  $V_{ce} = 0.2V$  (ish).
- $I(D1) = 51.11mA$ : Close to 58.0mA but a little off due to the LED's voltage drop being a little different from 1.9V

Ideally,  $V_{ce} = 0V$  when the switch is closed. NPN transistors are not ideal, however, so  $V_{ce}$  will be close to zero but not quite zero. This switch should work as long as

$$\beta I_b > I_c$$


$$100 \cdot 4.188mA > I_c$$

$$I_c < 418.8mA$$

As show, this switch should be able to turn on and off any load as long as it draws less than 418.8mA (ignoring the 200mA current limit of a 2N3904 transistor that is...)

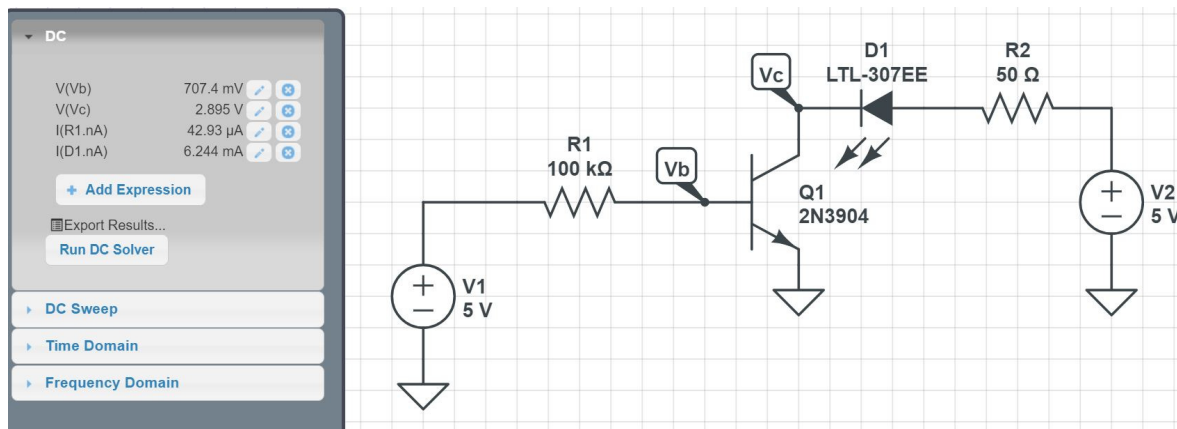If  $R_1$  is increased to 100k, then this switch should work for  $I_c < 4.188mA$ . Since we're pushing more than that through the diode, the transistor leaves the saturated region and enters the active region. This shows up with  $V_{ce} > 0.2V$






If R1 is increased to 100k, the transistor is no longer saturated ( $V_{ce} > 0.2V$ )

This is bad for several reasons:

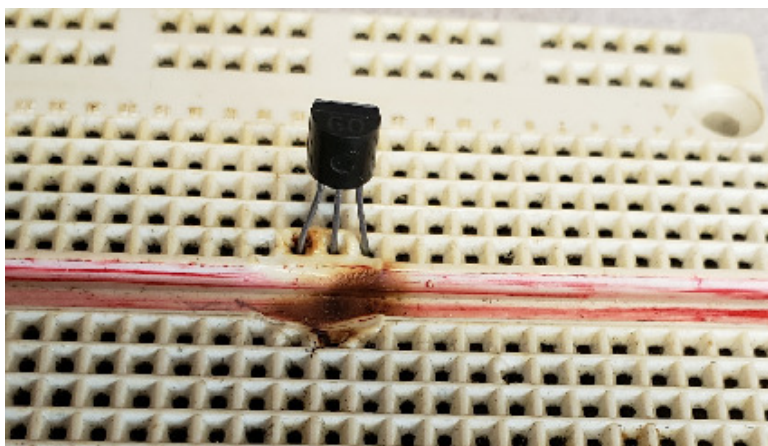- By placing the transistor in the active region, it starts to get hot ( $P = V \cdot I$ ).
- The current through the LED is no longer 58mA as calculated



If you operate a transistor in the active region, it will get hot (possibly melting your breadboard)

When designing a transistor switch, make sure that

$$\beta I_b > I_c$$

**Design of Transistor Switches:** In terms of design,

- Pick  $R_c$  to set the desired current
- Then pick  $R_b$  so that the transistor is saturated ( $I_b > I_c/100$ )

For example, design a circuit

- To turn on and off a red LED
- At 100mA when on,
- Using a 0V/5V input capable of driving at most 5mA.

Solution: First pick  $R_c$  to set the current to 100mA

$$R_c = \left( \frac{5V - 1.9V - 0.2V}{100mA} \right) = 29\Omega$$


Next, pick  $I_b$  so that the transistor is saturated

$$I_b > \left( \frac{I_c}{100} \right) = 1mA$$

Let  $I_b = 2mA$

$$R_b = \left( \frac{5V - 0.7V}{2mA} \right) = 2.15k\Omega$$

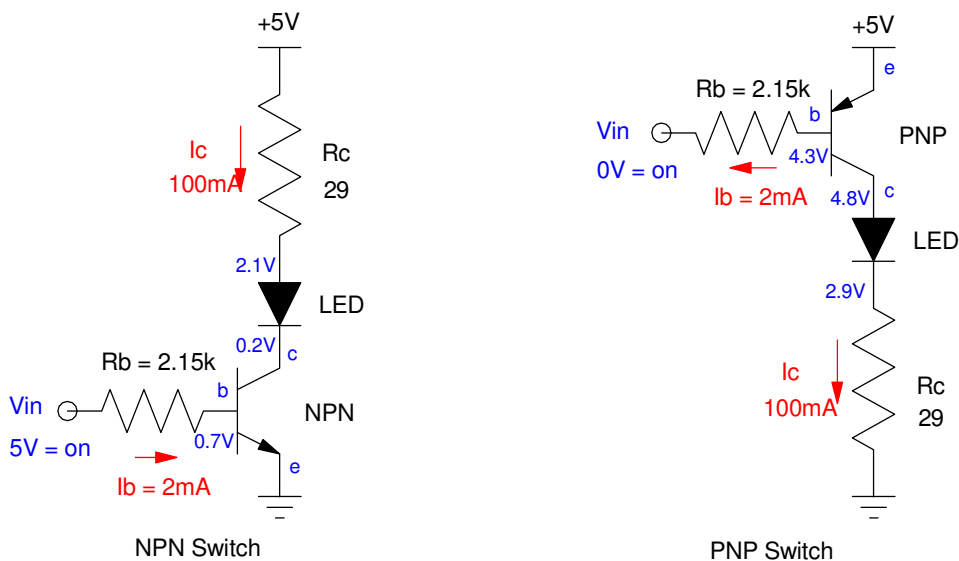Two versions of a BJT switch are then as follows.



Resulting Design for 2mA turning on and off 100mA through an LED

Note: If you want to reduce the current to the LED to 10mA (10x smaller), make  $R_c$  10x larger (290 Ohms). Everything else can remain the same.

**Example 2:** Have a Raspberry Pi-Pico turn on and off a red LED

- At 20mA
- Using an NPN transistor, and
- A PNP transistor

**NPN Solution:** The circuit design with an NPN transistor isn't much different. All you need to do is adjust  $R_b$  so that it draws 1mA when driven with 3.3V (the output of a Raspberry Pi Pico)


$$R_c = \left( \frac{5V - 1.9V - 0.2V}{20mA} \right) = 145\Omega$$

$$\beta I_b > I_c$$

$$I_b > \frac{20mA}{100} = 0.2mA$$

Let  $I_b = 1mA$  (allowing up to 100mA to flow through the transistor switch)
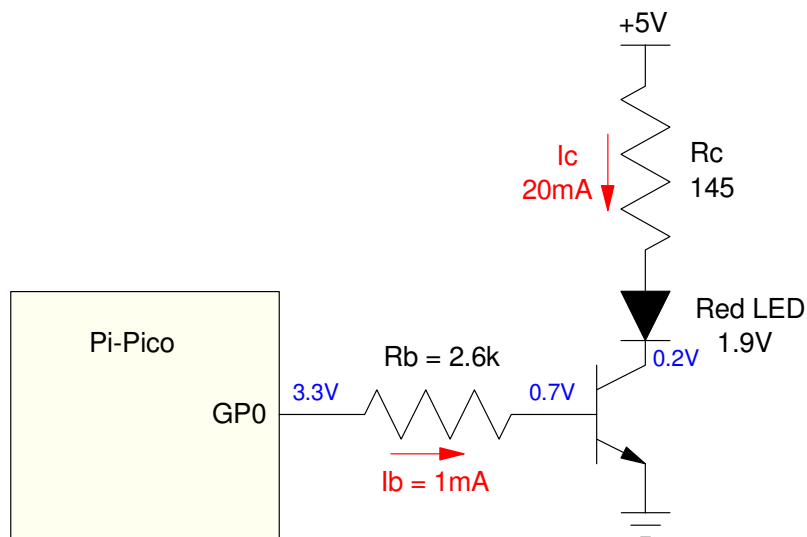
$$R_b = \left( \frac{3.3V - 0.7V}{1mA} \right) = 2.6k\Omega$$



Circuit for a Pi-Pico to turn on and off an LED at 20mA using an NPN transistor (LM3904)

**PNP Solution:** With a PNP transistor, the circuit changes slightly.

- The PNP transistor needs 5V to turn off, but
- A Pi-Pico only outputs 3.3V

One fix is to use a level shifter (last lecture) to bump up the Pico's output to +5V

When the Pico outputs 3.3V (red voltages):

- The op-amp outputs 5V ( $3.3V > 2V$ )
- There is no voltage across the diode in the PNP transistor, meaning  $I_b = 0$
- Meaning  $I_c = 0$


When the Pico outputs 0V (blue voltages)

- The op-amp outputs 0V ( $0V < 2V$ )
- $I_b$  is 1mA

$$I_b = \left( \frac{5V - 0.7V - 0V}{2.6k} \right) = 1mA$$

- $I_c = 20mA$
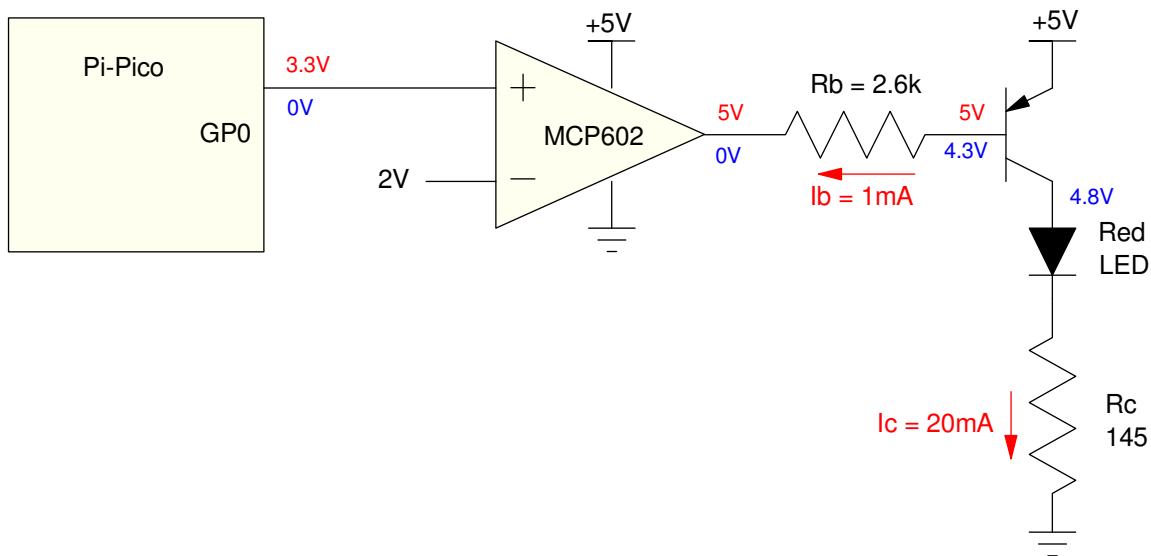
$$I_c = \left( \frac{5V - 0.2V - 1.9V}{145} \right) = 20mA$$



Circuit for a Pi-Pico to turn on and off an LED at 20mA using a PNP transistor (LM3906)

## Summary

Diodes can be used as electronic valves: they let you control block reverse current.

BJT transistors can be used as electronic switches. They let you turn on and off devices at currents that are higher than a typical op-amp or microcontroller can output.