
CircuitLab & Op-Amps


ECE 401 Senior Design I

Week #4

Please visit Bison Academy for corresponding lecture notes,
homework sets, and videos
www.BisonAcademy.com

CircuitLab and Simulations

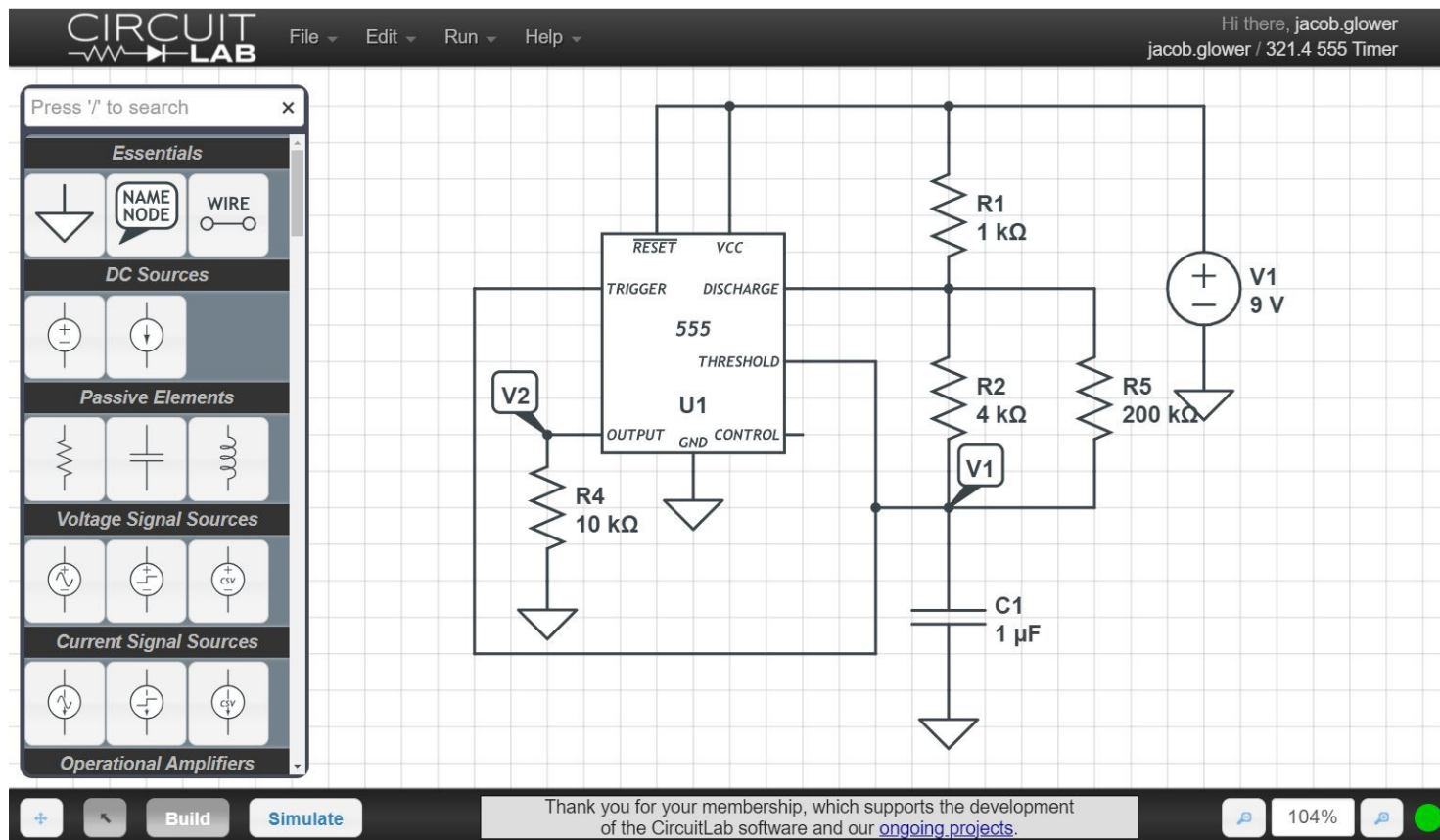CircuitLab is a circuit simulator, which is very similar to SPICE or PSpice, and has a graphical front end. The graphical front end makes CircuitLab very easy to use.



What CircuitLab Does

Lets you check your design using a nonlinear circuit simulator.

- Hand Calculations: Usually make approximations
 - Ideal Diode
 - $V_{ce(sat)} = 0.2V$
- CircuitLab: More accurate, nonlinear models

Lets you adjust your circuit if necessary

- Tweak to set the current through the diodes to 10mA
- Tweak to set the duty cycle to 50%
- etc.

Once your design is finalized, you can build it on a breadboard

Classes where CircuitLab is Useful

Circuits I and II

- Linear Circuits


Electronics I and II

- Nonlinear Circuits

Digital Systems

- Boolean Logic
- Controls Systems
- Dynamic Systems

Likewise, CircuitLab is pretty useful

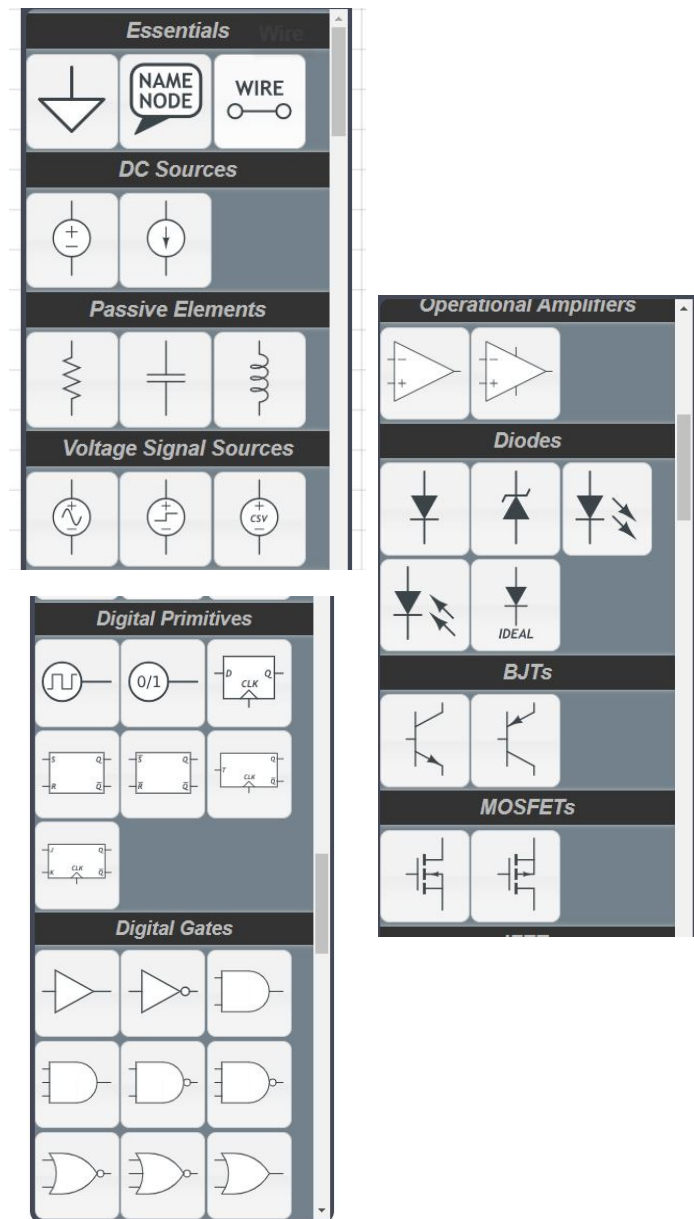

Signing Up for CircuitLab

There are several ways you can use CircuitLab:

- **Trial Version:** If you don't register or sign in, you're using the trial version. This limits you to 1/2 hour per session and you cannot save your work.
 - **Free Version:** Register with CircuitLab using your NDSU email address (@ndsu.edu). The ECE department pays for a site license - so all NDSU students can use CircuitLab for free. There is no time limit and you can save your work.
 - **Personal Version:** Sign up with your personal email account at a cost of \$24/year. Again, there is no time limit and you can save your work. Plus, you still have your work after you graduate.
-



Operational Amplifiers (Op-Amps)

One of the requirements for your 401 project is it must include an integrated circuit (IC). Usually, this is an op-amp, a 555 timer, or a PIC processor.

Op-amps are really useful devices that can do all sorts of things. With op-amps, you can build

- Comparitors
- Schmitt Triggers
- Half-wave and full-wave rectifiers,
- Envelope detectors
- Amplifiers
- Filters

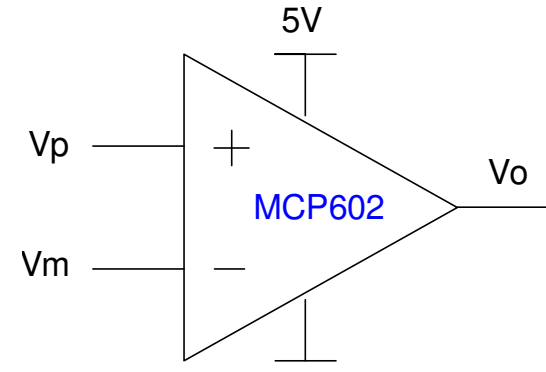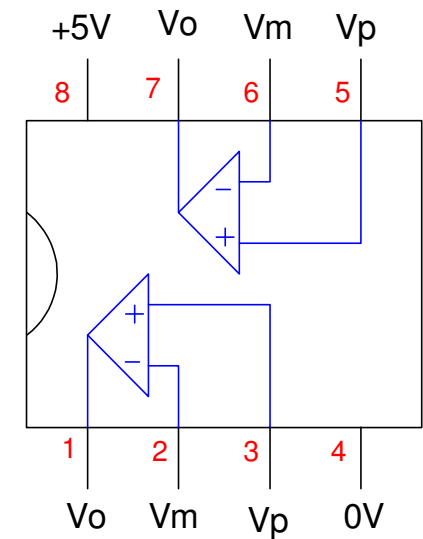to name just a few. Op-amps are just darn useful.



Op-Amps in CircuitLab

Two types of op-amps are available

- No power supply
 - Use for analog circuits (filters, amplifiers, etc)
- +/- Power Supply
 - Use for digital circuits (Comparitors, Schmitt Triggers)

The image shows the CircuitLab interface. On the left is a component palette with sections for Current Signal Sources, Operational Amplifiers, and Diodes. In the center, two op-amp symbols are placed on a grid: a black triangle labeled 'OA1 LM741' and a red triangle labeled 'OA2 MCP602'. On the right, a configuration panel for the selected component (MCP602) is open. It displays a list of op-amp models with 'MCP602' selected. The configuration fields are:


name:	<input type="text" value="OA2"/>	Part#:	<input type="text" value="MCP602"/>
A_OL:	<input type="text" value="500e3"/>	GBW:	<input type="text" value="2.8e6"/> Hz
R_O:	<input type="text" value="30"/> Ω	I_B:	<input type="text" value="1p"/> A
R_IN:	<input type="text" value="1e13"/> Ω	SR:	<input type="text" value="2.3e6"/> V/s

Buttons for 'Save Custom Device Model', 'View All Op-Amps In Stock', 'Datasheet', and 'Buy' are also visible.


Operational Amplifier Pin-Outs

Op-Amps usually come with two op-amps in an 8-pin package:

- Footprint is usually the same for most 8-pin op-amps
- Allows you to swap them in and out

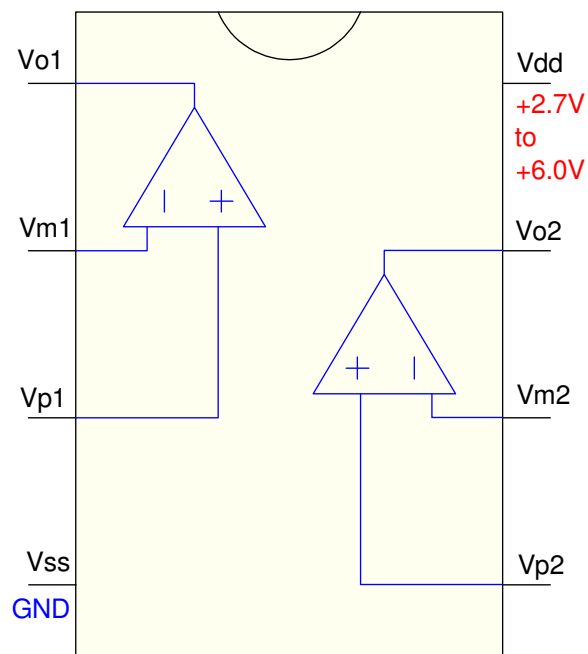

MCP602

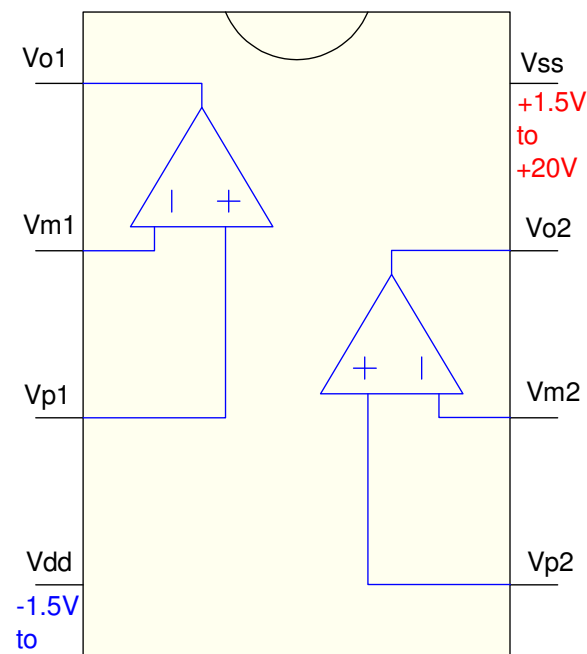

LM358

Op-Amp Parameters

Thousands of op-amps are available




ECE standardized on two

- MCP602: Digital circuits
- LM2904 or LM358: Analog circuits

	MCP602	LM2904 / LM358	Ideal
Input Resistance	1e13 Ohms	4G Ohm	infinite
Current Out (max)	25mA	40mA	infinite
Operating Voltage	2.7V - 6V	+/- 1.5V .. +/- 20V	any
Differential Mode Gain	500,000	140,000	infinite
Common Mode Gain	0.00003	0.00002	0
Slew Rate	2.3V/us	0.3V/us	infinite
Gain Bandwidth Product	2.8MHz	1.2MHz	infinite
Operating Range	-40C to +85C	-40C to +85C	infinite
Price (qty 100)	\$0.61	\$0.12	-

Digital Op-Amp Circuits

- Like lego blocks: Assemble to create a larger circuit

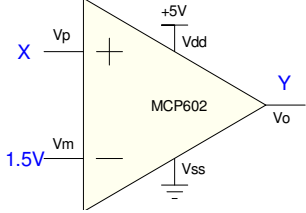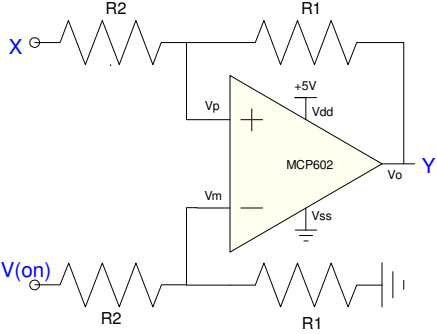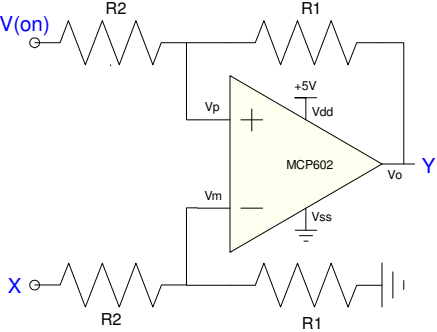Name	Description	Circuit
<p>Comparitor - Level Shifter (convert 0V/3.3V logic to 0V/5V logic)</p>	<p>$Y = (X > 1.5)$</p> <p>5V = true 0V = false</p>	
<p>Schmitt Trigger</p> <p>$V_{on} > V_{off}$</p>	<p>Set: $X > V_{on}$</p> <p>Clear: $X < V_{off}$</p>	
<p>Schmitt Trigger</p> <p>$V_{on} < V_{off}$</p>	<p>Set: $X < V_{on}$</p> <p>Clear: $X > V_{off}$</p>	


Example 1: Night Light (Comparitor)

Design a circuit so that a Pi-Pico can determine when a room is dark. Assume you have a light sensor with

- $R = 3k$ Ohms (room lights on)
- $R = 10k$ Ohms (room is dark)


Solution: Convert resistance to voltage using a voltage divider. Assume a $5k$ resistor.

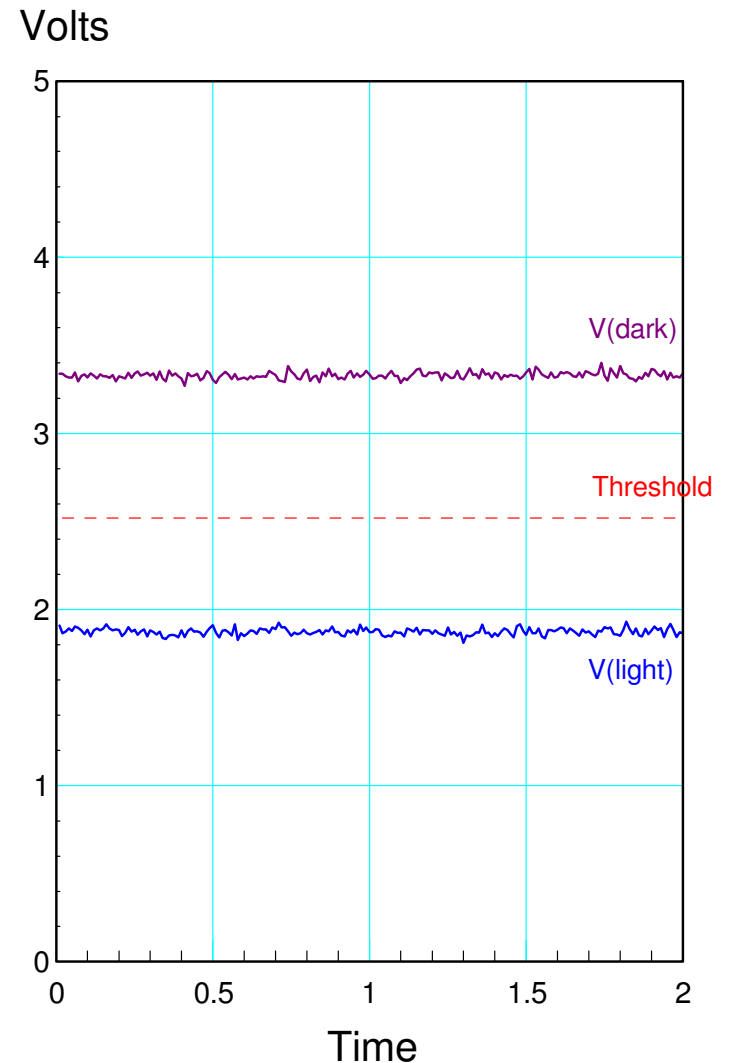Pick a voltage in-between, such as $2.50V$



Night-Light Schematics

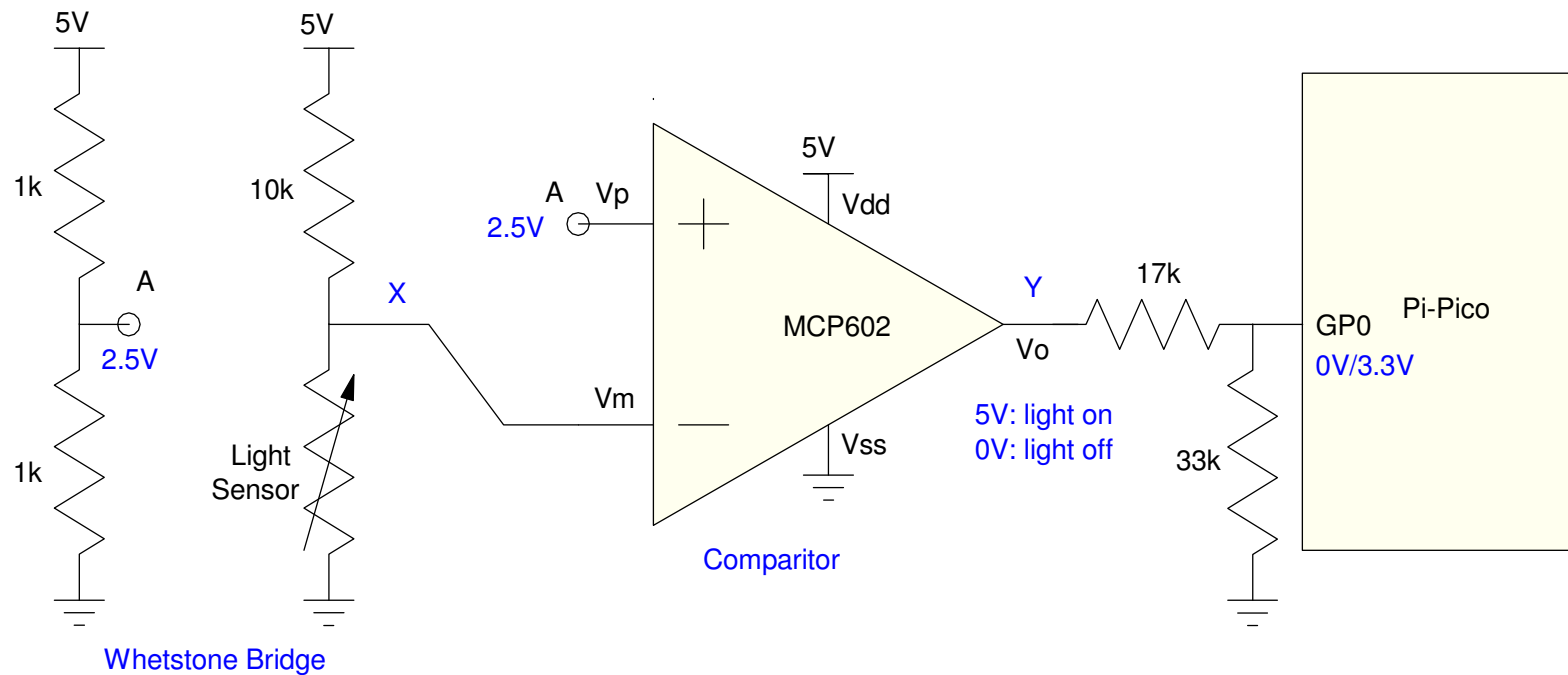- Switch at 2.5V
- Drop the output voltage to 3.3V
 - Avoid harming the Pi-Pico




CircuitLab Schematic

Use an op-amp with voltages specified

- Determines logic level 1 and 0

Sweep the voltage at X

- Does it switch at 2.5V?

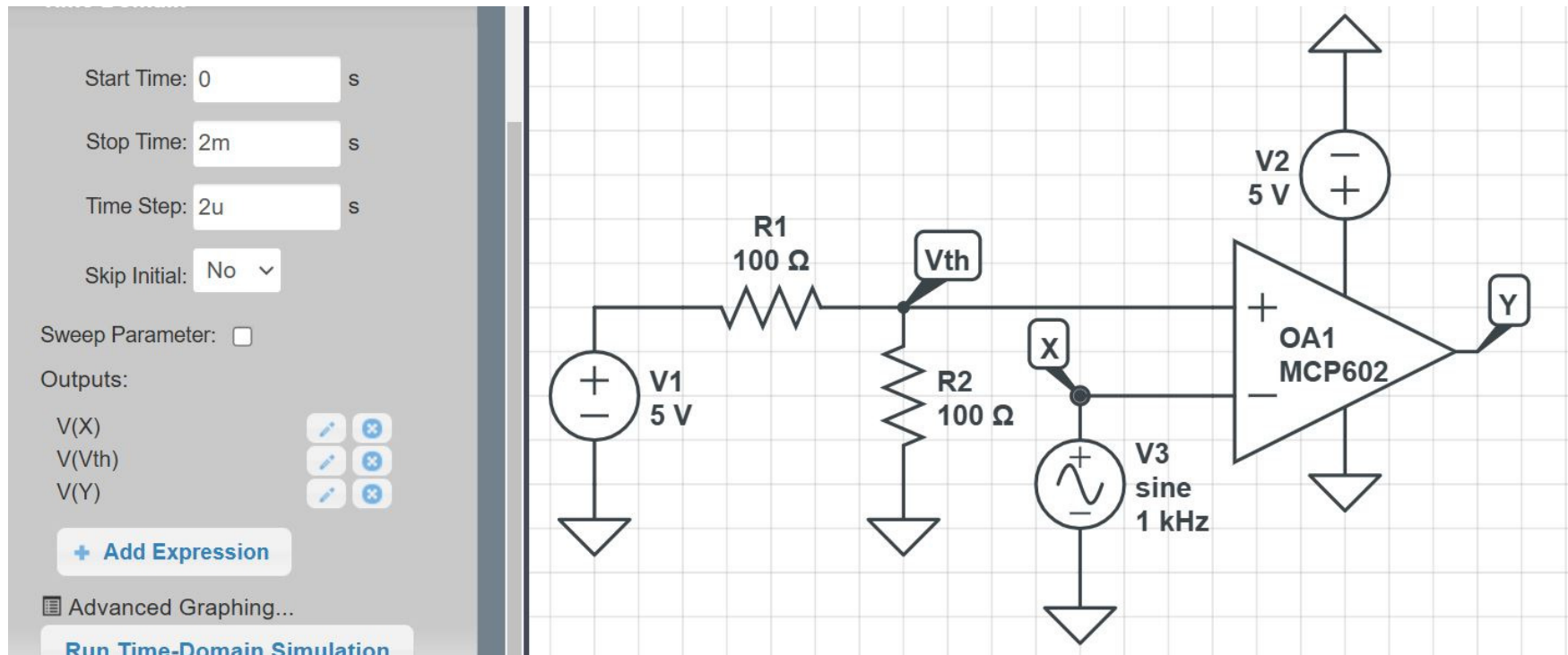


CircuitLab: Simulation Results

Run a time-domain simulation

- 2ms (two cycles)
- 2 μ s step size (1000 points per plot)\

Result

- Turns on at 2.5V & turns off at 2.5V

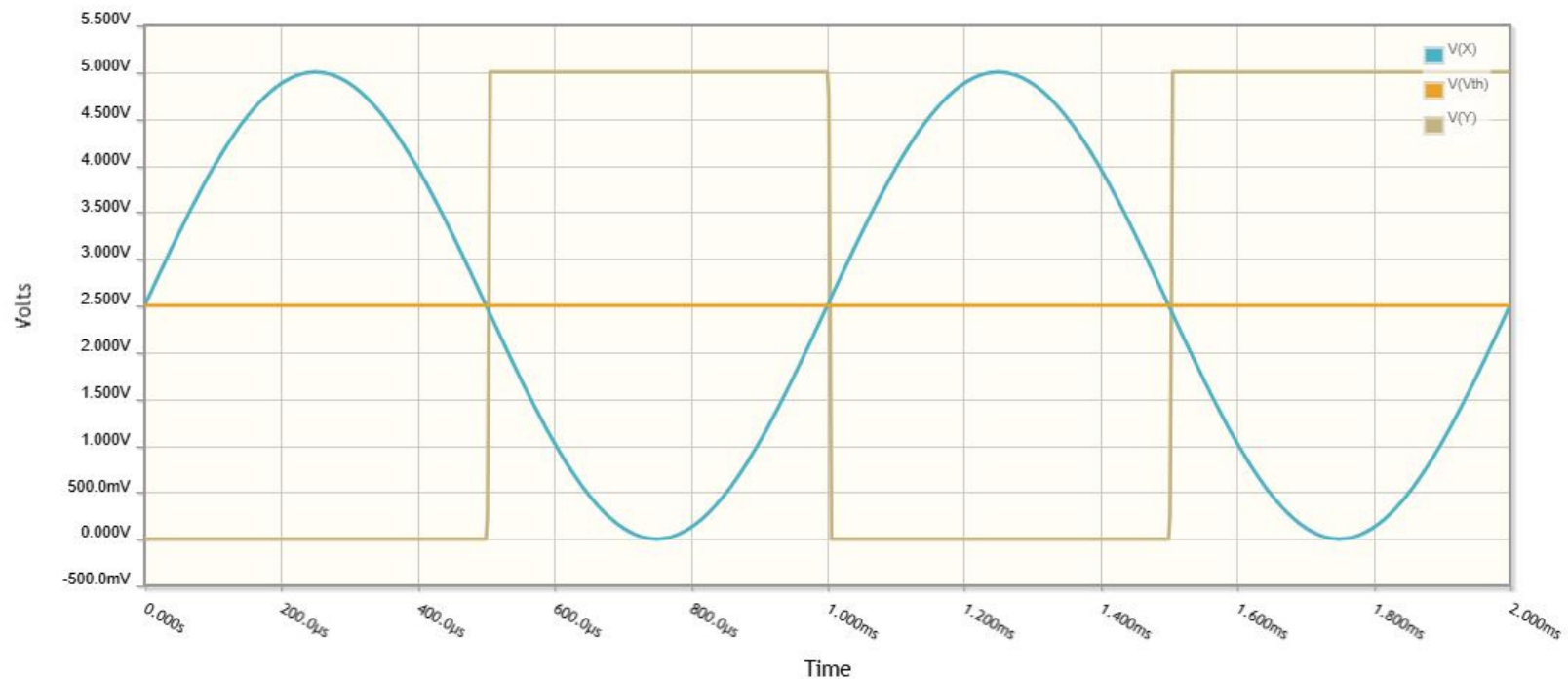


Example 2: Night Light (Schmitt Trigger)

Noise on the signal can create chatter when switching

- Add hysteresis to prevent this


Let the on-off voltages be

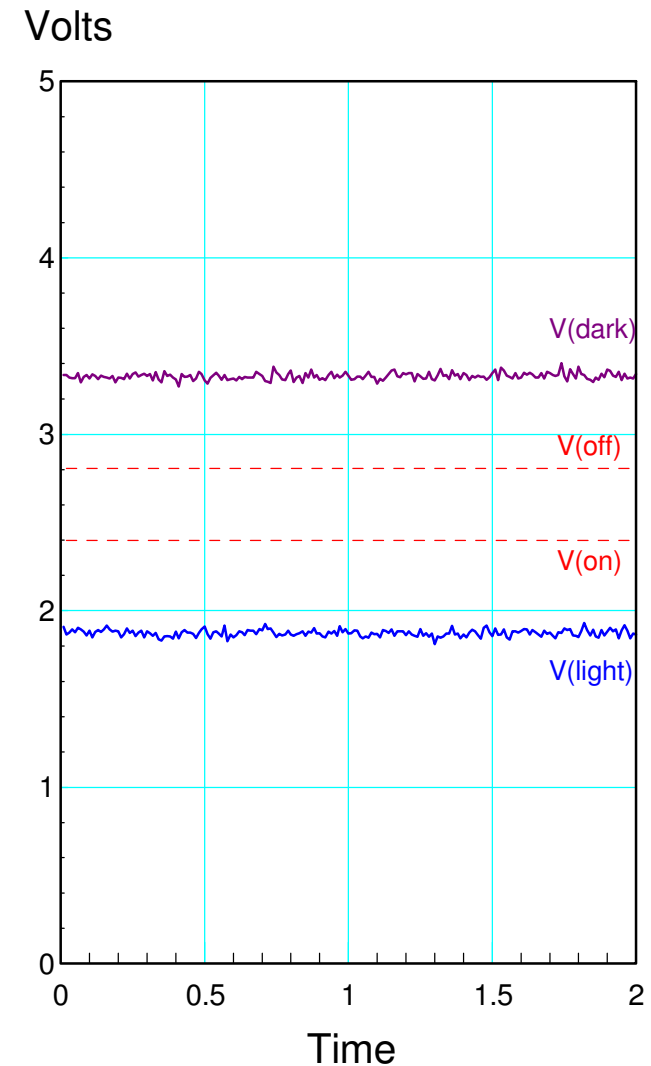- $V(\text{on}) = 2.4\text{V}$
- $V(\text{off}) = 2.8\text{V}$



Schmitt Trigger: Calculations

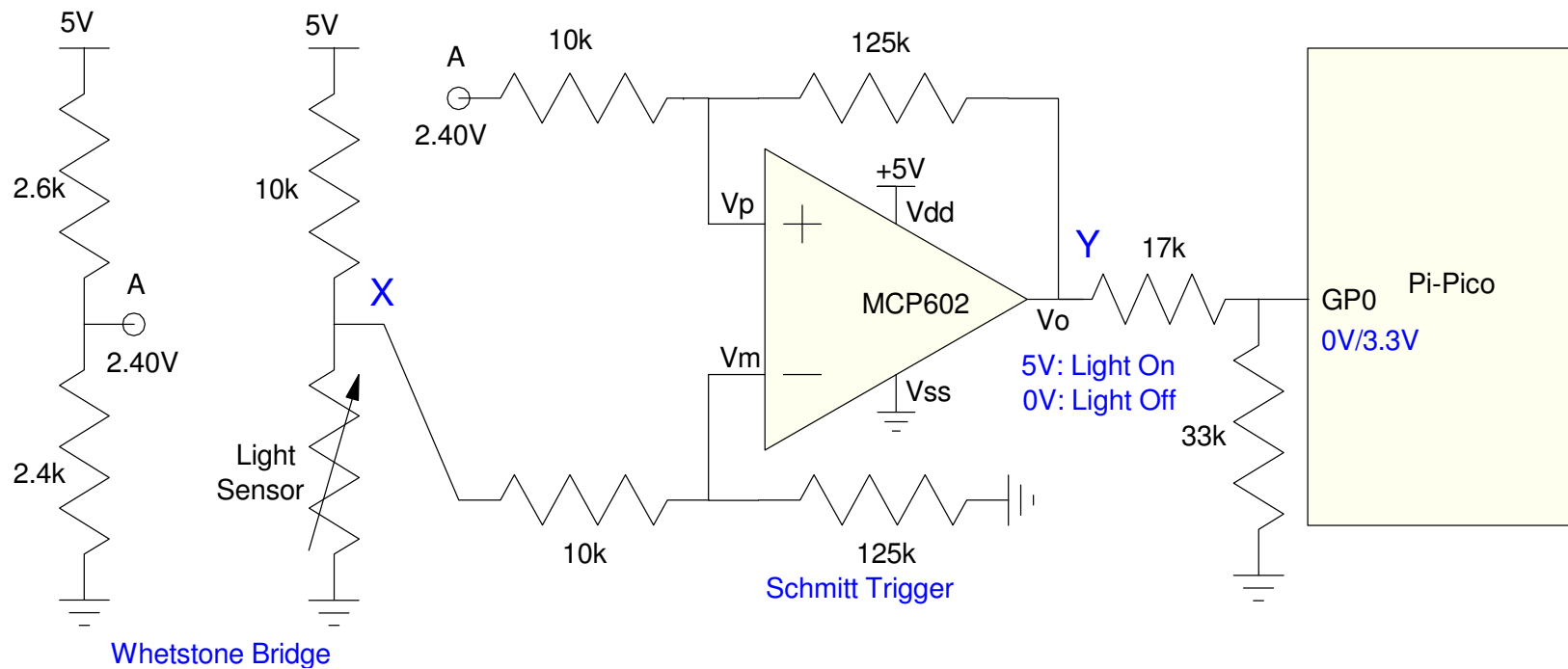
- Connect to the minus input (when X goes high, Y goes low)
- $V(\text{on}) = 2.40\text{V}$
- $\text{Gain} = (5\text{V} - 0\text{V}) / (2.8\text{V} - 2.4\text{V}) = 12.5$



CircuitLab Schematic

Sweep the voltage at X using a sine wave source

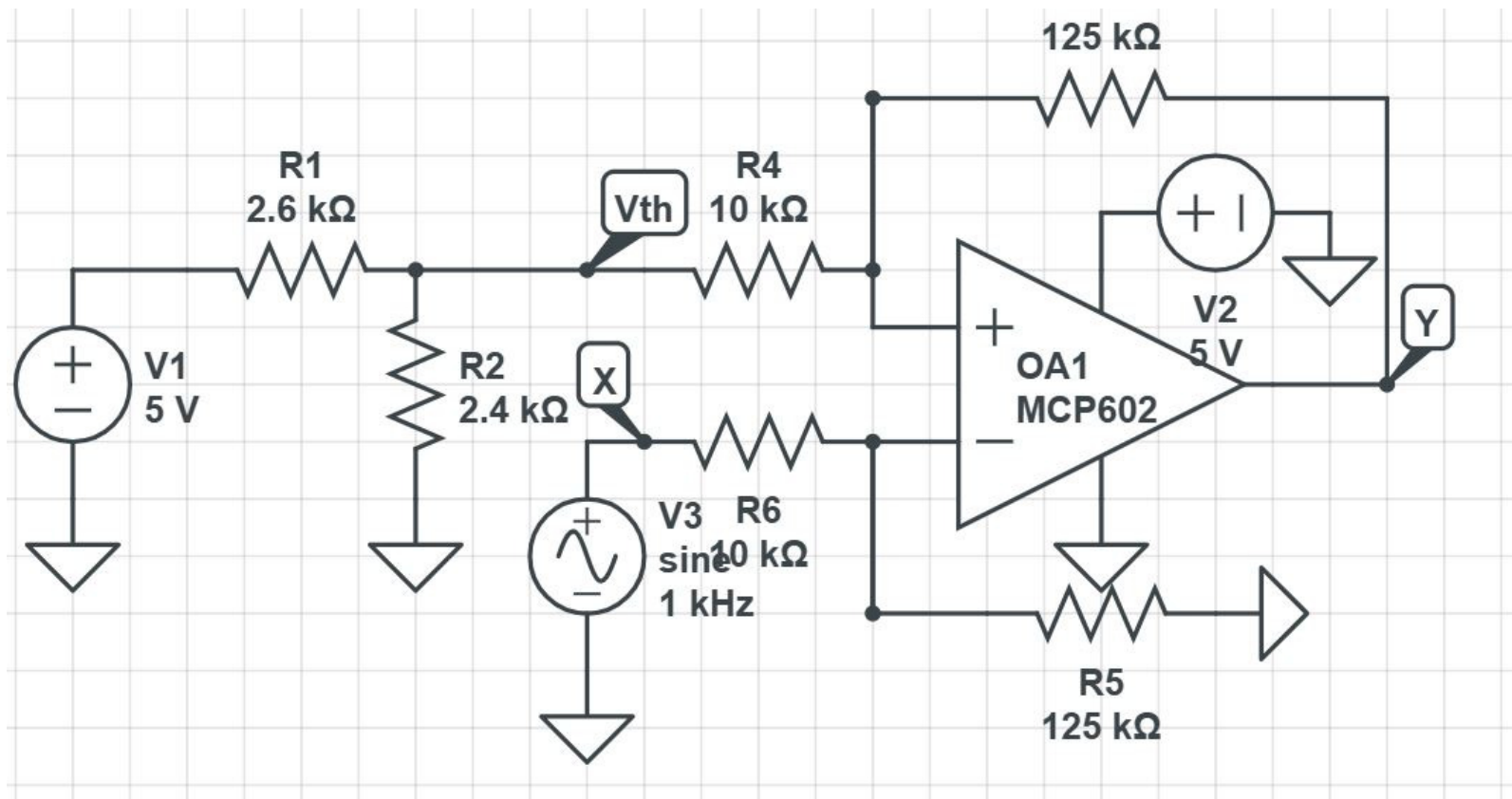
- Does Y turn on at 2.4V?
- Does Y turn off at 2.8V?



CircuitLab Simulation Results


Run a time-domain simulation

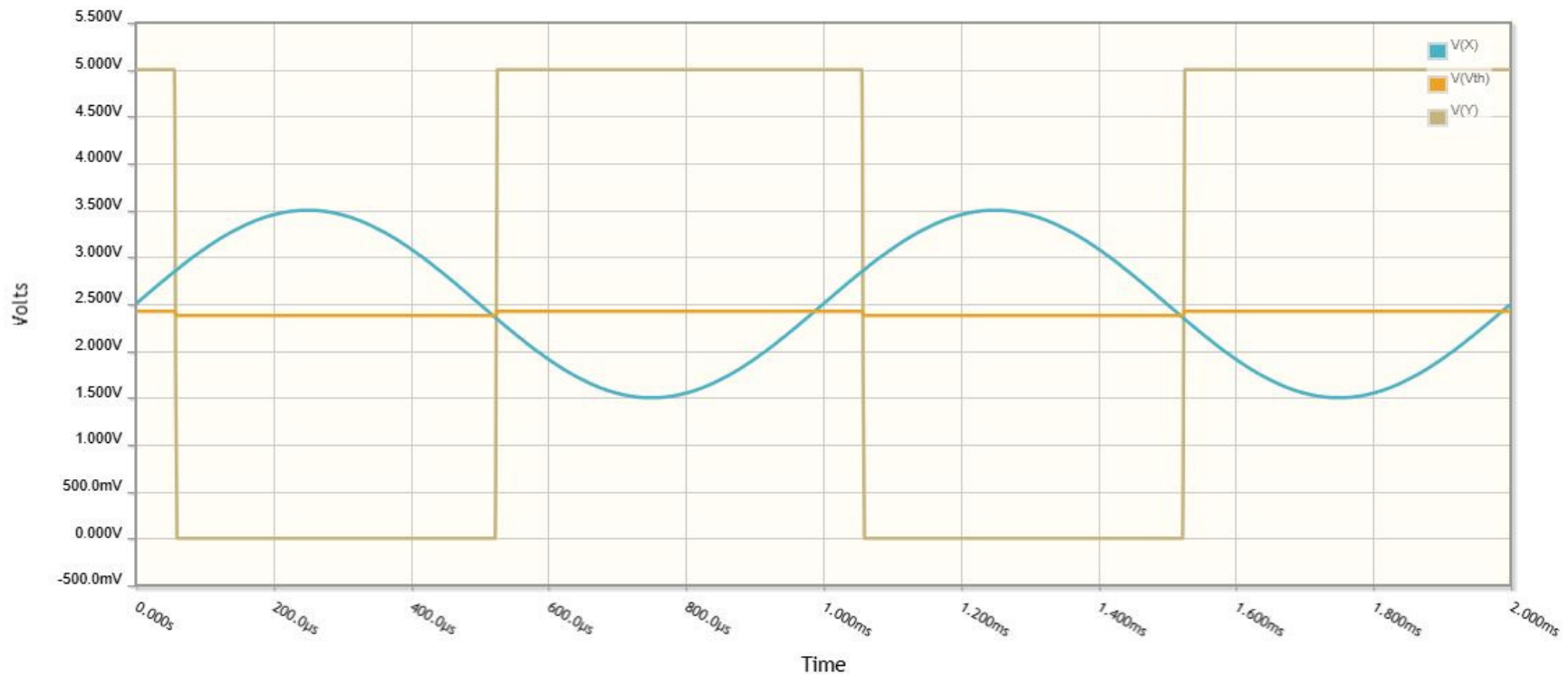- 2ms period (two cycles)
- 2 μ s step size (1000 points per plot)
- On & off voltages as expected




Op-Amp Circuits with Analog Outputs (Amplifiers)


Buffer: $Y = X$

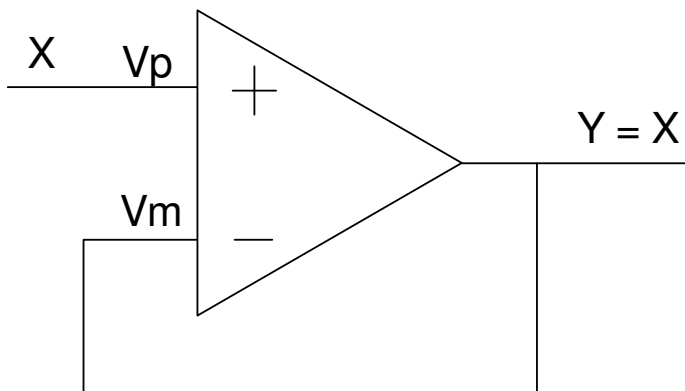

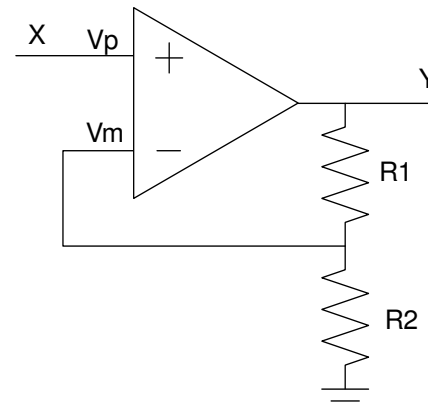
Non-Inverting Amplifier: $Y = (1 + R1/R2)*X$



Inverting Amplifier: $Y = -(R1/R2) X$

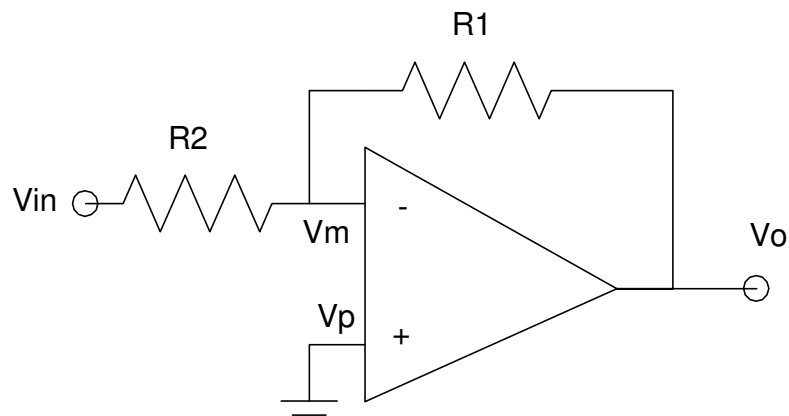

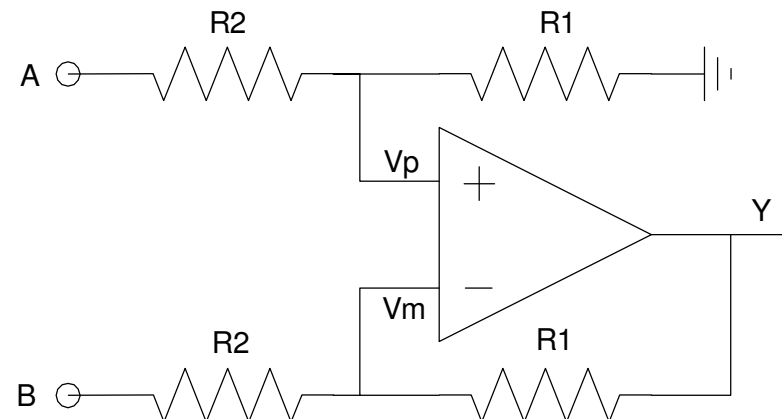Instrumentation Amplifier: $Y = (R1/R2)*(A-B)$



Equations for Op-Amp Amplifiers:

Voltage nodes tends to work best


- $V_p = V_m$ (1st equation)
- Voltage nodes to get the rest

Example:

- $V_p = V_m$
- $\left(\frac{V_p - A}{R_1}\right) + \left(\frac{V_p}{R_2}\right) = 0$
- $\left(\frac{V_m - B}{R_1}\right) + \left(\frac{V_m - Y}{R_2}\right) = 0$

Do some algebra

$$Y = \left(\frac{R_2}{R_1}\right)(A - B)$$

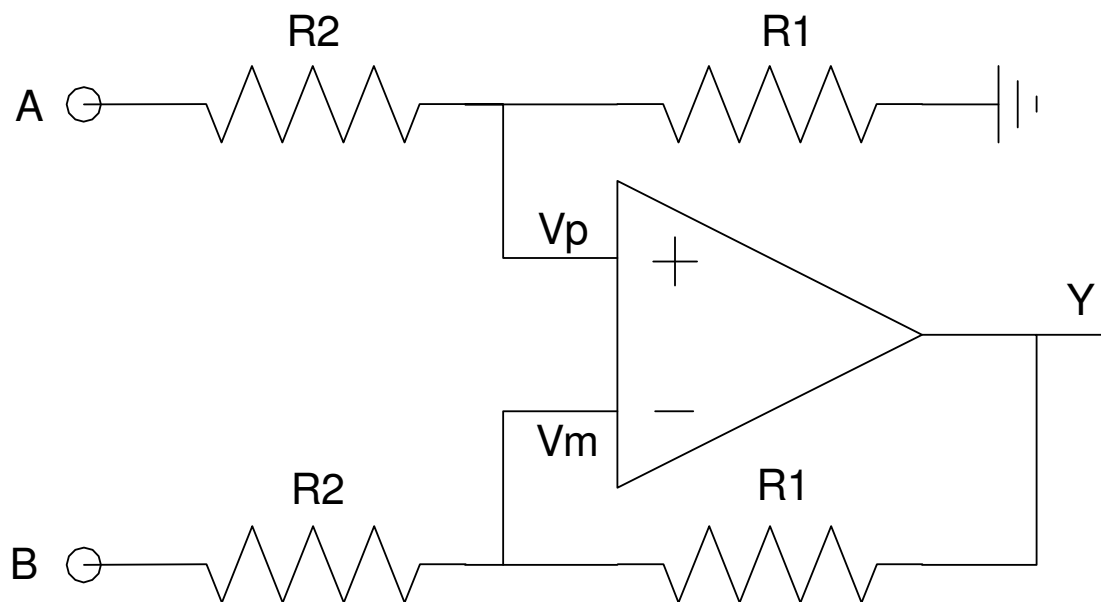

Example 1: Current Sensor


Problem: Measure current

Assume

- The current is 0 - 100mA
- The output is 0V - 3.3V


Solution:

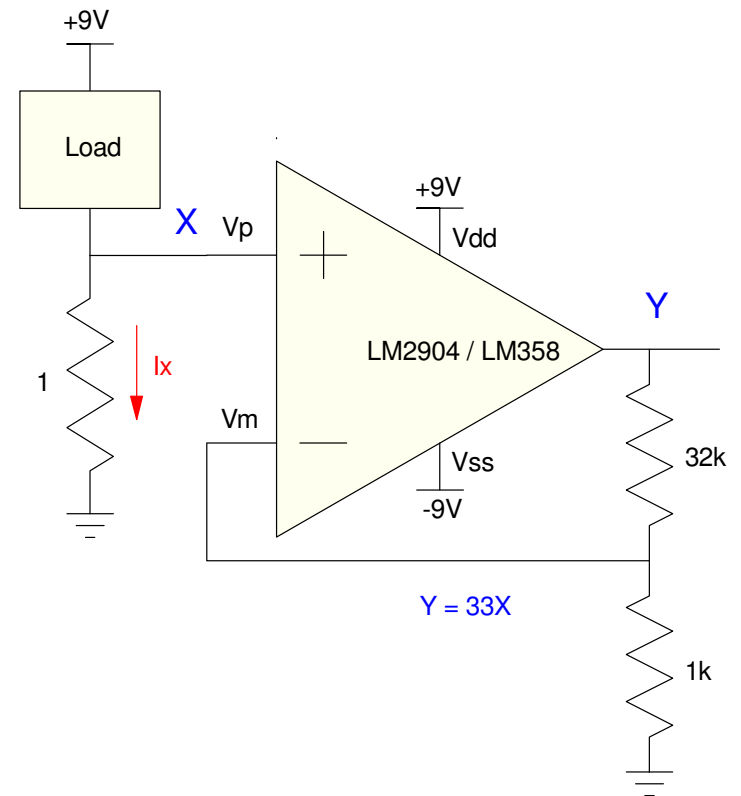- A 1 Ohm resistor converts I to V
- An amplifier converts 100mV to 3.3V
 - Gain = 33



CircuitLab Schematic

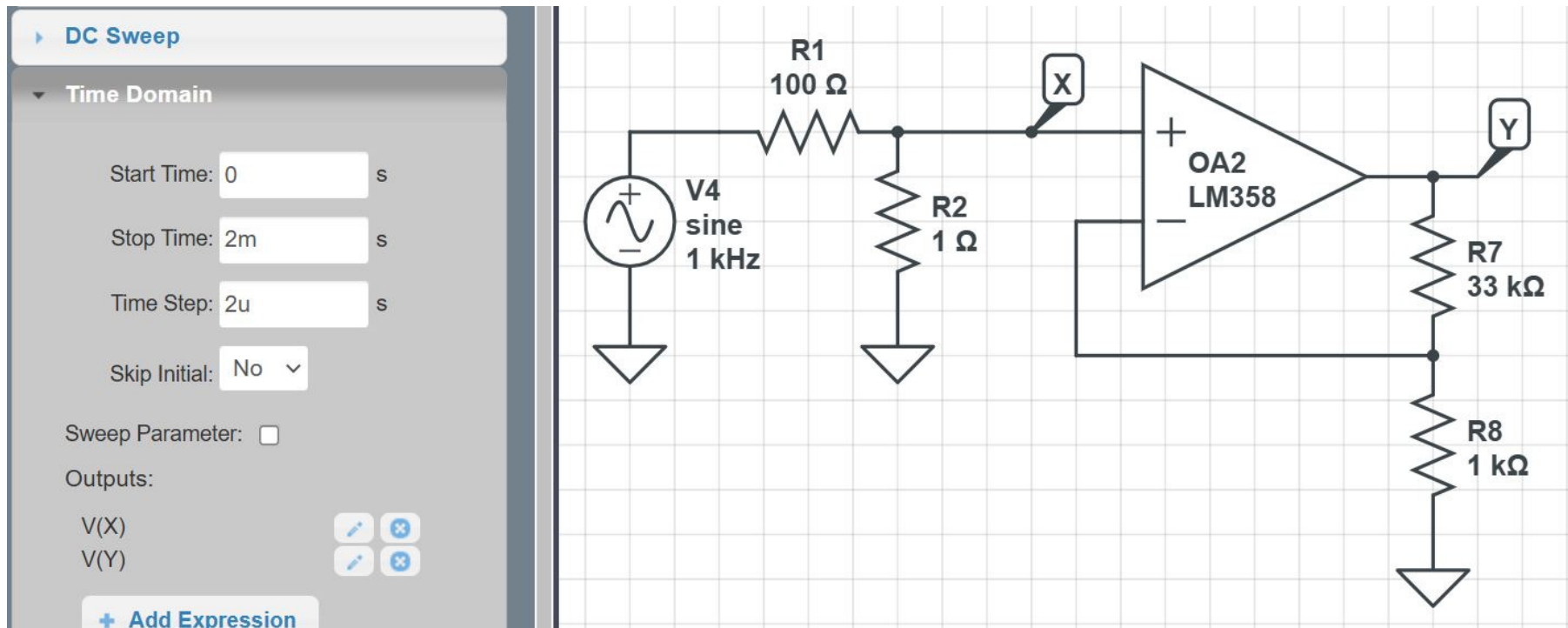- 10V & 100 Ohms sets the max current to 100mA
- Sine wave sweeps current from -100mA to +100mA
- Check voltage at Y




CircuitLab Simulation Results

Voltage at Y is a sine wave

- The amplifier is working

Peak voltage is 3.3V

- $100\text{mA} = 3.3\text{V}$

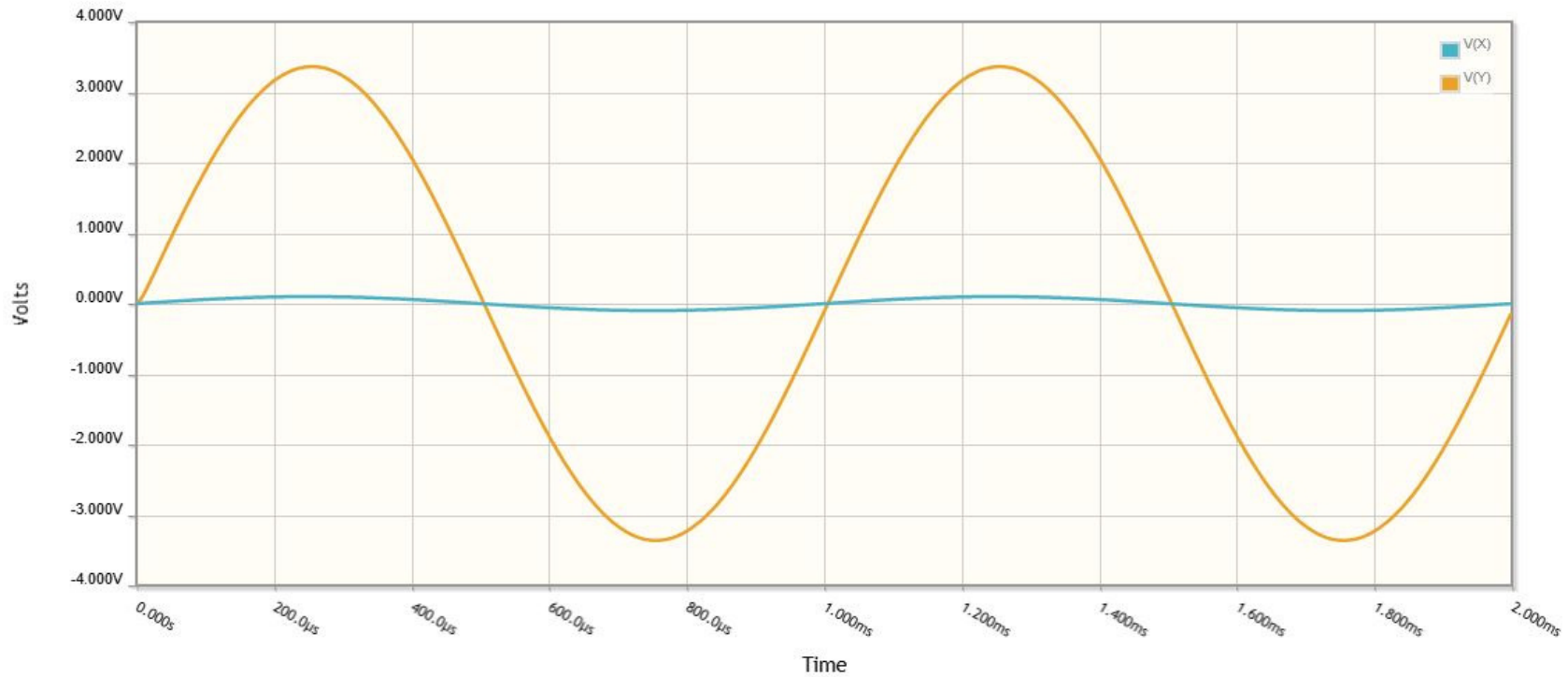


Example: Current Sensor (take 2)

Measure the current going to a lithium battery. Assume

- The current can be in the range of -2A to +2A.
- The output voltage should be -2V to +2V

Solution:

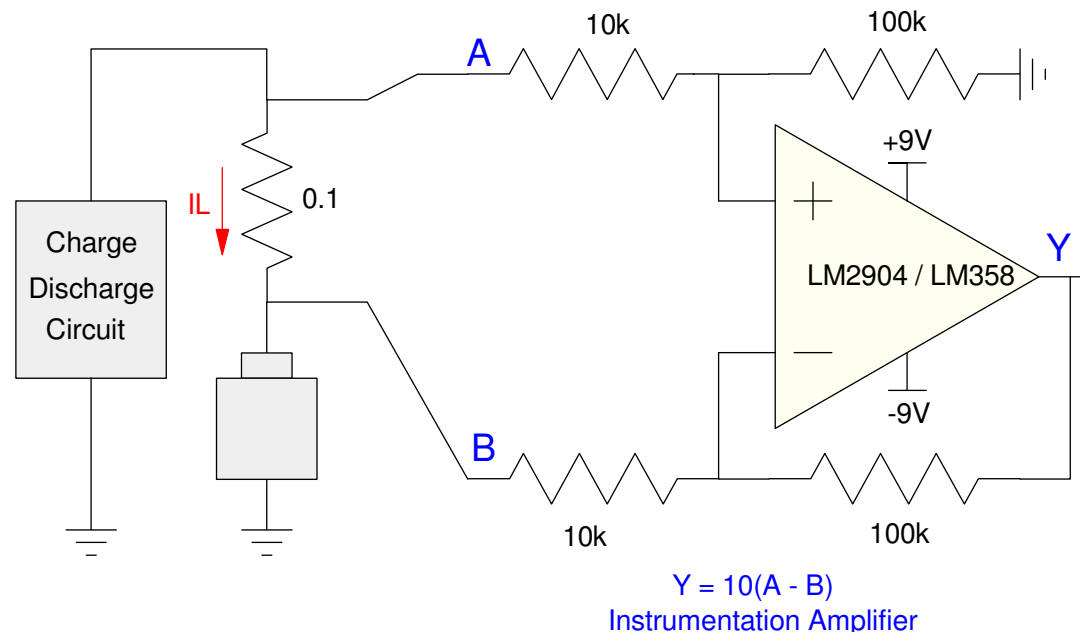- Use a 0.1 Ohm current sensing resistor
- Use an instrumentation amplifier to cancel out the offset




CircuitLab Schematic

Use a 10Vp source with 10 Ohms to set the max current to 1A

Use a sine wave to sweep current from -1A to +1A

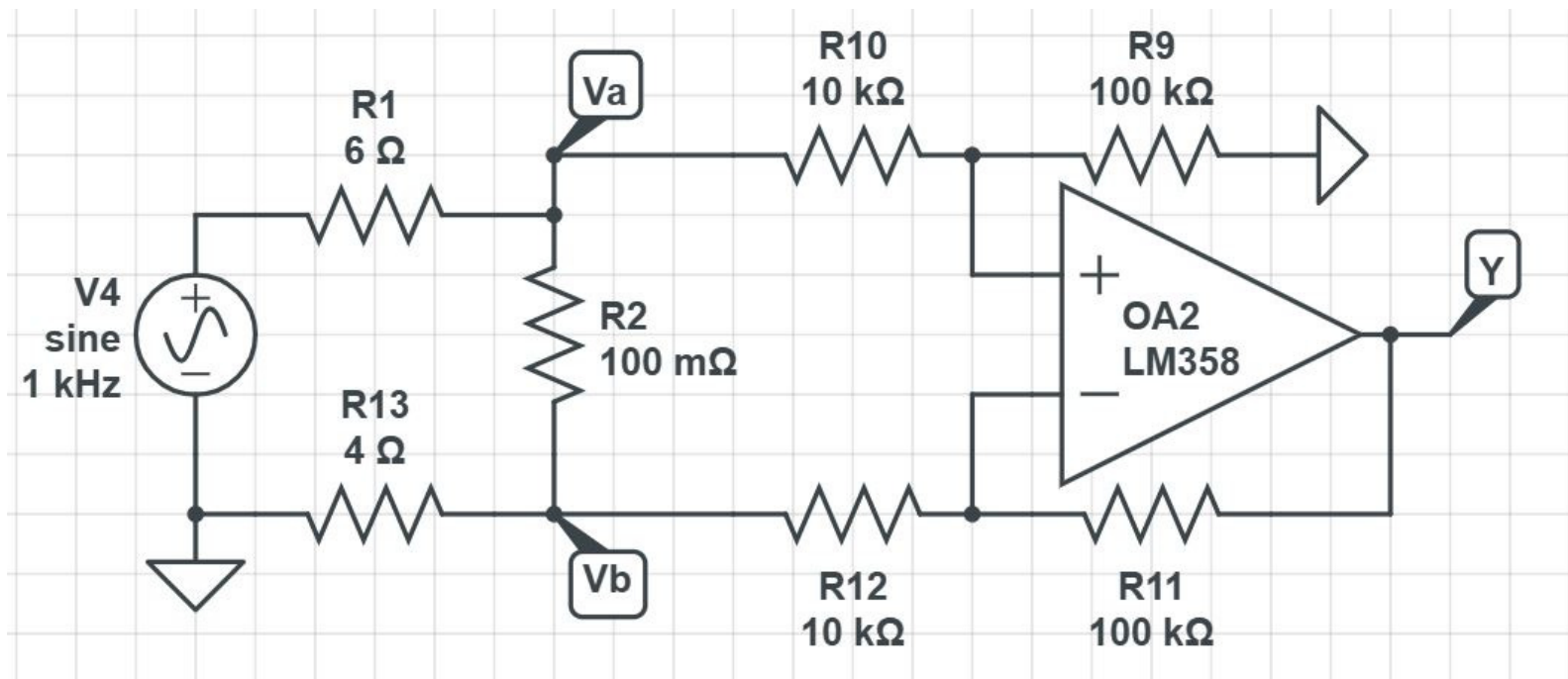Split the 10 Ohms to check how the circuit handles a DC offset




CircuitLab Simulation Results

Time-domain simulation


- 2ms duration (2 periods)
- 2 μ s step size (1000 points)

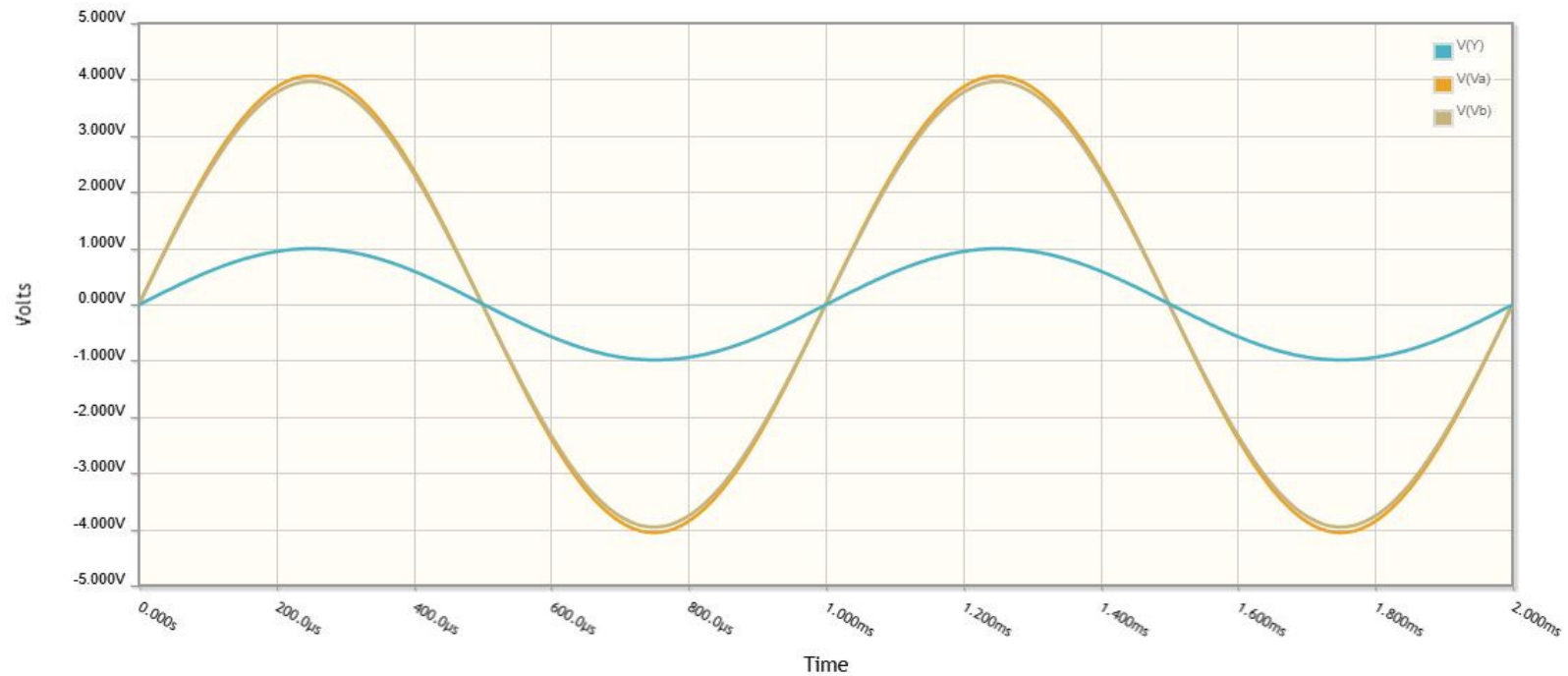Output is a sine wave (good) with the correct amplitude (1Vp)




Analog Filters


DC Block

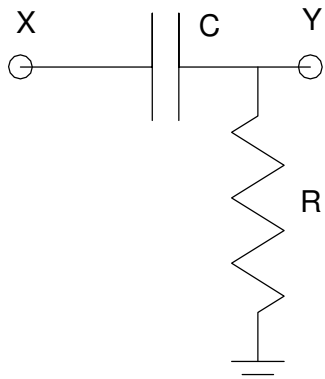


Low-Pass Filter: Real Poles

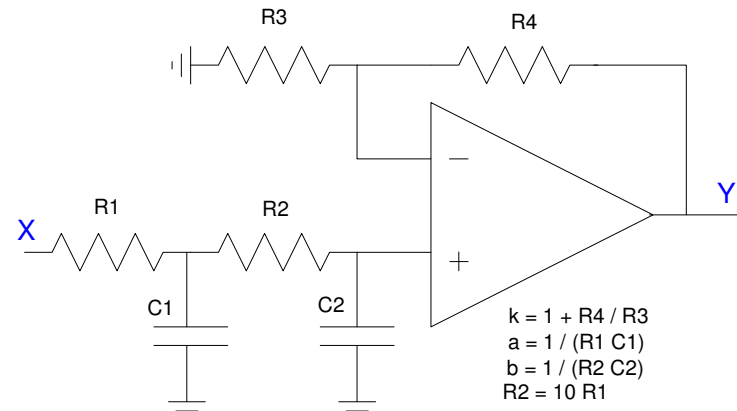

Low-Pass Filter: Single Real Pole

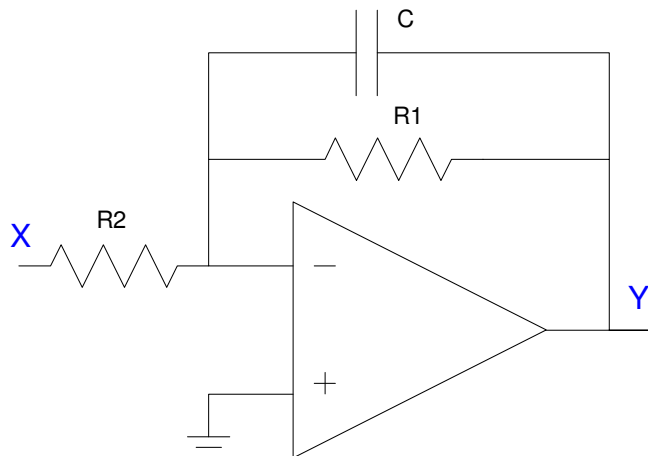

Low-Pass Filter: Complex Poles

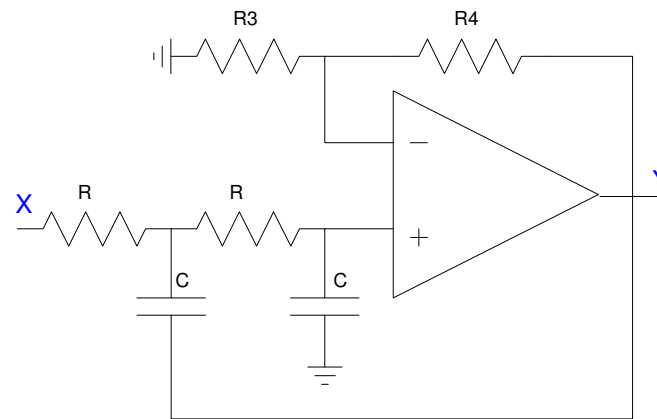


Example 1: $Y = \left(\frac{50}{(s+2)(s+3)} \right) X$

Use the circuit with two real poles. Let $R_1 = 100\text{k}$, $R_2 = 1\text{M}$

$$\left(\frac{1}{R_1 C_1} \right) = 2 \quad \Rightarrow C_1 = 50\text{nF}$$

$$\left(\frac{1}{R_2 C_2} \right) = 3 \quad \Rightarrow C_2 = 333\text{nF}$$

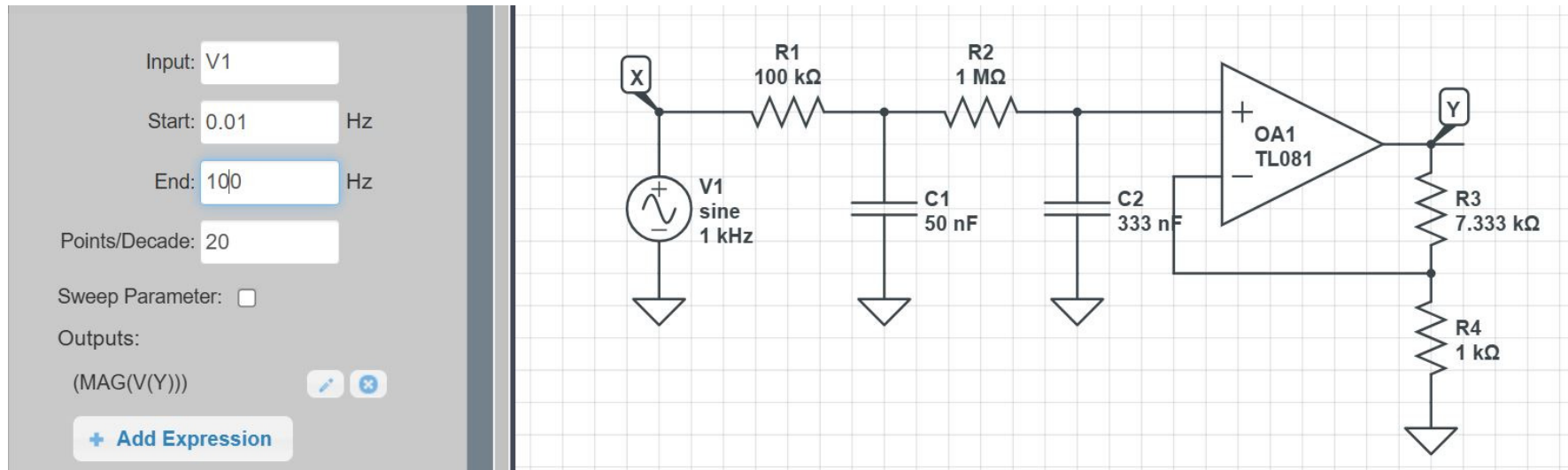
due to the lithium battery's voltage. Set the gain of the amplifier to 10



CircuitLab Simulation Results

Run a frequency sweep to see the characteristics of this filter

- 0.1 to 100 Hz
- 100 points per decade

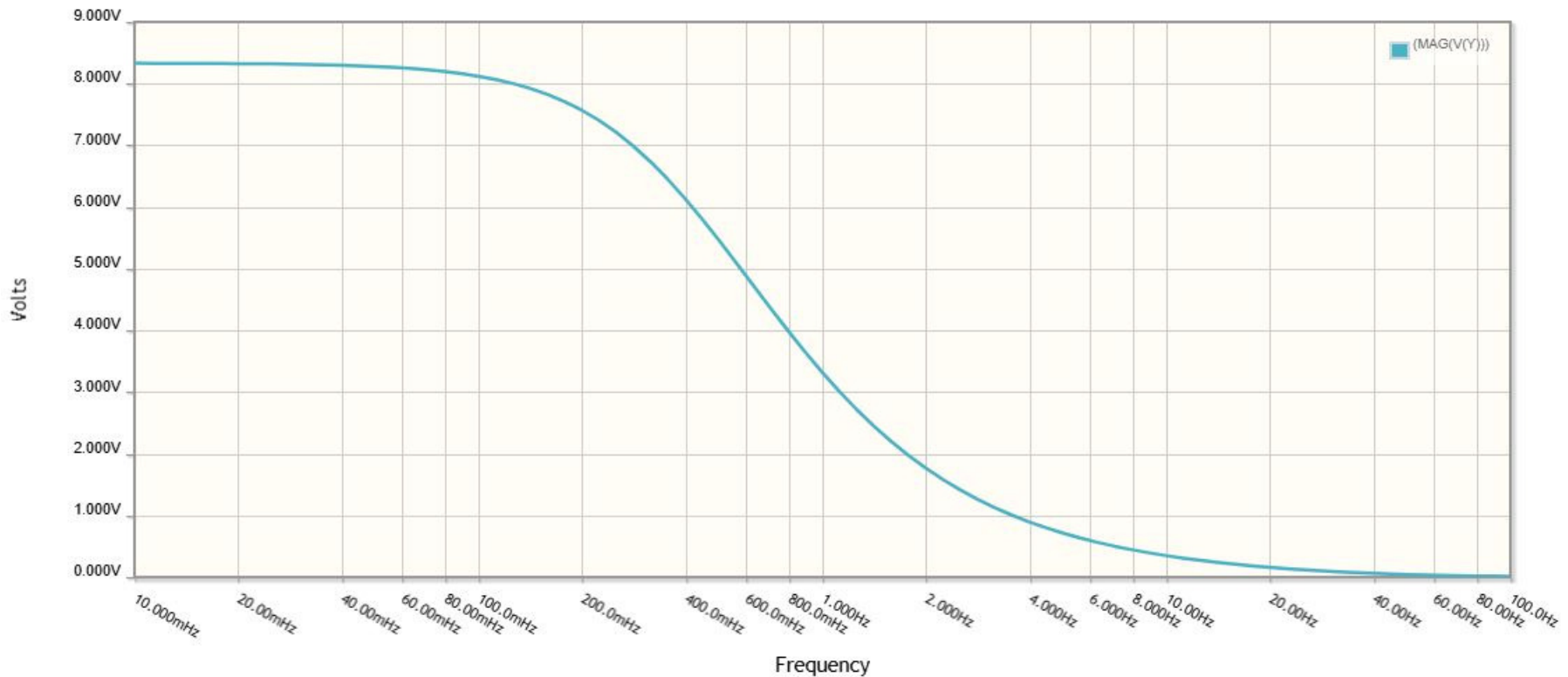


Example 2: $Y = \left(\frac{50}{s^2 + 2s + 50} \right) X$

Since this circuit has complex poles, use the low-pass filter circuit with complex poles

$$s = -7.071 \angle \pm 81.87^\circ$$

$$\frac{1}{RC} = 7.071 \quad \Rightarrow C = 1.414 \mu F$$
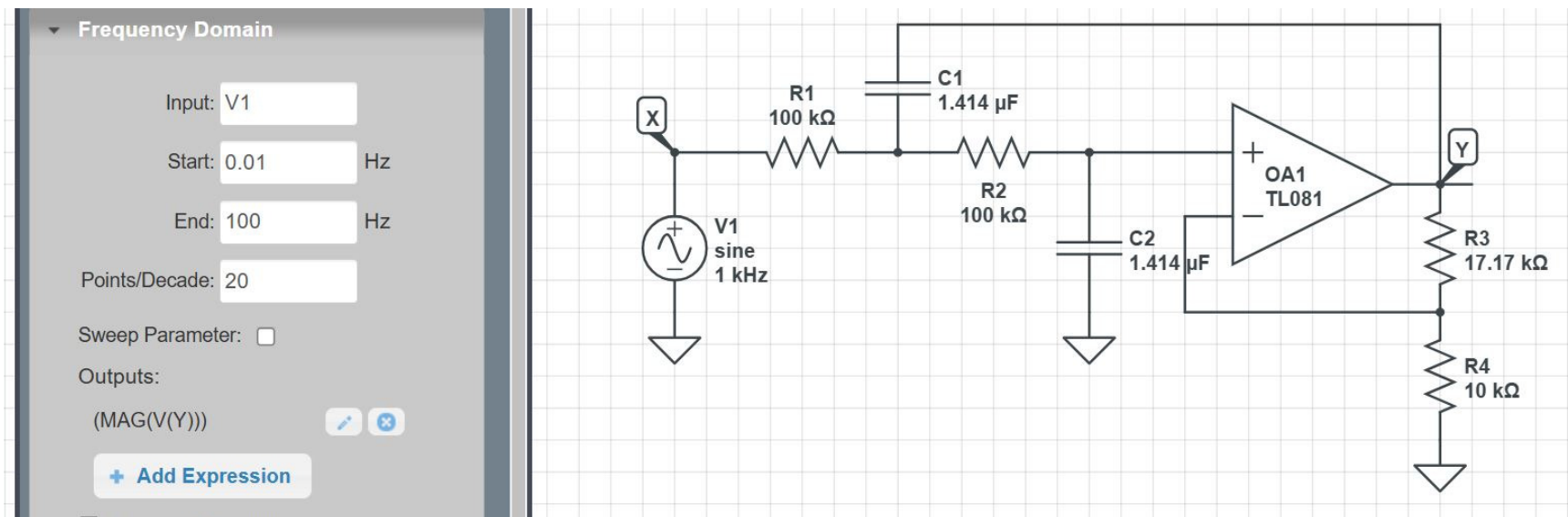
$$3 - k = 2 \cos \theta \quad \Rightarrow k = 1 + \frac{R_3}{R_4} = 2.717$$




CircuitLab Simulation Results

Run a frequency sweep to see the characteristics of this filter

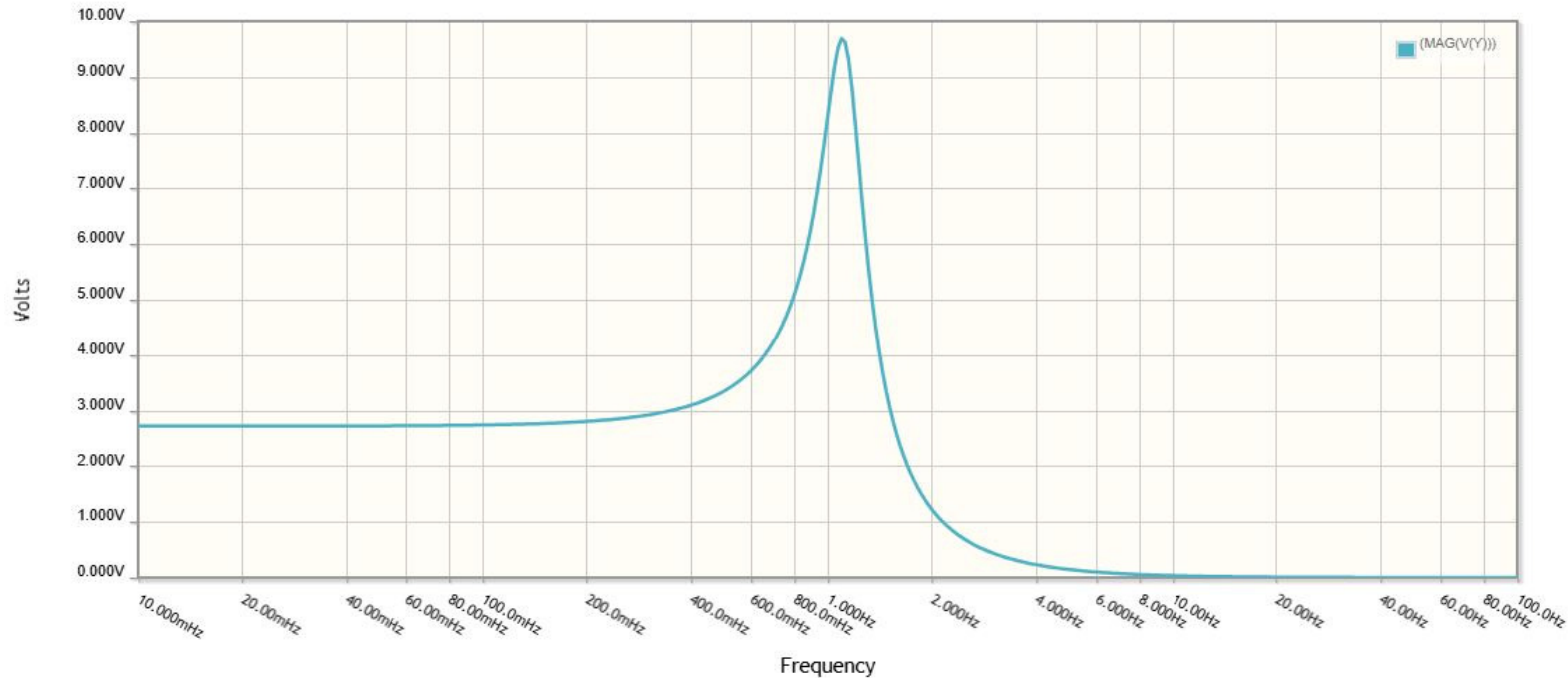- 0.1 to 100 Hz
- 100 points per decade

The complex pole shows up as a resonance at 7 rad/sec



Homework #4

- Due week #8

Simulate the major sections of your circuit using CircuitLab

- DC Analysis
 - Currents and voltages
- Transient Response (if applicable)
 - Simulate waveforms if using a 555 timer
 - Check resulting frequency and duty cycle

Compare the simulation results vs. your calculations

- Were your calculations correct?

Adjust your components to meet your requirements (if necessary)

Test Points: Include signals at test points

- +9V, +5V, ground
 - Emitter, Collector for transistors
 - Other points as needed to verify your circuit works correctly
-

Summary

Op-Amp circuits are kind of like legos

- Build up a circuit by piecing together op-amp circuits with different functions.
- One set of circuits are for digital outputs
- Another set is for analog outputs,
- Yet another set is for filters

CircuitLab lets you check your design

- Do the digital circuits switch at the correct voltages?
- Do amplifiers output a sine wave when the input is a sine wave?
 - With the correct amplitude?
- Do filters have the desired gain vs. frequency?

Note that the op-amp you use depends upon the type of circuit

- Digital circuits usually use an MCP602
 - Analog circuits usually use an LM2904 or LM358
-

