

---

# **Diodes, & Transistors**

**ECE 401 Senior Design I**

**Week #5**

Please visit Bison Academy for corresponding lecture notes,  
homework sets, and videos  
[www.BisonAcademy.com](http://www.BisonAcademy.com)

---

---

## Introduction

In ECE 401, you can choose from a dozen different circuits to build.

Regardless of which one you select, your overall design:

- Must operate at 5VDC
- Must have LEDs operating at 20mA +/- 5mA
- Must have one NPN and one PNP transistor (or more), capable of driving a 100mA load
- Must have at least one IC (Pi-Pico, MCP602 op-amp, 555 timer)

This lecture covers:

- Analysis and design of LED circuits,
  - Analysis and design of NPN and PNP electronic switches,
-

---



# Diodes

- Covered in ECE 320 Electronics I.

Diodes act as valves:

- Current allow current to flow from the anode to the cathode,
- Current block current from flowing the other way.

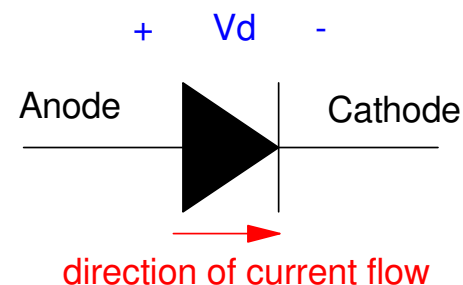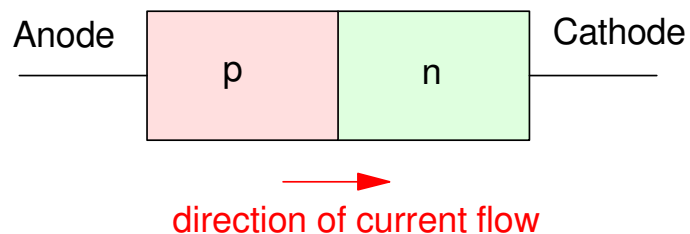Because of this, the symbol for a diode looks like an arrow: this arrow serves as a reminder for which way the current can flow.



Symbol for a diode: Diodes only allow current to flow from the anode to the cathode

---

# Diode VI Characteristics

Diodes are nonlinear devices


- This makes analysis of diode circuits difficult

Ideal Diode

- Simplified model of a diode
- $I_d = 0$  when  $V_d < V_f$
- $V_d = V_f$  when  $I_d > 0$

Not perfect, but usually good enough

- Use CircuitLab to get better answers

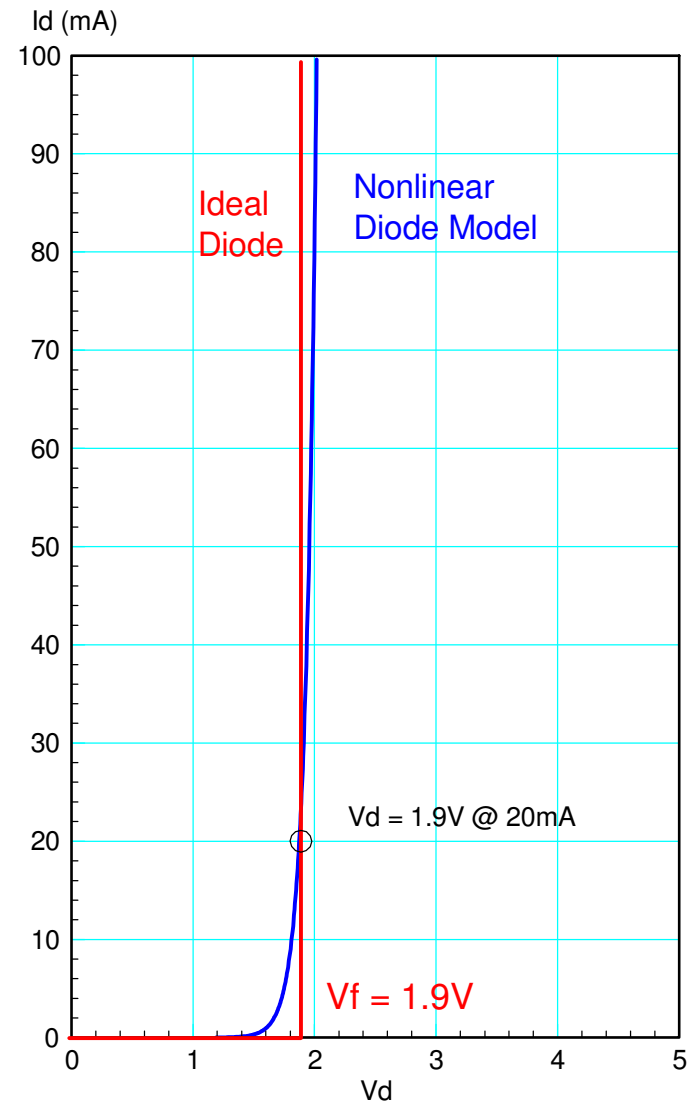


# Ideal Diode Model

$V_f$  acts like a turn-on voltage:

- Diode turns on if you apply more than  $V_f$
- Diode turns off if you apply less than  $V_f$

$V_f$  depends upon the diode

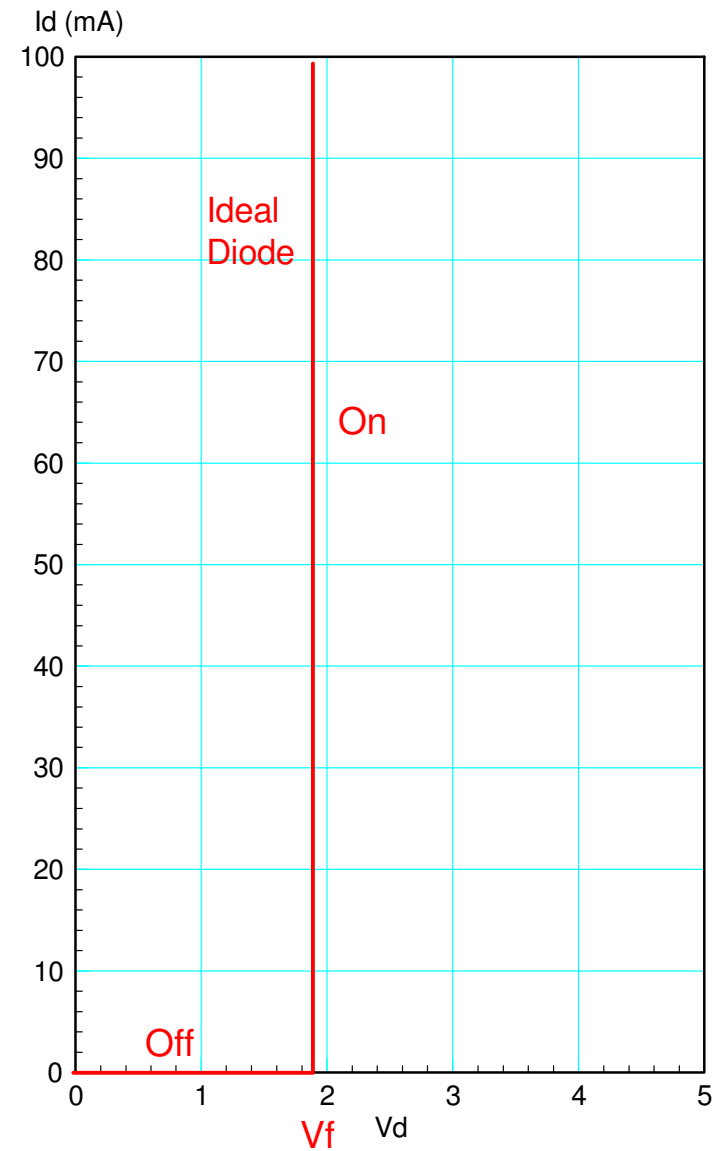- Germanium:  $V_f = 0.3V$
- Silicon:  $V_f = 0.7V$
- Red LED:  $V_f = 1.9V$
- Yellow LED:  $V_f = 2.0V$
- Green LED:  $V_f = 2.0V$  to  $3.0V$



# Diode Example (CircuitLab)

In CircuitLab, you can build this circuit through drag and drop.

- R rotates the element
- Double Click to change values
- k = 1000
- M = million
- m = milli
- u = micro



Make sure you have a ground (CircuitLab insists on this)

The screenshot displays the CircuitLab interface. On the left, a vertical toolbar contains various components: Essentials (down arrow, NAME NODE, WIRE), DC Sources (two diodes), Passive Elements (resistor, capacitor, inductor), and Voltage Signal Sources (AC sine wave, DC voltage, current source). The main workspace shows a circuit diagram with a sine wave source labeled 'V1 sine 1 kHz' connected to a diode labeled 'D1 1N4004'. A ground symbol is connected to the bottom terminal of the diode. On the right, a panel titled 'My Device Models' shows a list of diode models (1N4001 to 1N4005) with 'Buy' buttons. Below the list is a 'View All Diodes In Stock' button. To the right of the list is a detailed configuration panel for the selected diode (D1, Part#: 1N4004), showing parameters like L\_S, R\_S, C\_J0, and M\_J, along with 'Save Custom Device Model' and 'Import SPICE Model' buttons.

Once completed, you can determine the voltages and currents by

- Clicking on Add Expression and then click on the voltage node to see that voltage
- Click on one side of a resistor to see the current through that resistor

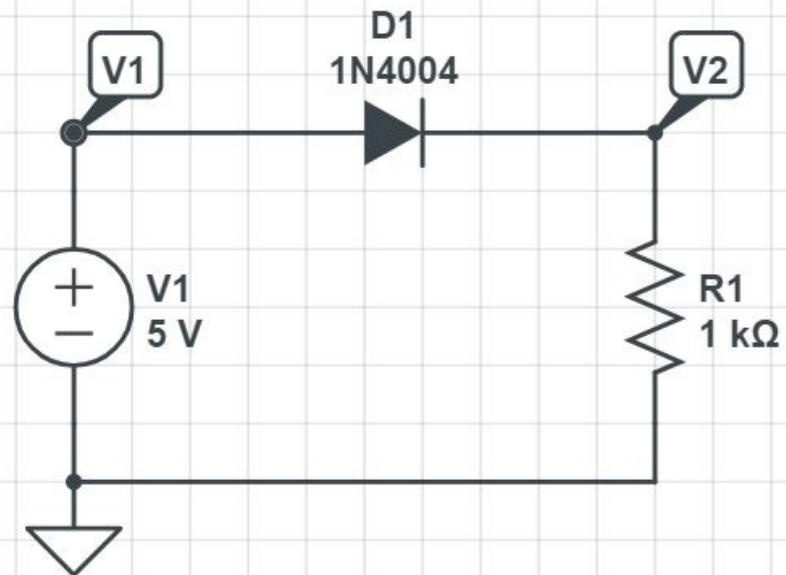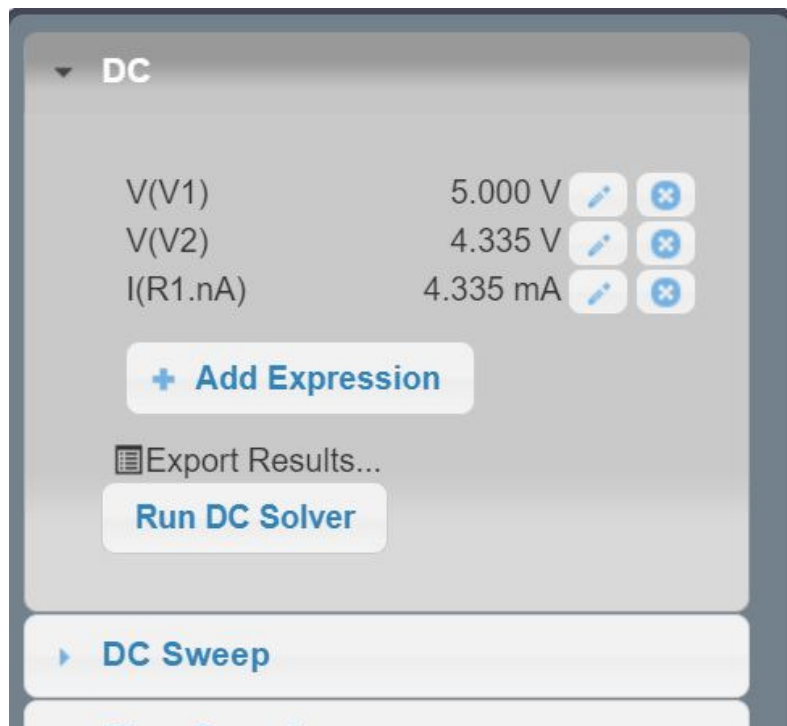
When the diode is turned on ( $I_d > 0$ ), the voltage drop is 0.7V (ish)



When you try to push current backwards, the diode turns off

- $I_d = 0$  (ideal diode)
- $I_d = -76.90\text{pA}$  (CircuitLab)

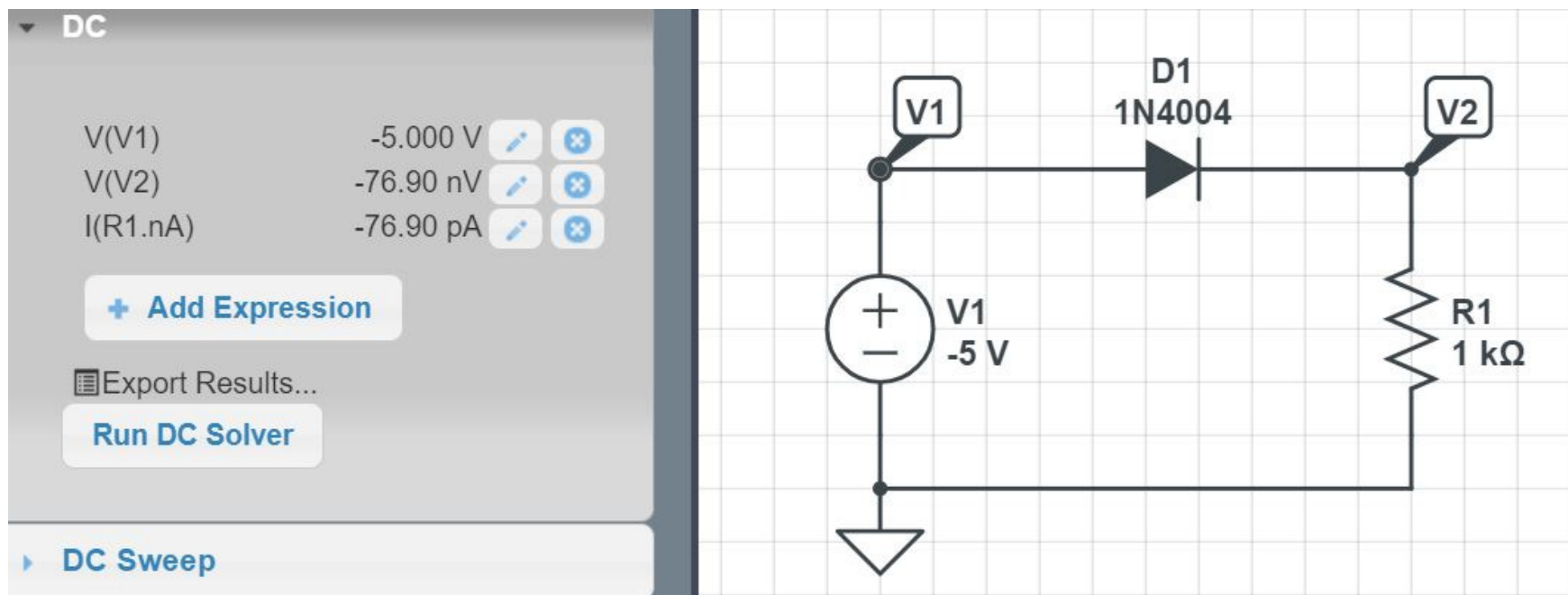
Diodes *do* conduct current when reverse biased, but it's really small





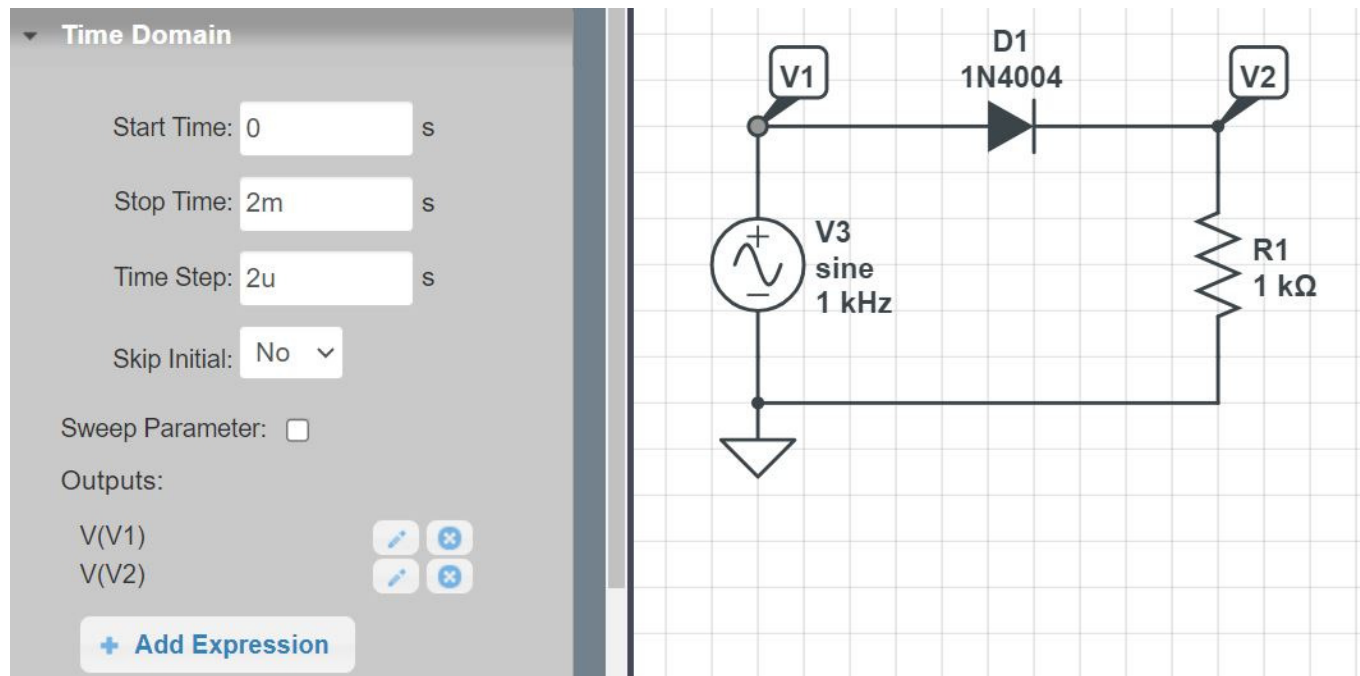
# CircuitLab & Time Domain Simulations

- Similar to an oscilloscope
- Apply a sine wave for V3
- Run the simulation for 2-3 cycles
- Set the sampling rate 1000x smaller (gives 1000 points on the graph)


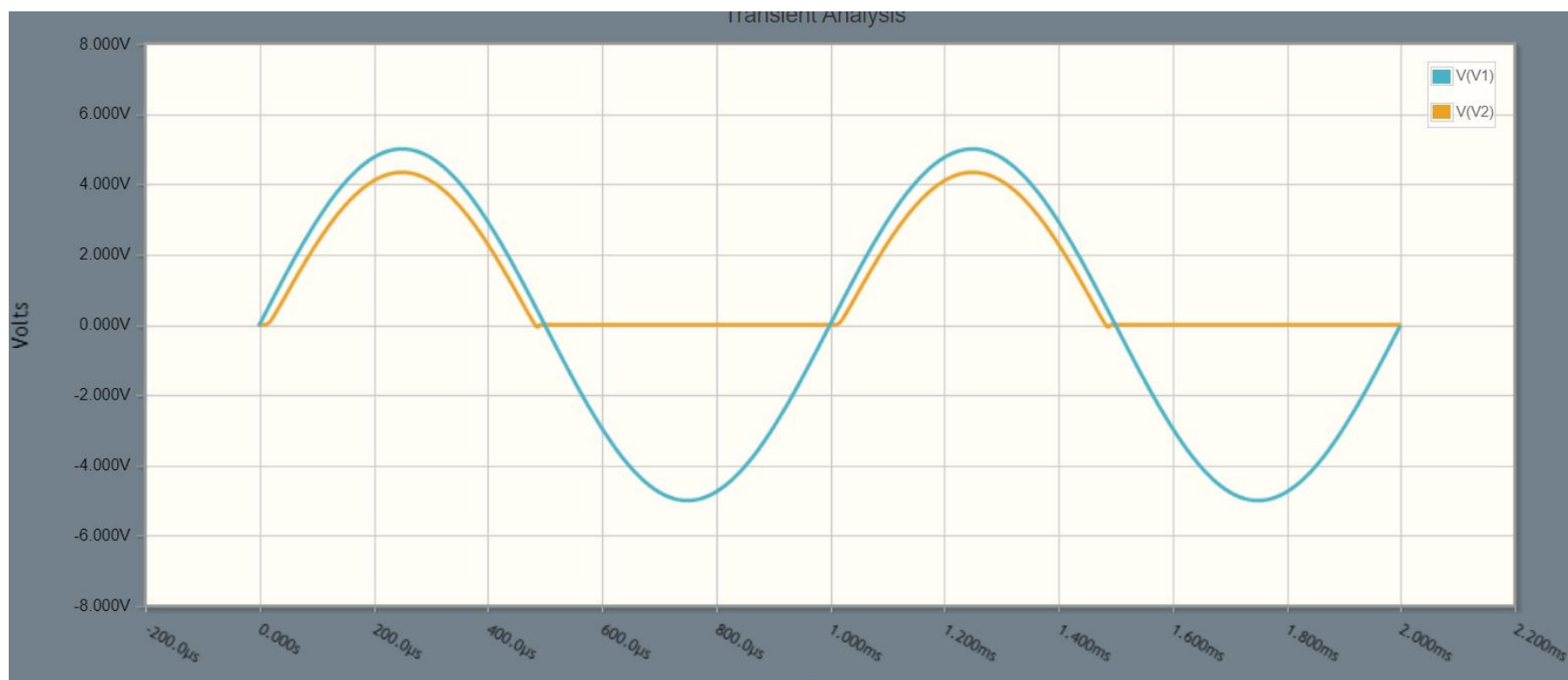
## Resulting Waveform:

- When  $V_{in} > 0.7V$ , the diode turns on
  - $V_{out} = V_{in} - 0.7V$  (ish)
- When  $V_{in} < 0.7V$ , the diode turns off
  - $V_{out} = 0V$



## Diode Circuit Analysis:


- Determine which diodes are on and off
  - Not always that easy
- Replace with the ideal diode model
- Determine voltages and currents

Calculations:

$$I_1 = \left( \frac{5V - 0.7V}{1k} \right) = 4.3mA$$

$$I_2 = \left( \frac{5V - 1.9V}{2k} \right) = 1.55mA$$
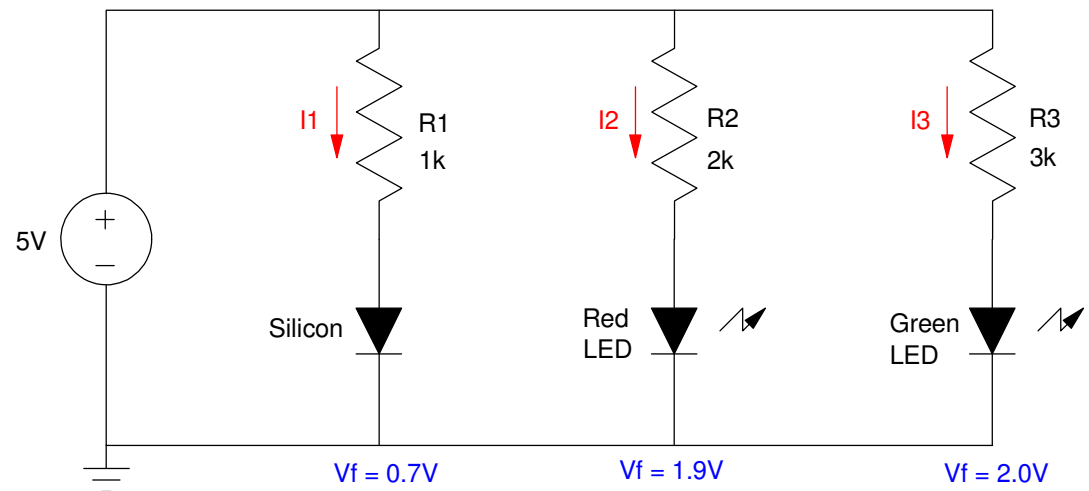
$$I_3 = \left( \frac{5V - 2.0V}{3k} \right) = 1.00mA$$



## Diode Circuit Design:


- Pick the current desired
  - Light is proportional to current
- Calculate the resistance needed

Example: Set  $I_d = 20\text{mA}$

$$R_1 = \left( \frac{5\text{V} - 0.7\text{V}}{20\text{mA}} \right) = 215\Omega$$

$$R_2 = \left( \frac{5\text{V} - 1.9\text{V}}{20\text{mA}} \right) = 155\Omega$$
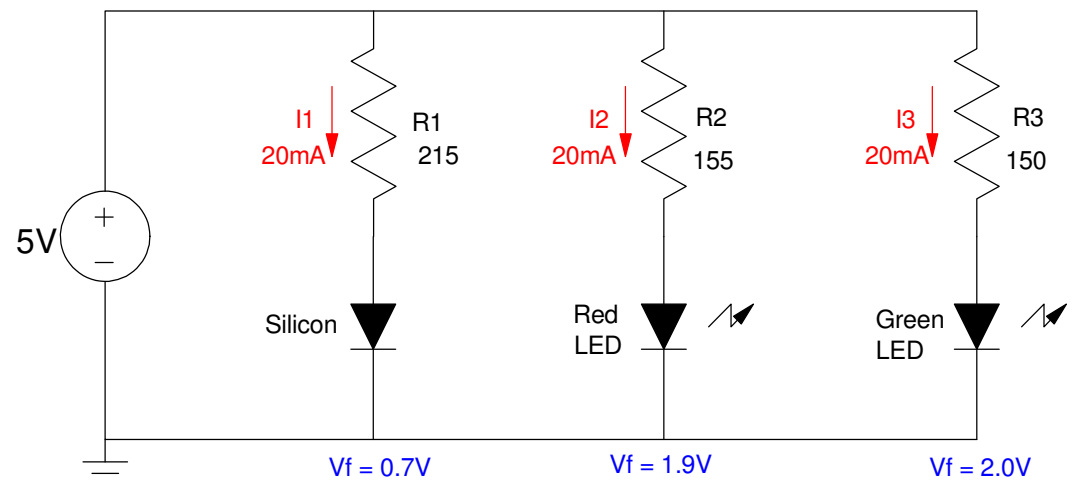
$$R_3 = \left( \frac{5\text{V} - 2.0\text{V}}{20\text{mA}} \right) = 150\Omega$$



---

## Light Emitting Diodes (LEDs)

LEDs are nothing more than diodes - except that they produce light proportional to the current flowing through them. As diodes, they can be approximated with an ideal-diode model:

- $I_d = 0$  if  $V_d < V_f$
- $V_d = V_f$  if  $I_d > 0$

The on-voltage ( $V_f$ ) depends upon the diode and is usually specified in the diode's data sheets:

LED	$V_f$	mcd	Wavelength	Cost	Digikey PN
Red	1.9V @ 20mA	30mcd @ 20mA	645nm	\$0.13	732-5016-ND
Yellow	2.0V @ 20mA	450mcd @ 20mA	592nm	\$0.18	732-5018-ND
Green	2.1V @ 20mA	140mcd @ 20mA	572nm	\$0.21	732-5017-ND

---

---


## With LEDs, brightness is proportional to current

Assuming a 9V source (the kit assume you're using a 9V battery). the current and brightness of the first diode (330 Ohms) is:

$$I = \left( \frac{9V - 2.0V}{330\Omega} \right) = 21.21mA$$

The brightness is then proportional to this current where 20mA = 450mcd:
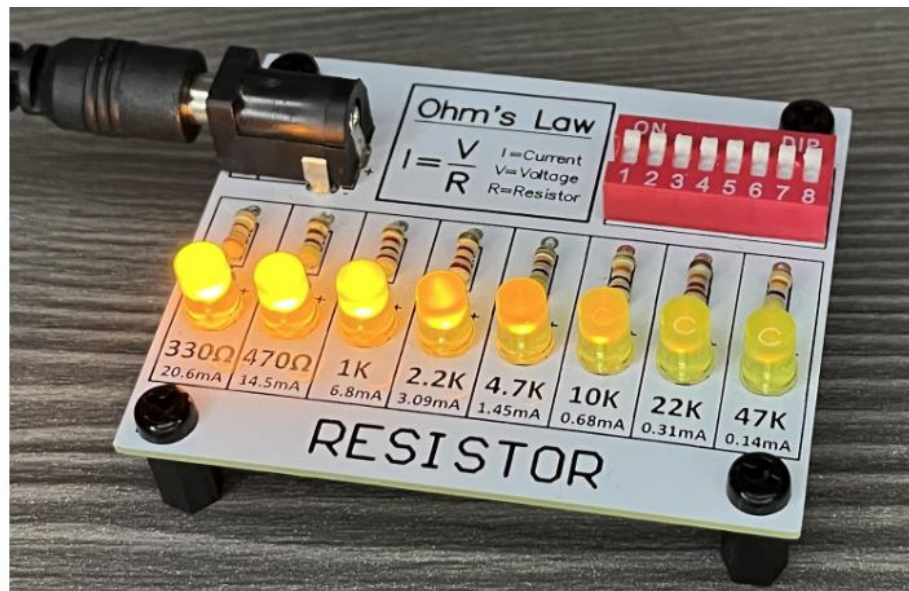
$$\left( \frac{21.21mA}{20mA} \right) 450mcd = 477.2mcd$$



---



# Voltage Regulation

In ECE 401,

- Power to your PCB comes from a 9V battery, while
- Your components on your PCB operate off of 5VDC.

Solution: Use a LM7805 regulator

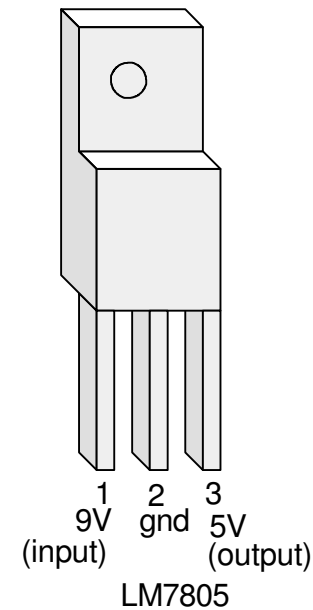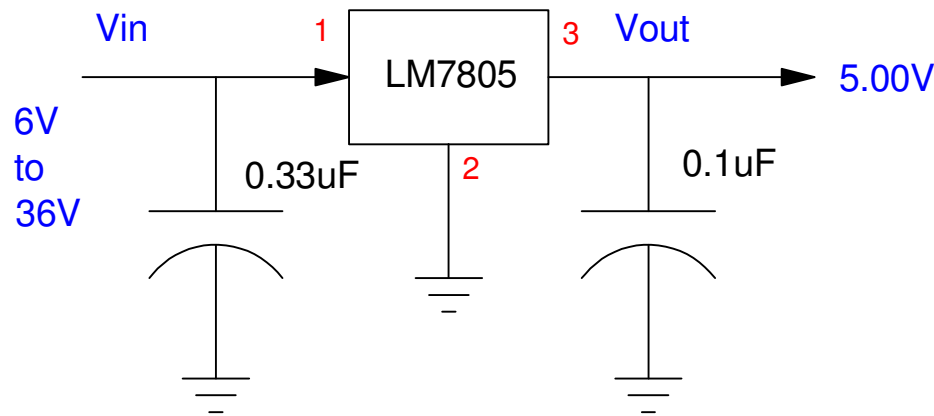- Pro: Simple circuit
- Con: Efficiency = 55% @ 9V




## Example:

- Convert 9V down to 5V, and
- Drive an LED at 10mA from the 5V source

Assuming a red LED
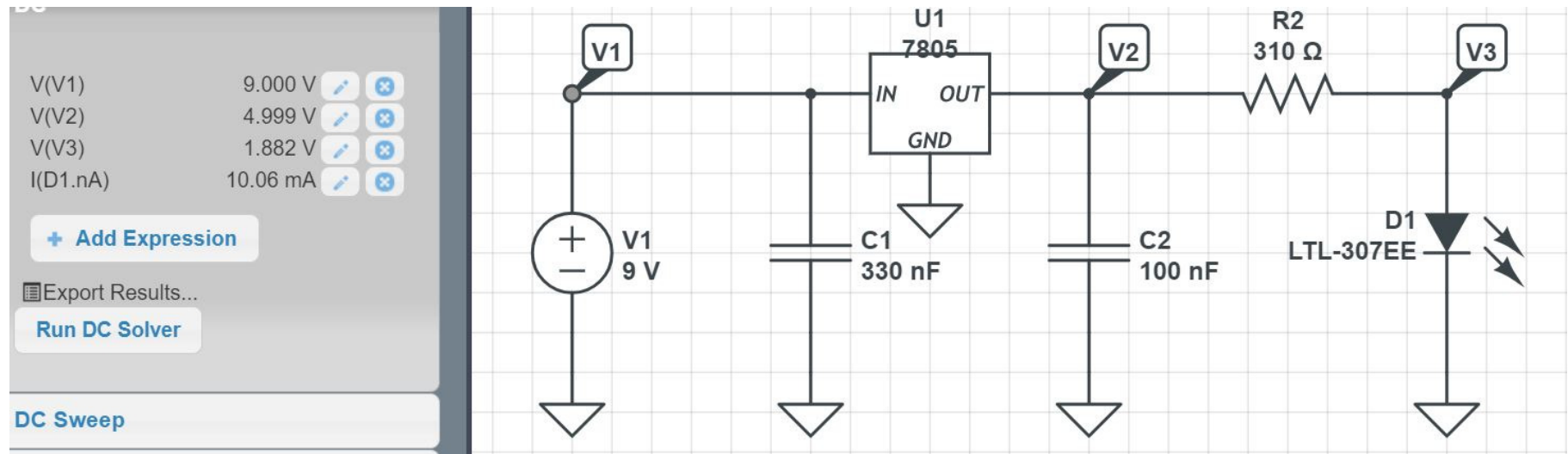
$$R = \left( \frac{5V - 1.9V}{10mA} \right) = 310\Omega$$





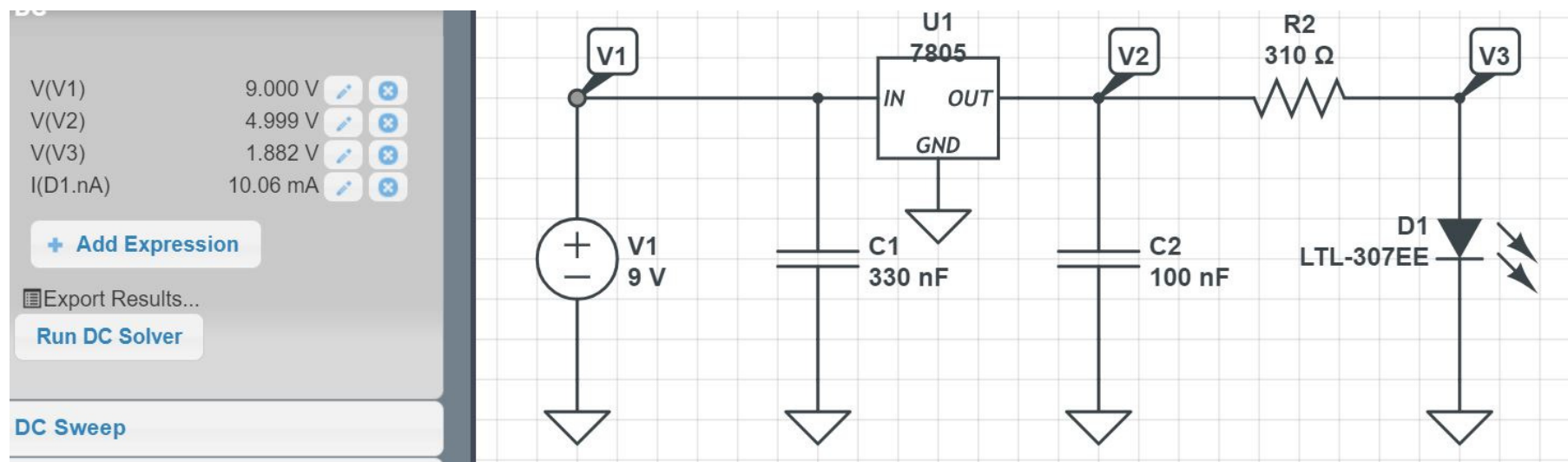
## Interpreting the Results:

- $V2 = 5V$  (close)
  - The 7805 is doing its job
- $V3 = 1.9V$  (close)
  - The red LED is on
- $I3 = 10mA$  (close)
  - $R2$  is correct

You could find tune  $R2$  if you really want  $10.00mA$  exactly.



---

# Reverse Polarity Protection & Overcurrent Protection

Another requirement for your PCB in ECE 401 is to add

- Reverse polarity protection
  - connecting 9V to your PCB backwards will not fry your PCB
- Overcurrent protection
  - if your circuit draws too much current, a fuse blows.

There are several ways to do this.


---

## Method #1: Diode + Fuse.

- Diodes do not allow current to flow backwards
  - Blocks current if the 9V battery is inserted backwards
- Fuse blows if the load is too much
  - 1 Ohm resistor replaces the fuse for ECE 401 (2 cents)

Problem:


- Drops 0.7V through the diode

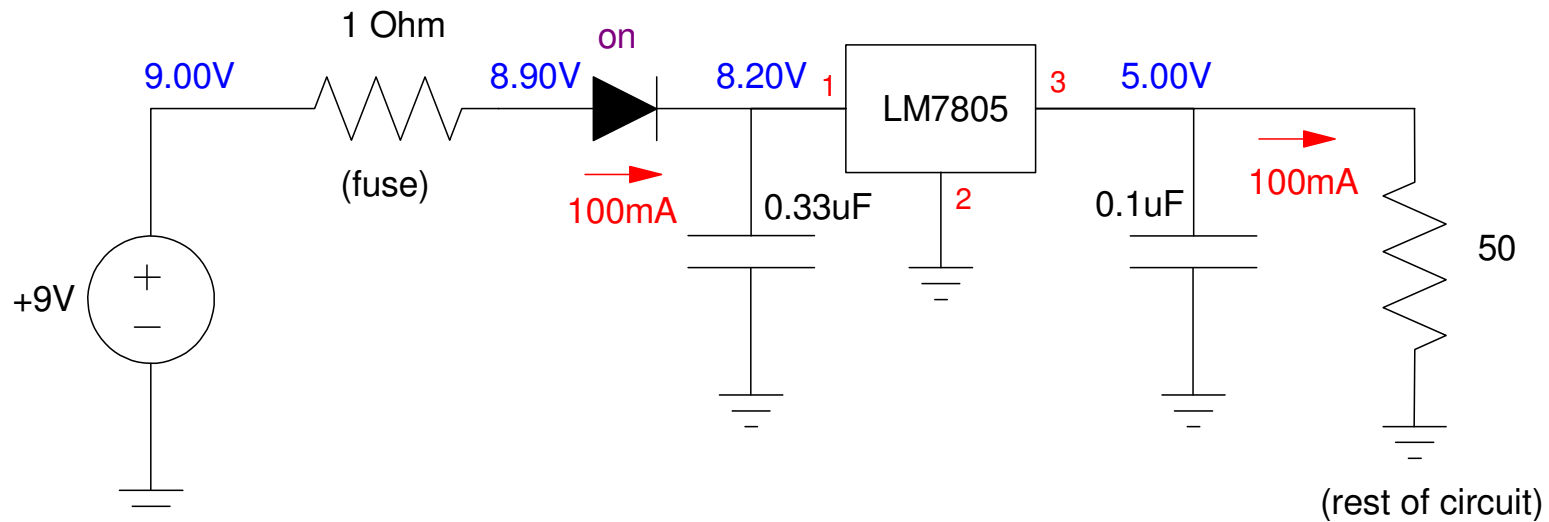
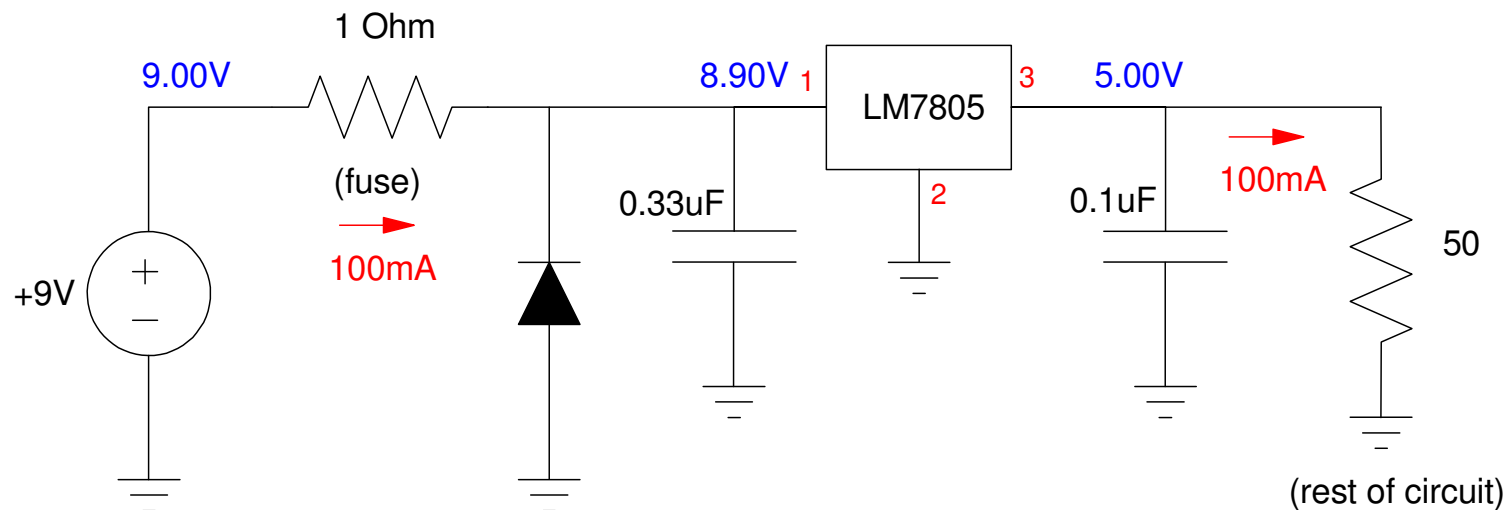
## Method #2: Fuse + Diode.

Add a reverse biased diode to ground

- If the 9V battery is connected correctly, the diode remains off.
- If the 9V battery is reversed,
  - The diode turns on, limiting the voltage to the LM7805 to  $-0.7V$ ,
  - The current through the fuse becomes large (9A), blowing the fuse.



---

# BJT Transistors

## Bipolar Junction Transistors

- Electronic switches (you can turn a device on and off using 0V & 5V),
- Which amplify current (1mA can turn on and off a device which draws 100mA)

The current amplification and the maximum current a given BJT transistor can handle depends upon which transistor you're using.

Spec	3904 NPN	3906 PNP
Current Gain (min)	100	100
Max Current	200mA	200mA
V <sub>be</sub>   (on)	0.7V	0.7V
V <sub>ce</sub>   (sat)	0.2V	0.2V
Cost (ea)	\$0.11	\$0.11



---

# NPN and PNP Transistors

Two types of BJT transistors exist:

- PNP: an electronic switch which connects your device to +5V, or
- NPN: an electronic switch which connects your device to ground.

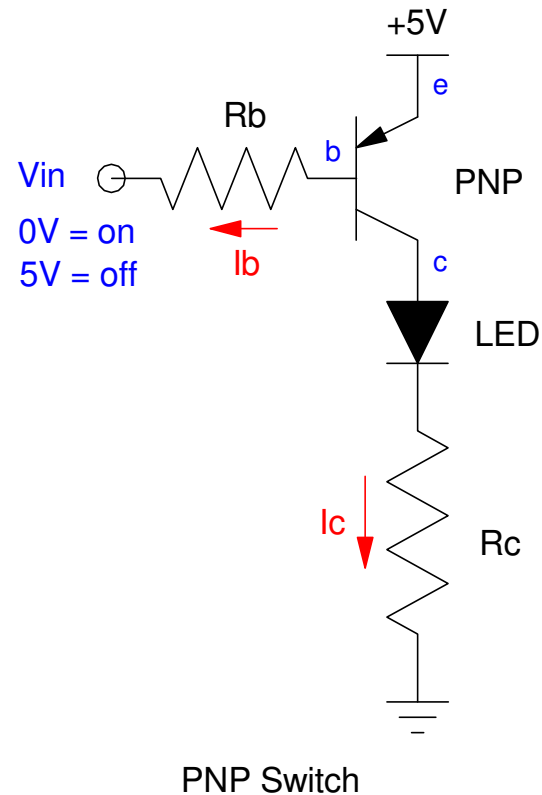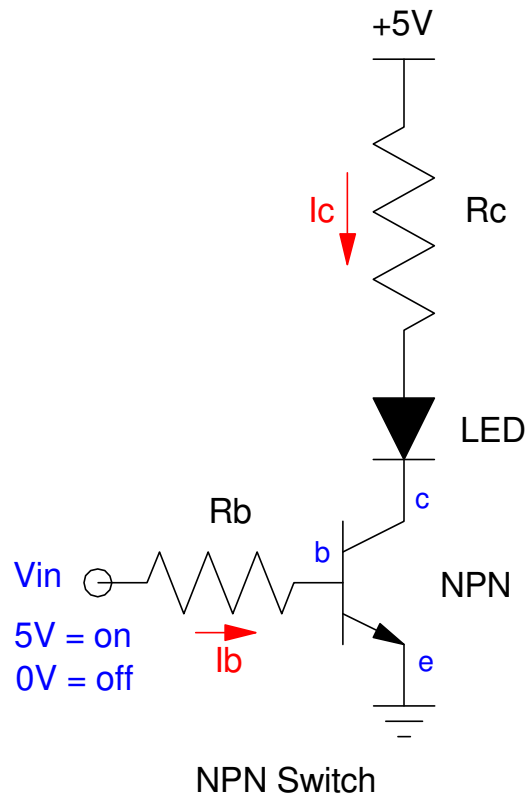The basic circuit for each of these are as follows:



## Diode from Base to Emitter

The arrow going between the base and the emitter is all important:


- It represents a diode (a pn junction)
- It tells you the direction current flows
- The base current controls the collector current

$I_b$  limits the collector current

$$I_c = \beta I_b = 100 I_b$$

It does this by dumping voltage

- Whatever it takes to set  $I_c$

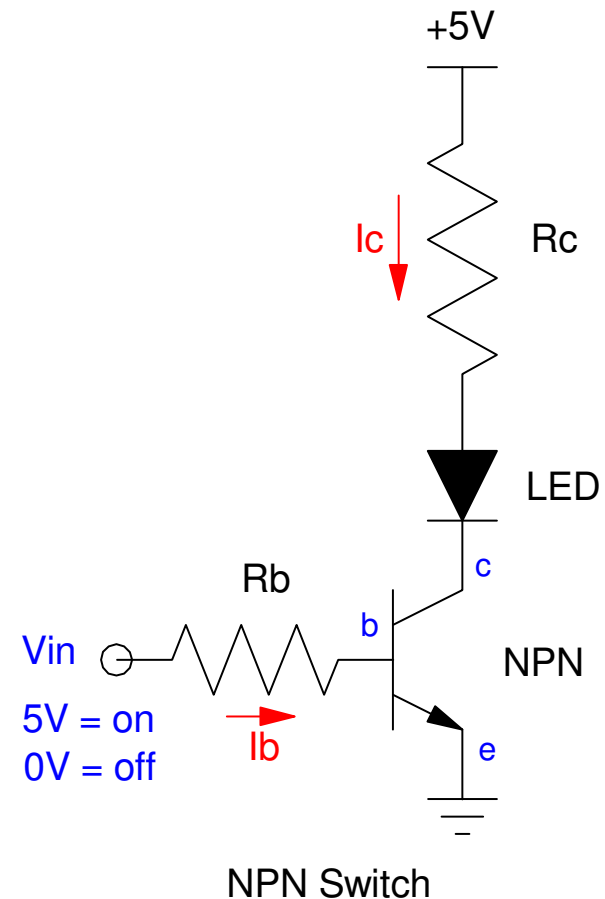


## Load Lines

A good way to see how a transistor switch operates

- When  $I_c = 0\text{mA}$ ,  $V_{ce} = 5\text{V}$ 
  - the x-axis intercept
- When  $V_{ce} = 0\text{V}$ ,  $I_c = 20\text{mA}$ 
  - the y-axis intercept

The line connecting these two points is called *the load line*.

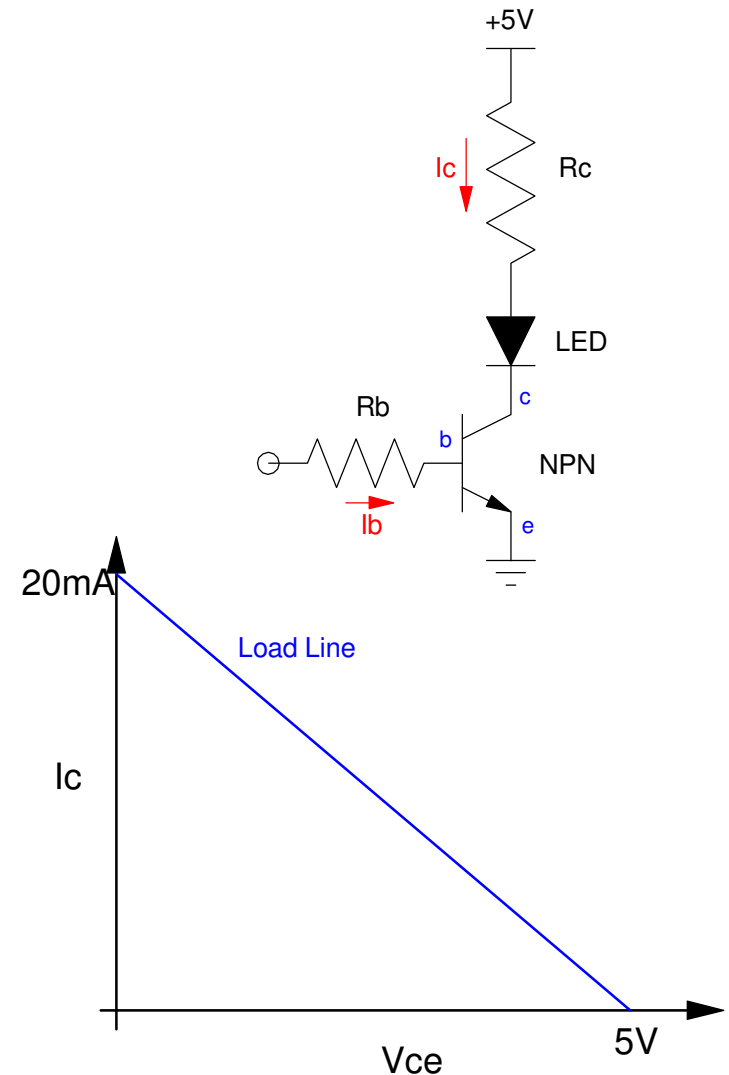Any solution has to be on the load line somewhere.





## Off State:


- $I_b = 0$
- $I_c = 100 \cdot I_b = 0$
- $V_{ce} = 5V$

## Active Region

- $0mA < I_b < 20mA$
- $5V > V_{ce} > 0.2V$
- $I_c = 100 \cdot I_b$
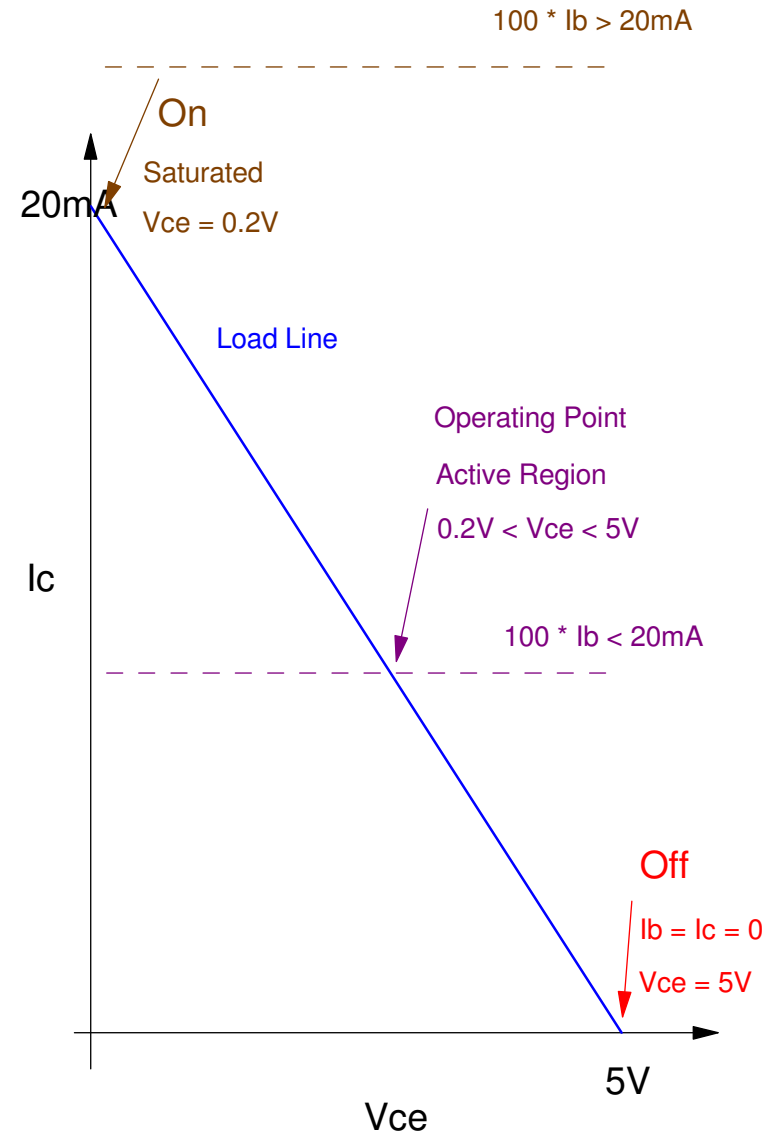
## On State

- Saturated Region
- $100 \cdot I_b > 20mA$
- $V_{ce} = 0.2V$



---

## The Active Region is Bad

You want to operate in the ON and OFF state

### Off State


- $I = 0$
- $P = V * I = 0$

### On State

- $V = 0.2V$  (almost zero)
- $I = 20mA$
- $P = 4mW$  (almost zero)
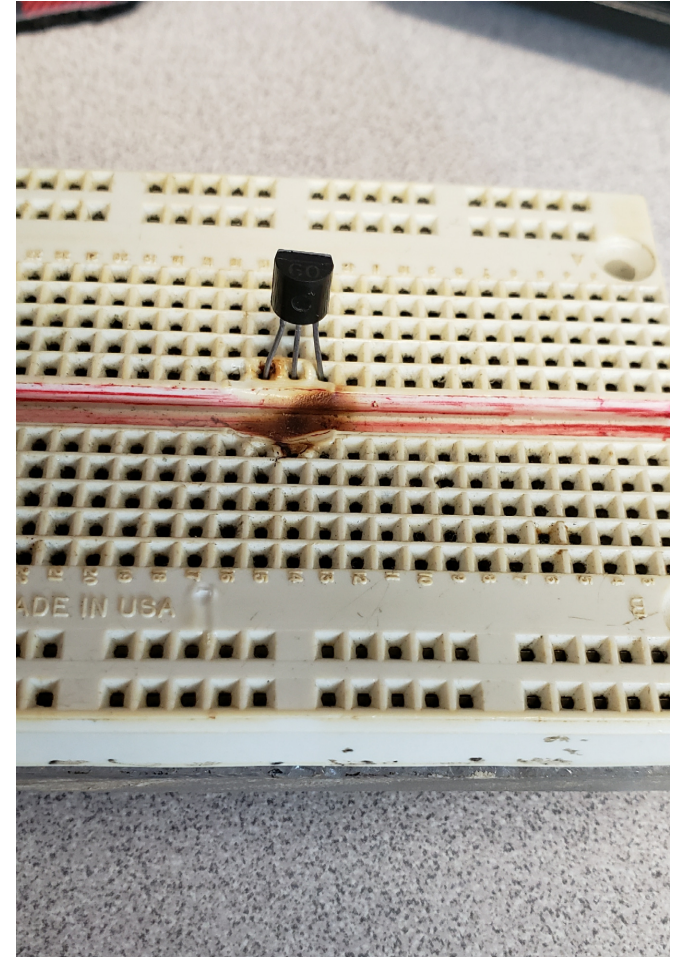
### Active Region

- $P = V * I$
- The transistor gets hot
- You start to melt your breadboard



## Analysis of Transistor Switches:

- Same equations for PNP and NPN

Off State

- Easy:  $I_b = I_c = 0$

On State:

$$V_{ce} = 200mV$$


$$I_c = \left( \frac{5V - V_f - V_{ce}}{R_c} \right)$$

$$I_b = \left( \frac{5V - 0.7V}{R_b} \right)$$

Check that you're saturated:

$$\beta I_b > I_c$$

$$I_b > \left( \frac{I_c}{100} \right)$$

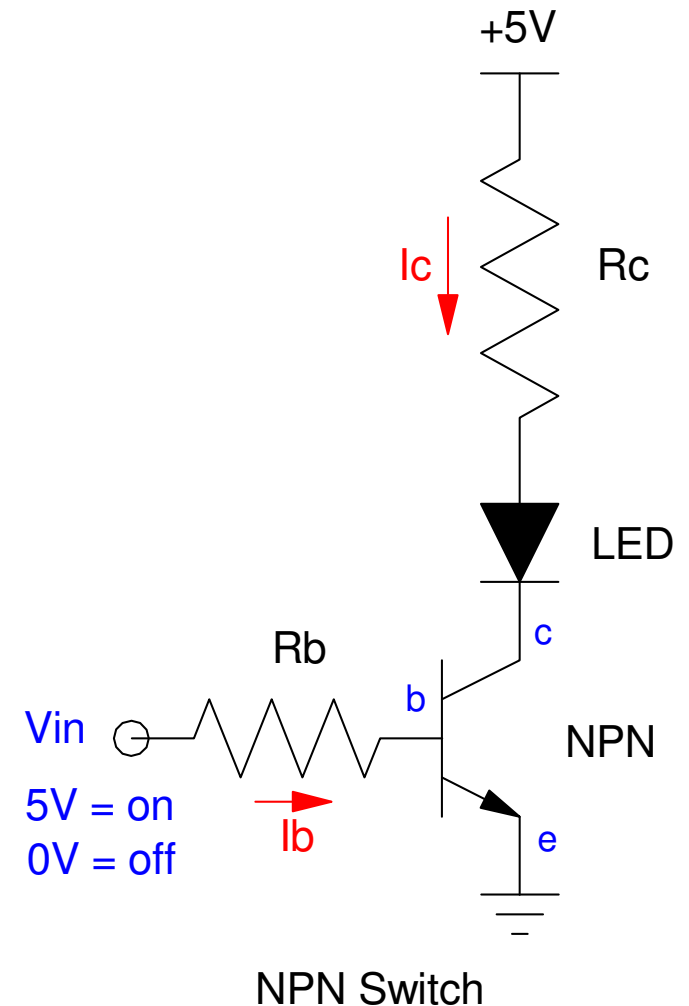

# BJT Switch Example


Assume

- $R_c = 50 \text{ Ohms}$
- $R_b = 1k \text{ Ohms}$
- $V_f = 1.9V$  (red LED)
- 3904 NPN transistor with a current gain of 100

What you expect when  $V_{in} = 5V$  is


- $V_b = 0.7V$  *the drop across a silicon diode*
- $V_c = 0.2V$  *saturated*
- $I_c = 58.0mA$
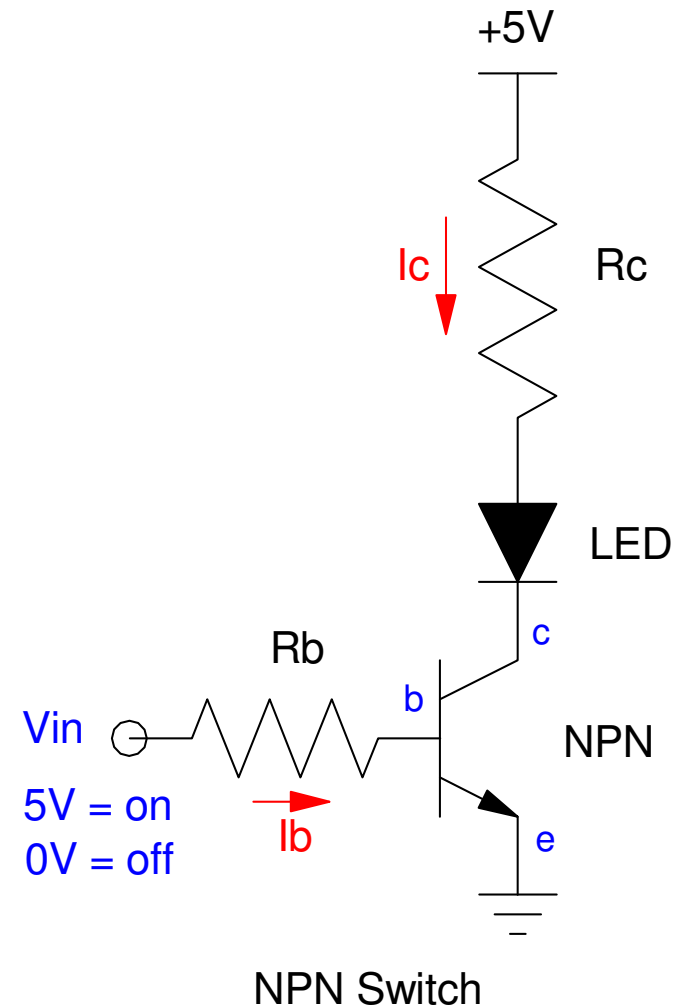
$$I_c = \left( \frac{5V - 1.9V - 0.2V}{50\Omega} \right) = 58.0mA$$



In CircuitLab, what you get is close but slightly different:

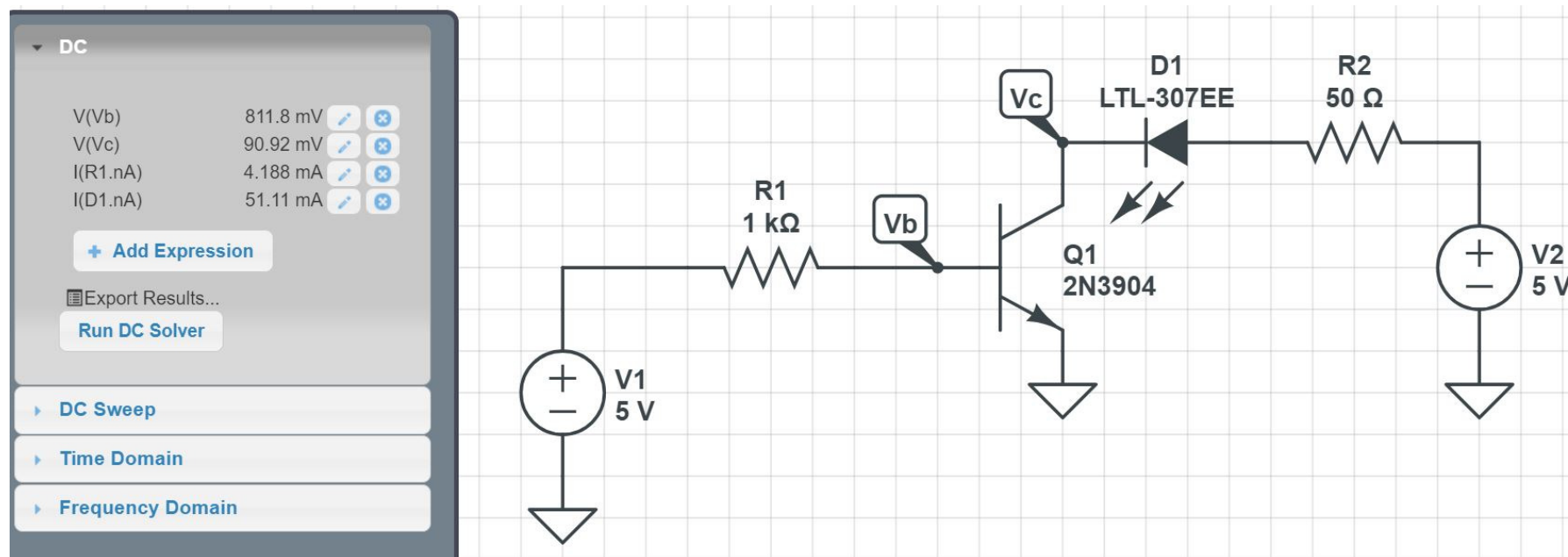- $V_b = 0.8118V$ 
  - calculated =  $0.7V$  (ideal diode)
- $V_c = 0.0909V$ 
  - calculated =  $0.2V$
- $I(D1) = 51.11mA$ 
  - Close to  $58.0mA$




# Operation in the Active Region

If  $I_b$  is too small, then the transistor enters the active region (bad)

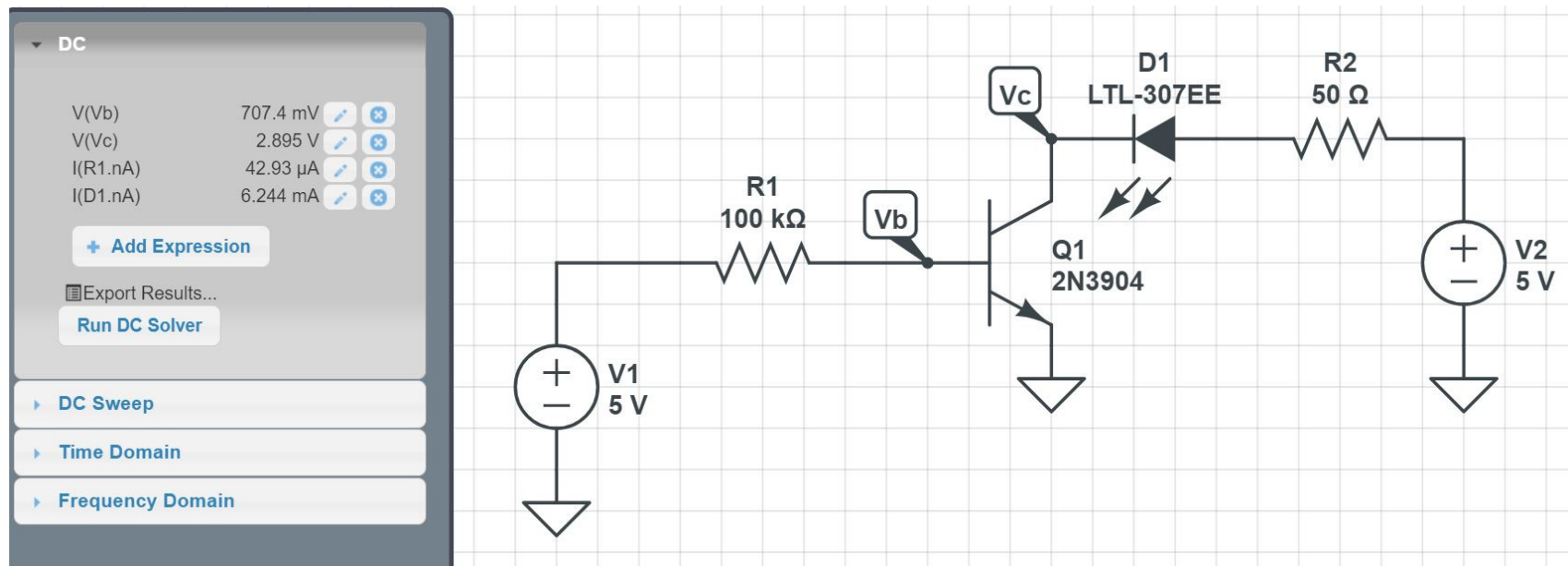Example: Increase  $R_b$  to 100k

- $I_b = 42.93\mu\text{A}$
- $I_c = \min(\beta I_b, \max(I_c)) = 6.21\text{mA}$
- $V_{ce} = 2.85\text{V}$  (active region)




---

## What happens when you operate in the active region?

- $I_c < 58\text{mA}$
- The transistor gets hot
  - and can melt the breadboard

Avoid operating in the active region when using a transistor as a switch

- Keep  $V_{ce} = 0.2\text{V}$  (ish)

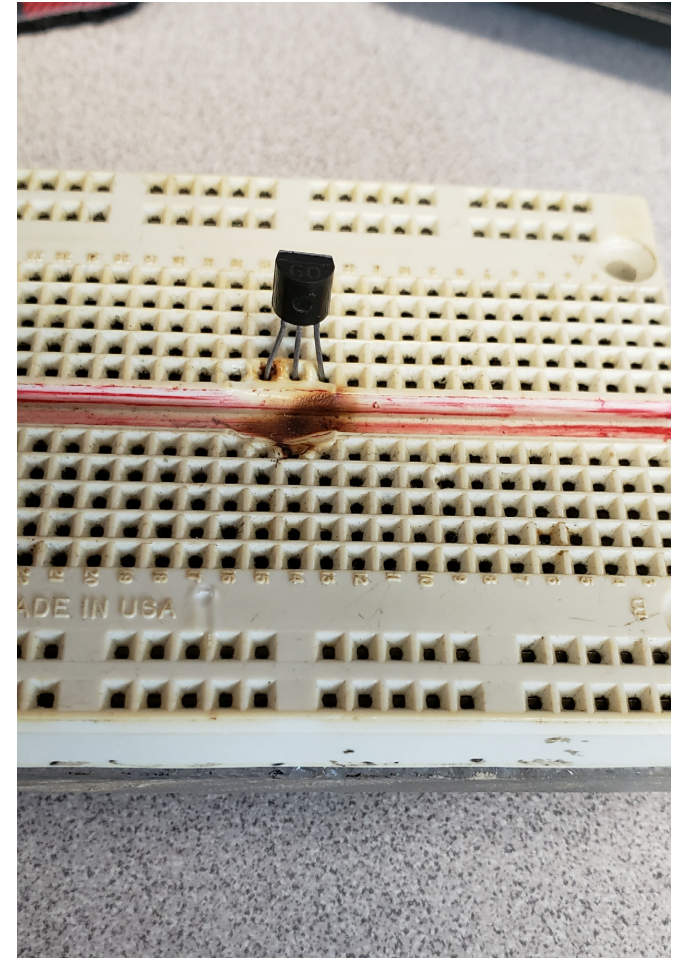


## Design of Transistor Switches:

- Pick  $R_c$  to set the desired current
- Pick  $R_b$  to saturate the transistor
  - $I_b > I_c/100$

For example, design a circuit

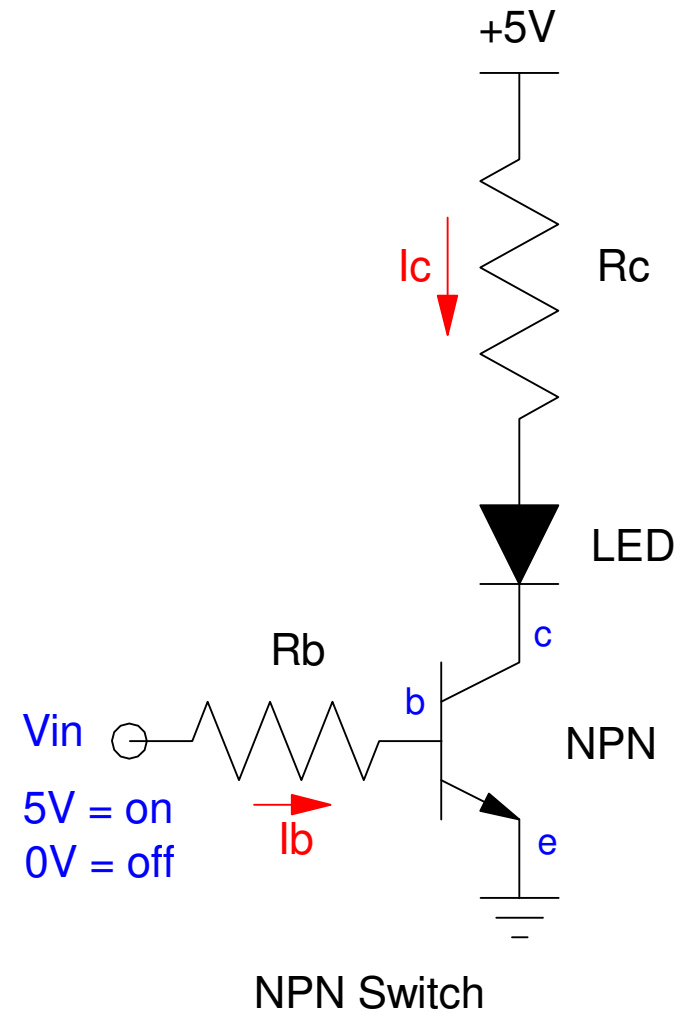- To turn on and off a red LED
- At 20mA when on,
- Using a 0V/5V input capable of driving at most 5mA.





## Solution:

First pick  $R_c$  to set the current to 20mA

$$R_c = \left( \frac{5V - 1.9V - 0.2V}{20mA} \right) = 145\Omega$$

Next, pick  $I_b$  so that the transistor is saturated


$$I_b > \left( \frac{I_c}{100} \right) = 0.2mA$$

Let  $I_b = 1mA$



$$R_b = \left( \frac{5V - 0.7V}{1mA} \right) = 4.3k\Omega$$

Same equations for a PNP switch

Resulting Circuit

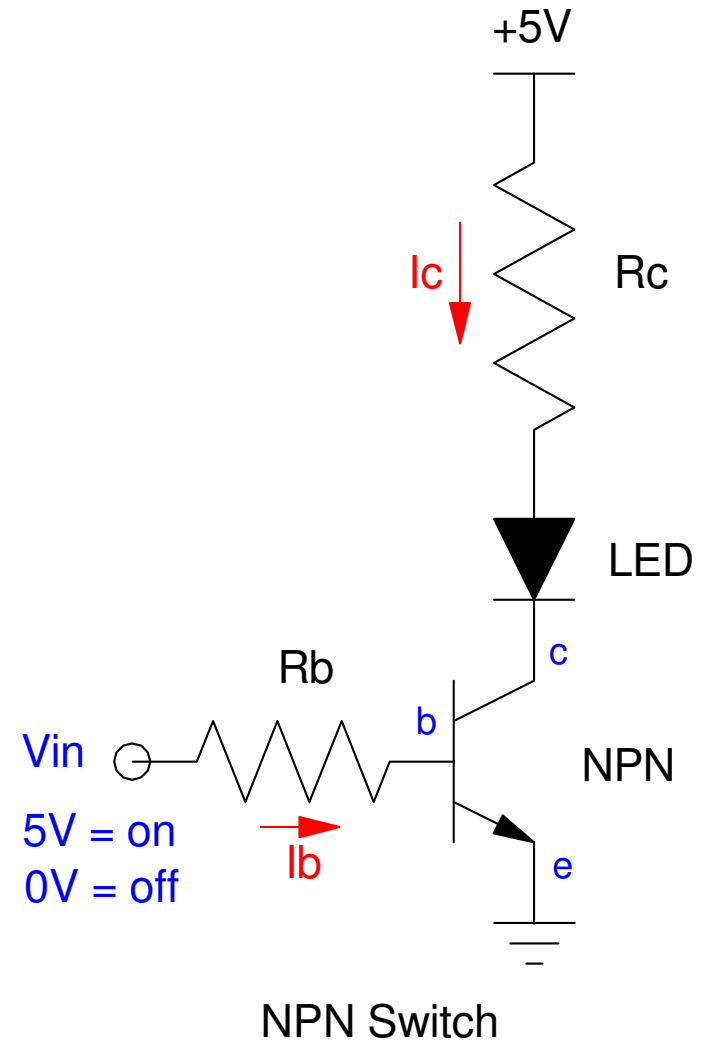

# NPN & PNP Switch

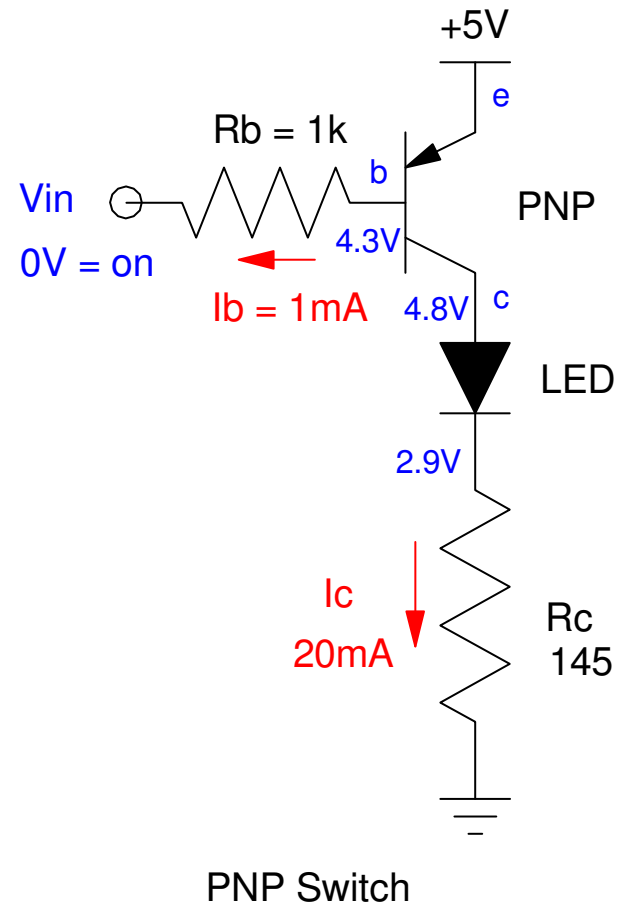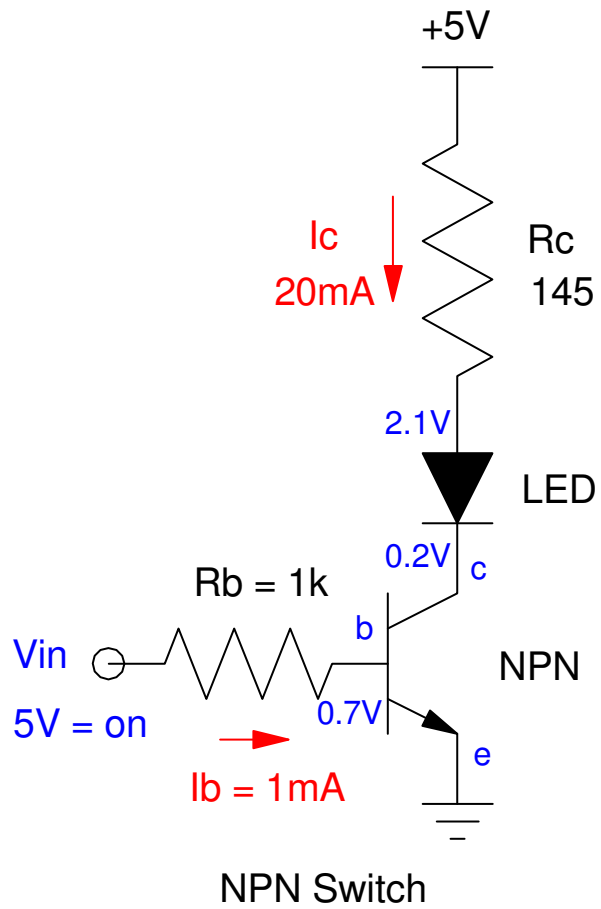

# NPN Switch with a Pi-Pico

Have a Raspberry Pi-Pico turn on and off a red LED

- At 20mA
- Using an NPN transistor

Pick  $R_c$  to set the current

$$R_c = \left( \frac{5V - 1.9V - 0.2V}{20mA} \right)$$

$$R_c = 145\Omega$$


Pick  $R_b$  to set the voltage

- Saturate the transistor

$$\beta I_b > I_c = 20mA$$

Let  $I_b = 1mA$
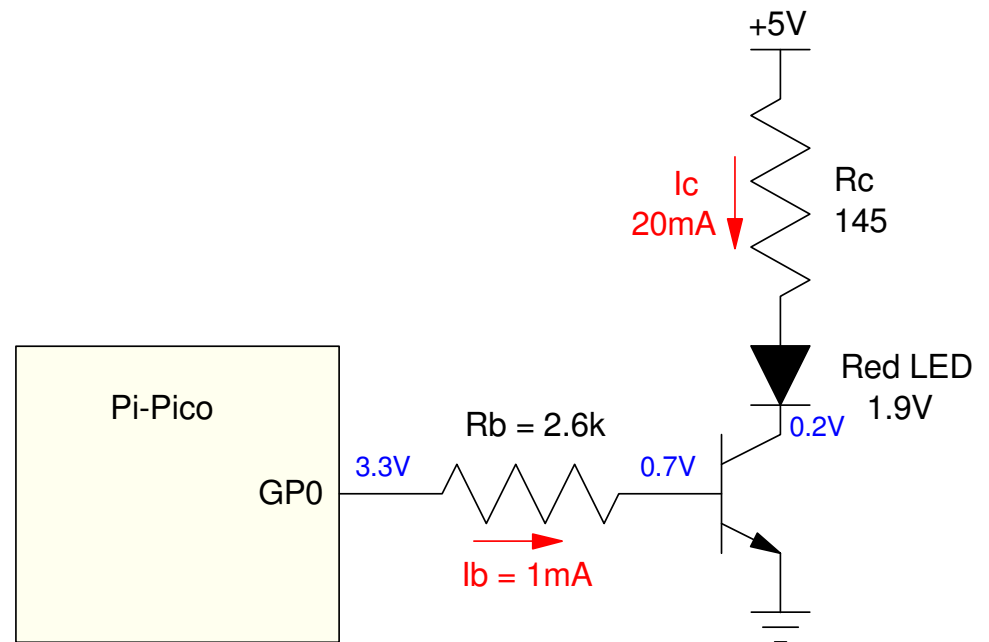
$$R_b = \left( \frac{3.3V - 0.7V}{1mA} \right) = 2.6k\Omega$$




# PNP Switch with a Pi-Pico

Have a Raspberry Pi-Pico turn on an off a red LED

- At 20mA
- Using a PNP transistor

Similar design but an op-amp

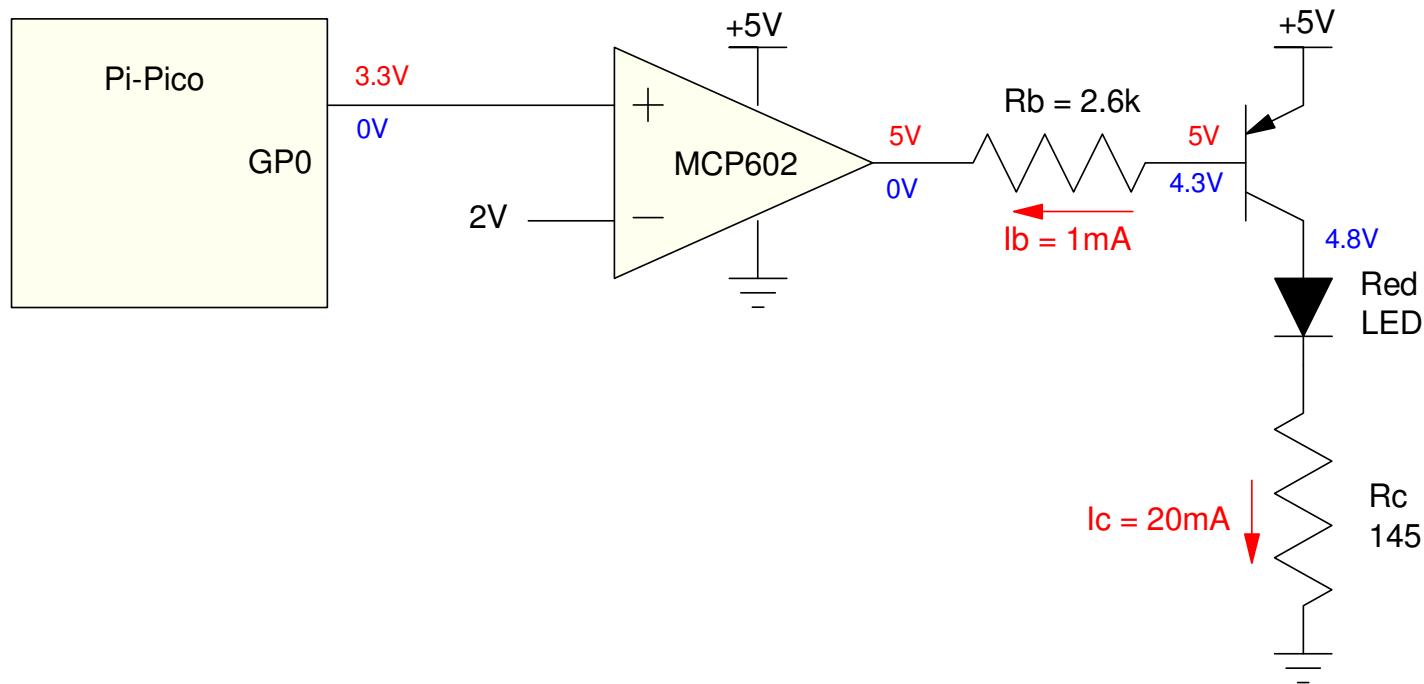- Level shifter circuit (convert 3.3V to 5.0V)



---

## Summary

Diodes can be used as electronic valves

- They let you control block reverse current.

BJT transistors can be used as electronic switches.

- They let you turn on and off devices
  - They amplify current, allowing larger loads to be turned on and off
-

---

## Homework #5:

- Due week #10

### Reminder: ECE 401 Circuit Requirements

- Must operate off of 5VDC
- Must include at least one integrated circuit
- Must include at least one LED with  $I_d = 20\text{mA} \pm 5\text{mA}$
- Must include at least one NPN and one PNP transistor
  - Use a LM7805 regulator to drop 9V to 5V
- Must have a reverse-polarity protection diode
- Must have a 1/4 Watt 1-Ohm resistor in series with the power supply

### 1. Build your circuit on a breadboard

- Power comes from a 9V battery
  - Include a photo in your OneNote document
-

---

## Homework #5 (cont'd)

### 2. Take measurements to verify your circuit works

- Include these measurements in your OneNote document
  - *Note where you these are recorded on your schematic.*
  - *These are the test points for your upcoming PCB)*
  
  - DC Measurements (all cases)
    - Vbat (9V)
    - Vreg (5V)
    - Vbe for the NPN transistor when ON
    - Vce for the NPN transistor when OFF
    - Current through the LED when ON
    - Total current draw
  
  - If using a 555 Timer, also provide waveforms (transient response: 2-3 cycles)
    - Waveform @ C1
    - Waveform @ Threshold
    - Waveform @ Discharge
    - Waveform @ Timer Out
-

---

## Homework #5 (cont'd)

- If using an op-amp (MCP602), also provide the following DC measurements:
  - Voltage at inverting input when on and off
  - Voltage at non-inverting input when on and off
  - Voltage at Op-Amp output when on and off
- If using a microcontroller (Raspberry Pi Pico)
  - Voltage at uP output when on (5V) and off (0V)
  - DC voltage at the PNP transistor ( $V_b$ ,  $V_c$ ,  $V_e$ )

### 3) Parts List

- Parts used in your breadboard
  - Vendor & Vendor number
  - Description
  - Price
-